


---

EECS 16A      Designing Information Devices and Systems I  
 Spring 2019      Discussion 7A


---

### 1. Passive Sign Convention and Power

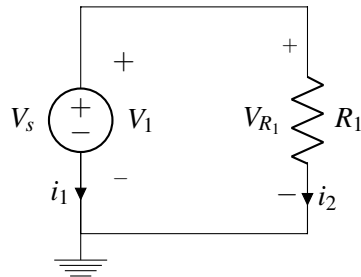- (a) Suppose we have the following circuit and label the currents as shown below. Calculate the power dissipated or supplied by every element in the circuit. Let  $V_s = 5\text{ V}$  and let  $R_1 = 5\ \Omega$ .



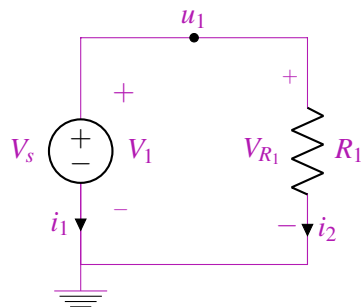**Answer:** We'll start by solving the circuit for the unknown node potentials and currents.



The KCL equation for the one node in this circuit is:

$$i_1 + i_2 = 0$$

The Element equations for the two elements in this circuit are:

$$u_1 - 0 = V_1 = V_s$$

$$u_1 - 0 = V_{R_1} = i_2 R_1$$

Solving the above equations with  $V_s = 5\text{ V}$  and  $R_1 = 5\ \Omega$ :

$$u_1 = 5\text{ V}$$

$$i_1 = -1\text{ A}$$

$$i_2 = 1\text{ A}$$

From above, we can solve for the power dissipated across the resistor:


$$P_{R_1} = IV = i_2 V_{R_1} = 1\text{ A} \cdot 5\text{ V} = 5\text{ W}$$

Next we can solve for the power dissipated across the voltage source:


$$P_{V_s} = IV = i_1 V_1 = i_1 V_s = -1 \text{ A} \cdot 5 \text{ V} = -5 \text{ W}$$

Notice we calculate a negative value for the power dissipated by the voltage source, implying the voltage source is adding power to the circuit.

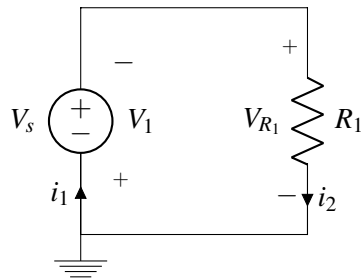- (b) Suppose we change the label of the currents in the circuit to be as shown below. Calculate the power dissipated or supplied by every element in the circuit. Let  $V_s = 5 \text{ V}$  and let  $R_1 = 5 \Omega$ .



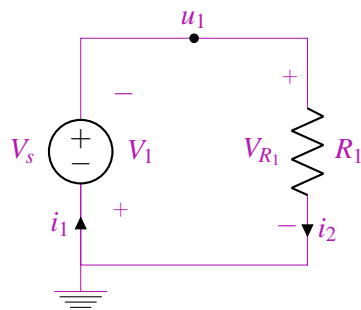**Answer:** We'll solve the circuit the same way as last time.



The KCL equation for the one node in this circuit is:

$$-i_1 + i_2 = 0$$

The Element equations for the two elements in this circuit are:

$$0 - u_1 = V_1 = -V_s$$

$$u_1 - 0 = V_{R_1} = i_2 R_1$$

Solving the above equations with  $V_s = 5 \text{ V}$  and  $R_1 = 5 \Omega$ :

$$u_1 = 5 \text{ V}$$

$$i_1 = 1 \text{ A}$$

$$i_2 = 1 \text{ A}$$

From above, we can solve for the power dissipated across the resistor:

$$P_{R_1} = IV = i_2 V_{R_1} = 1 \text{ A} \cdot 5 \text{ V} = 5 \text{ W}$$


Next we can solve for the power dissipated across the voltage source:

$$P_{V_s} = IV = i_1 V_1 = i_1 (-V_s) = 1 \text{ A} \cdot -5 \text{ V} = -5 \text{ W}$$

Notice here that the circuit has the same power dissipated by all the elements. This is because with both labeling of currents, we followed the passive sign convention.

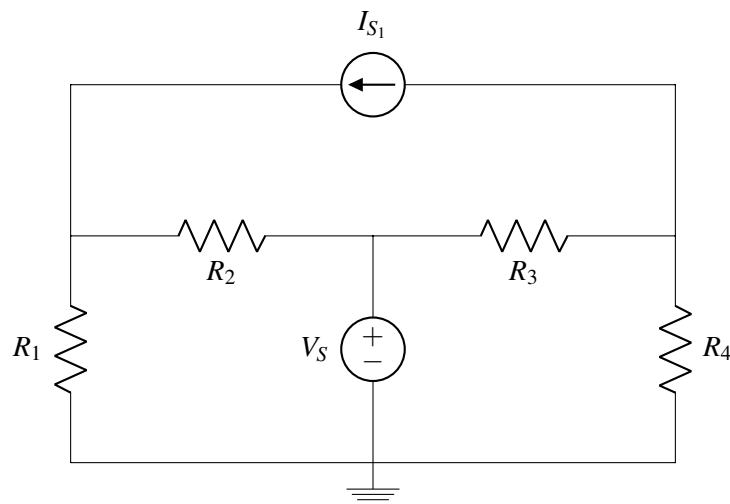
## 2. Circuit Analysis

Setup the matrix to solve for the voltages across and the currents flowing through each component.



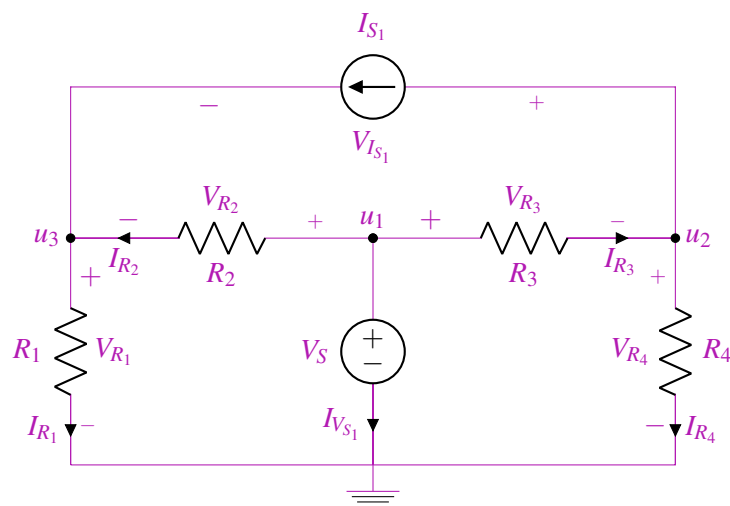**Answer:**

We first label all potentials, currents, and voltages.



We will use simplifications for the sources. Since we know  $V_S$ , and the voltage source is connected between  $u_1$  and ground, we know  $u_1 - 0 = V_S \implies u_1 = V_S$ . Similarly, we don't need to add variables for the current sources when writing KCL equations.

Let's start by writing KCL equations for the nodes  $u_2$  and  $u_3$ :

$$-I_{R3} + I_{S1} + I_{R4} = 0$$

$$-I_{R2} - I_{S1} + I_{R1} = 0$$

Now let's write element equations, we've already included the sources, so we only need to write equations for the resistors:

$$u_3 - 0 = I_{R1} R_1$$

$$V_s - u_3 = I_{R_2} R_2$$

$$u_2 - 0 = I_{R_4} R_4$$

$$V_s - u_2 = I_{R_3} R_3$$

Notice we have 6 equations for 6 unknowns. We can setup the matrix:

$$\begin{bmatrix} 0 & 0 & 1 & -1 & 0 & 0 \\ 0 & 0 & 0 & 0 & -1 & 1 \\ 0 & 1 & -R_1 & 0 & 0 & 0 \\ 0 & -1 & 0 & -R_2 & 0 & 0 \\ 1 & 0 & 0 & 0 & 0 & -R_4 \\ -1 & 0 & 0 & 0 & -R_3 & 0 \end{bmatrix} \begin{bmatrix} u_2 \\ u_3 \\ I_{R_1} \\ I_{R_2} \\ I_{R_3} \\ I_{R_4} \end{bmatrix} = \begin{bmatrix} I_{S_1} \\ -I_{S_1} \\ 0 \\ -V_s \\ 0 \\ -V_s \end{bmatrix}$$

### 3. Resist the Touch

In this question, we will be re-examining the 2-dimensional resistive touchscreen previously discussed in both lecture and lab. The general touch screen is shown in Figure 1 (a). The touchscreen has length  $L$  and width  $W$  and is composed of a rigid bottom layer and a flexible upper layer. The strips of a single layer are all connected by an ideal conducting plate on each side. The upper left corner is position  $(1, 1)$ .

The top layer has  $N$  vertical strips denoted by  $x_1, x_2, \dots, x_N$ . These vertical strips all have cross sectional area  $A$ , and resistivity  $\rho_x$ .

The bottom layer has  $N$  horizontal strips denoted by  $y_1, y_2, \dots, y_N$ . These horizontal strips all have cross sectional area  $A$  as well, and resistivity  $\rho_y$ .

Assume that all top layer resistive strips and bottom layer resistive strips are spaced apart equally. Also assume that all resistive strips are rectangular as shown by Figure 1 (b).

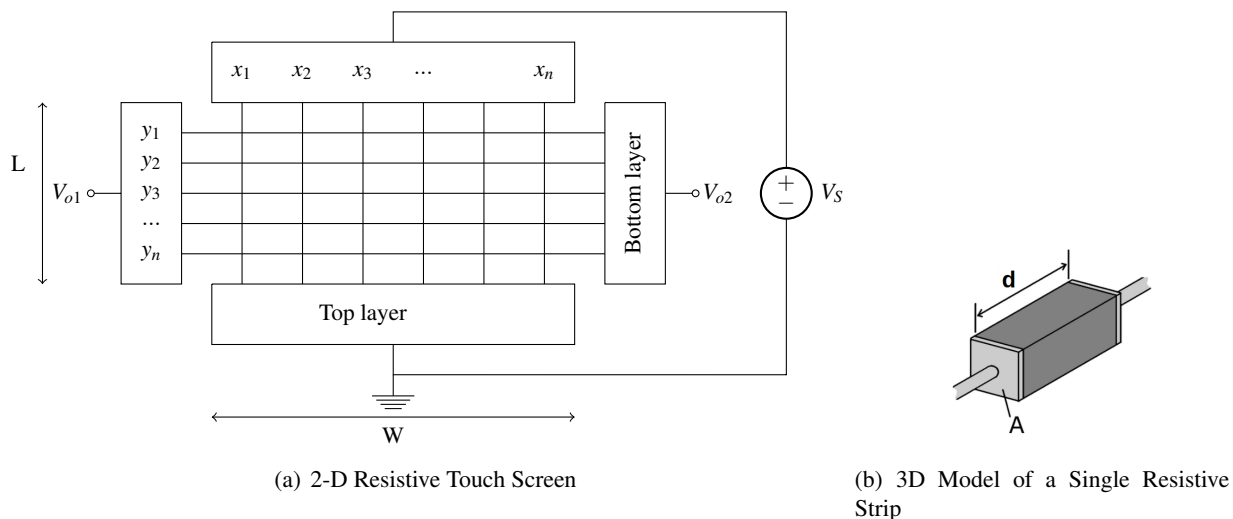


Figure 1:

- (a) (3 points) Figure 1(b) shows a model for a single resistive strip. Find the equivalent resistance  $R_x$  for the vertical strips and  $R_y$  for the horizontal strips, as a function of the screen dimensions  $W$  and  $L$ , the respective resistivities, and the cross-sectional area  $A$ .

**Answer:** The equation for resistance is  $R = \frac{\rho l}{A}$

Therefore,  $R_x = \frac{\rho_x L}{A}$ .

For the bottom,  $R_y = \frac{\rho_y W}{A}$ .

(b) (5 points) Consider a  $2 \times 2$  example for the touchscreen circuit.

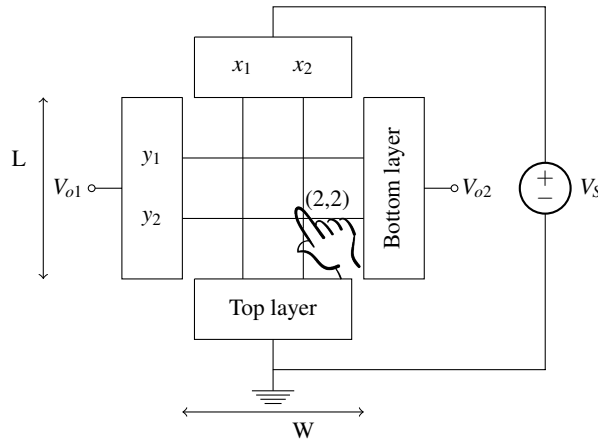



Figure 2:  $2 \times 2$  Case of the Resistive Touchscreen

Given that  $V_s = 3\text{V}$ ,  $R_x = 2000\Omega$ , and  $R_y = 2000\Omega$ , draw the equivalent circuit for when the point  $(2,2)$  is pressed and solve for the voltage at terminal  $V_{O2}$  with respect to ground.

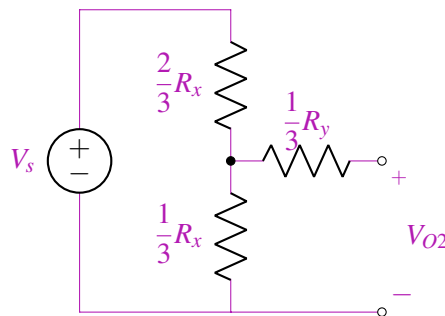**Answer:**

Since all of the resistive strips are equally spaced, the resistor above point  $(2,2)$  on strip  $x_2$  becomes  $\frac{2}{3}R_x$  and the resistor below point  $(2,2)$  on strip  $x_2$  becomes  $\frac{1}{3}R_x$ .

The bottom layer resistors, although they must be drawn in the equivalent circuit, do not affect the voltage at  $V_{O2}$  as they are open circuits.



Observing that the resistive strips form a voltage divider, we can determine  $V_{O2}$  using the voltage divider equation.

Therefore,  $V_{O2} = V_{(2,2)} = V_s \frac{\frac{1}{3}R_x}{\frac{1}{3}R_x + \frac{2}{3}R_x} = \frac{1}{3}V_s = 1\text{V}$ .

(c) (8 points) Suppose a touch occurs at coordinates  $(i, j)$  in Figure 1(a). Find an expression for  $V_{O2}$  as a function of  $V_s$ ,  $N$ ,  $i$ , and  $j$ . The upper left corner is the coordinate  $(1, 1)$  and the upper right coordinate is  $(N, 1)$ .

**Answer:**

$$\begin{aligned}V_{O2} &= \frac{\frac{N+1-j}{N+1}R_x}{R_x}V_s \\ &= \frac{N+1-j}{N+1}V_s\end{aligned}$$