


---

EECS 16A      Designing Information Devices and Systems I  
 Spring 2019      Discussion 8B

---
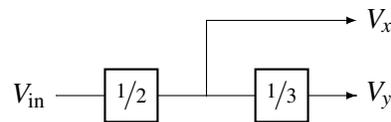
### 1. Modular Circuits

In this problem, we will explore the design of circuits that perform a set of (arbitrary) mathematical operations. (Note that the so-called analog signal processing – where these kinds of mathematical operations are performed on continuously-valued voltages by analog circuits – is extremely common in real-world applications; without this capability, essentially none of our radios or sensors would actually work.) Specifically, let's assume that we want to implement the block diagram shown below:



In other words, we want to implement a circuit with two outputs  $V_x$  and  $V_y$ , where  $V_x = \frac{1}{2}V_{in}$  and  $V_y = \frac{1}{3}V_x$ .

- Design two voltage divider circuits that each independently would implement the two multiplications shown in the block diagram above (i.e., multiply by  $1/2$  and multiply by  $1/3$ ). Note that you do not need to include the input voltage sources in your design – you can simply define the input to each block as being at the appropriate potential (e.g.,  $V_{in}$  or  $V_x$ ).
- Assuming that  $V_{in}$  is created by an ideal voltage source, implement the original block diagram as a circuit by directly replacing each block with the designs you came up with in part (a).
- For the circuit from part (b), do you get the desired relationship between  $V_y$  and  $V_x$ ? How about between  $V_x$  and  $V_{in}$ ? Be sure to explain why or why not each block retains its desired functionality.
- Now let's assume that we have discovered compose-able circuits that implement mathematical operations. In particular, we have these blocks that implement:
  - $V_o = 5V_i$
  - $V_o = -2V_i$
  - $V_o = V_{i_1} + V_{i_2}$


Using just these blocks, draw the block diagram that implements:

- $V_o = -12V_{in_1}$
- [PRACTICE]**  $V_o = -10V_{in_1} - 2V_{in_2}$
- [PRACTICE]**  $V_o = -V_{in_1} + V_{in_2}$


### 2. Op-Amps As Comparators

For each of the circuits shown below, plot  $V_{out}$  for  $V_{in}$  ranging from  $-10\text{V}$  to  $10\text{V}$  for part (a) and from  $0\text{V}$  to  $10\text{V}$  for part (b). Let  $A = 100$  for your plots. Note that in real op amps,  $A$  is typically much higher (i.e.  $10^4 - 10^7$ ).

(a)

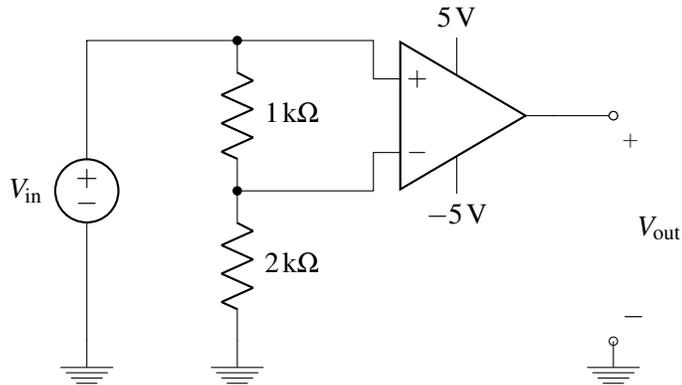


(b) [PRACTICE]

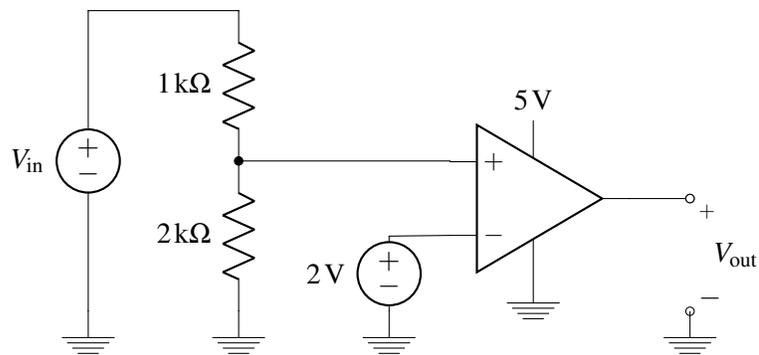


### 3. Current Sources And Capacitors

For the circuits given below, give an expression for  $v_{out}(t)$  in terms of  $I_s$ ,  $C_1$ ,  $C_2$ ,  $C_3$ , and  $t$ . Assume that all capacitors are initially uncharged, i.e. the initial voltage across each capacitor is  $0\text{V}$ .

(a)

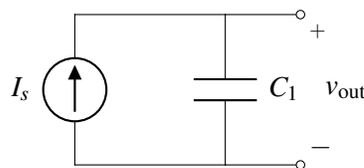


(b)

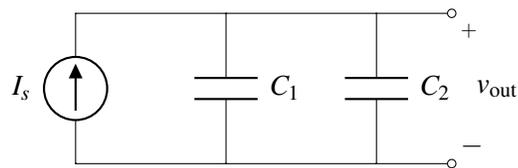

#### 4. Maglev Train Height Control System [PRACTICE]

One of the fastest forms of land transportation are trains that actually travel slightly elevated from ground using magnetic levitation (or “maglev” for short). Ensuring that the train stays at a relatively constant height above its “tracks” (the tracks in this case are what provide the force to levitate the train and propel it forward) is critical to both the safety and fuel efficiency of the train. In this problem, we’ll explore how the maglev trains use capacitors to keep them elevated. (Note that real maglev trains may use completely different and much more sophisticated techniques to perform this function, so if you e.g. get a contract to build such a train, you’ll probably want to do more research on the subject.)

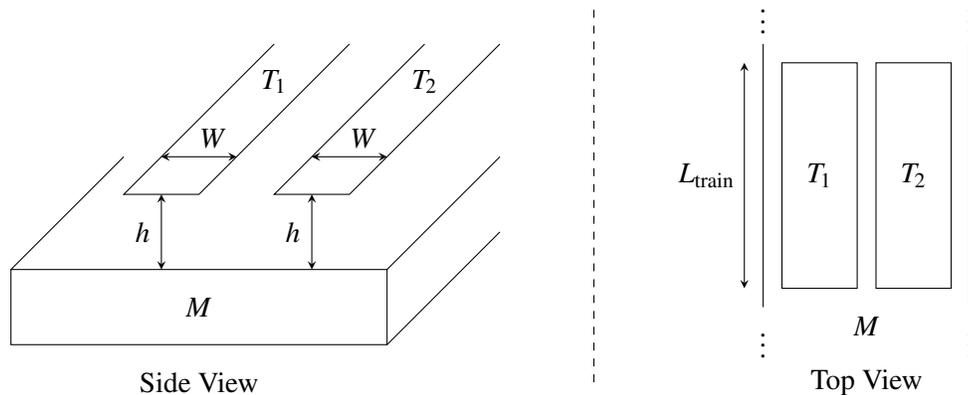- (a) As shown below, let’s imagine that all along the bottom of the train, we put two parallel strips of metal ( $T_1$ ,  $T_2$ ), and that on the ground below the train (perhaps as part of the track), we have one solid piece of metal ( $M$ ).



Assuming that the entire train is at a uniform height above the track and ignoring any fringing fields (i.e., all capacitors are purely parallel plate), as a function of  $L_{\text{train}}$  (the length of the train),  $W$  (the width of  $T_1/T_2$ ), and  $h$  (the height of the train off of the track), what is the capacitance between  $T_1$  and  $M$ ? How about the capacitance between  $T_2$  and  $M$ ?

- (b) Any circuit on the train can only make direct contact at  $T_1$  and  $T_2$ . To detect the height of the train, it would only be able to measure the effective capacitance between  $T_1$  and  $T_2$ . Draw a circuit model showing how the capacitors between  $T_1$  and  $M$  and between  $T_2$  and  $M$  are connected to each other.
- (c) Using the same parameters as in part (a), provide an expression for the capacitance between  $T_1$  and  $T_2$ .
- (d) So far we’ve assumed that the height of the train off of the track is uniform along its entire length, but in practice, this may not be the case. Suggest and sketch a modification to the basic sensor design (i.e., the two strips of metal  $T_1/T_2$  along the entire bottom of the train) that would allow you to measure the height at the train at 4 different locations.