

This homework is due March 15, 2019 at 23:59.

Self-grades are due March 19, 2019, at 23:59.

Submission Format

Your homework submission should consist of **one** file.

- `hw7.pdf`: A single PDF file that contains all of your answers (any handwritten answers should be scanned).


Submit the file to the appropriate assignment on Gradescope.

1. Fruity Fred

Fruity Fred just got back from Berkeley Bowl with a bunch of mangoes, pineapples, and coconuts. He wants to sort his mangoes in order of weight, so he decides to use his knowledge from EE16A to build a scale.

He finds two identical bars of material (M_1 and M_2) of length L (meters) and cross-sectional area A_c (meters²), which are made of a material with resistivity ρ . He knows that the length of these bars decreases by k meters per Newton of force applied, while the cross-sectional area remains constant.

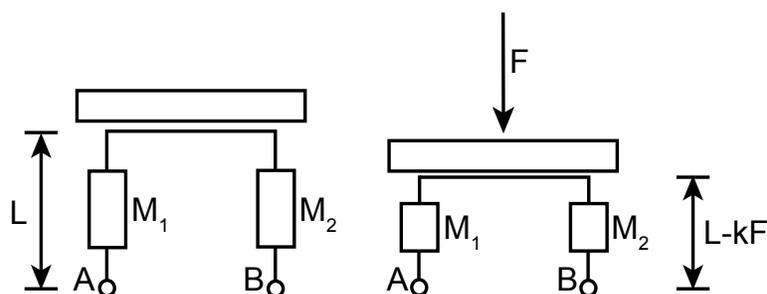He builds his scale as shown below, where the top of the bars are connected with an ideal electrical wire. The left side of the diagram shows the scale at rest (with no object placed on it), and the right side shows it when the applied force is F (Newtons), causing the length to decrease by kF meters. Fred's mangoes are not very heavy, so $L \gg kF$.




- Let R_{AB} be the resistance between nodes A and B . Write an expression for R_{AB} as a function of A_c , L , ρ , F , and k .
- Fred's scale design is such that the resistance R_{AB} changes depending on how much weight is placed on it. However, he really wants to measure a voltage rather than a resistance.


Design a circuit for Fred that outputs a voltage that is some function of the weight. Your circuit should include R_{AB} , and you may use any number of voltage sources and resistors in your design. Be sure to label where the voltage should be measured in your circuit. Also provide an expression relating the output voltage of your circuit to the force applied on the scale.

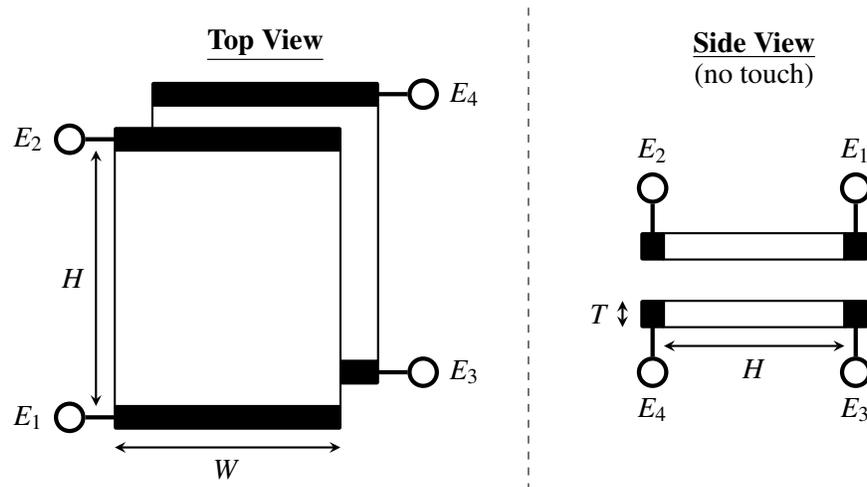2. Multitouch Resistive Touchscreen


In this problem, we will look at a simplified version of the multitouch resistive touchscreen. In particular, rather than measuring the position of two potential touch points in both dimensions (i.e. a pair of coordinates (x_1, y_1) and (x_2, y_2) corresponding to two touch positions), let's think about a version where we are interested in measuring only the vertical position of the two touch points (i.e. y_1 and y_2). Therefore, unlike the touchscreens we looked at in class, both of the resistive plates (i.e. both the top and the bottom plate) would have conductive strips placed along their top and bottom edges, as shown below.



- Assuming that both of the plates are made out of a material with $\rho = 1 \Omega\text{m}$ and that the dimensions of the plates are $W = 3 \text{ cm}$, $H = 12 \text{ cm}$, and $T = 1 \text{ mm}$, with no touches at all, what is the resistance between terminals E_1 and E_2 (which would be the same as the resistance between terminals E_3 and E_4)?
- Now let's look at what happens when we have two touch points. Let's assume that at wherever height the touch occurs, a perfect contact is made between the top plate and the bottom plate along the entire width of the plates (i.e. you don't have to worry about any lateral resistors), but that otherwise none of the electrical characteristics of the plates change. Defining the bottom of the plate as being $y = 0 \text{ cm}$ (i.e. a touch at E_1 would be at $y = 0 \text{ cm}$), let's assume that the two touches happen at $y_1 = 3 \text{ cm}$ and $y_2 = 7 \text{ cm}$ and that your answer to part (a) was $8 \text{ k}\Omega$ (which may or may not be the right answer). Draw a model with 6 resistors that captures the electrical connections between E_1 , E_2 , E_3 , and E_4 and calculate their resistances. Note that for clarity, the system has been redrawn below to depict this scenario.

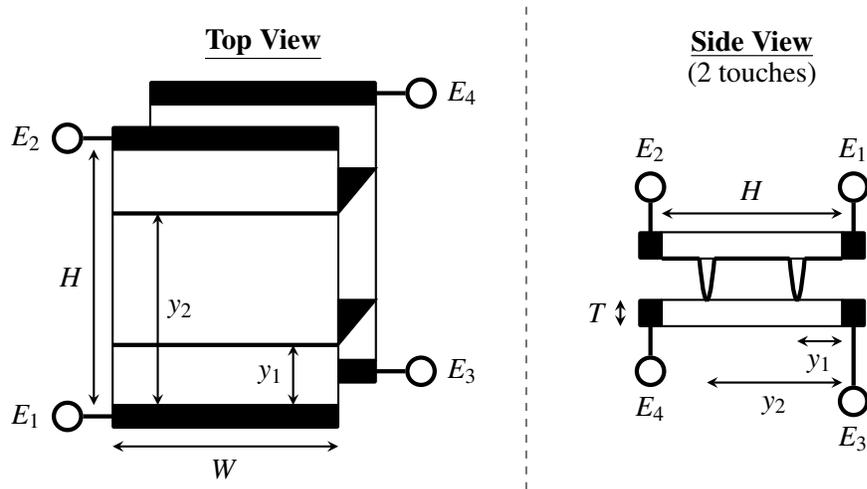

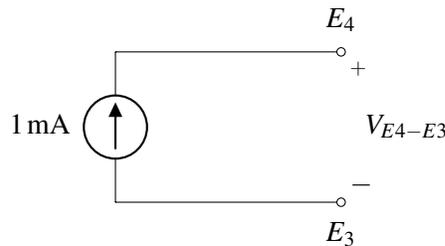(c) Using the same assumptions as part (b), if you drove terminals E_3 and E_4 with a 1 mA current source (as shown below) but left terminals E_1 and E_2 open-circuited, what is the voltage you would measure across $E_4 - E_3$ (i.e. V_{E4-E3})?



(d) Now let's try to generalize the situation by assuming that the two touches can happen at any two arbitrary points y_1 and y_2 , but with y_1 defined to always be less than y_2 (i.e. y_1 is always the bottom touch point). Leaving the setup the same as in part (c) except for the arbitrary y_1 and y_2 , by measuring only the voltage between E_4 and E_3 , what information can you extract about the two touch positions? Please be sure to provide an equation relating V_{E4-E3} to y_1 and y_2 as a part of your answer, and note that you may want to redraw the model from part (b) to help you with this.


(e) One of your colleagues claims that by measuring the appropriate voltages, not only can they extract what both y_1 and y_2 are in this system, but they can even do so by formulating a system of three independent voltage equations related to y_1 and y_2 . As we will see later, this will allow us to gain some robustness to noise in the voltage measurements.

In order to facilitate this, write equations relating V_{E4-E2} and V_{E1-E3} to y_1 and y_2 . (The third voltage we'll use is V_{E4-E3} , which you should have already derived an equation for in the previous part of the problem.)

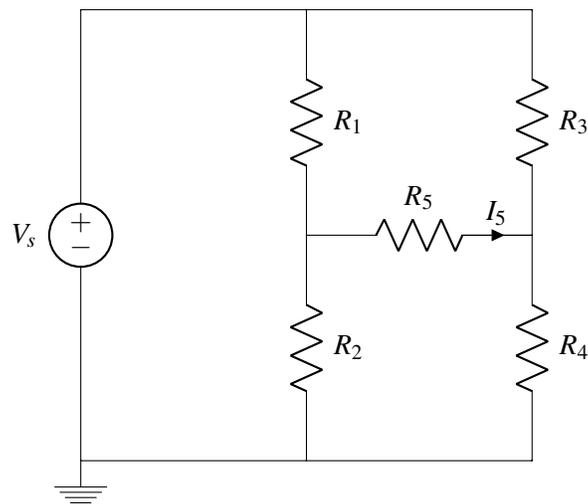3. The Shortcut-seekers' Guide to Circuit Analysis

Using the fast circuit analysis method outlined in the lecture, write down the equations for node potentials. Solve the following circuit for the potentials at each node and the current (I_5) through resistor R_5 . The ground node is labeled for you. You may use a numerical tool, such as IPython.

$$V_s = 5\text{ V}, R_1 = 1\ \Omega, R_2 = 2\ \Omega, R_3 = 3\ \Omega, R_4 = 4\ \Omega, R_5 = 5\ \Omega$$



4. Cell Phone Battery

As great as smartphones are, one of their main drawbacks is that their batteries don't last a very long time. A Google Pixel, under somewhat regular usage conditions (internet, a few cat videos, etc.) uses 0.3 W of power. We will model the battery as a voltage source (which, as you know, will maintain a voltage across its terminals regardless of current through it) with one caveat: they have a limited amount of charge, or capacity. When the battery runs out of charge, it no longer provides a constant voltage, and your phone dies. Typically, engineers specify battery capacity in terms of mAh, which indicates how many mA of current the battery can supply for one hour before it needs to be recharged. The Pixel's battery has a battery capacity of 2770 mAh and operates at a voltage of 3.8 V.

- When a battery's capacity is depleted, it no longer operates as a voltage source. How long will a Pixel's full battery last under regular usage conditions?
- How many coulombs of charge does the battery contain? Recall that $1 \text{ C} = 1 \text{ A} \times 1 \text{ s}$, which implies that $1 \text{ mC} = 1 \text{ mAs}$. An electron has approximately $1.602 \times 10^{-19} \text{ C}$ of charge. How many usable electrons worth of charge are contained in the battery when it is fully charged?
- Suppose the cell phone battery is completely discharged and you want to recharge it completely. How much energy (in J) is this? Recall that a J is equivalent to a W s.
- Suppose PG&E charges \$0.12 per kWh. Every day, you completely discharge the battery (meaning more than typical usage) and you recharge it every night. How much will recharging cost you for the month of October (31 days)?
- The battery has internal circuitry that prevents it from getting overcharged (and possibly exploding!). The circuitry is also used to transfer power into the chemical reactions that store the energy. We will model this internal circuitry as being one resistor with resistance R_{bat} , which is typically a small, non-negative resistance. Furthermore, we'll assume that all the energy dissipated across R_{bat} goes to recharging the battery. Suppose the wall plug and wire can be modeled as a 5 V voltage source and 200 m Ω resistor, as pictured in Figure 1. What is the power dissipated across R_{bat} for $R_{\text{bat}} = 1 \text{ m}\Omega$, 1 Ω , and 10 k Ω ? How long will the battery take to charge for each of those values of R_{bat} ?

5. Maximum Horsepower

You are an engineer working on an electric car. Your job is to design a motor to be used on the car. Specifically, you are designing the resistance of this motor. The battery used by this car has some series resistance (R_s), as modeled by the circuit shown below:



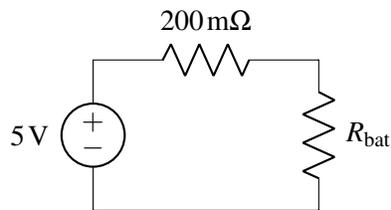


Figure 1: Model of wall plug, wire, and battery.

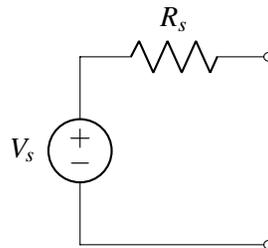

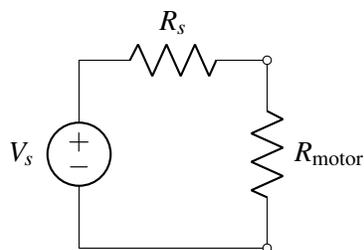You attach your motor to the battery as shown below.



- Calculate the power P_s delivered by the voltage source in terms of V_s , R_s , and R_{motor} .
- Now calculate the power P_{motor} dissipated by the load resistor in terms of V_s , R_s , and R_{motor} .
- Suppose we wanted to maximize the power dissipated across the load. Find the optimal value for R_{motor} in terms of R_s .
Hint: Use calculus.
- Now you've switched teams to designing the battery. Your job is now to pick the optimal R_s for maximizing the power delivered to the motor. What value of R_s should you pick?
Hint: Don't use calculus.

6. Homework Process and Study Group

Who else did you work with on this homework? List names and student ID's. (In case of homework party, you can also just describe the group.) How did you work on this homework?