

EE 16A

Nandish Mehta (nandish@berkeley.edu)



Design Example: Current source

→ Build current source using opamps, resistor, and voltage source


→ for any load voltage o/p current is constant.

Design Procedure

1) Goal

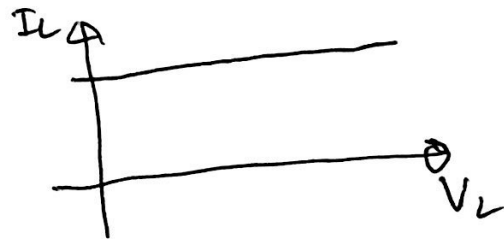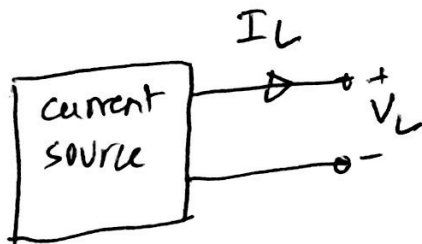


2) Approach

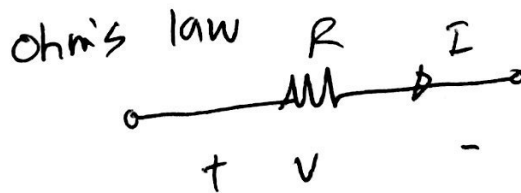


$$I = V/R$$

3) Implementation

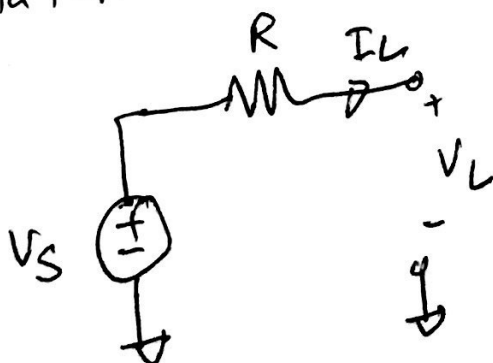



4) Verification / Testing

②

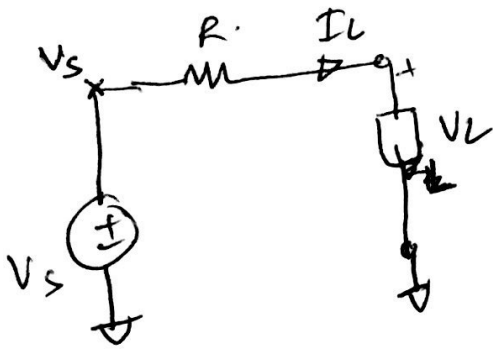


$$\frac{V_S - V_L}{R} = I_L$$

issue: I_L changes with V_L

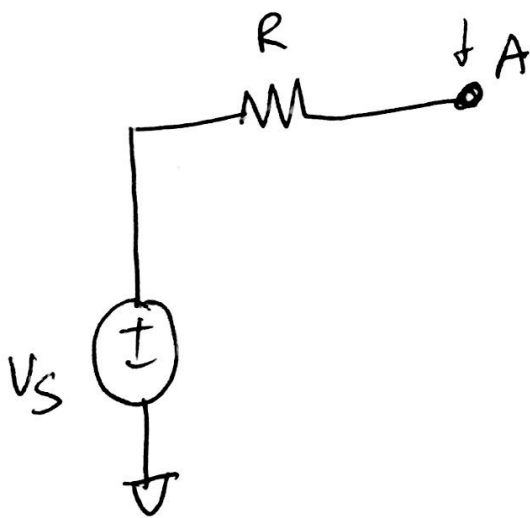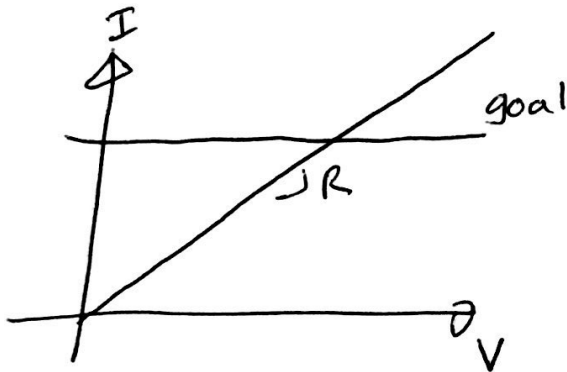


Fix: Use an op-amp

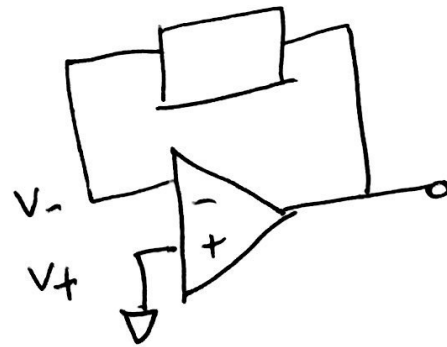

NFB exist ✓

$$GR=2 \Rightarrow V_- = V_+$$

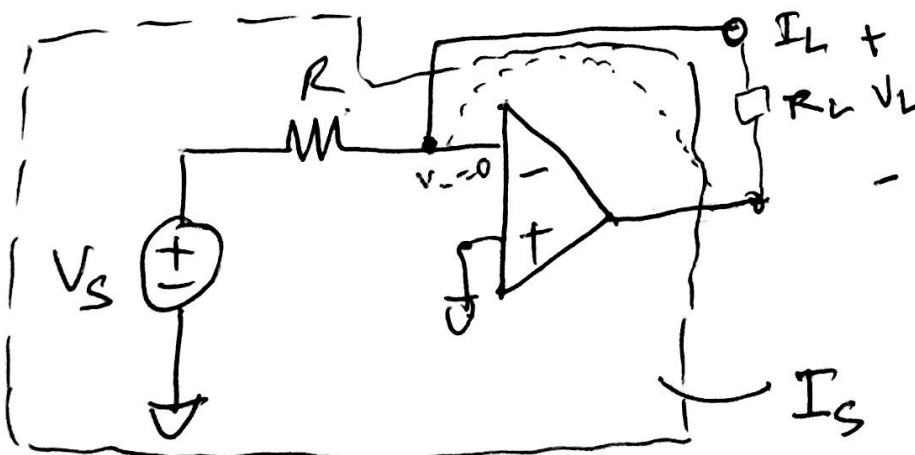



$$I_L = \frac{V_S}{R}$$

$$\text{@ } V_+ = V_-$$

Issues:



- 1) ~~Negative~~ -ve f/B exist
- 2) V_L is fixed. for $R_L = 0$ $V_L = 0$



Test for type of f/B

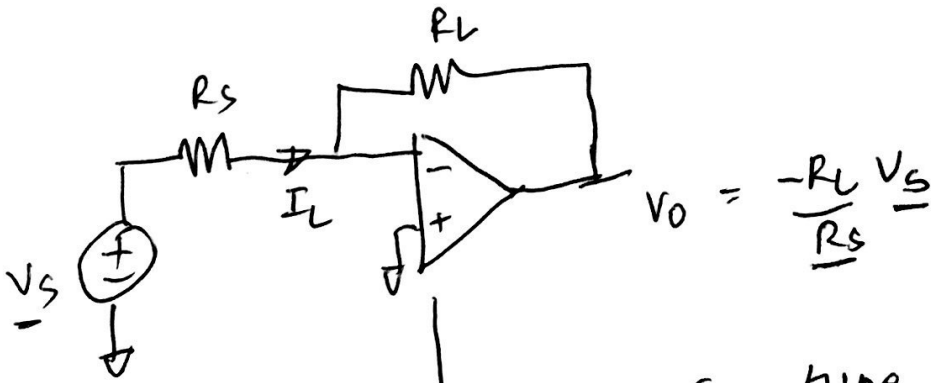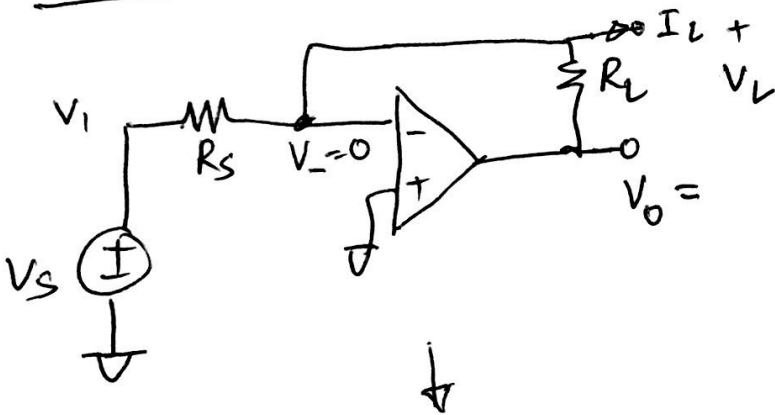


$$V_O = -\frac{R_L}{R_S} V_S$$

Check for type of f/B

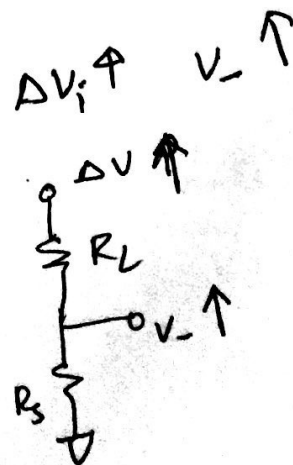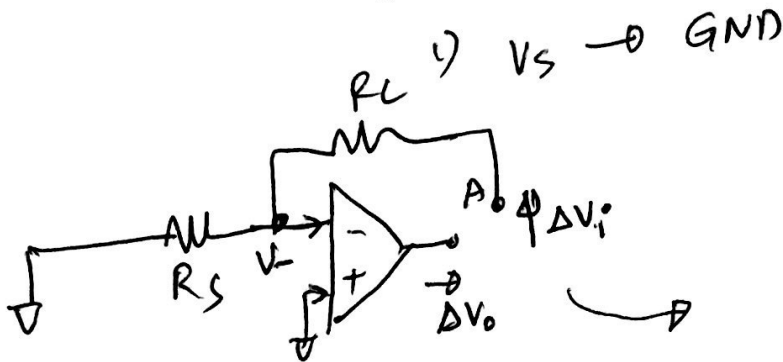


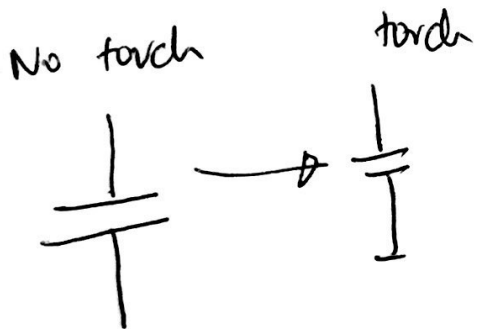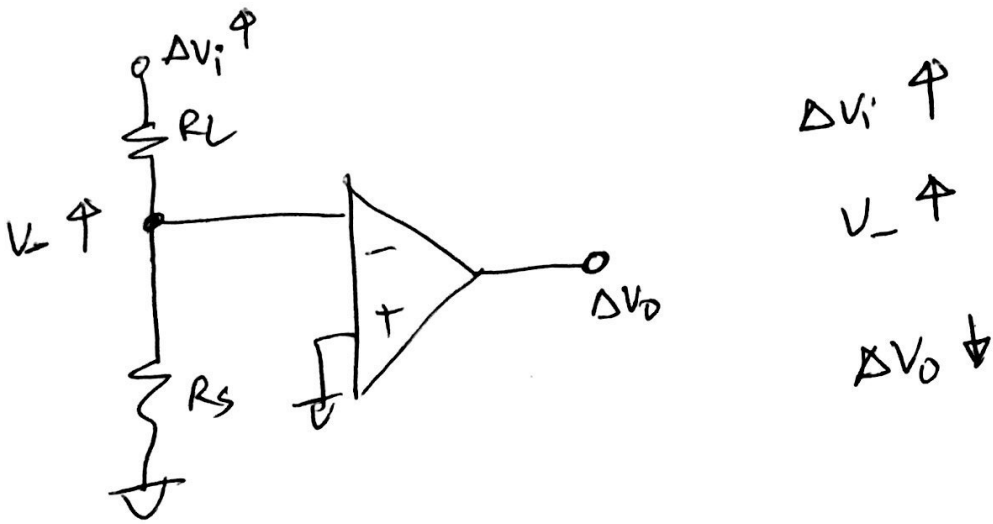

What type of f/B?

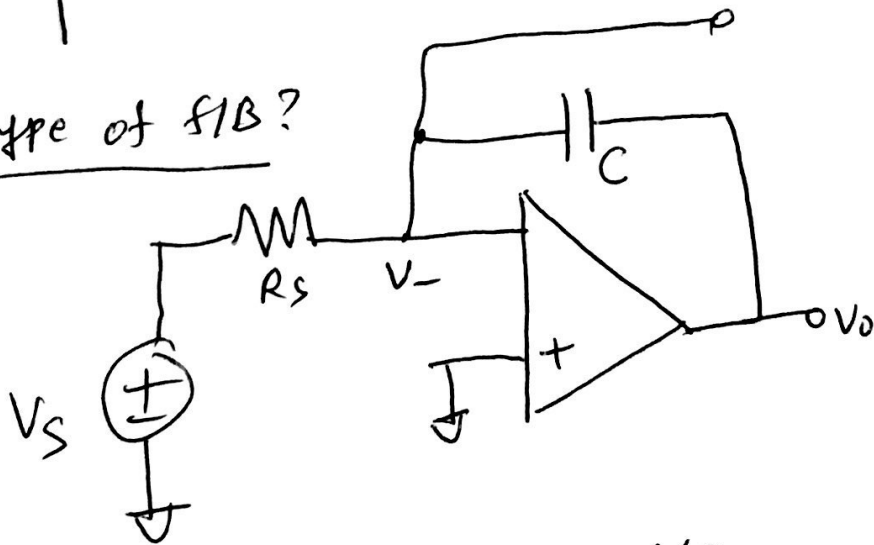

- 1) -ve 2) +ve 3) No f/B

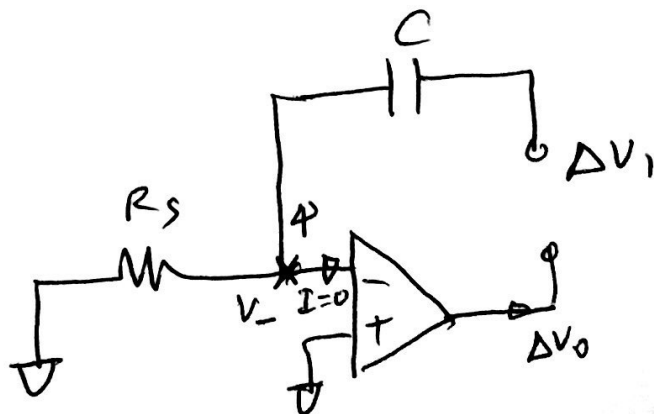



test

$\Delta V_i \uparrow$
 $V_- \uparrow$
 $\Delta V_o \downarrow$

f/B we receive


NFB

Circuit of touch-screen sensor

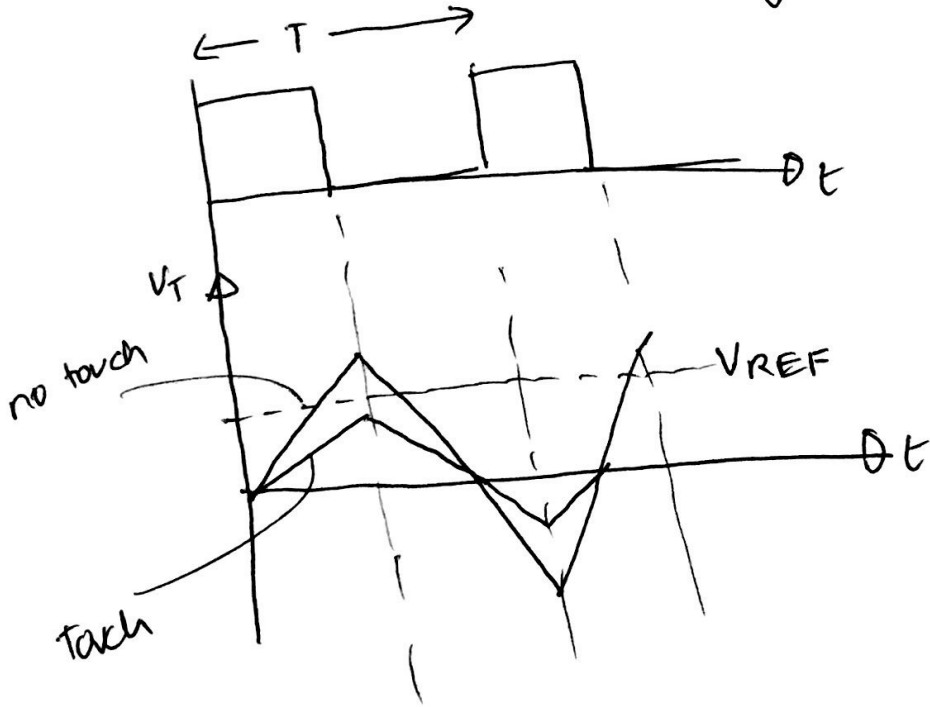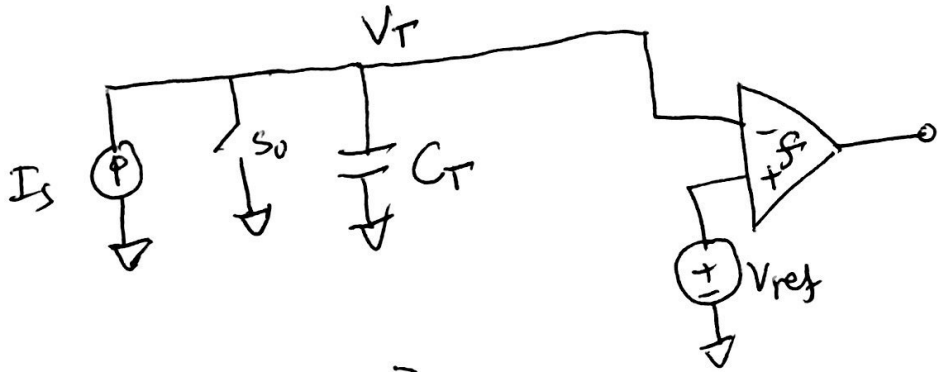


~~No~~ No-touch
 $C_T = C_{T1}$

Touch
 $C_T = C_{T2}$

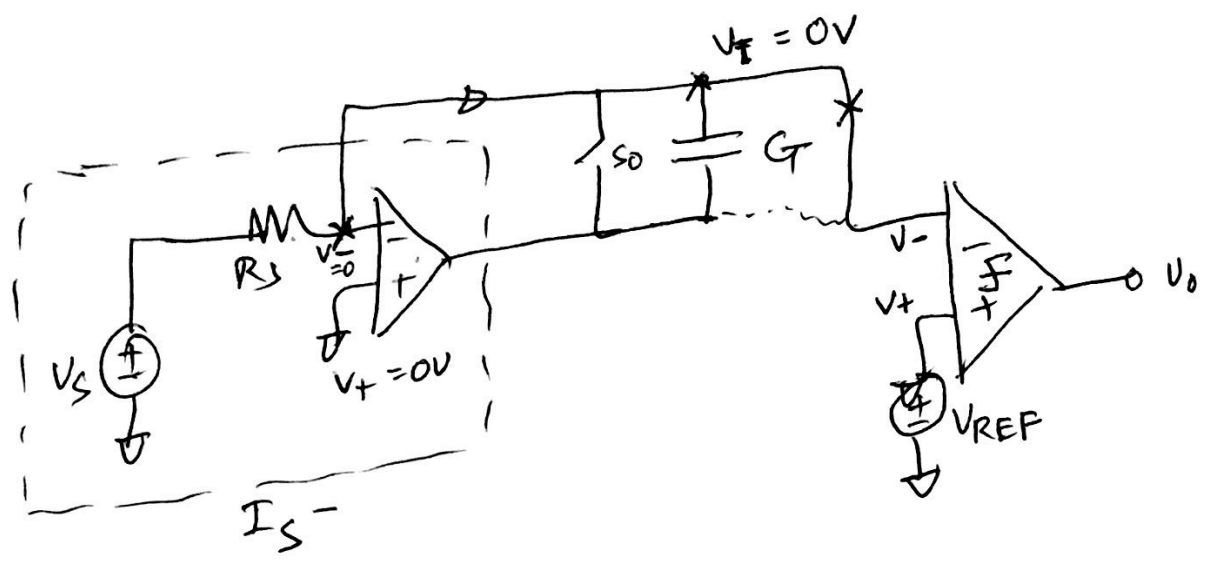

GR-2 $V_- = V_+$ \Downarrow

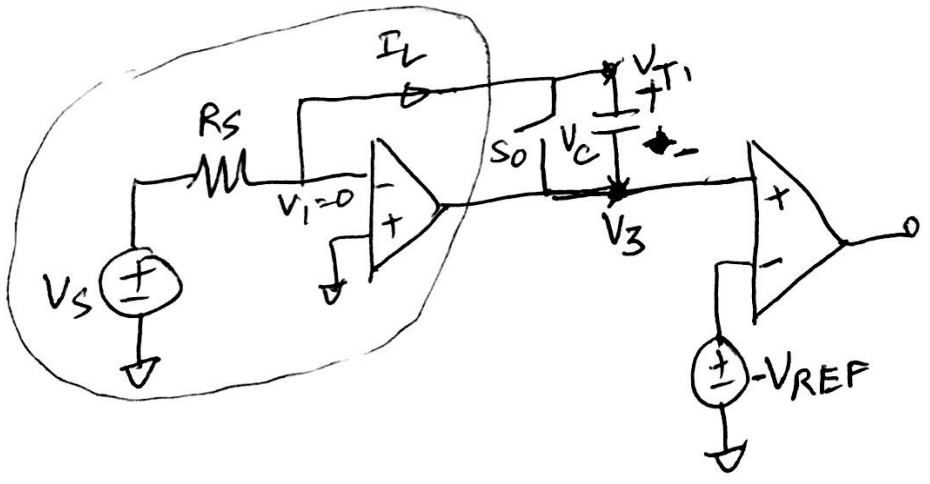


~~$V_C = I_L$~~

$$I_C = I_L = C_T \frac{dV_C}{dt}$$

$$I_L = \frac{C_T V_C}{T}$$

$$V_C = \frac{I_L T}{C_T}$$

$$I_L = \frac{V_s}{R}$$

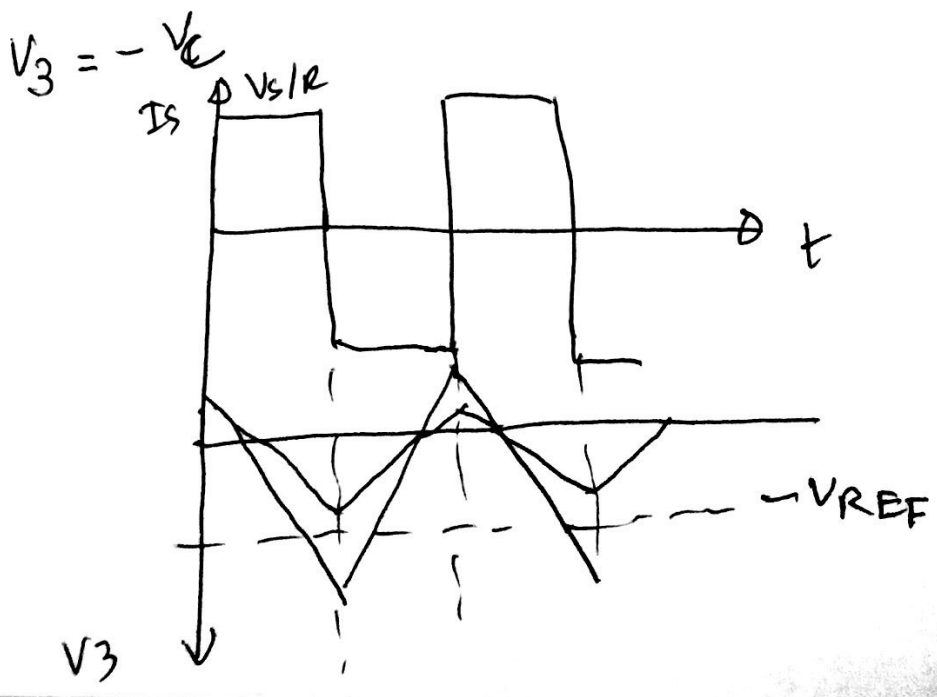

⑦

No. torch $C_T = C_{T1}$
Torch $C_T = C_{T2}$

