

(21)


Lecture 4 - Module 2

EE16A

- * An interesting circuit - continued
- * ZD touchscreen
- * A faster circuit analysis

Note 14

An interesting circuit

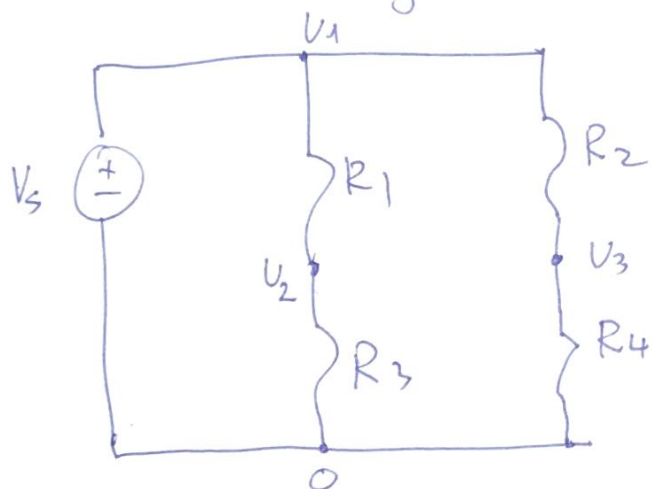

$$U_2 = ? \quad U_3 = ?$$

$$U_2 - 0 = \frac{R_3}{R_1 + R_3} \cdot (U_1 - 0) \quad \text{with } U_1 \rightarrow V_s$$

$$U_2 = \frac{R_3}{R_1 + R_3} \cdot V_s$$


$$U_3 = \frac{R_4}{R_2 + R_4} \cdot V_s$$

Let's have: $R_3 = k R_1$ & $R_4 = k R_2$

$$\left. \begin{aligned} U_2 &= \frac{k \cdot R_1}{R_1 + k R_1} V_s = \frac{k}{1+k} V_s \\ U_3 &= \frac{k \cdot R_2}{R_2 + k R_2} V_s = \frac{k}{1+k} V_s \end{aligned} \right\} \Rightarrow U_2 = U_3$$

(2)

Let's add a resistor:

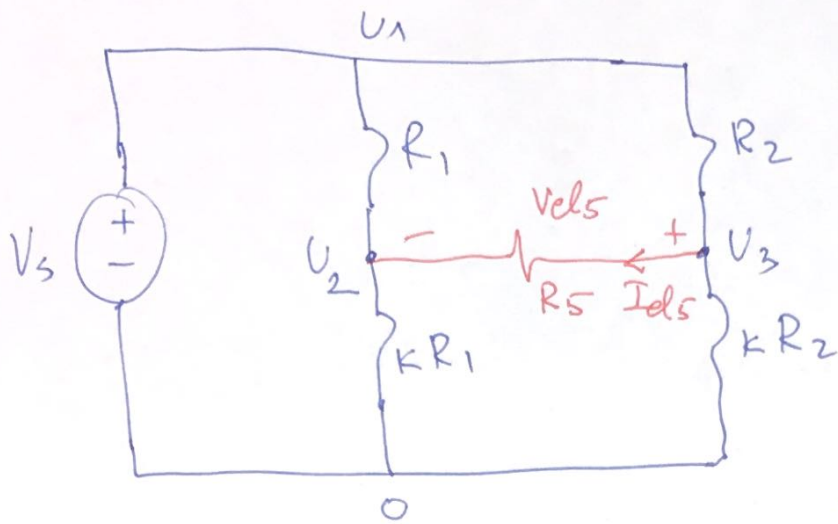

$$V_{e5} = U_3 - U_2 \quad (\text{voltage def})$$

$$V_{e5} = R_5 \cdot I_{e5} \quad (\text{elem. I-V def})$$

Bold assumption:

$$V_{e5} = 0$$


$$\text{If } V_{e5} = 0 \Rightarrow I_{e5} = \frac{V_{e5}}{R_5} \overset{0}{=} 0$$

$$\text{solved previously for } I_{e5} = 0 \Rightarrow U_2 = U_3 = \frac{k}{1+k} V_s$$


$$\Rightarrow V_{e5} = 0 \quad \text{b.c. } V_{e5} = U_3 - U_2 = \frac{k}{1+k} V_s - \frac{k}{1+k} V_s = 0$$

(L3) 2D Touchscreen:


Top view:

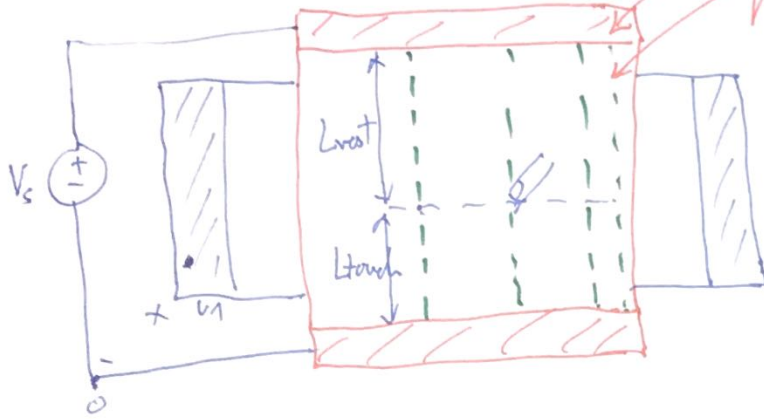

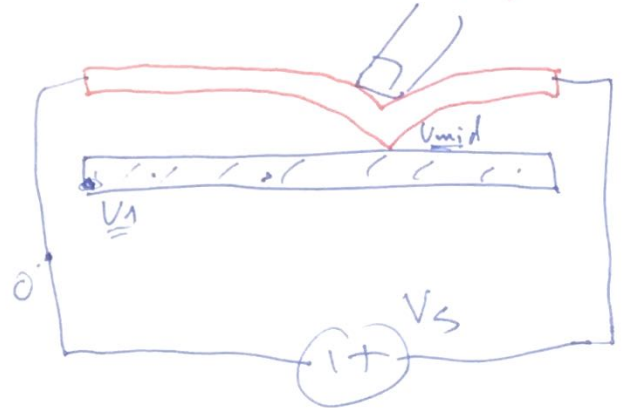good conductor (low ϵ) - model as wires
poor conductor (high ϵ) - model as $R's$



Model:

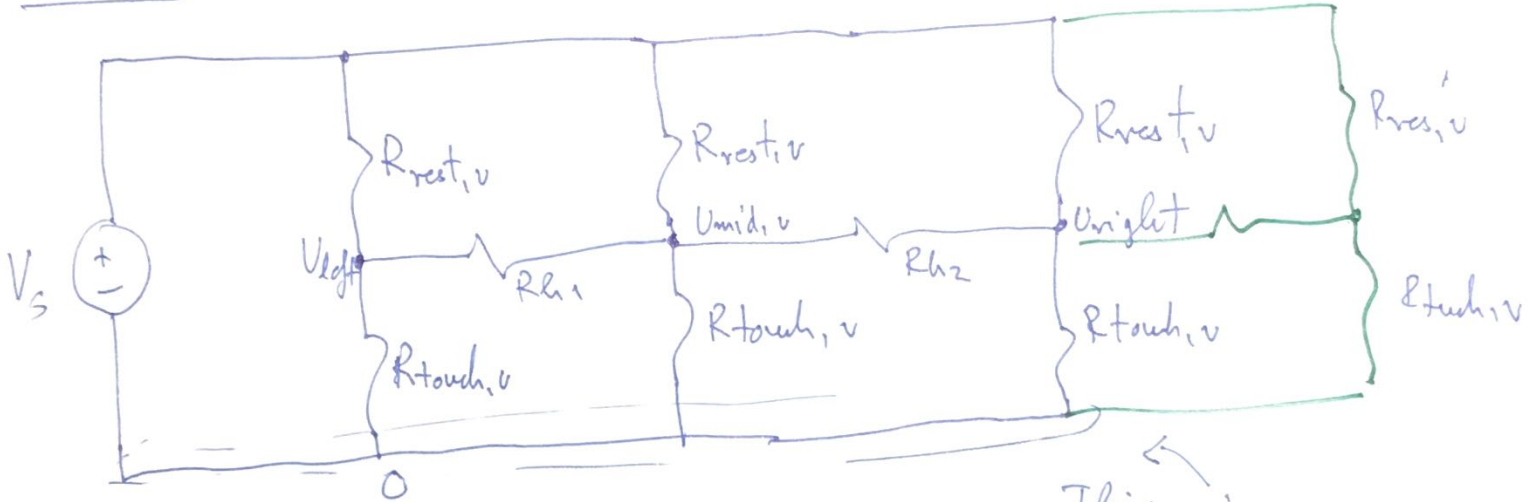

$$U_{mid,v} = \frac{R_{touch,v}}{R_{rest,v} + R_{touch,v}} \cdot V_s$$

$$= \frac{\epsilon \cdot \frac{L_{touch,v}}{A}}{\epsilon \cdot \frac{L_{rest,v}}{A} + \epsilon \cdot \frac{L_{touch,v}}{A}} \cdot V_s$$

This is our "interesting" circuit b/c all resistors are proportional in all vertical branches.

$$L_{rest,v} + L_{touch,v} =$$

$$= L_{1,v} \left[U_{mid,v} = \frac{L_{touch,v}}{L_{1,v}} \cdot V_s \right]$$

vertical finger position info

$$U_1 = U_{mid,v}$$



$$U_{mid,v} = U_{left} = U_{right}$$

$$I_{Rh1} = 0, I_{Rh2} = 0$$

voltage div to solve for $U_{mid,v}$

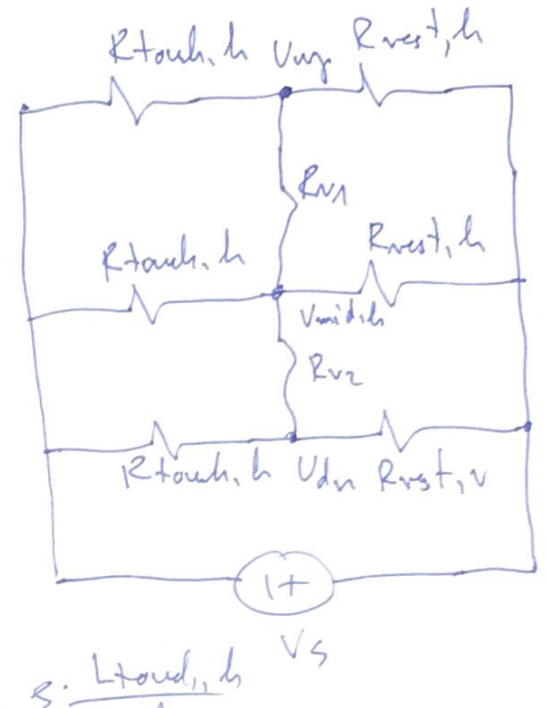
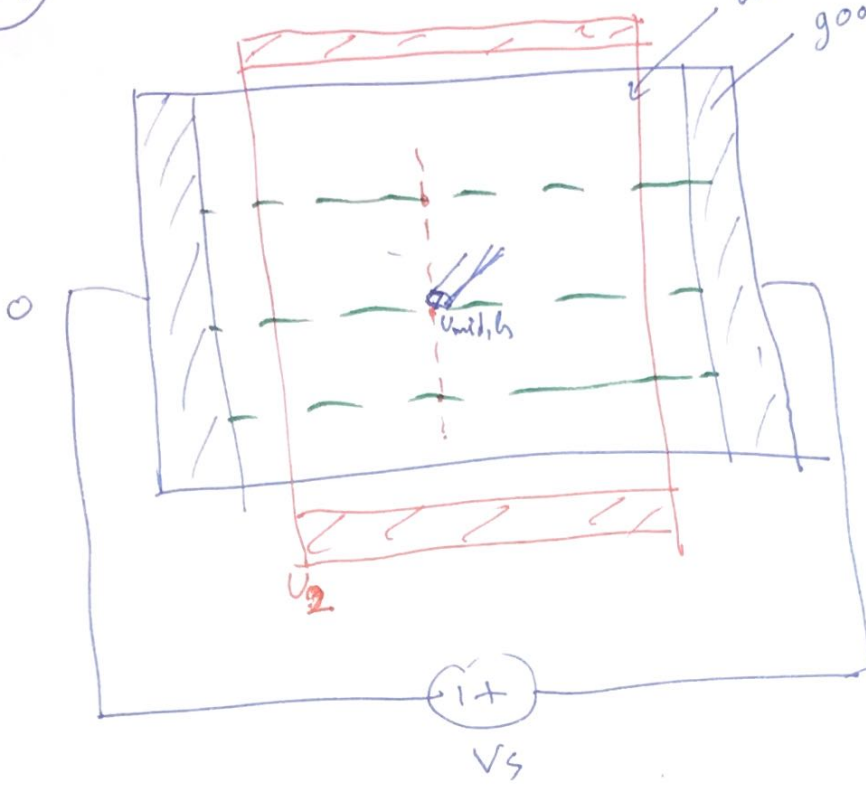
Q4

bad conductor (P's)
good conductor (wire)



$$U_{avg} = U_{dn} = U_{mid,h} = \frac{R_{touch,h}}{R_{touch,h} + R_{rest,h}} \cdot V_s$$

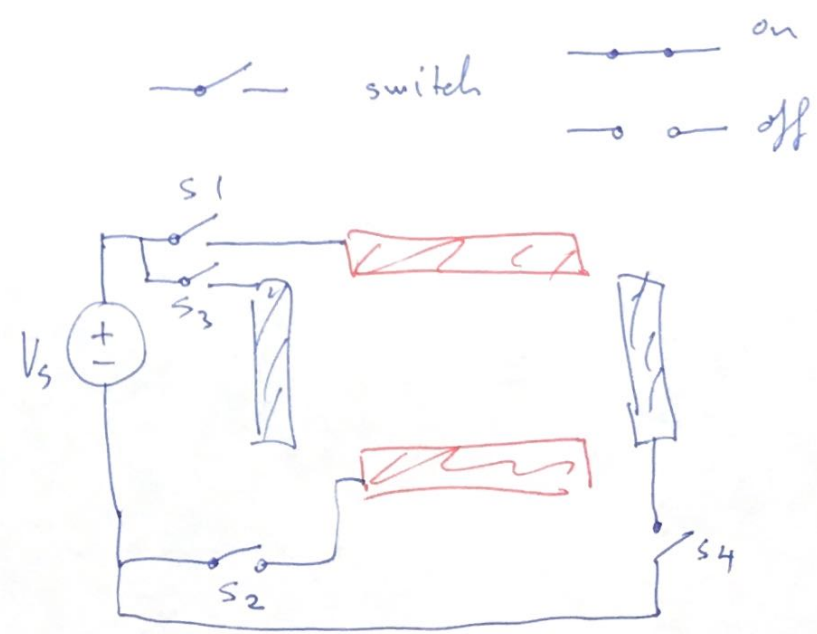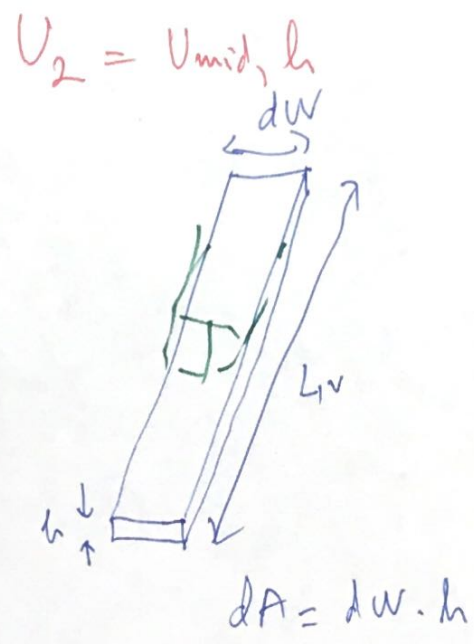
$$U_{mid,h} = \frac{\epsilon_0 dW \cdot V_s}{L_1}$$



Step 1: S_1, S_2 on, S_3, S_4 off
 Step 2: S_1, S_2 off, S_3, S_4 on

(25)

Faster circuit analysis:

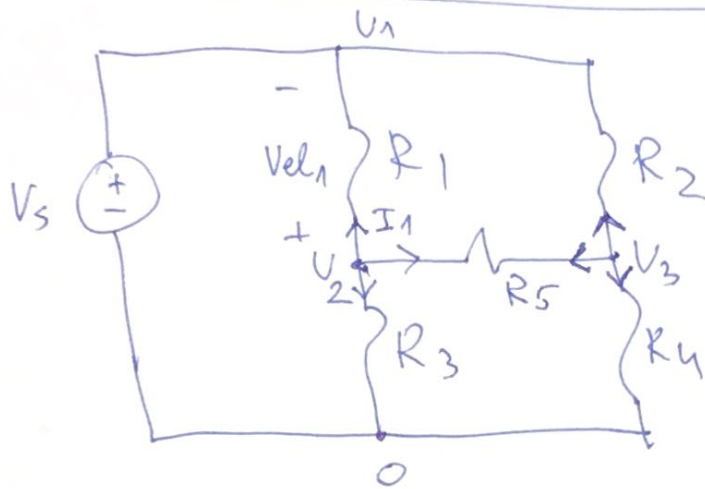

step 1: Label the nodes (unknowns & ref node)

step 2: Write the equations for nodes that have voltage source between them.

$$U_1 - 0 = V_s \Rightarrow \boxed{U_1 = V_s}$$

step 3: Write KCLs & IR element combo including any possible current sources

For node 2: $I_1 = \frac{U_2 - U_1}{R_1} = \frac{V_{el1}}{R_1}$ (elem. def)

Magic:


Apply to U_2 : $\frac{U_2 - U_1}{R_1} + \frac{U_2 - 0}{R_3} + \frac{U_2 - U_3}{R_5} = 0$

Apply to U_3 : $\frac{U_3 - U_1}{R_2} + \frac{U_3 - U_2}{R_5} + \frac{U_3 - 0}{R_4} = 0$

From U_2 : $U_2 \left(\frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_5} \right) - \frac{1}{R_5} \cdot U_3 = \frac{V_s}{R_1}$

From U_3 : $U_2 \left(-\frac{1}{R_5} \right) + U_3 \left(\frac{1}{R_2} + \frac{1}{R_5} + \frac{1}{R_4} \right) = \frac{V_s}{R_2}$

(26)

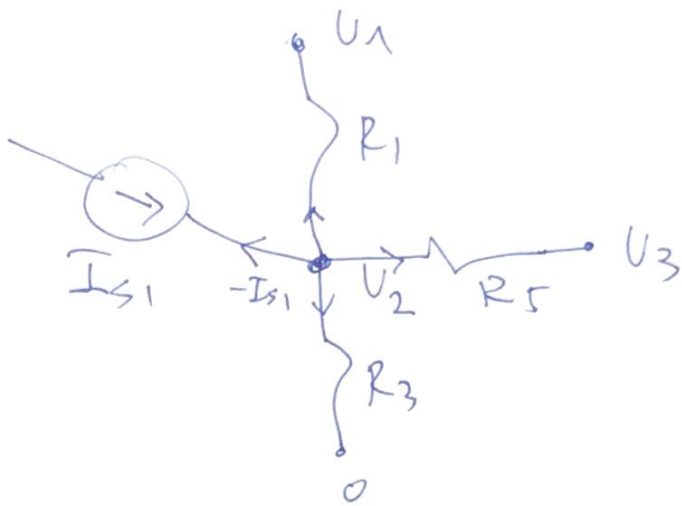

From U_2 :

$$\frac{U_2 - U_1}{R_1} + \frac{U_2 - U_3}{R_5} + \frac{U_2 - 0}{R_3} - I_{s1} = 0$$

"Nodal" analysis