

Today: * Superposition } Circuit Jedi
 Note 15 * Equivalence } techniques

Goal: Want to design interesting systems
 - Need the tools that provide insight

Reminder: Circuit analysis objective:

Find $\vec{x} = \begin{bmatrix} I_1 \\ \vdots \\ I_m \\ V_1 \\ \vdots \\ V_k \end{bmatrix}$ for some ckt matrix A and some stimulus vector $\vec{b} = \begin{bmatrix} I_{s1} \\ \vdots \\ I_{sl} \\ V_{s1} \\ \vdots \\ V_{s_{m+k-l}} \end{bmatrix}$ \leftarrow independent sources

$A\vec{x} = \vec{b} \Rightarrow \vec{x} = A^{-1}\vec{b}$

formulation solution

$I_i = \alpha_1 I_{s1} + \dots + \alpha_l I_{sl} + \dots + \alpha_{m+k-l} V_{s_{m+k-l}}$

and $V_j = \beta_1 I_{s1} + \dots + \beta_{m+k-l} V_{s_{m+k-l}}$

lin. combination of sources

$I_i = I_{i,1} + \dots + I_{i,l} + \dots + I_{i,m+k}$




\Rightarrow can calculate I_i by calculating $I_{i,1} \dots I_{i,m+k}$ separately (i.e. by nulling all the other sources)

(2)




What does it really mean to "null a source"?



\Rightarrow
 $V_s = 0$

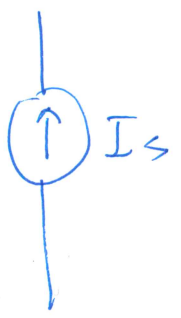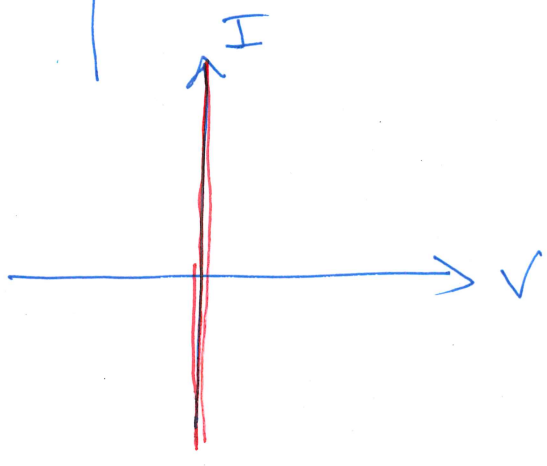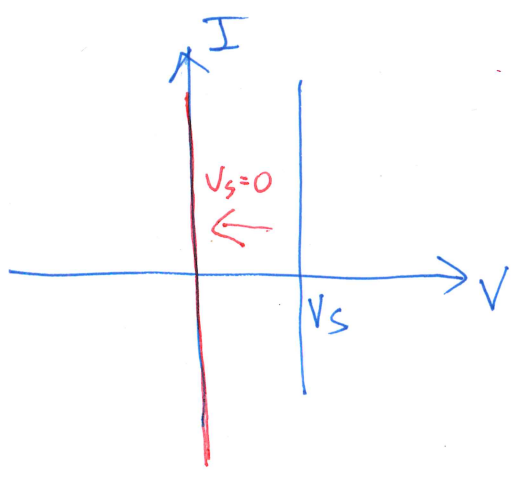


\Rightarrow
 $I_s = 0$

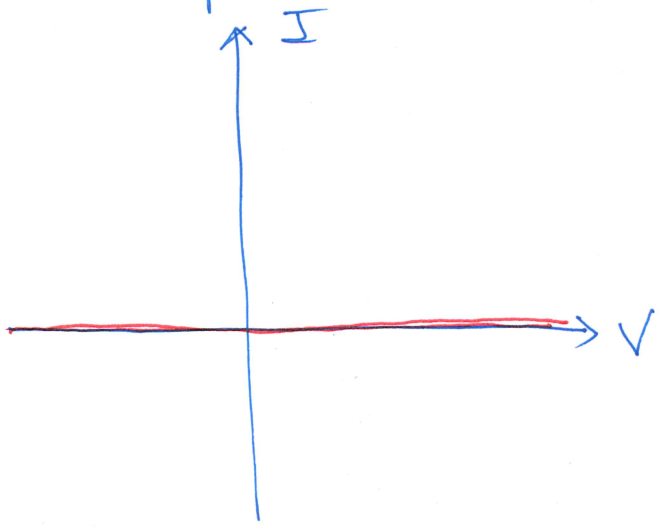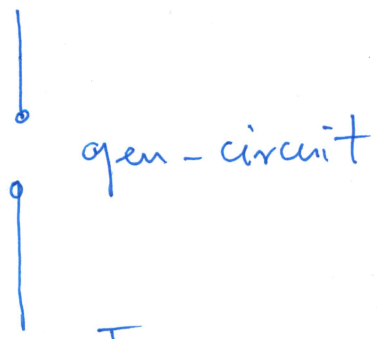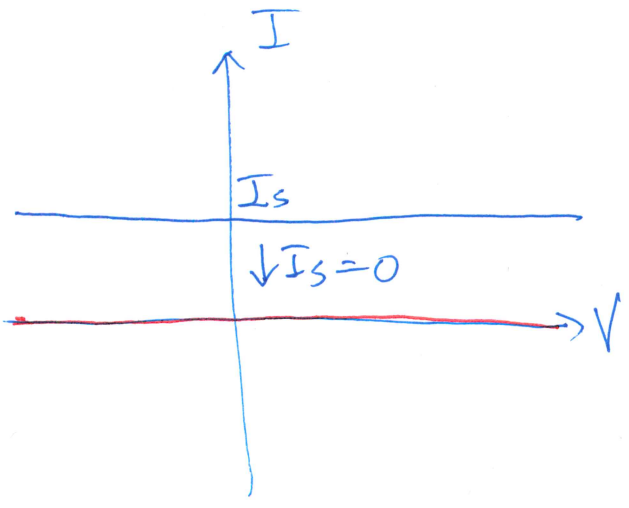

Q3

Superposition: Find I's and V's by turning independent sources "on" one at a time and solving the circuit.

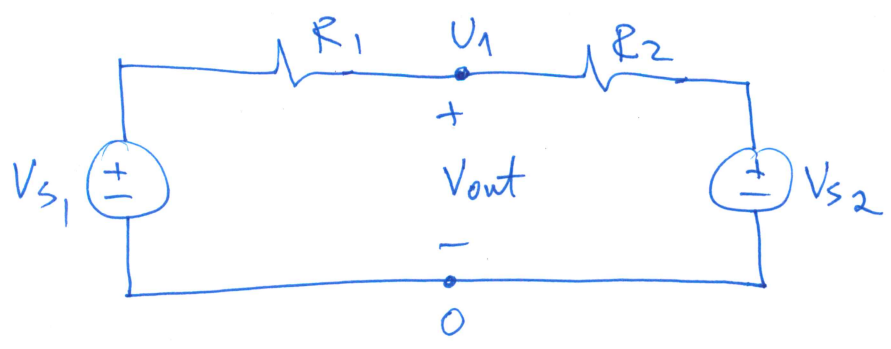
Example: "Mystery circuit" function \rightarrow voltage
summer



$$U_1 - 0 = V_{out}$$

$$U_1 = V_{out}$$

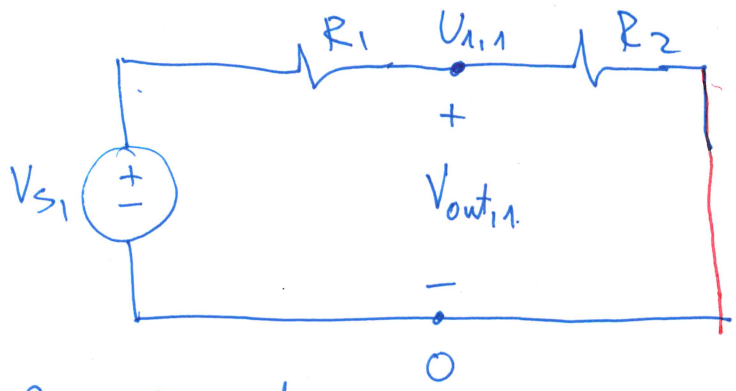
step 1: Compute a response to V_{s1} (set $V_{s2} = 0$)



voltage divider 😊

$$V_{out,1} = \frac{R_2}{R_1 + R_2} \cdot V_{s1}$$

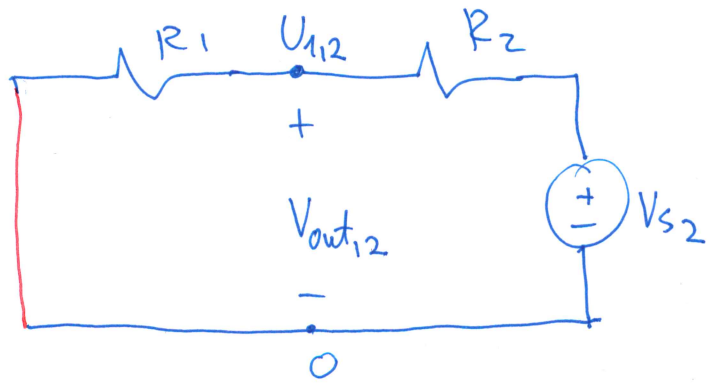step 2: Compute a response to V_{s2} (set $V_{s1} = 0$)



voltage divider 😊


$$V_{out,2} = \frac{R_1}{R_1 + R_2} \cdot V_{s2}$$

$$V_{out} = V_{out,1} + V_{out,2} = \underbrace{\frac{R_2}{R_1 + R_2}}_{\alpha < 1} V_{s1} + \underbrace{\frac{R_1}{R_1 + R_2}}_{\beta < 1} V_{s2}$$



$$U_1 = U_{1,1} + U_{1,2}$$

(4)

Equivalence:


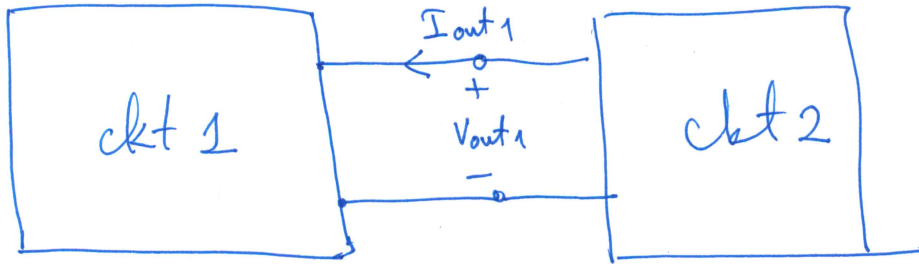


||)

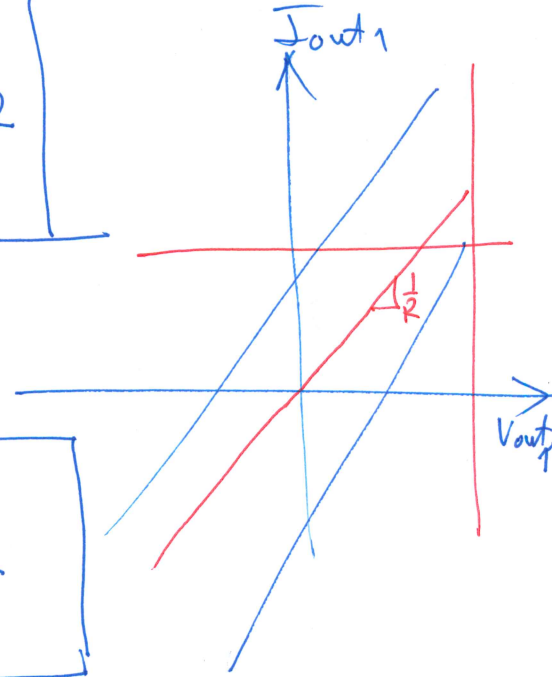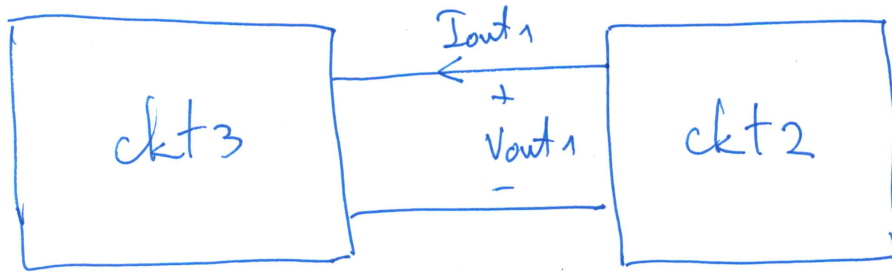

In circuits, two elements are equivalent if they have the same I-V characteristics.

example:

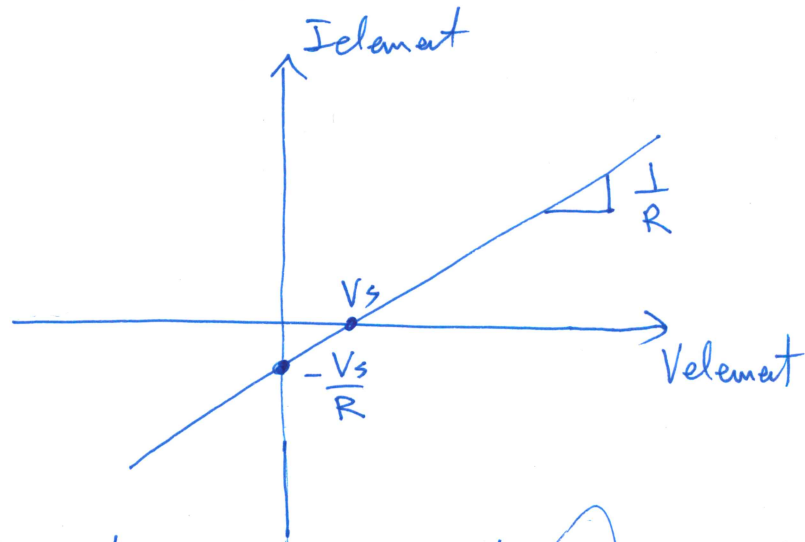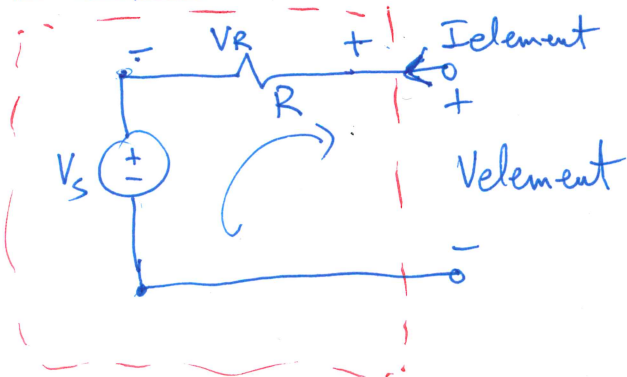


$$\frac{V_{element} - V_s}{R} = I_{element} \Rightarrow I_{element} = \left(\frac{1}{R}\right) V_{element} - \frac{V_s}{R}$$

KVL: $V_s + V_R = V_{element}$


$V_R = V_{element} - V_s$

$I_{element} \cdot R = V_{element} - V_s$



25

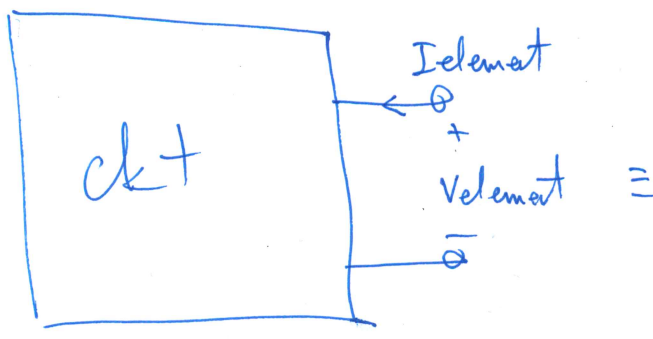

Thevenin equivalent:

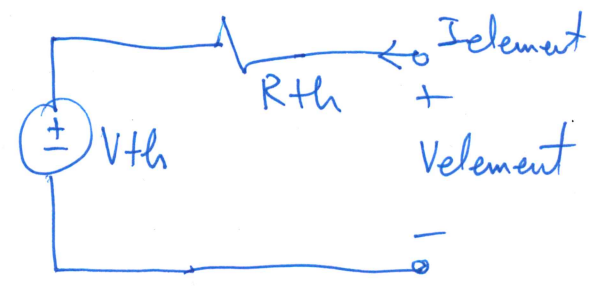

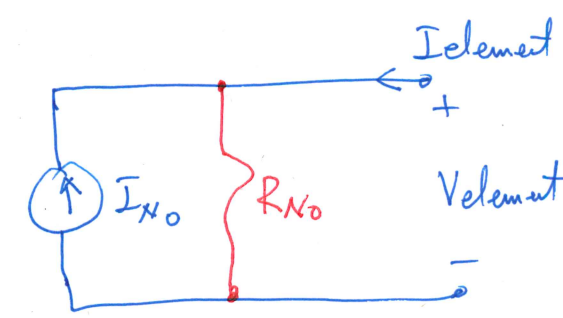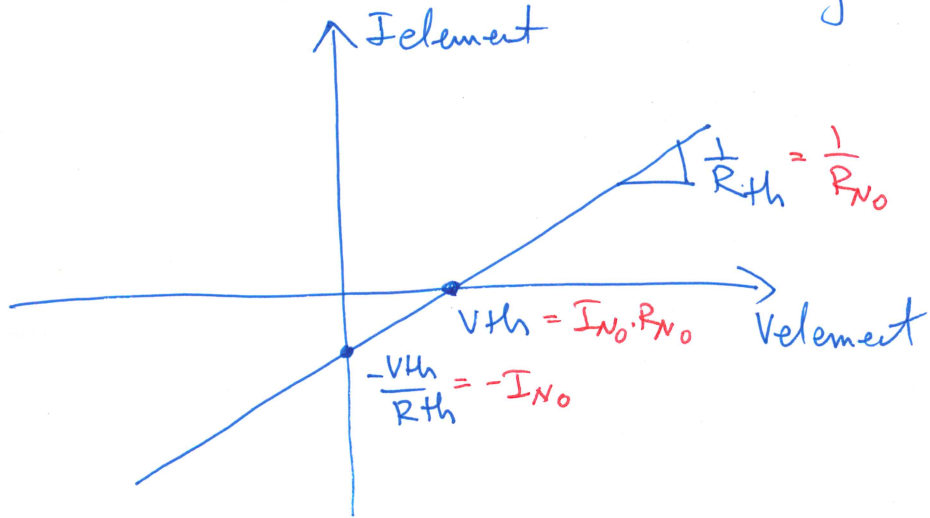
Need a min. of two elements (a resistor and a source) to create any I-v line.




Norton equivalent:

To find V_{th} : "Connect" an "open-circuit", across two terminals and measure $V_{open-circuit} = V_{th}$

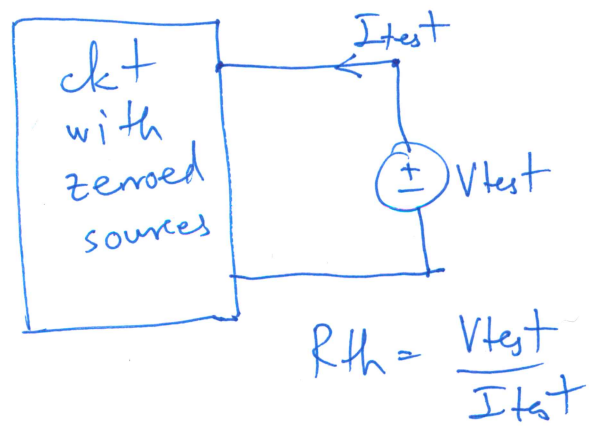To find R_{th} : Zero-out ("null") all independent sources (to find a slope)




or

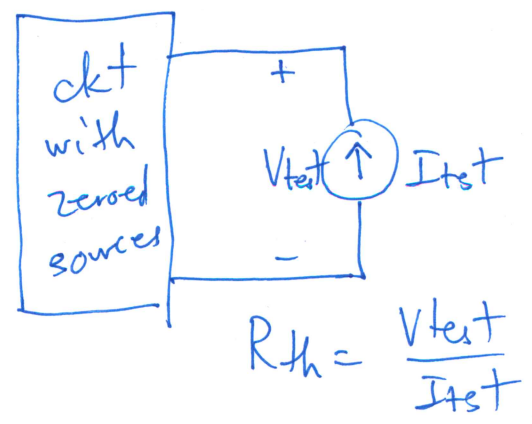


16



Dependent sources :

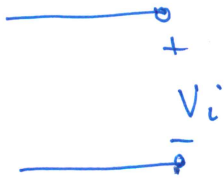


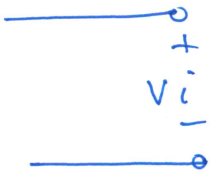
Voltage - controlled
voltage source (VCVS)



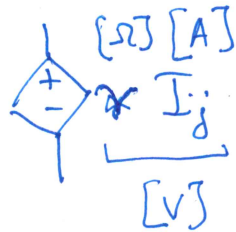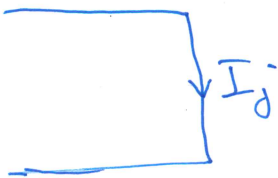Voltage - controlled current - source
(VCCS)



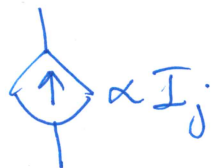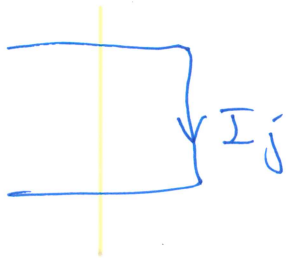
Current - controlled
voltage - source
(CCVS)




Current - controlled
current - source
(CCCS)

(7)

Example 1:

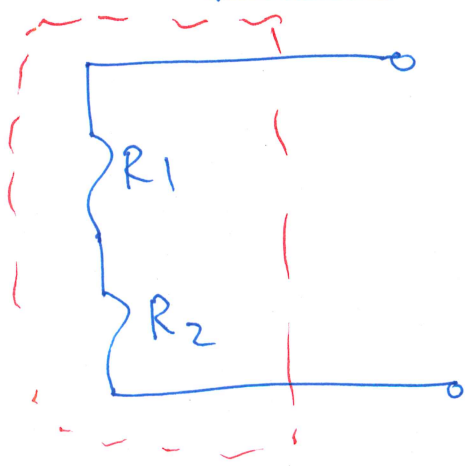


=>

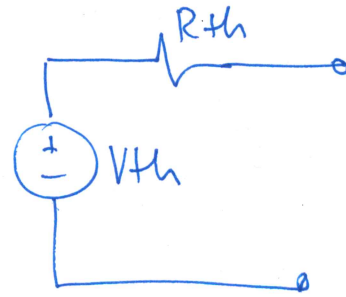


step 1: attach o.c. & measure $V_{th} = V_{o.c.}$

$$V_{th} = V_{o.c.} = 0$$

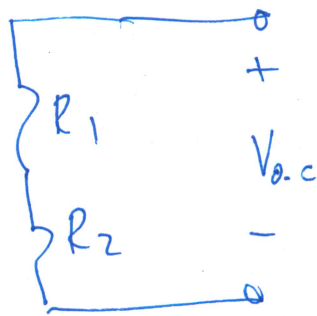

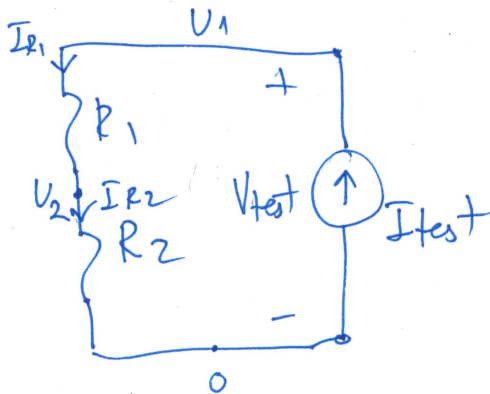step 2: Null sources & apply test current



$$V_{test} = I_{test} \cdot R_2 + I_{test} \cdot R_1$$

$$= (R_1 + R_2) I_{test}$$


$$R_{th} = \frac{V_{test}}{I_{test}} = R_1 + R_2$$

KCL:

$$\begin{cases} I_{R1} = I_{test} \\ I_{R2} = I_{R1} \end{cases}$$


"in series" means that same current flows through the elements in series.

(8)

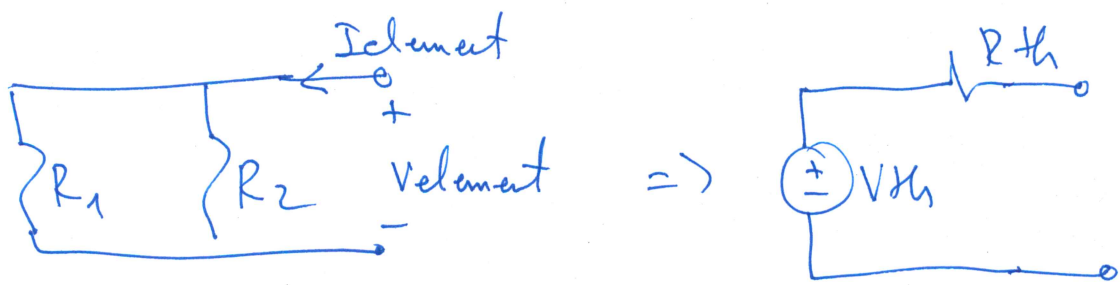

step 1: $V_{Th} = 0$

step 2:

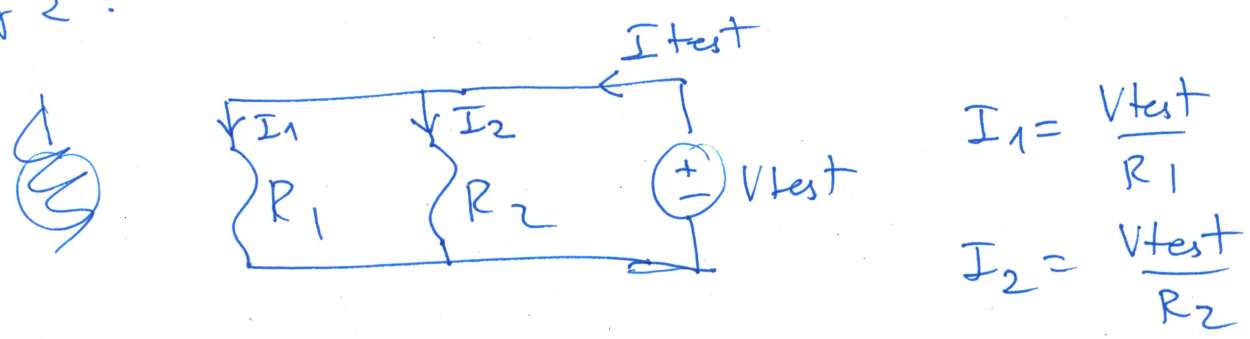

KCL: $I_1 + I_2 = I_{test}$

$$V_{test} \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = I_{test}$$

$$R_{Th} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2} = R_1 \parallel R_2$$

↑
parallel operator



"In parallel" means voltage across them is the same.