


Today:
Note 19

- * NFB inspection
- * Summing op-amp / Neuron
- * Cascading ckt blocks (building larger functions)

Determining the polarity of the NFB:

- 1 Turn-off all independent sources
- 2 Apply a disturbance at the output & follow the path through the feedback to see if the disturbance is suppressed at the output.


example:

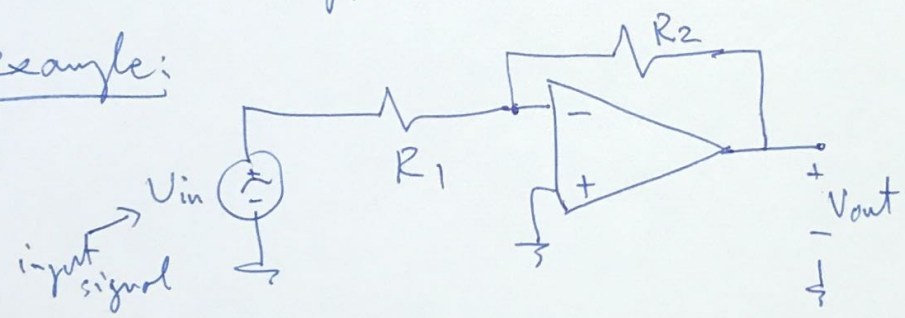


check for NFB:

step 1:

Null the indep. sources

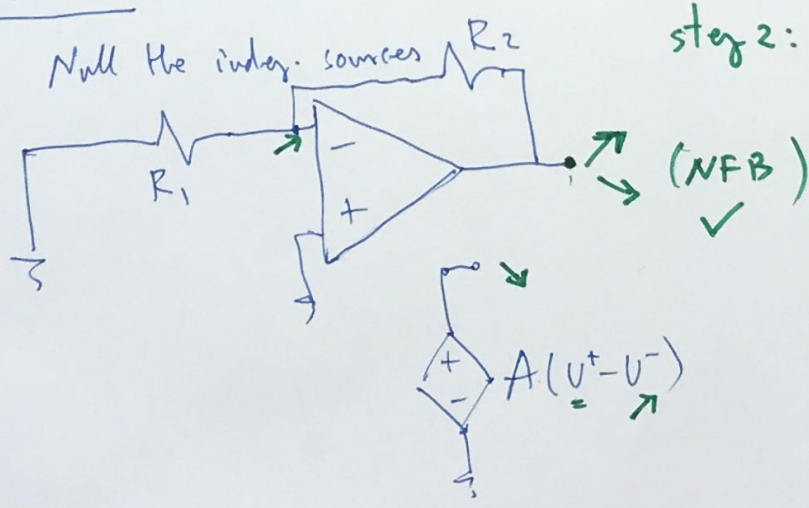


step 2: Apply disturbance to output

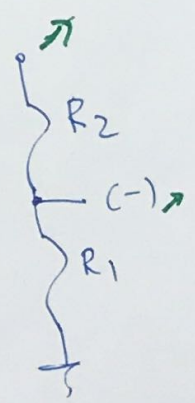

Since NFB => can apply GR#2 => $U^- = U^+$

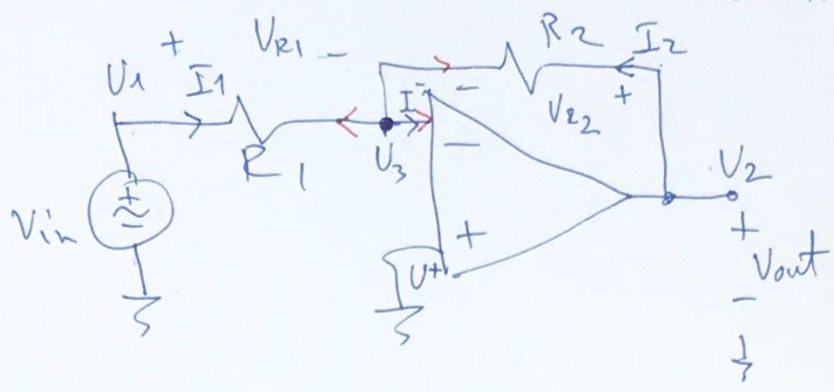(2)

Solve: NFB \Rightarrow GR#2 applies $U^+ = U^-$



solve for V_{out} as a fun. of V_{in} .

$U_1 = V_{in}$

$U_2 = V_{out}$

$U_3 = 0$ (ckt is in NFB \Rightarrow GR#2 applies $U^+ = U^-$)

also $U^+ = 0$ (in this ckt) $\Rightarrow U^- = 0$

$U_3 = U^-$

$V_{R1} = I_1 R_1$ } (elem. equations)

$V_{R2} = I_2 R_2$

$V_{R1} = V_1 - U_3 = V_{in}$ (voltage def)

$V_{R2} = V_2 - U_3 = V_{out}$

(KCL) $-I_1 + (-I_2) + I^- = 0$ also $I_1 + I_2 = I^-$

GR#1: $I^- = 0 \Rightarrow I_1 + I_2 = 0$

$V_{in} = I_1 R_1, V_{out} = I_2 R_2$

$\frac{V_{in}}{R_1} + \frac{V_{out}}{R_2} = 0 \Rightarrow V_{out} = -\frac{R_2}{R_1} V_{in}$

$A_v = \frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$ (inverting amplifier)

↑ voltage gain of the amplifier in NFB

(3)

A faster way:

GR2: $V^+ = V^-$ since in NFB, $V_3 = V^- \Rightarrow V_3 = 0$
 $V^+ = 0$


GR1 & KCL:

$$\frac{V_3 - V_1}{R_1} + \frac{V_3 - V_2}{R_2} + I^- = 0$$

$$-\frac{V_{in}}{R_1} - \frac{V_{out}}{R_2} = 0$$


$$V_{out} = -\frac{R_2}{R_1} V_{in}$$

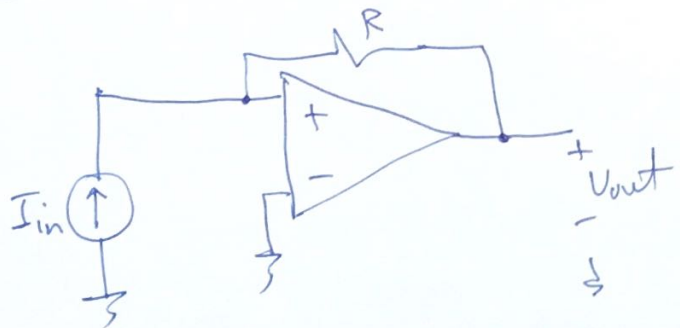Another example: (trans-resistance amplifier)





check NFB:

GR#1: $I^+ = 0$ always
 $I^- = 0$

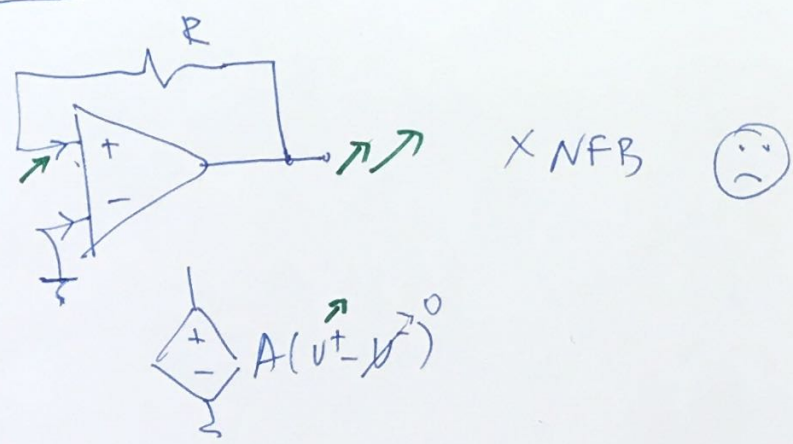

24

Flip the polarity :

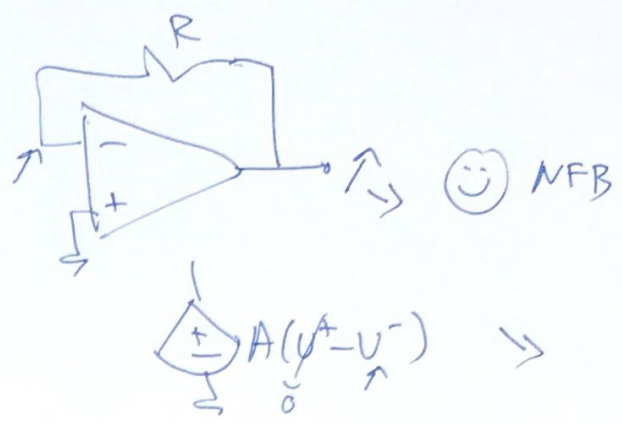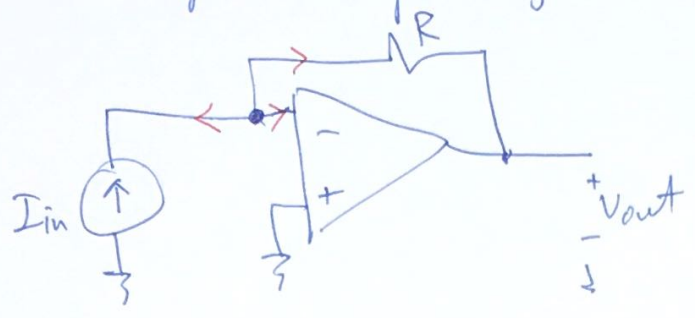

✓ NFB : $U^+ = U^-$
 $U^+ = 0$ } $\Rightarrow U^- = 0$


$(-I_{in}) + \frac{U^- - V_{out}}{R} + I = 0$ GR#1

$-\frac{V_{out}}{R} = I_{in}$


$V_{out} = -RI_{in}$

$\frac{V_{out}}{I_{in}} = -R$

25 Another example:

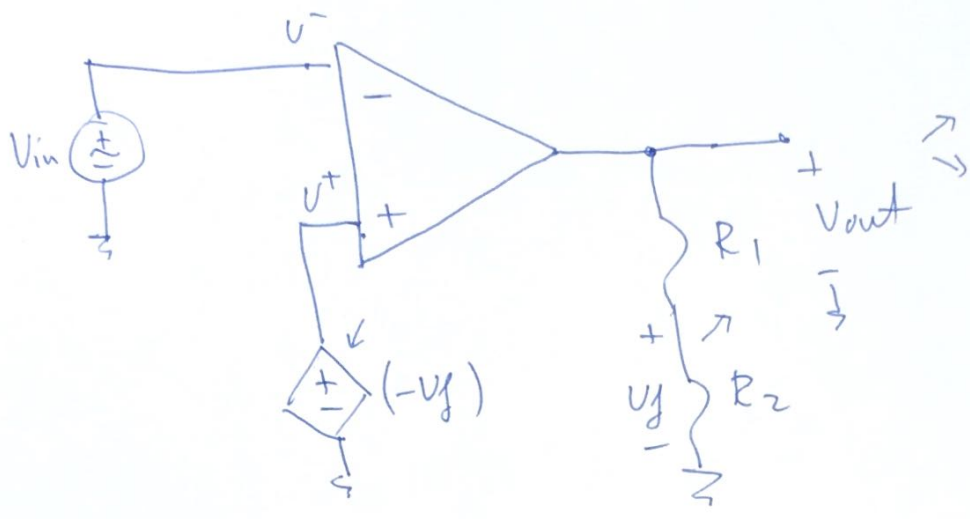

check NFB:

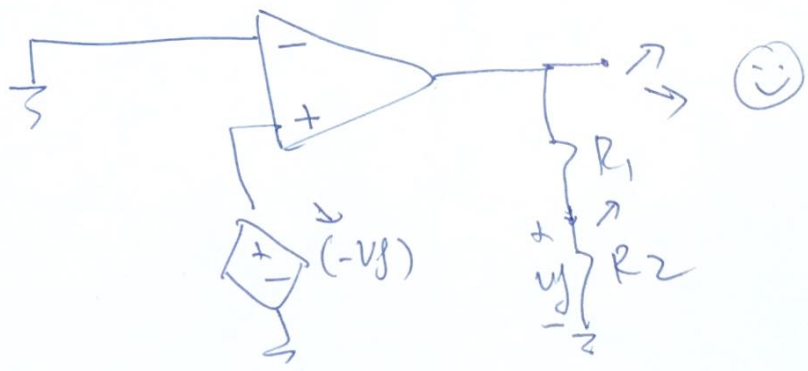


solve: NFB: $U^+ = U^- \Rightarrow \left. \begin{matrix} U^+ = -V_f \\ U^- = V_{in} \end{matrix} \right\} \underline{-V_f = V_{in}}$

$V_f = \frac{R_2}{R_1 + R_2} V_{out} \rightarrow -V_{in} = \frac{R_2}{R_1 + R_2} V_{out}$

$V_{out} = - \left(1 + \frac{R_1}{R_2} \right) V_{in}$

$A_v = \frac{V_{out}}{V_{in}} = - \left(1 + \frac{R_1}{R_2} \right)$

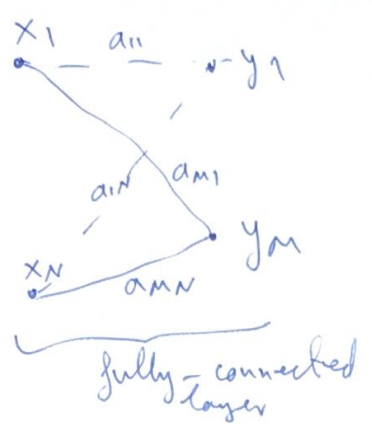
Q6 Building energy-efficient deep neural network:



$$\vec{y} = A \vec{x}$$

$$\begin{bmatrix} y_1 \\ \vdots \\ y_M \end{bmatrix} = \begin{bmatrix} a_{11} & \dots & a_{1M} \\ \vdots & & \vdots \\ a_{M1} & \dots & a_{MN} \end{bmatrix} \begin{bmatrix} x_1 \\ \vdots \\ x_N \end{bmatrix}$$

(inverting summer)

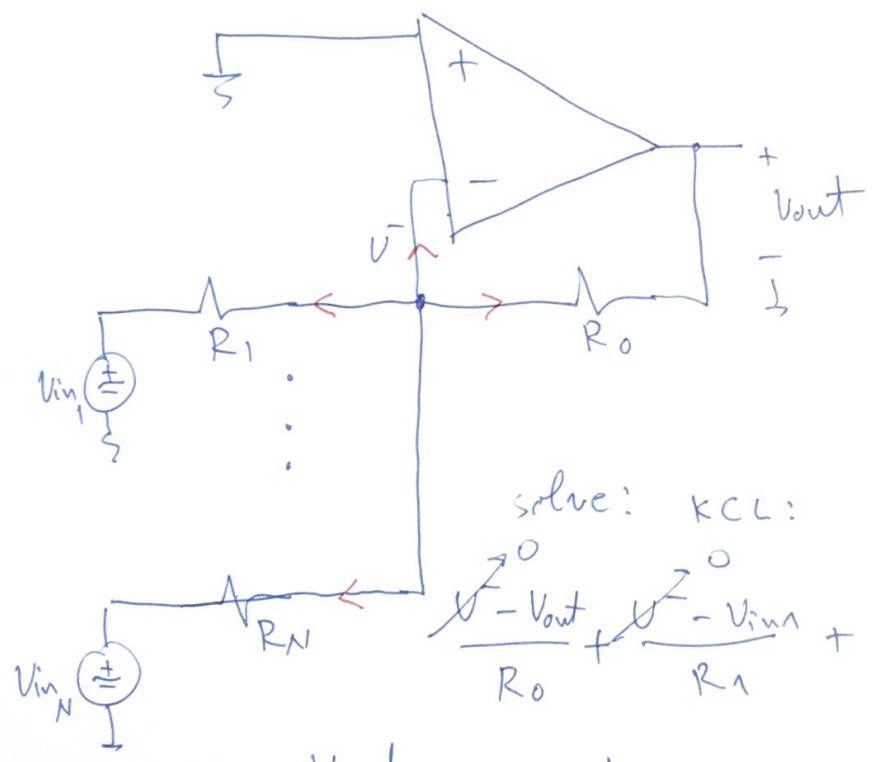

$$V_{out} = -\frac{R_o}{R_1} V_{in1} - \dots - \frac{R_o}{R_N} V_{inN}$$

solve: KCL:

$$\frac{0 - V_{out}}{R_o} + \frac{0 - V_{in1}}{R_1} + \dots + \frac{0 - V_{inN}}{R_N} + I = 0$$

(G2#2)
u₂ = 0

$$\frac{V_{out}}{R_o} = -\frac{1}{R_1} V_{in1} + \dots + \left(-\frac{1}{R_N}\right) V_{inN}$$


$$V_{out} = \left(-\frac{R_o}{R_1}\right) V_{in1} + \dots + \left(-\frac{R_o}{R_N}\right) V_{inN}$$

\uparrow \uparrow \uparrow \uparrow
 y_1 a_{11} x_1 a_{1N} x_N


(7)

Think in block diagrams:

Concept:

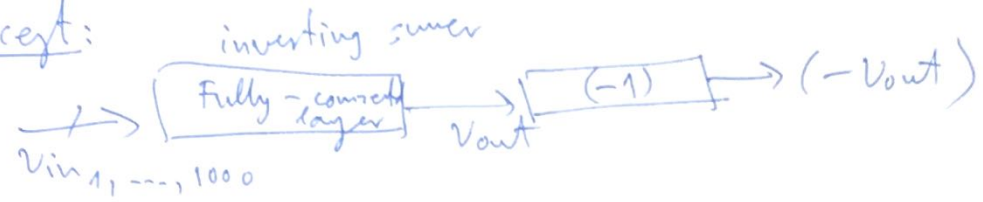

Implement:

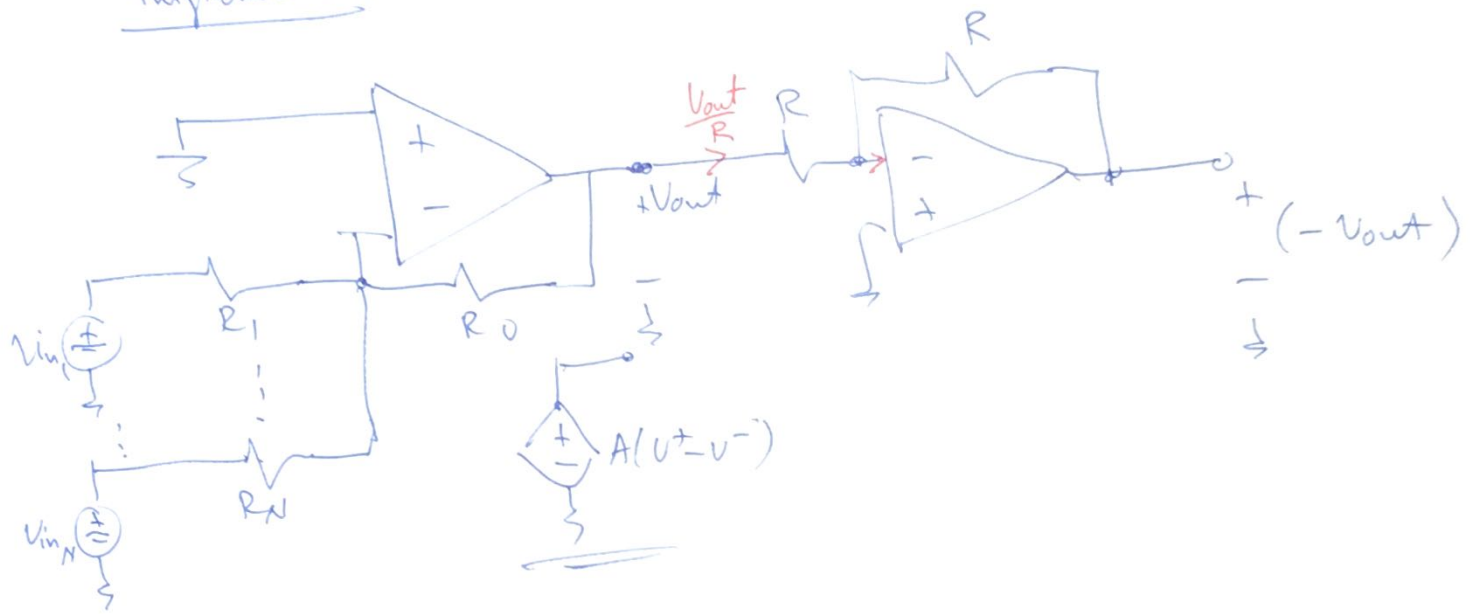

Cascading the blocks (sof way):

