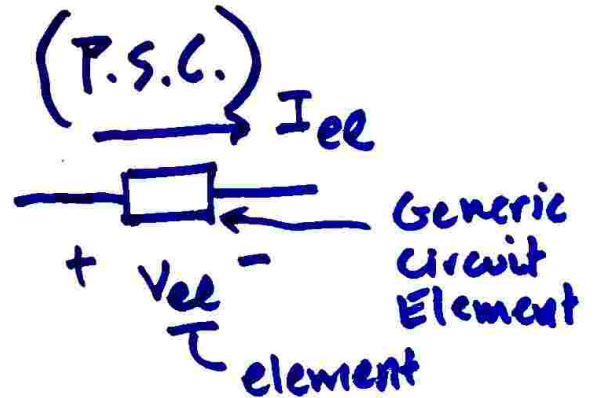


Passive Sign Conventio



Approach to Circuit Analysis :

- KCL, KVL equations
- Component equations (Ohm's Law)

Technique :

Node Voltage Analysis (NVA)

(Often implemented by computer programs like SPICE, which was invented at Berkeley)

# IEEE MILESTONE IN ELECTRICAL ENGINEERING AND COMPUTING

SPICE (Simulation Program with Integrated Circuit Emphasis)  
1969-1970

SPICE (Simulation Program with Integrated Circuit Emphasis) was created at UC Berkeley as a class project in 1969-1970. It evolved to become the worldwide standard integrated circuit simulator. SPICE has been used to train many students in the intricacies of circuit simulation. SPICE and its descendants have become essential tools employed by virtually all integrated circuit designers.

February 2011



## Procedure :

### STEP 1:

Choose a reference voltage  
i.e. GND,  $\perp$ ,  $\parallel$

### STEP 2:

Mark the known voltages

### STEP 3:

Mark the unknown voltages

### STEP 4:

Mark the element  $I_{el}$ ,  $V_{el}$

### STEP 5:

KCL for all nodes with  
unknown node voltages

$$I_{R_1} + I_{R_2} = \emptyset$$

### STEP 6:

Write the component equations

...



STEP 6:

Write the component eqns.

$$I_{R_1} = \frac{V_{R_1}}{R_1} \quad I_{R_2} = \frac{V_{R_2}}{R_2}$$

(ohm's law :  $V=IR$ )

Replace component voltages ( $V_{R_1}, \dots$ )  
with the node voltages ( $V_{n_1}$ )

$$V_{R_1} = V_{n_1} - \phi$$

$$V_{R_2} = V_{n_1} - V_s$$

Rewrite comp eqns in terms  
of node voltages

$$I_{R_1} = \frac{V_{R_1}}{R_1} = \frac{V_{n_1}}{R_1}$$

$$I_{R_2} = \frac{V_{R_2}}{R_2} = \frac{V_{n_1} - V_s}{R_2}$$

STEP 7:Substitution (6)  $\rightarrow$  (5)

Component eqns

KCL eqns

$$\frac{V_{n_1}}{R_1} + \frac{V_{n_1} - V_s}{R_2} = \phi$$


$$\text{"} \quad \text{"} \quad \text{"} = \phi$$

$$I_{R_1} + I_{R_2} = \phi$$

STEP 8:solve! (for  $V_{n_1}$ )

$$V_{n_1} = V_s \cdot \frac{R_1}{R_1 + R_2}$$

Voltage Divider

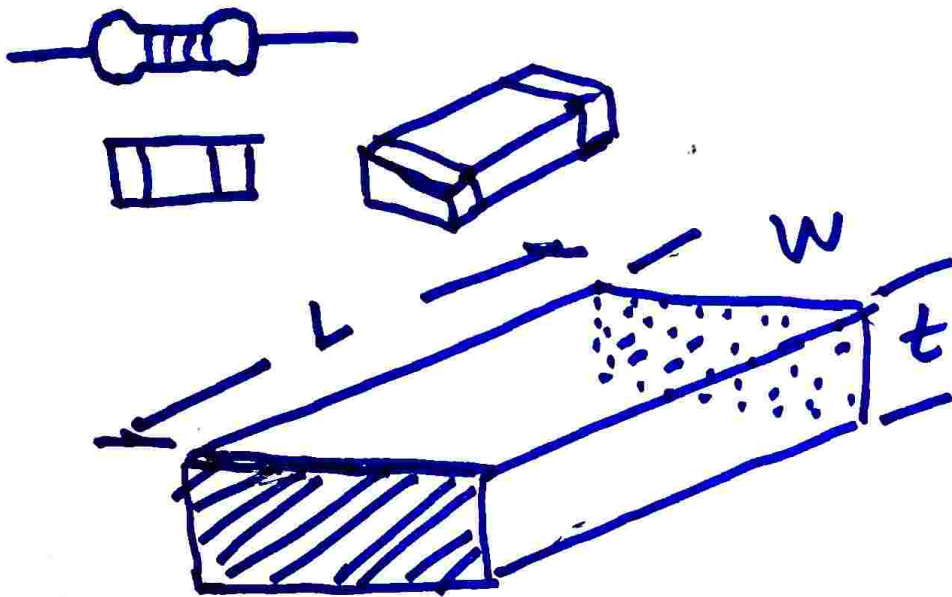
RESISTORS

$$R \propto \frac{L}{W \cdot t} = \frac{L}{A}$$

$$R = \rho \frac{L}{W \cdot t}$$

↑  
Resistivity  $[\Omega \cdot m]$



Material	Resistivity / $\Omega\text{m}$
copper	$1.7 \times 10^{-8}$
aluminium	$2.7 \times 10^{-8}$
graphite	$8.0 \times 10^{-6}$
silicon	$2.3 \times 10^3$
quartz	$5.0 \times 10^{10}$

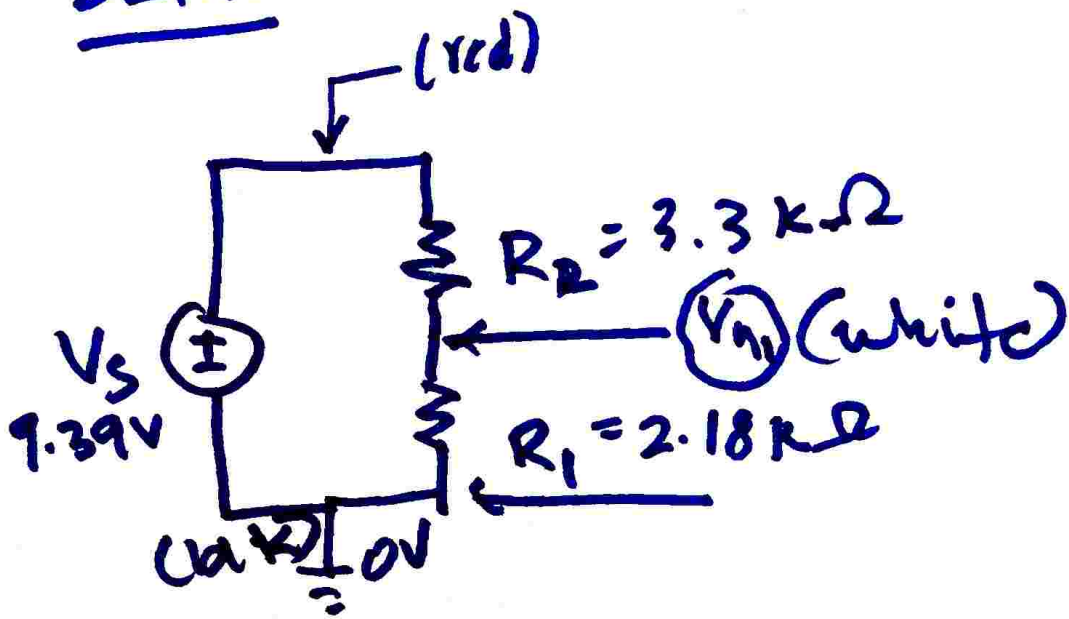DEMO

$$\begin{aligned} V_{m_1} &= V_S \left( \frac{R_1}{R_1 + R_2} \right) \\ &= 9.39\text{V} \left( \frac{2.18}{2.18 + 3.3} \right) \\ &= 3.74\text{V} \end{aligned}$$






# TOUCHSCREEN

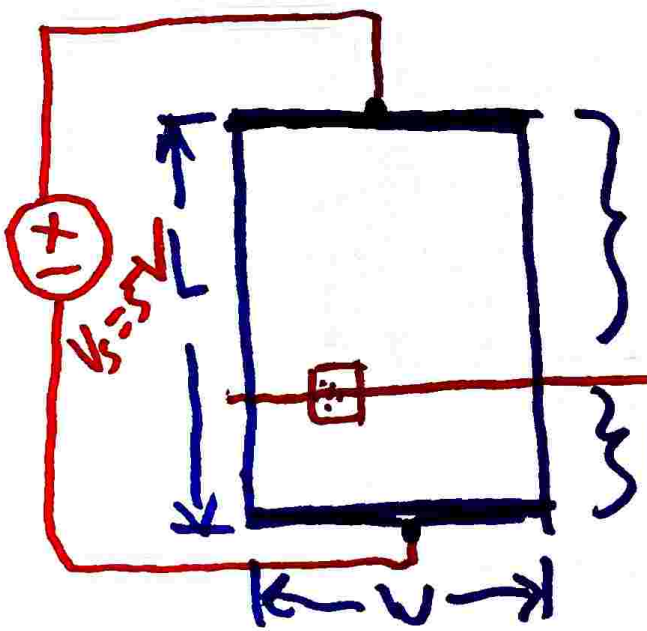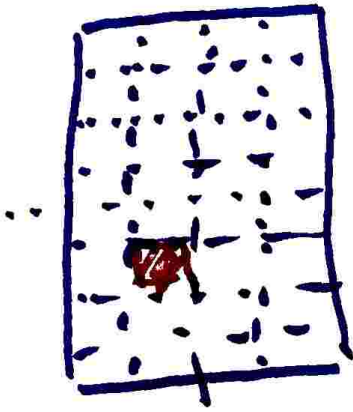

$$L_0 = L - y_1$$

$$L_0 = y_1$$

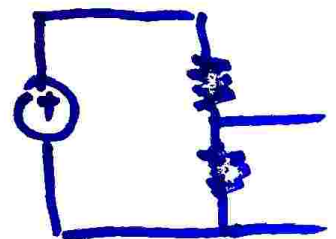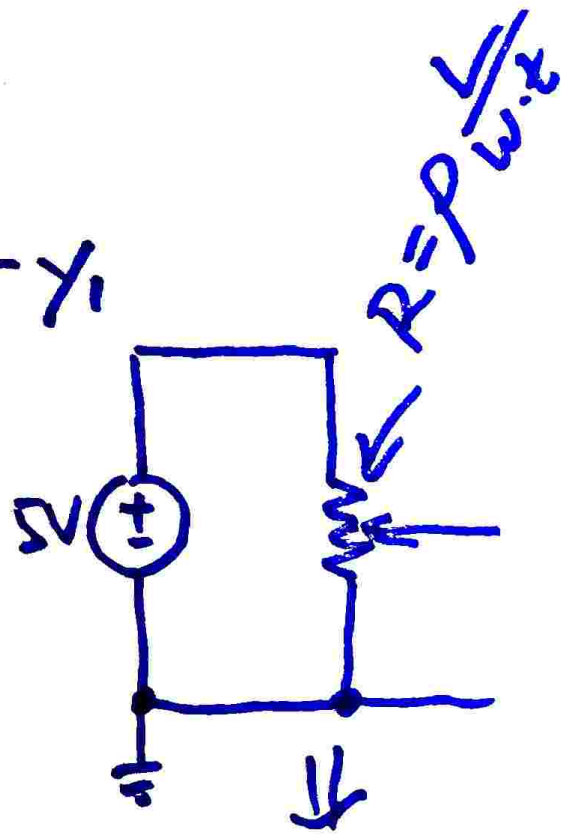

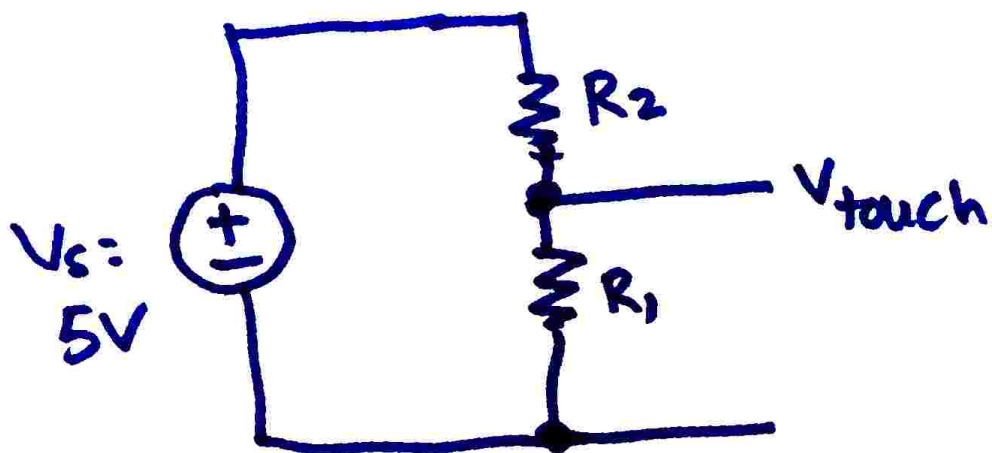


$$R_1 = \rho \frac{y_1}{w \cdot t}$$

$$R_2 = \rho \frac{L - y_1}{w \cdot t}$$

$$V_{\text{touch}} = V_s \frac{R_1}{R_1 + R_2}$$


$$V_{\text{touch}} = V_s \frac{y_1}{L}$$

# ID Touch Screen

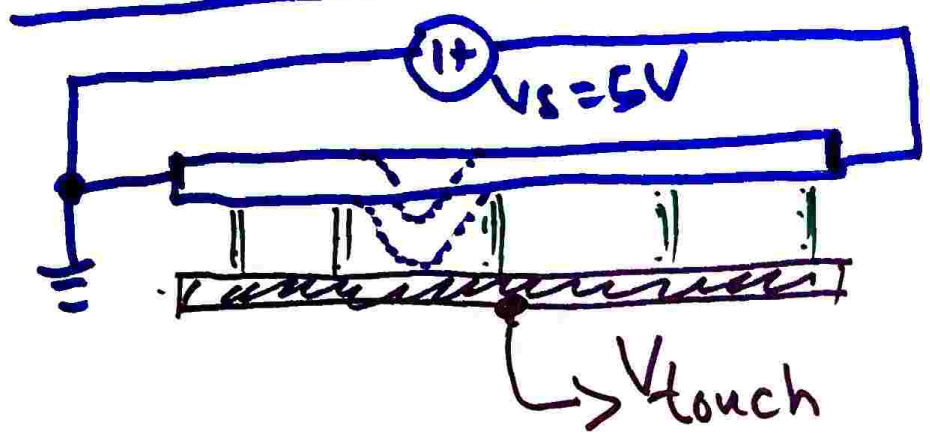


# Voltmeter / Ammeter / DMM

Digital Multi Meter

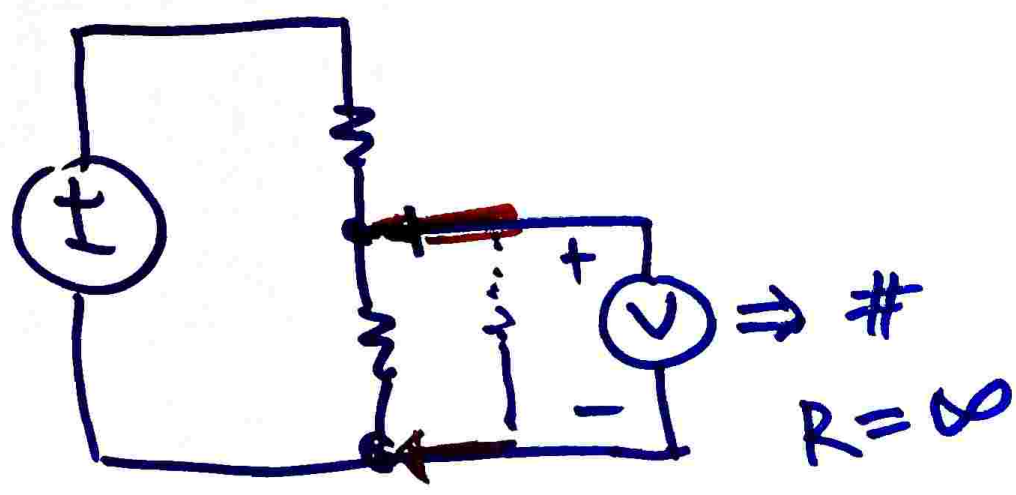

Ammeter

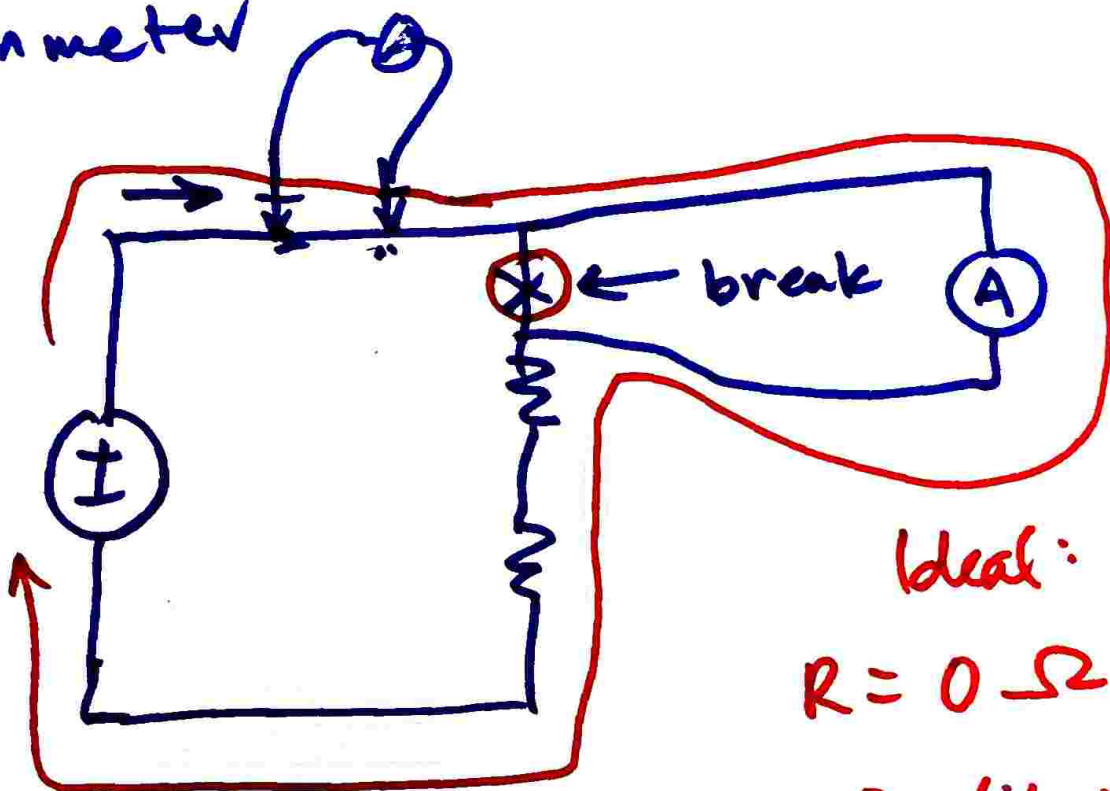

Ideal:

$$R = 0 \Omega$$

Reality:

$$0.1 \Omega$$