


EECS 16A, Module 2, Lecture 4

Topics

- Finish up 2D resistive touchscreen
- Equivalence
- Controlled Sources
- Superposition



2.4.2

2D Resistive Touch Screen

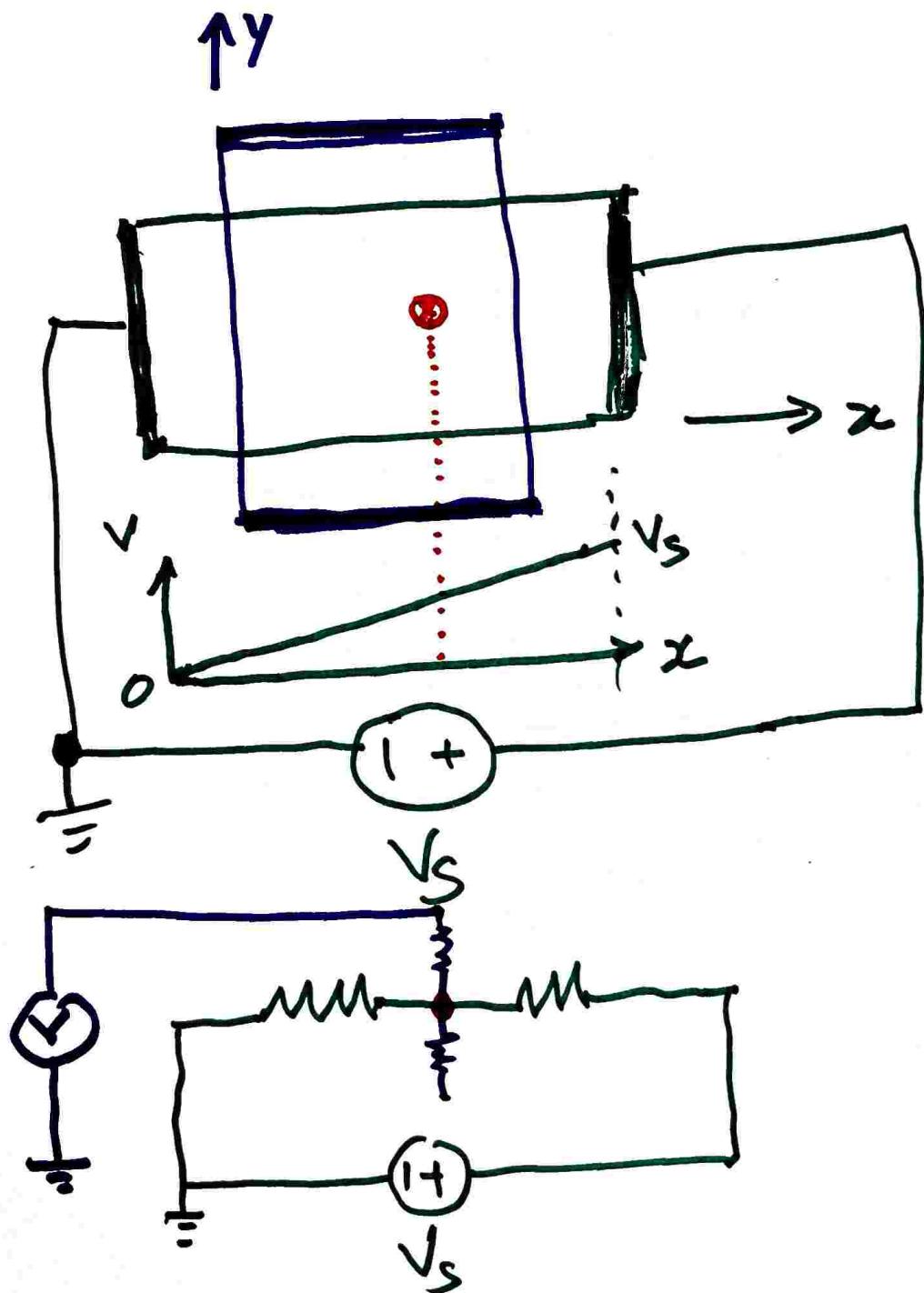


2.4.3


Equivalence

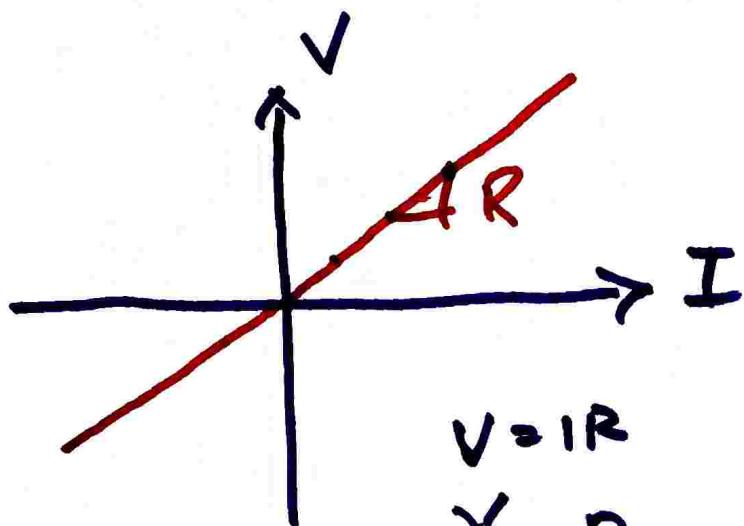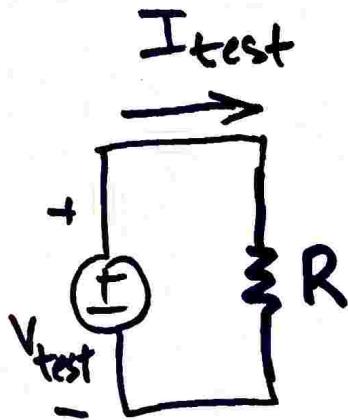

~~Series~~ I_{test}

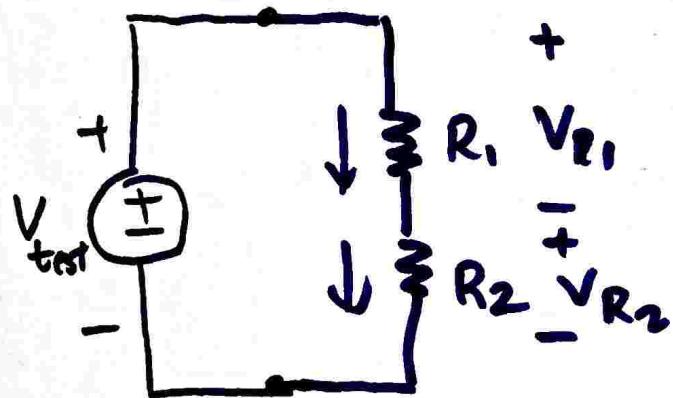
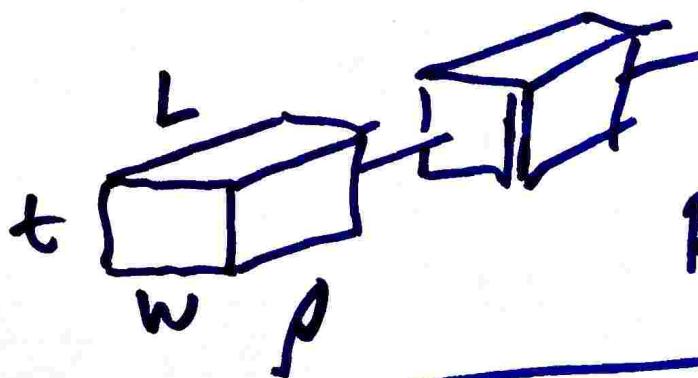
$$V_{\text{test}} = \underbrace{(R_1 + R_2)}_{R_{\text{eq}}} I_{\text{test}}$$




$$R = \rho \frac{L}{W \cdot t}$$

Equivalence: Displays same $I \cdot V$ characteristics

2.4.4

Parallel

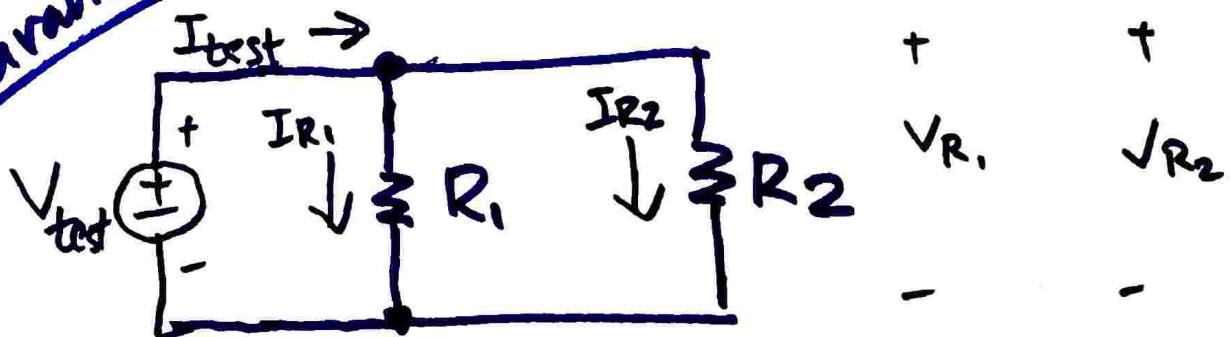

$$I_{\text{test}} = I_{R_1} + I_{R_2}$$

$$I_{\text{test}} = \frac{V_{\text{test}}}{R_1} + \frac{V_{\text{test}}}{R_2}$$

$$I_{\text{test}} = V_{\text{test}} \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$



$$\frac{I_{\text{test}}}{V_{\text{test}}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{R_{\text{req}}}$$

$$\frac{V_{\text{test}}}{I_{\text{test}}} = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

$$R_{\text{req}} = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

$$R_1 \parallel R_2 \equiv \frac{R_1 \cdot R_2}{R_1 + R_2}$$




24.5

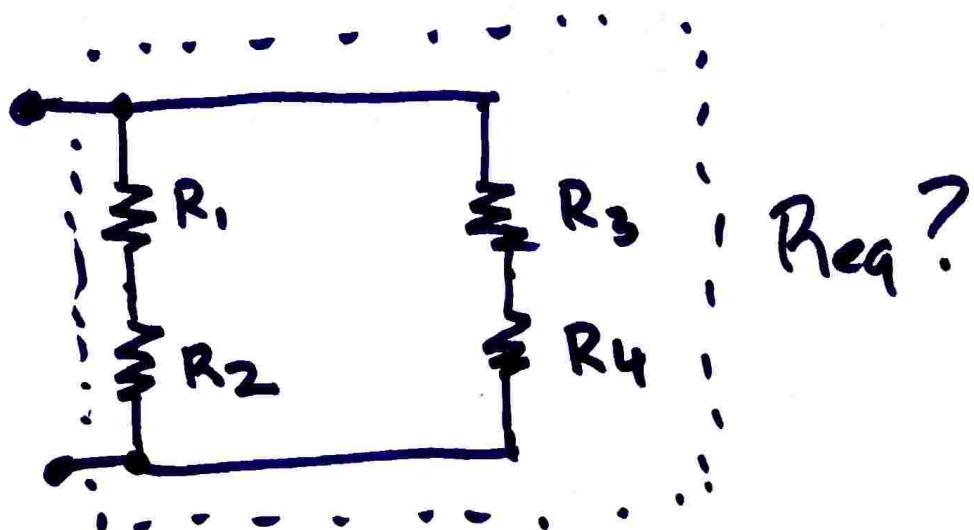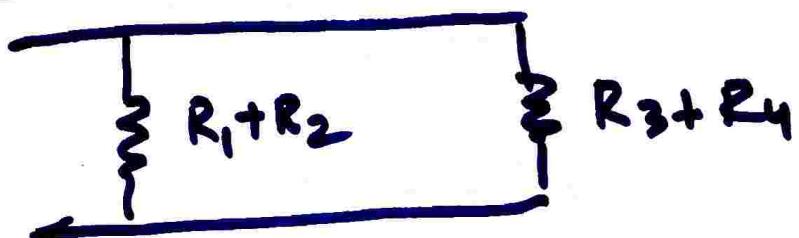Step 1:Step 2:

$$\overline{\overline{(R_1+R_2)} \parallel (R_3+R_4) }$$

$$Req = \frac{(R_1+R_2)(R_3+R_4)}{R_1+R_2+R_3+R_4}$$

Wheatstone Bridge

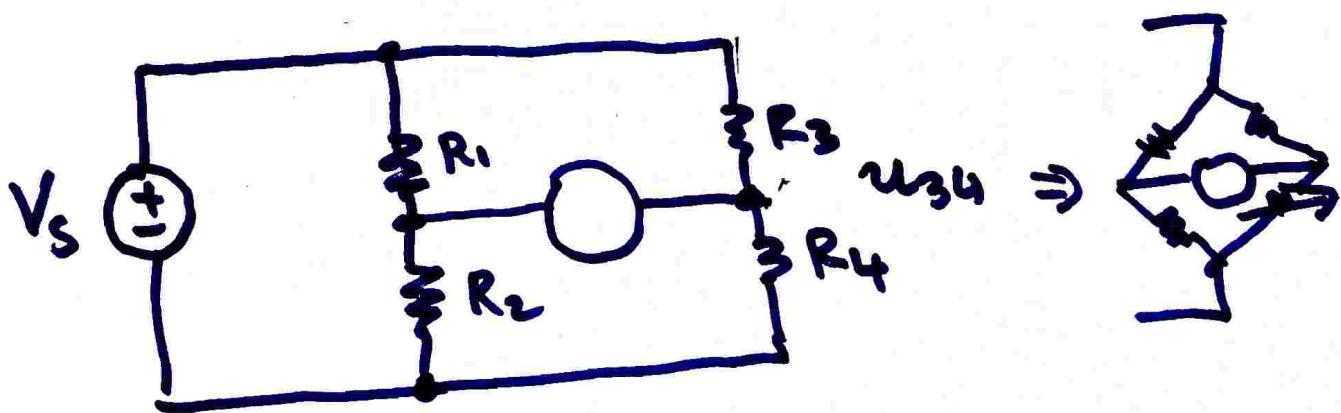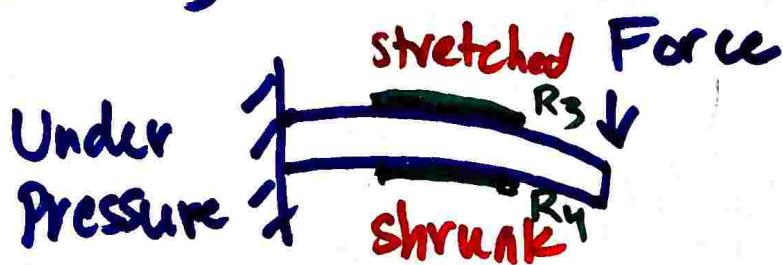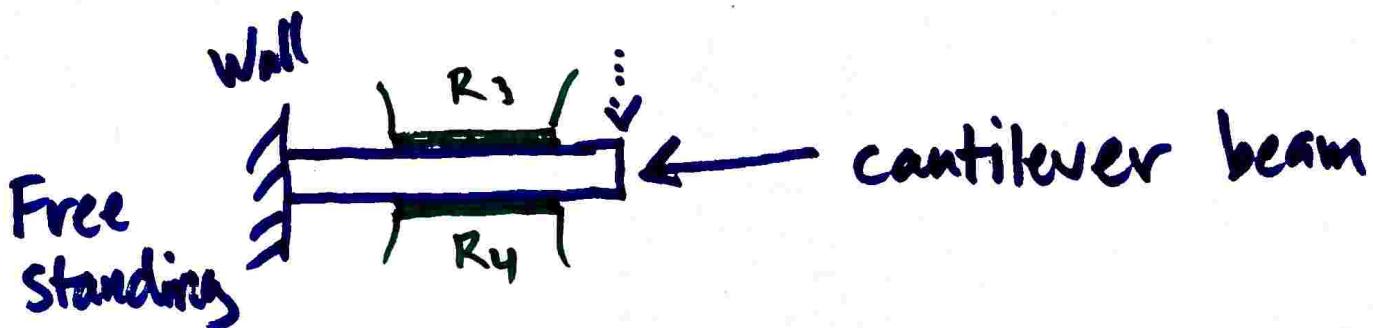

$$R_1 = R_2$$


$$R_3 = R_4$$

$$u_{34} = V_s \frac{R_4}{R_3 + R_4}$$


2.4.7

Controlled Sources

VCVS

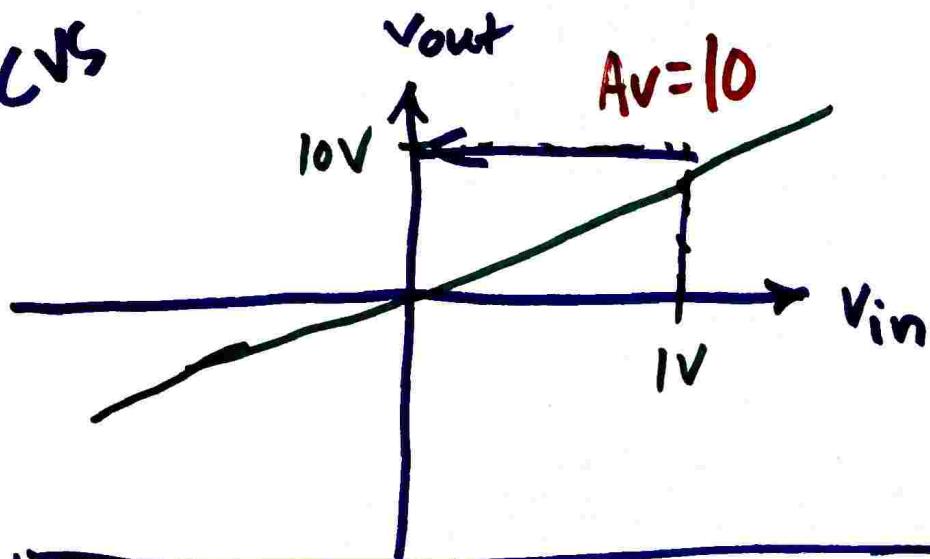

Gain:
 $10x$

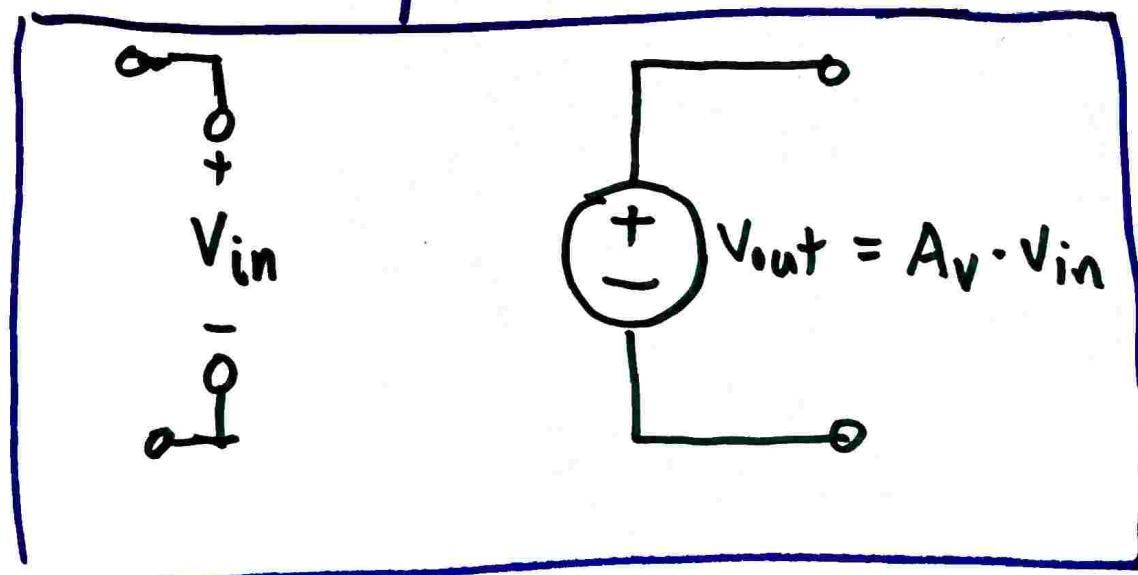


Voltage Controlled Voltage Source

VCVS


_ C _ S

2.4.8



VCCS

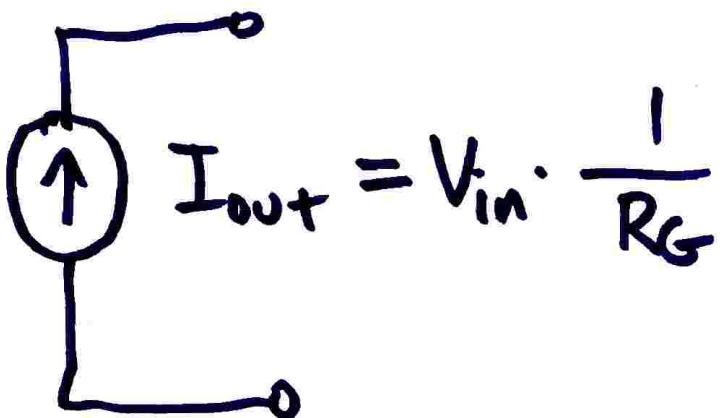

CCVS

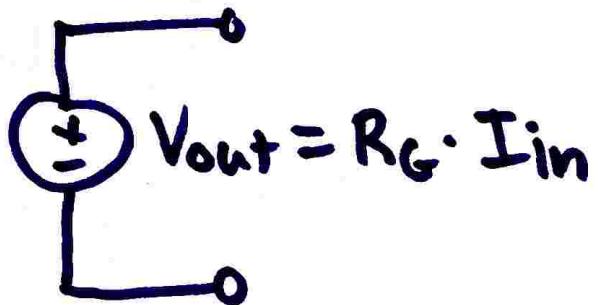


CCCS

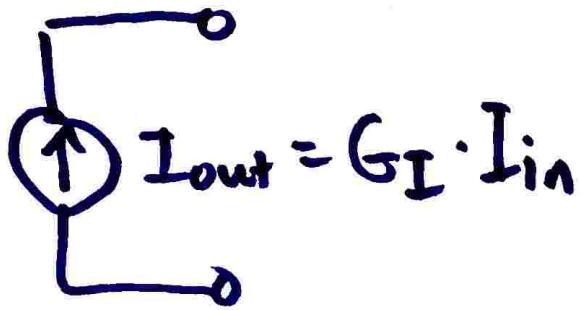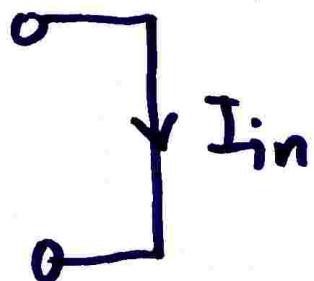

2.4.9

Superposition

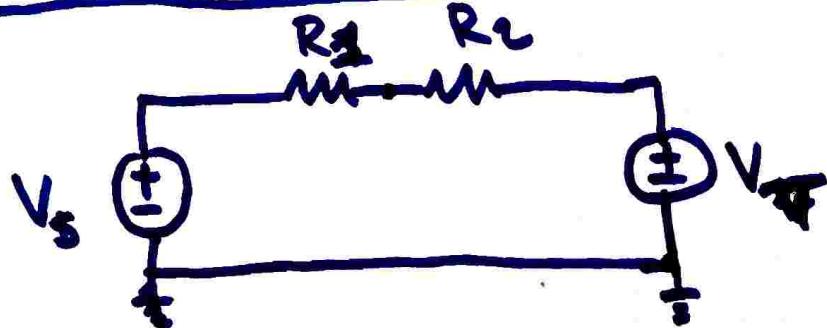

$$\vec{A}\vec{x} = \vec{b}$$


$$\vec{A}^{-1}\vec{A}\vec{x} = \vec{A}^{-1}\vec{b}$$

$$\vec{x} = \vec{A}^{-1}\vec{b}$$

Given a circuit w/ multiple sources

- 1) Zero all the sources except one, and then solve
- 2) Repeat for each source
- 3) Sum the results

2.4.9.a

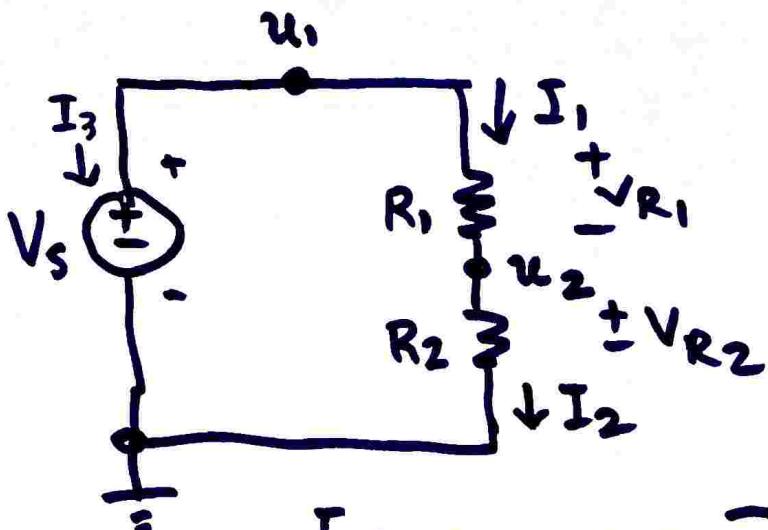

KCL:

$$I_1 + I_3 = 0$$

$$-I_1 + I_2 = 0$$


KVL + Sub:

$$R_1 I_1 - u_1 + u_2 = 0$$


$$R_2 I_2 - u_2 = 0$$

$$\left[\begin{array}{ccccc} 1 & 0 & 1 & 0 & 0 \\ -1 & 1 & 0 & 0 & 0 \\ R_1 & 0 & R_2 & 0 & 0 \\ 0 & R_2 & 0 & 0 & 1 \\ 0 & 0 & 0 & 1 & 0 \end{array} \right] \left[\begin{array}{c} I_1 \\ I_2 \\ I_3 \\ u_1 \\ u_2 \end{array} \right] = \left[\begin{array}{c} V_s \\ 0 \\ 0 \\ 0 \\ V_s \end{array} \right]$$

$A \quad \vec{x} = \vec{b}$

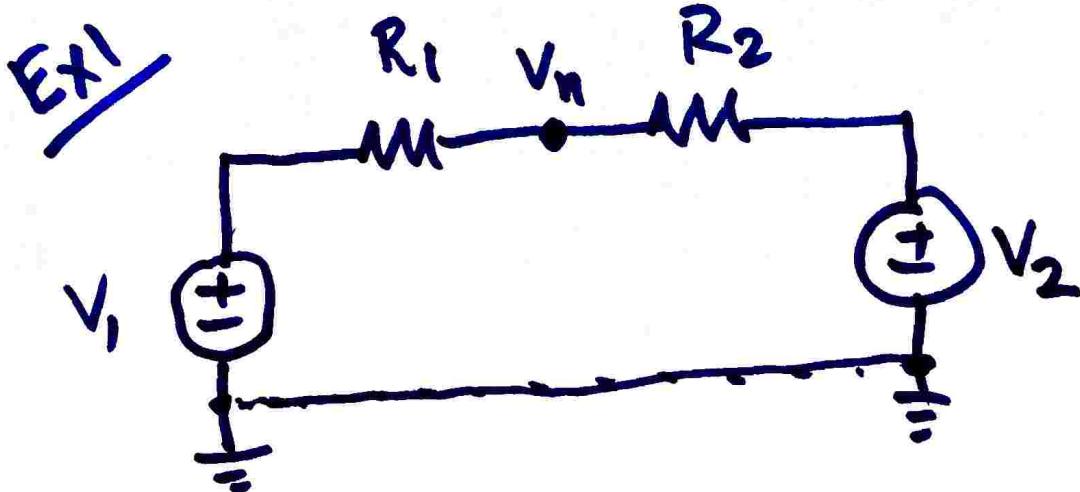


1) Zero $V_1 = 0$

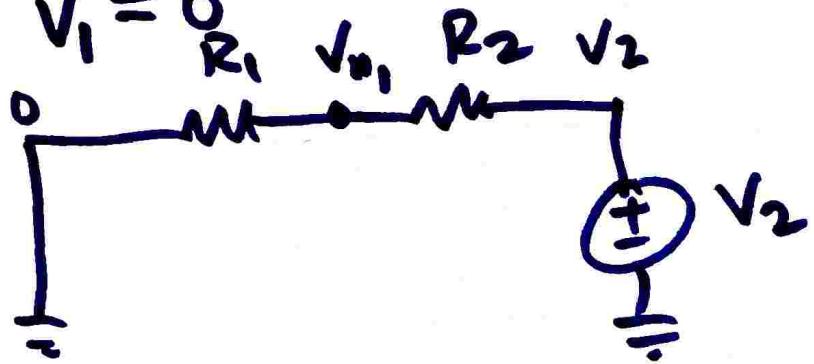

$$V_{n1} = V_2 \cdot \left(\frac{R_1}{R_1 + R_2} \right)$$



2) Zero $V_2 = 0$

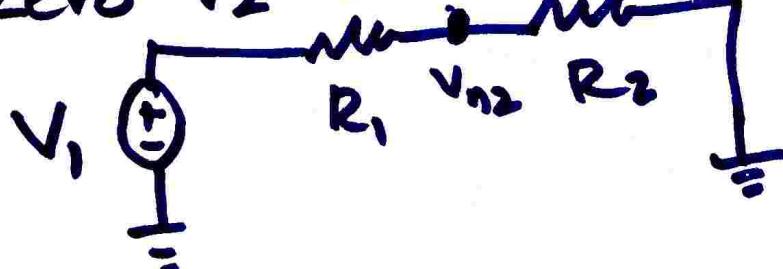


$$V_{n2} = V_1 \cdot \left(\frac{R_2}{R_1 + R_2} \right)$$

3) $V_n = V_{n1} + V_{n2} = V_2 \left(\frac{R_1}{R_1 + R_2} \right) + V_1 \left(\frac{R_2}{R_1 + R_2} \right)$

$$V_n = \frac{V_1 R_2 + V_2 R_1}{R_1 + R_2}$$

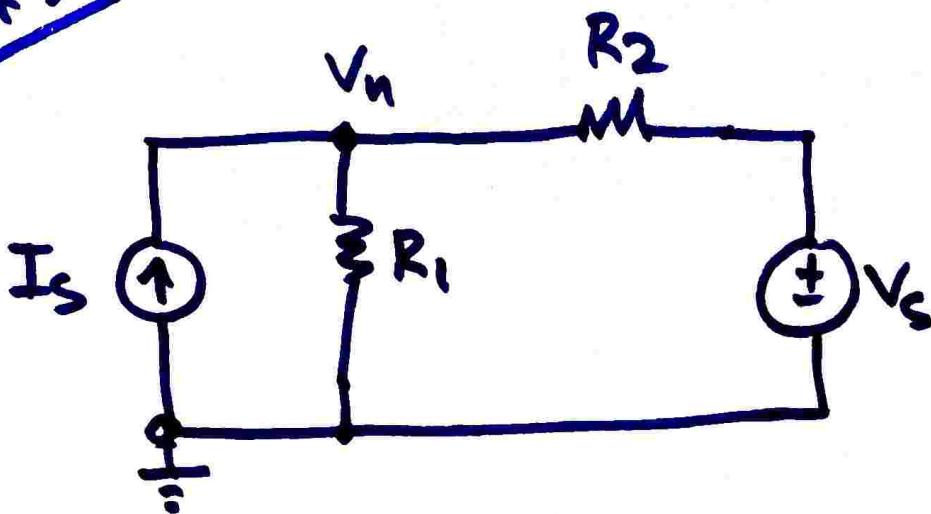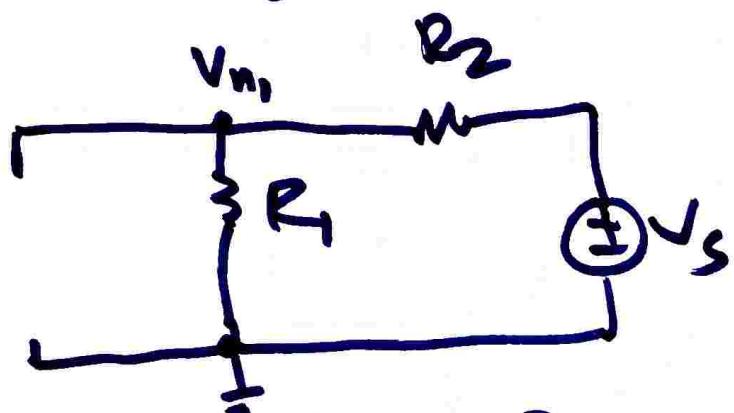Ex 21) Zero I_s 

$$V_{m1} = V_s \left(\frac{R_1}{R_1 + R_2} \right)$$

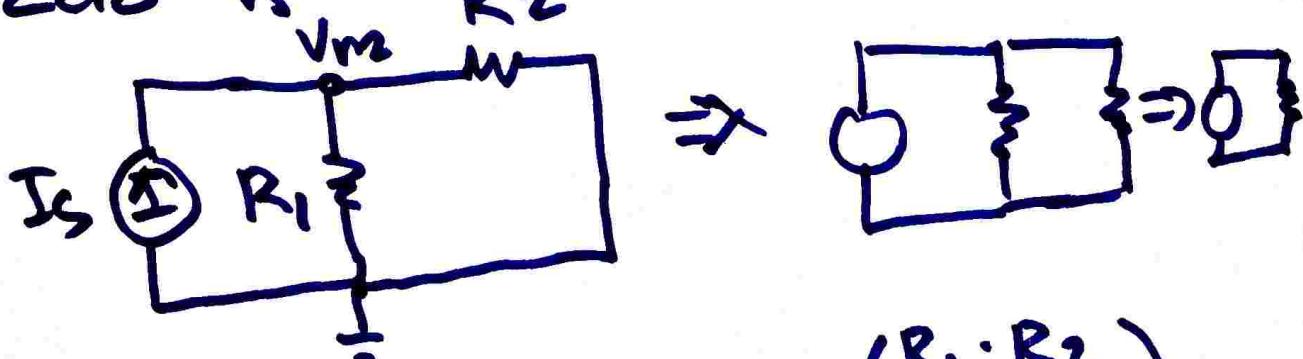2) zero V_s 

$$V = IR = I_s \cdot R_{eq} = I_s \left(\frac{R_1 \cdot R_2}{R_1 + R_2} \right)$$

2.4.12

3)

$$V = V_{n_1} + V_{n_2}$$

$$V = V_s \left(\frac{R_1}{R_1 + R_2} \right) + I_s \left(\frac{R_1 \cdot R_2}{R_1 + R_2} \right)$$

$$V = \left(\frac{R_1}{R_1 + R_2} \right) (V_s + I_s \cdot R_2)$$