

---


EECS 16A    Designing Information Devices and Systems I    Discussion 8B  
Spring 2021

---


### 1. Capacitance Equivalence

For the structures shown below, assume that the plates have a depth  $L$  into the page and a width  $W$  and are always a distance  $d$  apart. The dielectric between the plates has absolute permittivity  $\epsilon$ . For the following calculations, assume the capacitance is purely parallel plate, i.e. ignore fringing field effects.

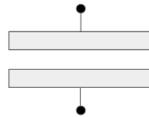
- (a) What is the capacitance of the structure shown below?



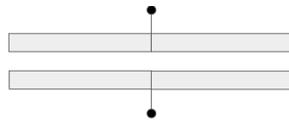
- (b) Suppose that we take two such structures and put them next to each other as shown below. What is the capacitance of this new structure?



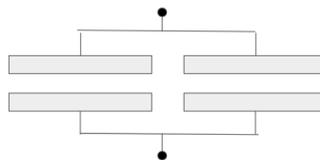
- (c) Now suppose that rather than connecting them together as shown above, we connect them with an ideal wire as shown below. What is the capacitance of this structure?



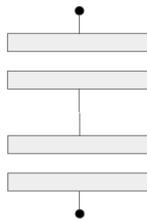- (d) Suppose that we now take two capacitors and connect them as shown below. What is the capacitance of the structure?



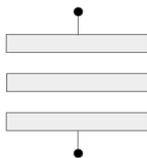- (e) What is the capacitance of the structure shown below?




## 2. Voltages Across Capacitors

For the circuits given below, determine the voltage across each capacitor and calculate the charge and energy stored on each capacitor (assume all capacitors start *uncharged*, and then we've let the system reach steady state). We are also given  $C_1 = 1\ \mu\text{F}$ ,  $C_2 = 3\ \mu\text{F}$ , and  $V_s = 1\ \text{V}$ .


Recall charge has units of Coulombs (C), and capacitance is measured in Farads (F) =  $\frac{\text{Coulomb}}{\text{Volt}}$ .

It may also help to note metric prefix examples:  $3\ \mu\text{F} = 3 \times 10^{-6}\text{F}$ .


(a)

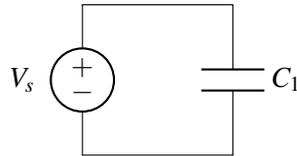

(b)

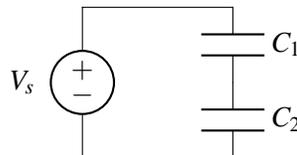

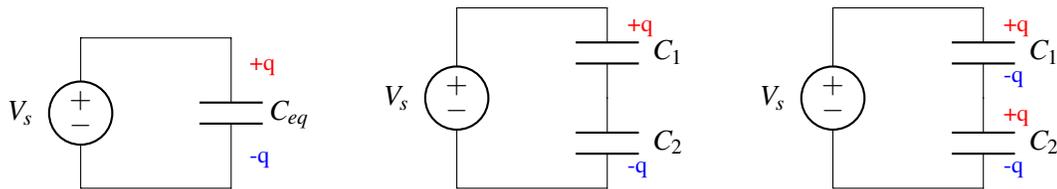**Helpful diagrams** for considering the charges capacitors linked in series:  
(without any initial charges)



**Left:** Our series capacitors may be modeled as one equivalent capacitor  $C_{eq}$ , which after some time is charged up by  $V_s$  to have  $+q$  on the top plate and  $-q$  on the bottom plate.


**Middle:** We return to the 2-capacitor picture, but carry this insight of equivalent charge with us. Now the charge  $+q$  is on the top plate of capacitor  $C_1$ , and  $-q$  is on the bottom plate of capacitor  $C_2$ .

**Right:** Since capacitor plates have opposite & equal charges, we attain this final right diagram.

As another conceptual check, we notice that the node between  $C_1$  and  $C_2$  is isolated from any other connections and should always remain *charge neutral*. From the diagram right we see this is maintained since  $(+q) + (-q) = 0$ .

### 3. Capacitors and Charge Conservation

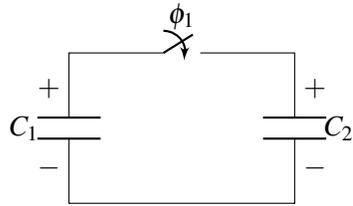- (a) Consider the circuit below with  $C_1 = C_2 = 1 \mu\text{F}$  and an open switch. Suppose that  $C_1$  is initially charged to  $+1 \text{ V}$  and that  $C_2$  is charged to  $+2 \text{ V}$ . How much charge is on  $C_1$  and  $C_2$ ?



- (b) Now the switch is closed (i.e. the capacitors are connected together.) What are the voltages across and the charges on  $C_1$  and  $C_2$ ?