

Reference Circuits

<p>Voltage Divider</p> <p>$V_{R2} = V_1 \left(\frac{R_2}{R_1 + R_2} \right)$</p>	<p>Inverting Amplifier</p> <p>$V_{out} = V_{in} \left(-\frac{R_f}{R_i} \right)$</p>	<p>Noninverting Amplifier</p> <p>$V_{out} = V_{in} \left(1 + \frac{R_{top}}{R_{bottom}} \right)$</p>
<p>Current Divider</p> <p>$I_1 = I_5 \left(\frac{R_2}{R_1 + R_2} \right)$</p>	<p>Inverting Amplifier with Reference</p> <p>$V_{out} = V_{in} \left(-\frac{R_f}{R_i} \right) + V_{REF} \left(\frac{R_f}{R_i} + 1 \right)$</p>	<p>Noninverting Amplifier with Reference</p> <p>$V_{out} = V_{in} \left(1 + \frac{R_{top}}{R_{bottom}} \right) - V_{REF} \left(\frac{R_{top}}{R_{bottom}} \right)$</p>
<p>Voltage Summer</p> <p>$V_{out} = V_1 \left(\frac{R_2}{R_1 + R_2} \right) + V_2 \left(\frac{R_1}{R_1 + R_2} \right)$</p>	<p>Unity Gain Buffer</p> <p>$V_{out} = V_{in}$</p>	


$$V_o = \left(V_1 \left(\frac{R_2}{R_1 + R_2} \right) + V_2 \left(\frac{R_1}{R_1 + R_2} \right) \right) \left(1 + \frac{R_t}{R_b} \right)$$

1. Testing for Negative Feedback


While it is tempting to say "if the feedback voltage is connected to the negative op-amp terminal, then we have negative feedback," **this is not always true**. Here is a two-step procedure for determining if a circuit is in negative feedback:

- Step 1: Zero out all independent sources**, replacing voltage sources with wires and current sources with opens as we did in superposition. You do not need to zero out the voltage sources that serve as the power supplies to the op-amp, since they are not treated as signals and almost considered part of the op-amp.
- Step 2: Wiggle the output and check the loop.** The goal is to see how the feedback loop responds to a change. Assume that the output increases slightly. Check the direction of change of the feedback signal and the error signal from the circuit. Any change in the error signal will cause a new change in the output. This change is the feedback loop's response to the initial change.
 - If the error signal decreases, then the output must also decrease. This is the opposite direction we initially assumed, i.e. the loop is trying to correct for the change. So the circuit is in negative feedback.
 - If the error signal instead increased, then the output would also increase. This is the same direction we initially assume, i.e. the initial increase lead to further increase. We call this positive feedback.

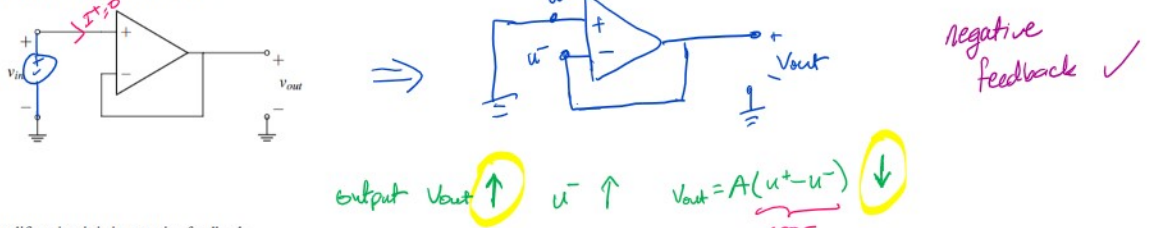(a) Show that the voltage buffer circuit is in negative feedback.




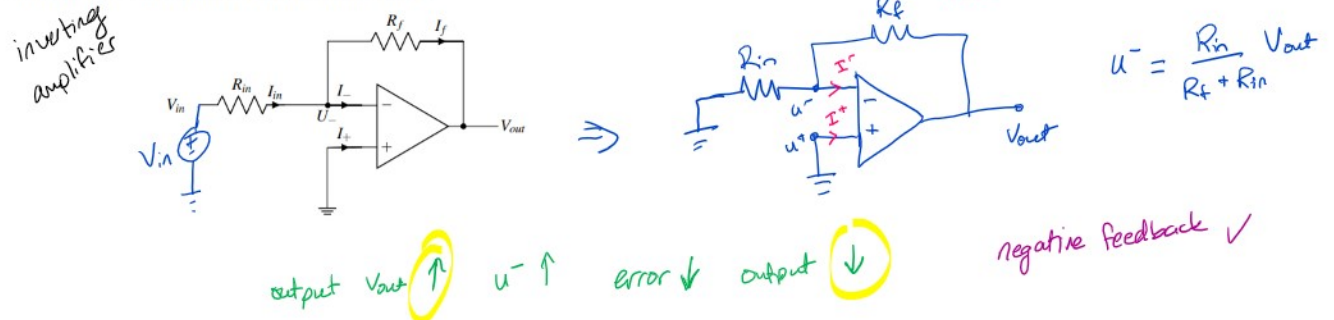(b) Show that the inverting amplifier circuit is in negative feedback.



2. Multiple Inputs To One Op-Amp

Voltage Summer

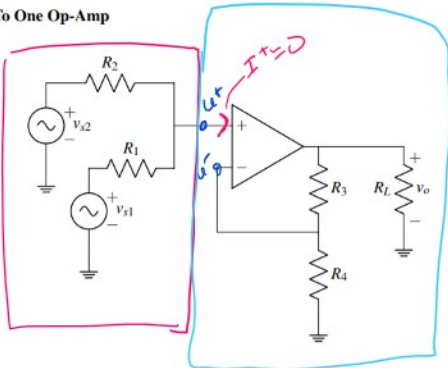

Negative feedback/ideal

golden rules

- ① $I^+ = I^- = 0$
- ② $u^+ = u^-$


noninverting amplifier

* Superposition 2 options


- ① use to find u^+
- or
- ② use to find v_o

we are going to use this approach

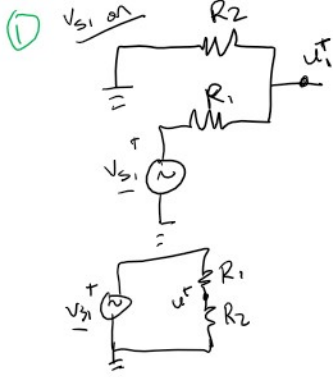(a) For the circuit above, find an expression for v_o . (Hint: Use superposition.)



$$u_1^+ = \frac{R_2}{R_1 + R_2} V_{s1}$$

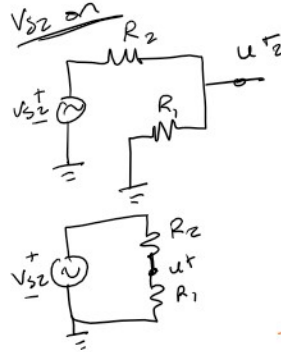


$$u_2^+ = \frac{R_1}{R_1 + R_2} V_{s2}$$

$$u^+ = u_1^+ + u_2^+ = \frac{R_2}{R_1 + R_2} V_{s1} + \frac{R_1}{R_1 + R_2} V_{s2}$$

$$v_o = \frac{R_3 + R_4}{R_4} \left(\frac{R_4}{R_3 + R_4} v_o \right)$$

$$v_o = v_o$$

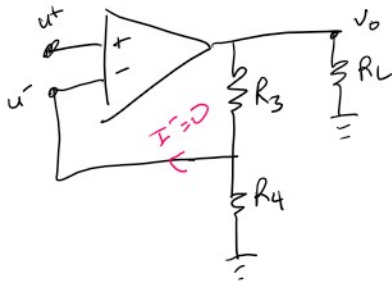

* $u^+ = u^-$



$$u^- = \frac{R_4}{R_3 + R_4} v_o$$

$$u^+ = \frac{R_4}{R_3 + R_4} v_o$$

$$v_o = \frac{R_3 + R_4}{R_4} u^+ = \left(1 + \frac{R_3}{R_4} \right) u^+$$

$$v_o = \left(1 + \frac{R_3}{R_4} \right) \left(\frac{R_2}{R_1 + R_2} V_{s1} + \frac{R_1}{R_1 + R_2} V_{s2} \right)$$

②

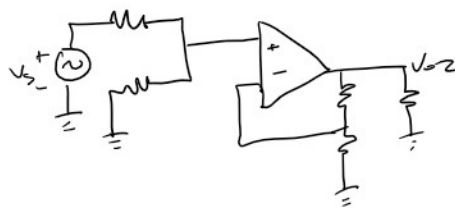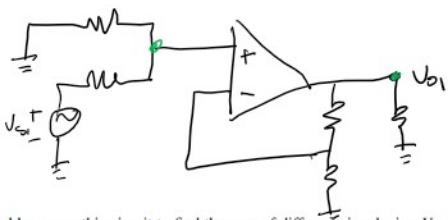

$$v_o = v_{o1} + v_{o2}$$

(b) How could you use this circuit to find the sum of different signals, i.e. $V_{s1} + V_{s2}$? What about taking the sum and adding multiplying by 2, i.e. $2(V_{s1} + V_{s2})$?

$v_o = V_{s1} + V_{s2}$ by choosing R_1, R_2, R_3, R_4

$$R_1 = R_2$$

$$R_3 = R_4$$


$$v_o = \underbrace{\left(1 + \frac{R_3}{R_4} \right)}_2 \left(\frac{1}{2} V_{s1} + \frac{1}{2} V_{s2} \right) = (1+1) \left(\frac{1}{2} V_{s1} + \frac{1}{2} V_{s2} \right) = V_{s1} + V_{s2}$$

3. Modular Op-Amp Circuits

Let's expand our toolbox of op-amp circuits that perform mathematical operations by designing blocks that implement the following operations

(a) Scale the input voltage so that: $V_{out} = +5V_{in}$

noninverting amp

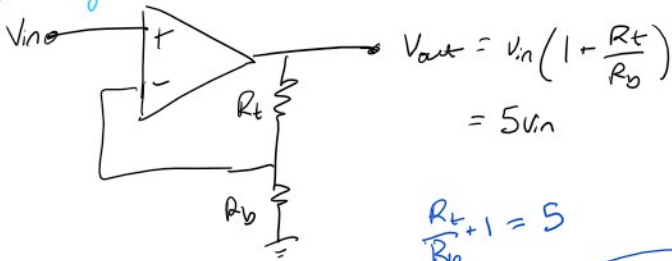


$$V_{out} = V_{in} \left(1 + \frac{R_t}{R_b} \right) = 5V_{in}$$

$$\frac{R_t}{R_b} + 1 = 5$$

$$\frac{R_t}{R_b} = 4 \quad \boxed{R_t = 4R_b}$$

(b) Scale and invert the input voltage so that: $V_{out} = -2V_{in}$

inverting amp

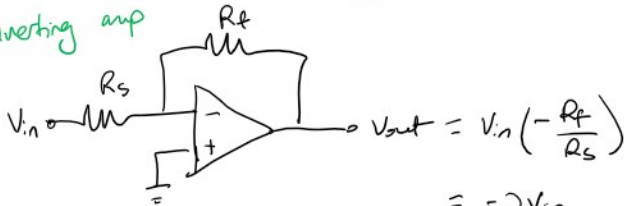

$$V_{out} = V_{in} \left(-\frac{R_f}{R_s} \right) = -2V_{in}$$

$$-\frac{R_f}{R_s} = -2 \quad \boxed{R_f = 2R_s}$$

(c) Sum two input voltages together so that: $V_{out} = V_{in1} + V_{in2}$


** same as 2b*

$$V_{out1} = V_1 \left(\frac{R_2}{R_1 + R_2} \right) + V_2 \left(\frac{R_1}{R_1 + R_2} \right) = \frac{1}{2}V_1 + \frac{1}{2}V_2$$

$$V_{out2} = V_{out1} \left(1 + \frac{R_b}{R_b} \right) = 2V_{out1} \quad \boxed{R_t = R_b}$$

$$V_{out2} = \left(1 + \frac{R_t}{R_b} \right) \left(V_1 \left(\frac{R_2}{R_1 + R_2} \right) + V_2 \left(\frac{R_1}{R_1 + R_2} \right) \right) = V_1 + V_2$$

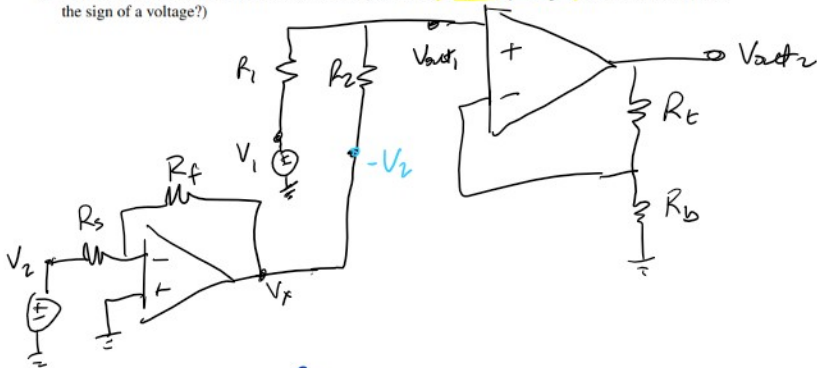(d) (PRACTICE) Take the difference of two voltages so that: $V_{out} = V_{in1} - V_{in2}$. (Hint: how do you invert the sign of a voltage?)



$$R_f = R_s$$

$$V_x = -\frac{R_f}{R_s} V_2 = -V_2$$


Use the reference above for help!

Would connecting any of these blocks together modify their intended functionality?

Reference Circuits

<p>Voltage Divider</p> $V_{R2} = V_S \left(\frac{R_2}{R_1 + R_2} \right)$	<p>Inverting Amplifier</p> $V_{out} = V_{in} \left(-\frac{R_f}{R_i} \right)$	<p>Noninverting Amplifier</p> $V_{out} = V_{in} \left(1 + \frac{R_{f2}}{R_{in2}} \right)$
<p>Current Divider</p> $I_1 = I_S \left(\frac{R_2}{R_1 + R_2} \right)$	<p>Inverting Amplifier with Reference</p> $V_{out} = V_{in} \left(-\frac{R_f}{R_i} \right) + V_{REF} \left(\frac{R_f}{R_i} + 1 \right)$	<p>Noninverting Amplifier with Reference</p> $V_{out} = V_{in} \left(1 + \frac{R_{f2}}{R_{in2}} \right) - V_{REF} \left(\frac{R_{f2}}{R_{in2}} \right)$
<p>Voltage Summer</p> $V_{out} = V_1 \left(\frac{R_2}{R_1 + R_2} \right) + V_2 \left(\frac{R_1}{R_1 + R_2} \right)$	<p>Unity Gain Buffer</p> $V_{out} = V_{in}$	


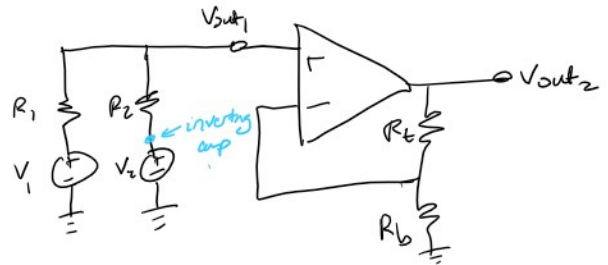
** combine w/ noninverting amp w/ gain of 2*



4. Practice: Dividers for Days

(a) Solve the following circuit for v_x .


* voltage summer

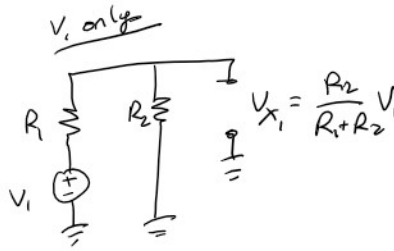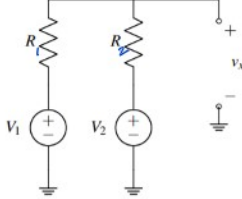

$$V_x = \frac{R_2}{R_1 + R_2} V_1 + \frac{R_1}{R_1 + R_2} V_2$$

if $R_1 = R_2 = R$
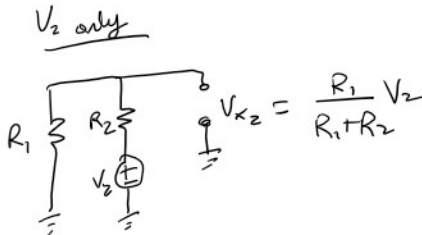
$$V_x = \frac{1}{2} V_1 + \frac{1}{2} V_2$$



(b) You have access to two voltage sources, V_1 and V_2 . You can use two resistors (as long as $0 \leq R < \infty$). How would you design a circuit that produces a voltage $v_x = \frac{1}{3} V_1 + \frac{2}{3} V_2$?

$$V_x = \frac{R_2}{R_1 + R_2} V_1 + \frac{R_1}{R_1 + R_2} V_2$$

$$= \frac{1}{3} V_1 + \frac{2}{3} V_2$$

$$R_1 = 2R_2$$

using voltage summer circuit

(c) You have two current sources I_1 and I_2 . You also have a load resistor $R_L = 6k\Omega$. Similar to the first part, you can use whatever resistors you want (as long as they are finite integer multiples of $1k\Omega$). How would you design a circuit such that the current running through R_L is $I_L = \frac{2}{5}(I_1 + I_2)$?

* similar to how a voltage summer is 2 voltage dividers when we use superposition, we can design a circuit that is 2 current dividers when we use superposition


* reference circuit current divider



$$I_1 = \frac{R_2}{R_1 + R_2} I_s$$

$$I_2 = \frac{R_1}{R_1 + R_2} I_s$$

can derive using NVA

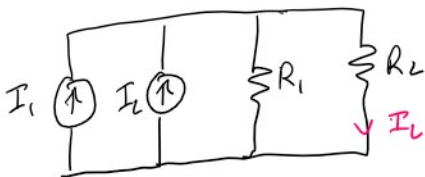

I_1 only



$$\frac{R_1}{R_1 + R_L} = \frac{2}{5}$$


$$5R_1 = 2(R_1 + R_L)$$

$$3R_1 = 2R_L$$

$$R_1 = \frac{2}{3} R_L$$

* $R_L = 6k\Omega$
 $R_1 = 4k\Omega$

I_2 only

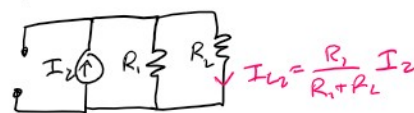

$$I_L = I_{L1} + I_{L2}$$

$$= \frac{R_1}{R_1 + R_L} I_1 + \frac{R_2}{R_1 + R_L} I_2$$

$$= \frac{R_1}{R_1 + R_L} (I_1 + I_2)$$

$$= \frac{2}{5} (I_1 + I_2)$$