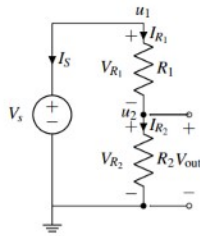


1. Voltage Divider

For the circuit below, your goal will be to find the voltage V_{out} in terms of the resistances R_1 , R_2 , and V_s , using **NVA (Node Voltage Analysis)**. The labeling steps (steps 1-4) have already been done for you.




$$V_s = u_1 - 0$$

Here is a reminder of the labeling steps followed to get the circuit diagram above:

- **Step 1:** Select a reference (ground) node. Any node can be chosen for this purpose. We will measure all of the voltages in the rest of the circuit relative to this point.
- **Step 2:** Label all nodes with voltage set by voltage sources.
- **Step 3:** Label remaining nodes.
- **Step 4:** Label element voltages and currents, following **Passive Sign Convention** (discussed below).

Passive sign convention

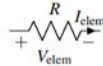
The **passive sign convention** dictates that positive current should *enter* the positive terminal and *exit* the negative terminal of an element. Below is an example for a resistor:



As long as this convention is followed consistently, it does not matter which direction you arbitrarily assigned each element current to; the voltage referencing will work out to determine the correct final sign. When we discuss *power* later in the module, you will see why we call this convention "passive."

$$V_{element} = (\text{node voltage @ + terminal}) - (\text{node voltage @ - terminal})$$

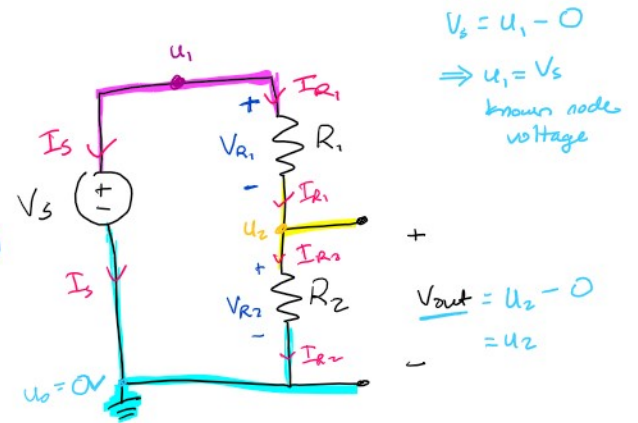To achieve your goal of *finding* V_{out} , perform the rest of the NVA steps in the boxes below:



Step 5: Write KCL equations for all nodes with unknown voltages.

$$u_2$$

KCL @ a node:
 $I_{in} = I_{out}$
 $0 = I_{out} - I_{in}$

KCL @ u_2 :
 $I_{in} = I_{out}$
 $I_{R1} = I_{R2}$

Step 8: Substitute expressions found in step 7 into the KCL equations from step 5.

$$I_{R1} = I_{R2}$$

$$\frac{V_s - u_2}{R_1} = \frac{u_2}{R_2}$$

* 1 eqn, 1 unknown u_2

Step 6: Find expressions for all element currents in terms of element voltages and characteristics.

Ohm's Law:
 $V = IR$ $I = \frac{V}{R}$

$$V_{R1} = I_{R1} R_1$$

$$V_{R2} = I_{R2} R_2$$

$$I_{R1} = \frac{V_{R1}}{R_1} \quad I_{R2} = \frac{V_{R2}}{R_2}$$

Step 9: Solve for the node voltage values. At this point the analysis procedure is effectively complete - all that's left to do is solve the system of linear equations (by applying Gaussian Elimination, inverting **A**, etc.) to find the values for the u 's. Then we can go back to our Step 7 equations and calculate the I 's. Note that in our circuit, $V_{out} = u_2 - 0 = u_2$.

$$\frac{V_s - u_2}{R_1} = \frac{u_2}{R_2}$$

$$\frac{V_s}{R_1} = \frac{u_2}{R_2} + \frac{u_2}{R_1} = u_2 \left(\frac{1}{R_2} + \frac{1}{R_1} \right)$$

$$\frac{V_s}{R_1} = u_2 \left(\frac{R_1 + R_2}{R_1 R_2} \right)$$

$$u_2 = \left(\frac{R_2}{R_1 + R_2} \right) V_s$$

Step 7: Substitute all element voltages with node voltages found in your step 6 equations.

$V_{element}$
 plug in step 6 eqns
 * $u_1 = V_s$

$$V_{R1} = u_1 - u_2$$

$$V_{R2} = u_2 - 0 = u_2$$

$$I_{R1} = \frac{V_{R1}}{R_1} = \frac{u_1 - u_2}{R_1} = \frac{V_s - u_2}{R_1}$$

$$I_{R2} = \frac{V_{R2}}{R_2} = \frac{u_2}{R_2}$$

$$V_{out} = u_2 = \frac{R_2}{R_1 + R_2} V_s$$


* $V_{out} = V_{R2}$

KCL @ a node:

$$I_{in} = I_{out}$$

KVL for a loop:

$$\sum V = 0$$

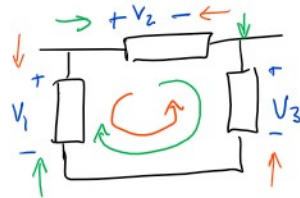

If arrow goes through negative terminal first → has + sign

$$V_1 - V_2 - V_3 = 0$$


$$-V_1 + V_2 + V_3 = 0$$

Note: don't see KVL in NVA because element/node voltage eqns (Velement) provides the same info

2. A Simple Circuit

Use KVL and/or KCL to solve the following circuits.

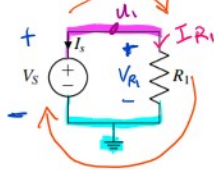- (a) For this problem assume $V_S = 1V$ and $R_1 = 1k\Omega$. Find the current, I_S flowing through the voltage source.



$$\text{KVL: } +V_S - V_{R_1} = 0$$

$$V_S = V_{R_1}$$

Velement
★ if we do element/node voltage eqns

$$V_S = u_1 - 0$$

$$V_{R_1} = u_1 - 0 \Rightarrow V_S = V_{R_1}$$


Ohm's Law: $V_{R_1} = I_{R_1} R_1$ $I_{R_1} = \frac{V_{R_1}}{R_1} = \frac{V_S}{R_1}$

KCL @ u_1 : $I_{in} = I_{out}$

$$0 = I_S + I_{R_1}$$

$$\rightarrow I_S = -I_{R_1} = -\frac{V_S}{R_1} = -1mA$$

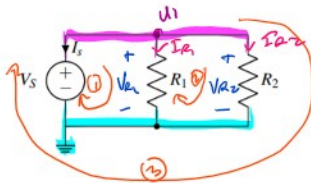- (b) For this problem assume $V_S = 1V$, $R_1 = 2k\Omega$, and $R_2 = 2k\Omega$. Find the current, I_S flowing through the voltage source.



$$\text{KVL: } \textcircled{1} V_S - V_{R_1} = 0$$

$$\textcircled{2} V_{R_1} - V_{R_2} = 0$$

$$\textcircled{3} V_S - V_{R_2} = 0$$

$$\rightarrow V_S = V_{R_1} = V_{R_2}$$

note $\textcircled{1} + \textcircled{2} = \textcircled{3}$

only 2 lin ind eqns

★ Velement would give us the same info

Ohm's Law

$$I_{R_1} = \frac{V_{R_1}}{R_1} = \frac{V_S}{R_1}$$

$$I_{R_2} = \frac{V_{R_2}}{R_2} = \frac{V_S}{R_2}$$

KCL @ u_1 : $I_{in} = I_{out}$


$$0 = I_S + I_{R_1} + I_{R_2}$$

$$I_S = -(I_{R_1} + I_{R_2})$$

$$= -\left(\frac{V_S}{R_1} + \frac{V_S}{R_2}\right) = -1mA$$

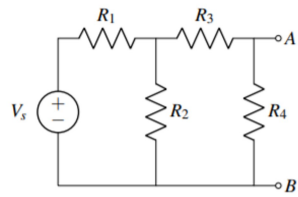3. (PRACTICE) KVL and KCL

For the circuit shown below, $V_s = 5\text{ V}$, $R_1 = R_2 = 4\text{ k}\Omega$, and $R_3 = R_4 = 2\text{ k}\Omega$.



(a) For the circuit above, write KVL equations for each loop and KCL equations for each node.

(b) Solve for the voltage between A and B using the equations from part (a).