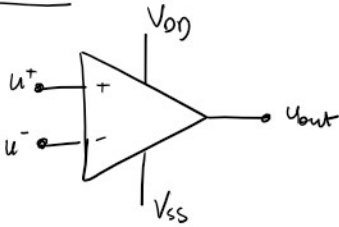



Op Amps



Complex circuit that we analyze using an equivalent circuit



* dependent source

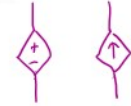


depend on other voltages or currents in the circuit with a gain

↳ scalar multiplier

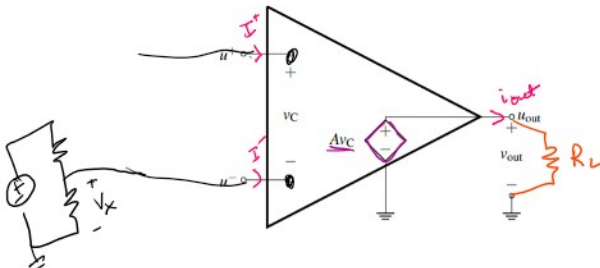I. Op-Amp Rules and Negative Feedback Rules

Here is an equivalent circuit of an op-amp (where we are assuming that $V_{SS} = -V_{DD}$) for reference:



(a) What are the currents flowing into the positive and negative terminals of the op-amp (i.e., what are I^+ and I^-)? Based on this answer, what are some of the advantages of using an op-amp in your circuit designs?

$I^+ = I^- = 0$ * because op-amp circuits @ u^+, u^-

Useful because it doesn't load a circuit connected to the nodes u^+, u^-



* won't change our circuit

(b) Suppose we add a resistor of value R_L between u_{out} and ground. What is the value of v_{out} ? Does your answer depend on R_L ? In other words, how does R_L affect A_{vC} ? What are the implications of this with respect to using op-amps in circuit design?

$v_{out} = A_{vC}$
 ↳ doesn't depend on R_L
 * i_{out} does depend on R_L

* useful because v_{out} won't change no matter what we load it with

Loading a circuit

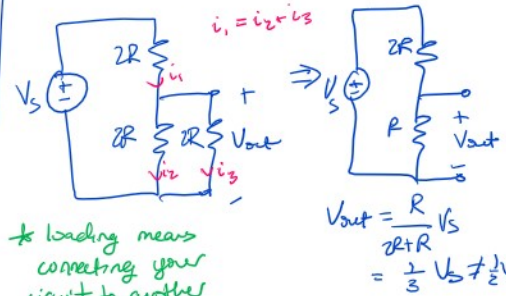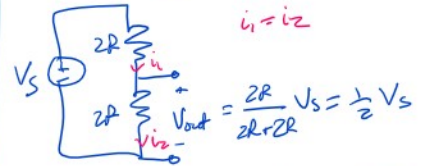

* loading means connecting your circuit to another circuit that will draw a current and change the original circuit's behavior

Negative Feedback

feedback: output is fed back into the input u^+, u^-

negative feedback: feedback ↑ output ↓

Ideal Op Amp in Neg Feedback

can use the golden rules

- ① $I^+ = I^- = 0$ * applies all the time
- ② $u^+ = u^-$



* most op amp problems in this course are in neg feedback

* can typically assume it's in neg feedback when v_{out} is somehow connected to u^-

* ideal: $A \rightarrow \infty$

↳ don't use dependent source model

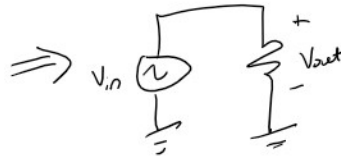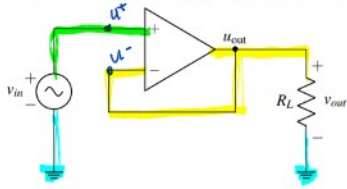For the rest of the problem, consider the following op-amp circuit in negative feedback:



(c) Assuming that this is an ideal op-amp, what is v_{out} ?

$$u^- = u_{out} = V_{out}$$

$$u^+ = V_{in}$$

* golden rule #2: $u^+ = u^-$


$$u^+ = u^-$$

$$V_{out} = V_{in}$$

* doesn't depend on R_L

(d) Draw the equivalent circuit for this op-amp and calculate v_{out} in terms of A , v_{in} , and R_L for the circuit in negative feedback. Does v_{out} depend on R_L ? What is v_{out} in the limit as $A \rightarrow \infty$?

using equivalent circuit:

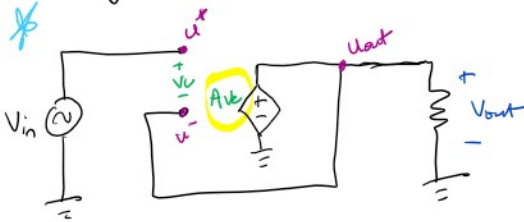

$$V_{out} = U_{out} - 0$$

$$= A V_C$$

$$= A (V_{in} - V_{out})$$

$$V_C = u^+ - u^-$$

$$= V_{in} - U_{out}$$

$$= V_{in} - V_{out}$$

$$V_{out} + A V_{out} = A V_{in}$$

$$V_{out} (1 + A) = A V_{in}$$

$$V_{out} = \frac{A}{1 + A} V_{in}$$

← non ideal

ideal: $A \rightarrow \infty$

$$\lim_{A \rightarrow \infty} V_{out} = \lim_{A \rightarrow \infty} \left(\frac{A}{1 + A} V_{in} \right) = \lim_{A \rightarrow \infty} \left(\frac{1}{\frac{1}{A} + 1} V_{in} \right)$$


$$V_{out} = V_{in}$$

← ideal! consistent w/ part c

* if $u^+ = u^-$
 $V_C = 0$
 $V_{out} = A V_C = \infty \cdot 0$

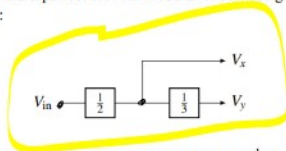
2. Modular Circuit Buffer

Let's try designing circuits that perform a set of mathematical operations using op-amps. While voltage dividers on their own cannot be combined without altering their behavior, op-amps can preserve their behavior when combined and thus are a perfect tool for modular circuit design. We would like to implement the block diagram shown below:





In other words, create a circuit with two outputs V_x and V_y , where $V_x = \frac{1}{2} V_{in}$ and $V_y = \frac{1}{3} V_x = \frac{1}{6} V_{in}$.

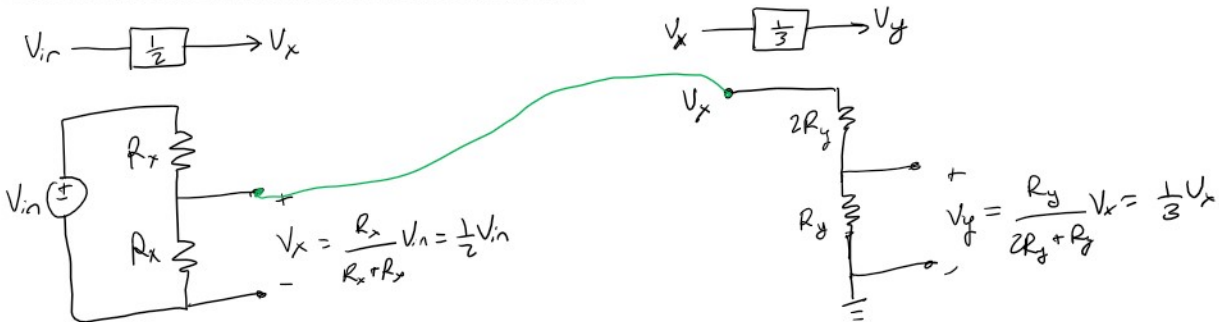(a) Draw two voltage dividers, one for each operation (the 1/2 and 1/3 scalings). What relationships hold for the resistor values for the 1/2 divider, and for the resistor values for the 1/3 divider?



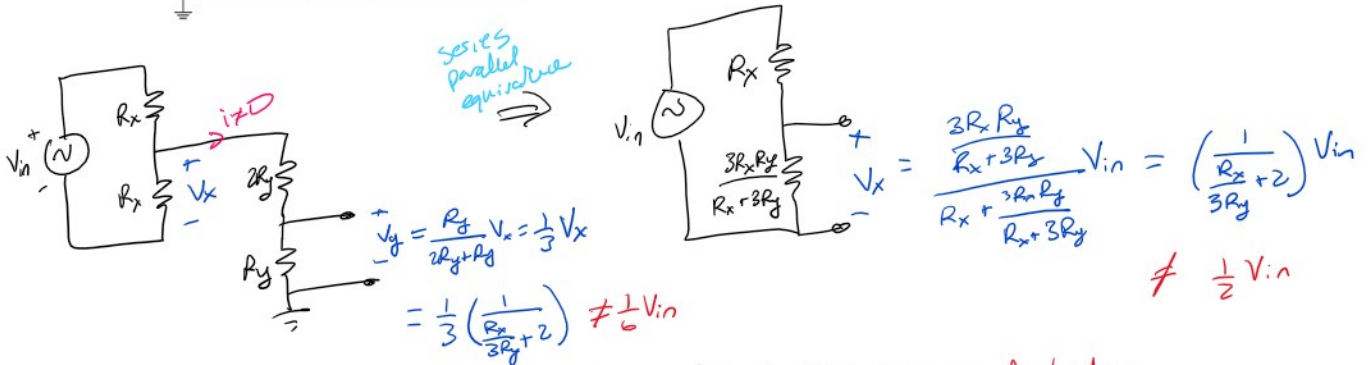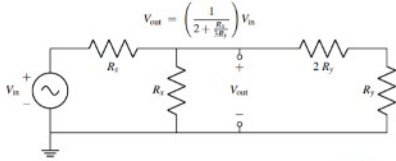(b) If you combine the voltage dividers, made in part (a), as shown by the block diagram (output of the 1/2 voltage divider becomes the source for the 1/3 voltage divider circuit), do they behave as we hope (meaning $V_y = \frac{1}{3}V_x = \frac{1}{6}V_{in}$)?

HINT: The following circuit and formula may be handy:




* do not achieve desired effect because of loading

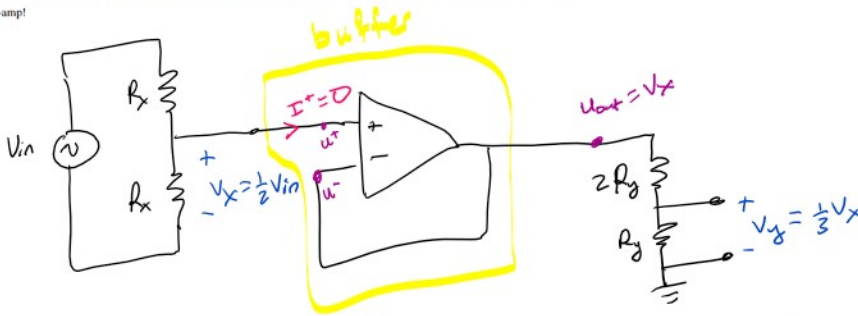
(c) Perhaps we could use an op-amp (in negative-feedback) to achieve our desired behavior. Modify the implementation you tried in part (b) using a negative feedback op-amp in order to achieve the desired V_x, V_y relations $V_x = (1/2)V_{in}$ and $V_y = (1/3)V_x = (1/6)V_{in}$.

HINT: Place the op-amp in between the dividers such that the V_x node is an input into the op-amp, while the source of the 2nd divider is the output of the op-amp!

assume ideal neg feedback
 $\rightarrow u^+ = u^-$
 $V_x = V_{out}$



3. (Practice) An Inverting Amplifier

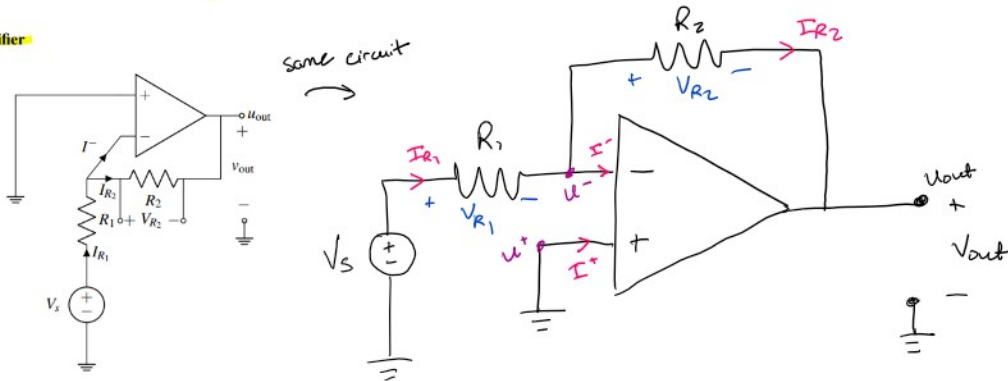

Calculate v_{out} as a function of V_s and R_1 and R_2 .

* assume ideal
negative feedback? yes!
 \rightarrow can use golden rules
① $u^+ = u^-$
② $I^+ = I^- = 0$

same circuit \rightarrow

$u^+ = 0 \rightarrow u^- = 0$

KCL @ u^- : $I_{R_1} = I_{R_2} + I^-$

Ohm's Law: $I_{R_1} = \frac{V_{R_1}}{R_1} = \frac{V_s - u^-}{R_1} = \frac{V_s}{R_1}$

$I_{R_2} = \frac{V_{R_2}}{R_2} = \frac{u^- - V_{out}}{R_2} = \frac{-V_{out}}{R_2}$

Solve: $I_{R_1} = I_{R_2}$

$\frac{V_s}{R_1} = \frac{-V_{out}}{R_2}$

$V_{out} = -\frac{R_2}{R_1} V_s$