

Welcome to EECS 16A!

Designing Information Devices and Systems I





Ana Claudia Arias and Miki Lustig
Fall 2021


Module 2
Lecture 4
2D Touchscreen
(Note 14)




Resistive Touch Screen

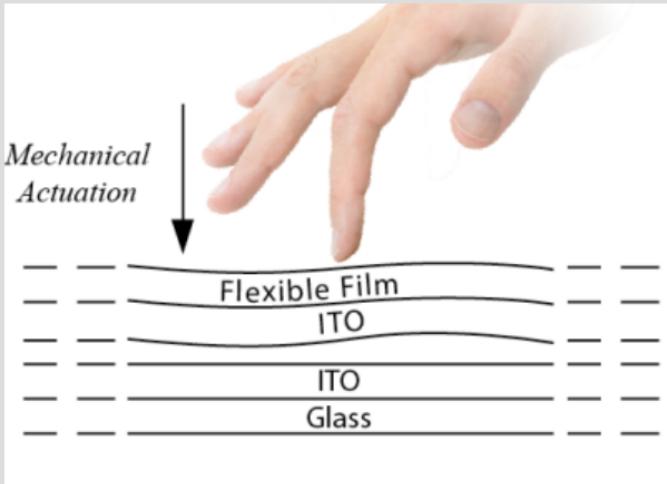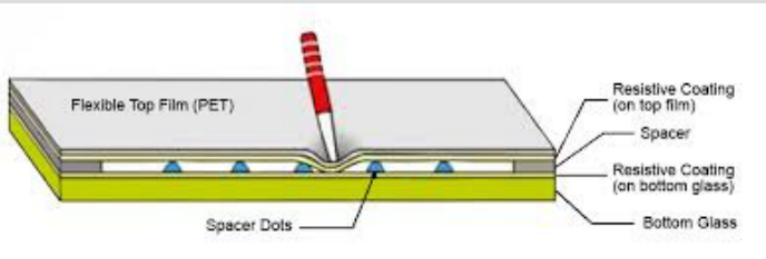




Bottom Layer: Resistive Layer

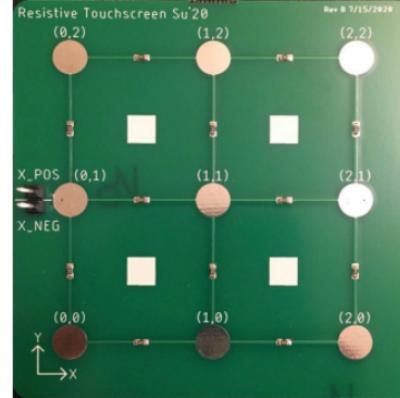

Top Layer: Flexible Resistive Layer

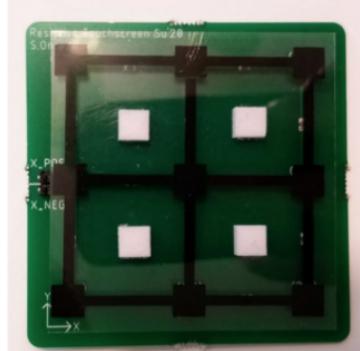


Resistive Touch Screen

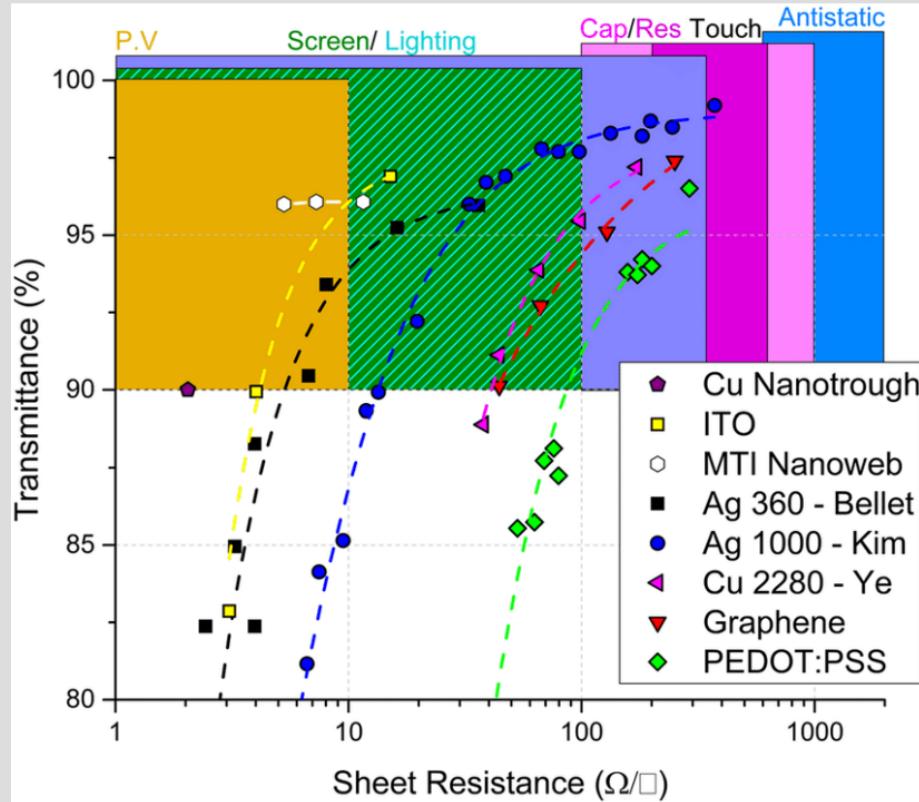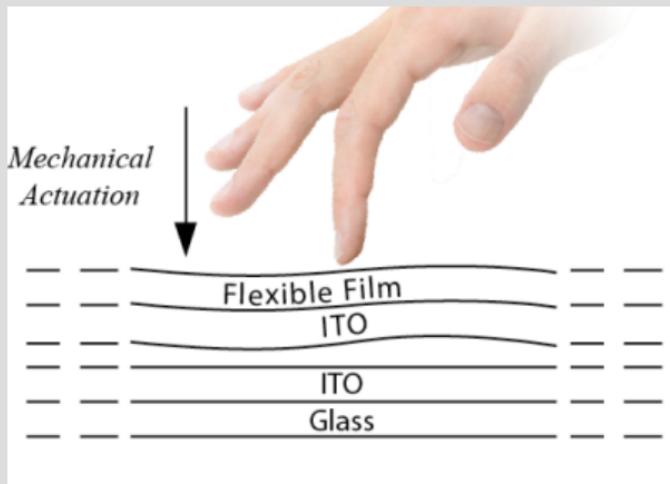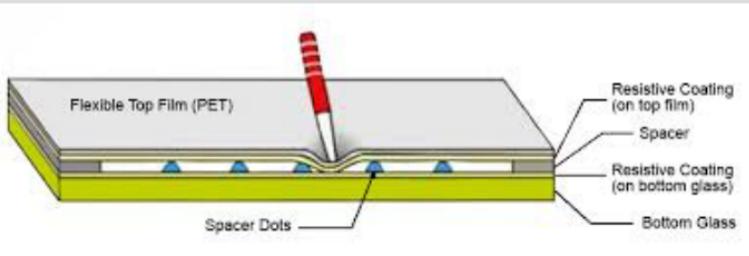

Resistance, Resistivity, Conductivity – Properties of Materials

Material	Electrical characteristics	
	Electrical Resistivity ($\Omega \times \text{cm}$)	Electrical Conductivity ($\Omega^{-1} \times \text{cm}^{-1}$)
Cu	0.034×10^{-5}	29×10^5
Fe	32.54×10^{-5}	0.031×10^5
Ag	0.36×10^{-5}	2.8×10^5
Al	0.03×10^{-5}	33.3×10^5
Ni	0.046×10^{-5}	21.7×10^5
Cu-Fe	33.37×10^{-5}	0.030×10^5
Cu-Ag	2.71×10^{-5}	0.37×10^5
Al-Ni	0.564×10^{-5}	1.77×10^5

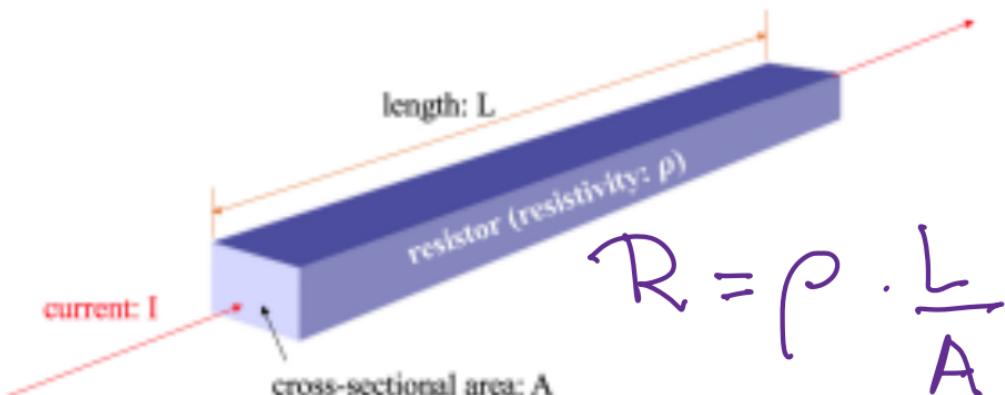

$$R = \rho \cdot \frac{L}{A}$$

Note 12


- longer the wire \rightarrow the more E is lost
- Wide wires \rightarrow lower resistance
- Wire properties depend on materials choice.

ρ = resistivity
(property of materials)

$\frac{L}{A}$ ∴ geometric parameters
(property of the wire)

Resistive Touch Screen

Problem: to find the location of touch.

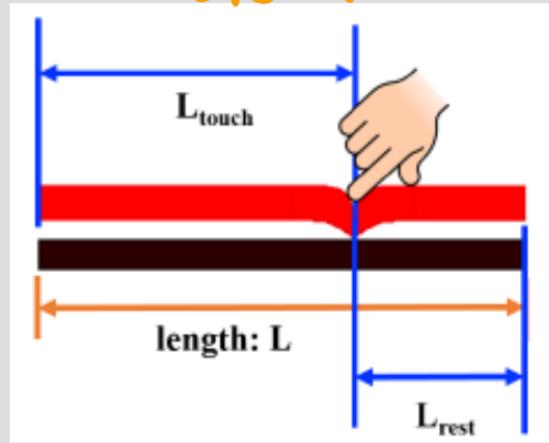



Go from **mechanical** to
electrical quantity.

Want to measure $\frac{h_{touch}}{L}$

h_{touch} is unknown

Resistive Touch Screen – First model

$U_{mid} = ?$

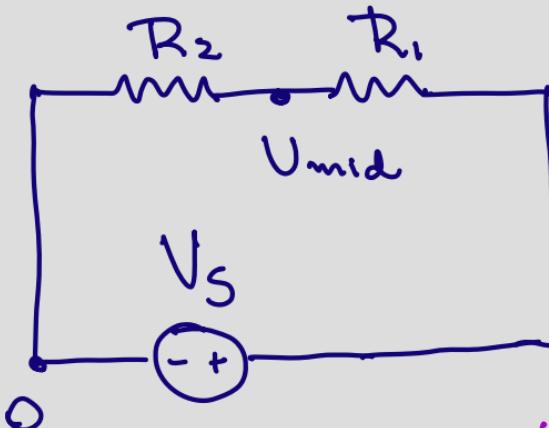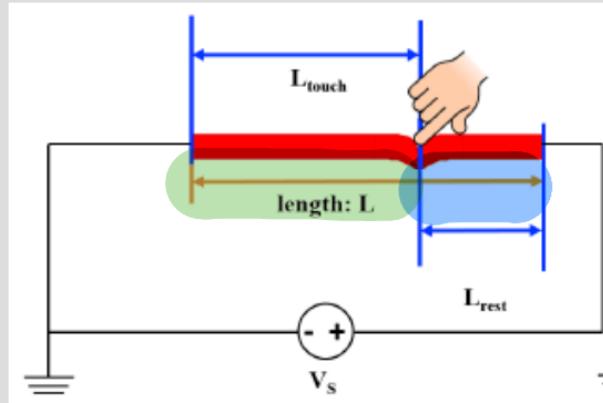

$$U_{mid} = \frac{R_2}{R_2 + R_1} \cdot V_s \quad (\text{Voltage Divider})$$


$$U_{mid} = \frac{\cancel{\rho} \cdot h_{touch}/\cancel{A}}{\cancel{\rho} \cdot h_{touch} + \cancel{\rho} \cdot h_{rest}/\cancel{A}} \cdot V_s$$

$$U_{mid} = \frac{h_{touch}}{h_{touch} + h_{rest}} \cdot V_s = \frac{h_{touch}}{h} \cdot V_s$$

$$R_1 = \rho \cdot \frac{h_{rest}}{A}$$


$$R_2 = \rho \cdot \frac{h_{touch}}{A}$$

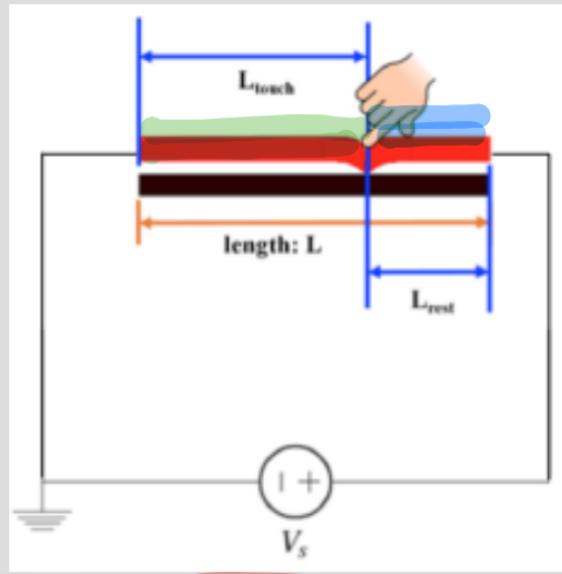Resistive Touch Screen – More realistic model



⇒ Model 1

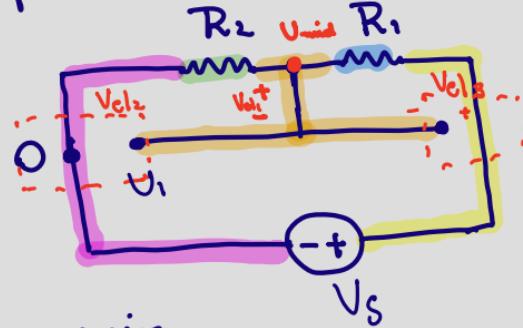- Add ideal wire to represent bottom plate



$e|_1$: wire

$e|_2$: open-circuit (V_{el2})


$e|_3$: open-circuit (V_{el3})

Model 0

$$U_{mid} = \frac{R_2}{R_1 + R_2} \cdot V_s$$

Voltage Divider

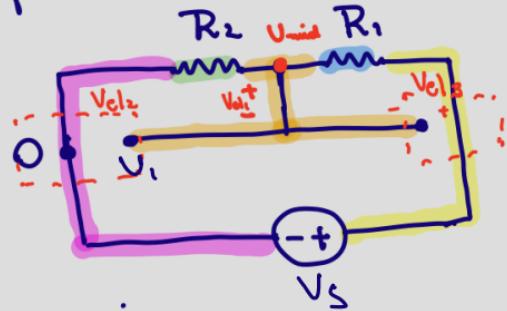Resistive Touch Screen – More realistic model



e_{l_1} : wire

e_{l_2} : open-circuit (V_{l_2})

c_{l_3} : open-circuit (V_{l_3})

Voltage Definition

$$E_{l_2} \therefore V_{l_2} = V_1 - 0$$

$$E_{l_1} \therefore V_{l_1} = U_{mid} - V_1$$

KVL

$$U_{mid} - 0 = V_{l_2} + V_{l_1}$$

$$U_{mid} = V_{l_2} + V_{l_1}^0$$


$$U_{mid} = V_{l_1}^0 + U_1$$

e_{l_1} is a wire $\therefore V_{l_1} = 0$


$$U_{mid} = V_1$$

By measuring V_{l_2}
We get U_{mid} for
any touch

Resistive Touch Screen – More realistic and better model

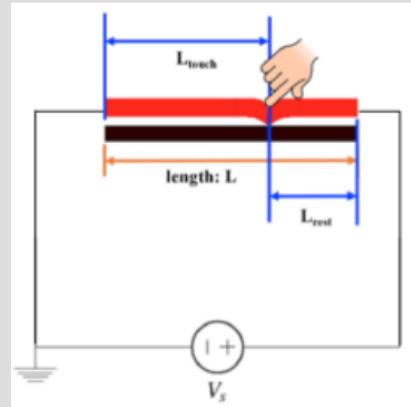

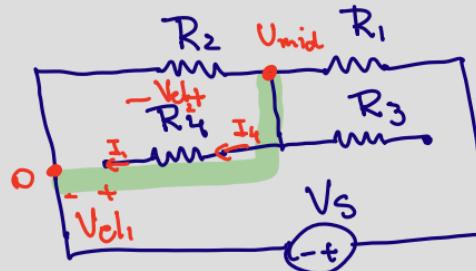Model 2 - imperfect conductor (resistor)
(top and bottom plates)



KCL for el₂

$$I_1 = I_4$$

$$I_1 = 0 \therefore I_4 = 0$$

In this model we added:

el₁: open-circuit

el₂: resistor (R_4)

KVL

$$V_{el1} + V_{el2} = V_{mid} - 0$$


$$V_{el1} + R_4 \cdot I_4 = V_{mid}$$

$$V_{el2} = R_4 \cdot I_4 \text{ (Ohm's Law)}$$

$$V_{mid} = V_{el1}$$

* By measuring V_{el1} we get V_{mid} for any L_{touch} ;
independently of materials used in bottom pane!

An interesting circuit

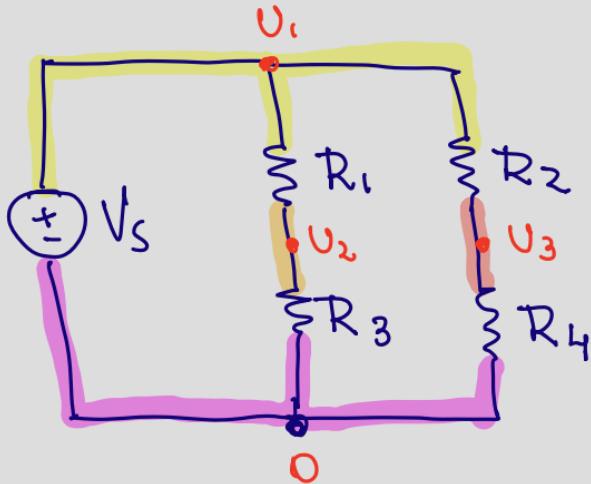

- What are U_2 and U_3 ?


$$U_2 = \frac{R_3}{R_1 + R_3} \cdot V_s$$

$$U_3 = \frac{R_4}{R_2 + R_4} \cdot V_s$$

$$U_2 - 0 = \frac{R_3}{R_1 + R_3} \cdot (V_s - 0)$$


$$U_3 - 0 = \frac{R_4}{R_2 + R_4} \cdot (V_s - 0)$$

$$U_1 - 0 = V_s$$

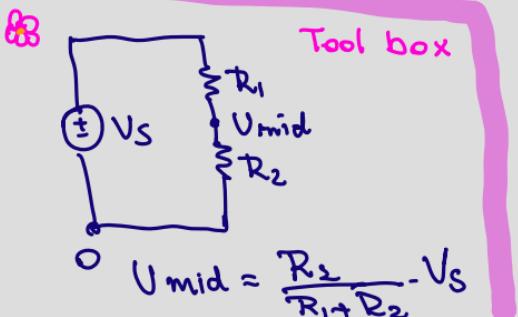

$$U_{mid} = \frac{R_2}{R_1 + R_2} \cdot V_s$$

An interesting circuit

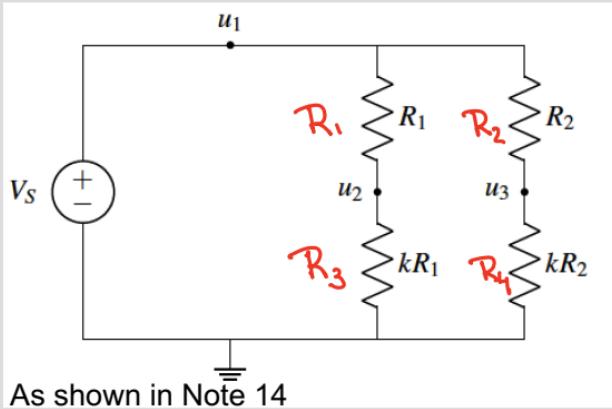

Power supply keeps
U in wires equal
to V_s regardless of
how many branches
we have!

$$U_2 = \frac{R_3}{R_1 + R_3} \cdot V_s$$

$$U_3 = \frac{R_4}{R_2 + R_4} \cdot V_s$$



$$U_2 = \frac{kR_1}{R_1 + kR_1} \cdot V_s \quad \therefore U_2 = \frac{k}{1+k} V_s$$

$$U_3 = \frac{kR_2}{R_2 + kR_2} \cdot V_s \quad \therefore U_3 = \frac{k}{1+k} V_s$$

$$U_2 = U_3$$

wow!

Let's add on more resistor

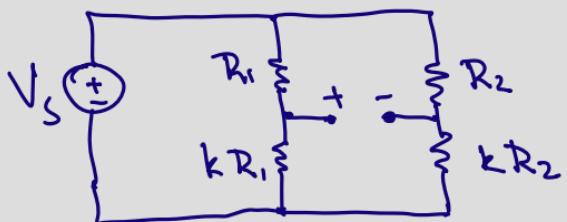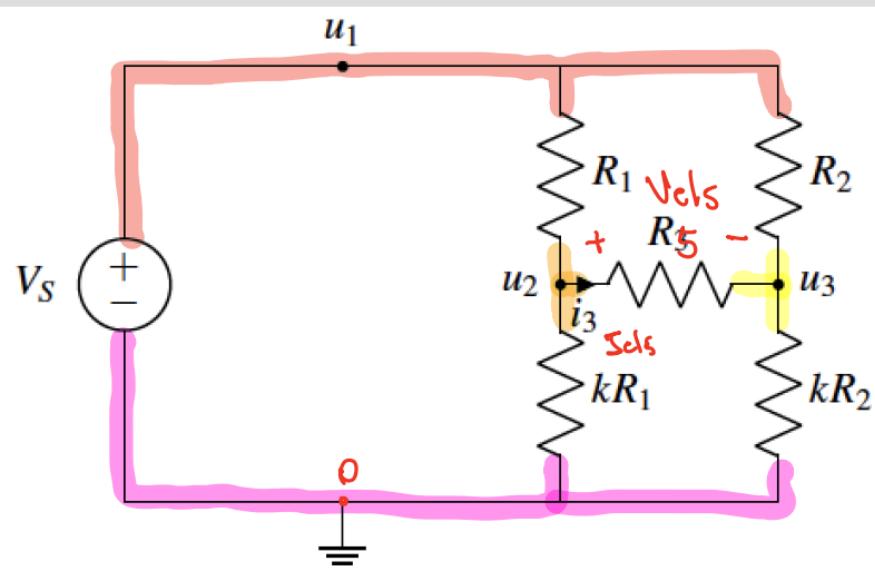

$\text{Elem}_5 = \text{resistor } (R_5)$

$V_{els} = U_2 - U_3$ (Voltage Def.)

Bold Assumption

$$V_{els} = 0$$

$$\text{if } V_{els} = 0 \Rightarrow I_{els} = \frac{V_{els}}{R_5} = 0$$



$$\text{if } I_{els} = 0$$

The circuit is the same as the one we already analysed without R_5 .

We showed : $U_2 = U_3$

$$\boxed{V_{els} = U_2 - U_3 = 0}$$

2D Touch Screen

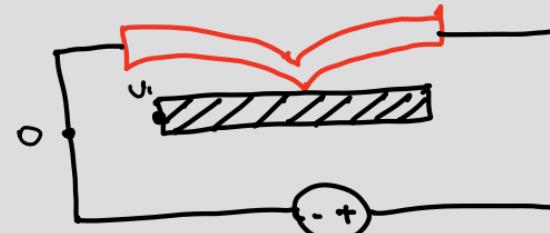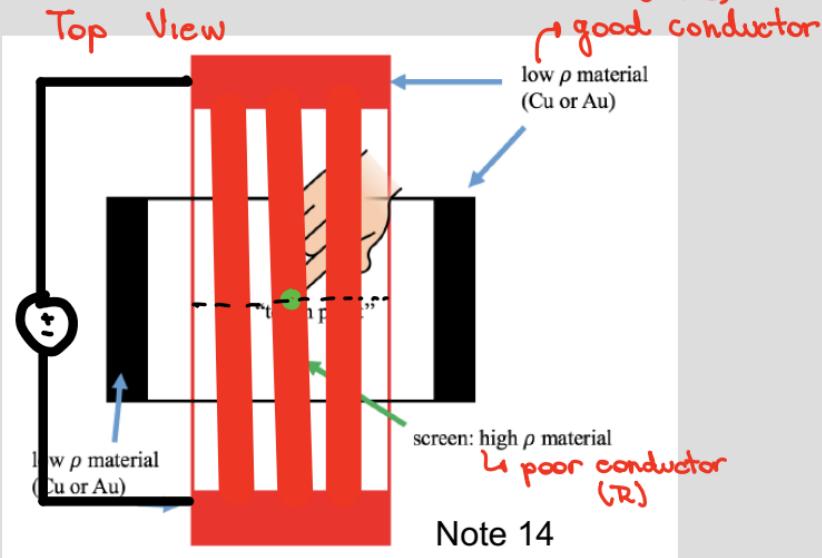


This is our interesting circuit

$$V_{midv} = V_{left} = V_{right}$$


$$V_{midv} = \frac{R_{touch}}{R_{rest} + R_{touch}} \cdot V_s$$

$$R_{rest} + R_{touch}$$
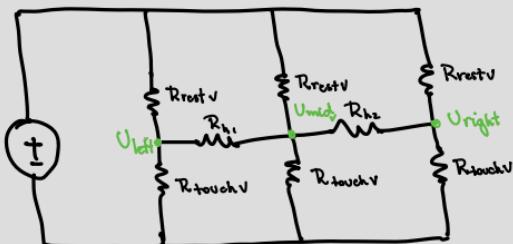
$$V_{midv} = \frac{\rho \frac{h_{touch}}{A}}{\rho \frac{h_{rest}}{A} + \rho \frac{h_{touch}}{A}} \cdot V_s$$



Top Plate Model

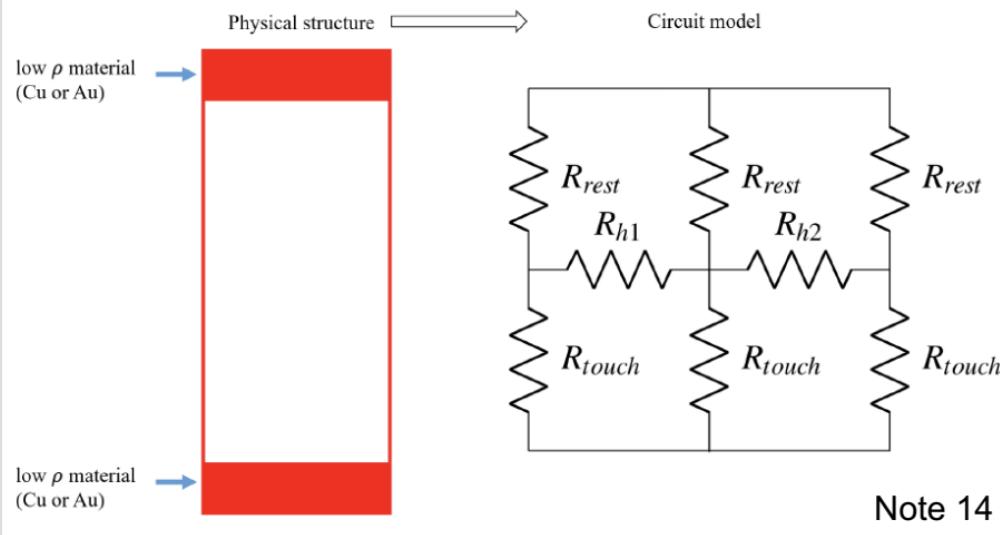


$$U_{midv} = \frac{h_{touch}}{L_{rest} + h_{touch}} \cdot V_s$$

* This gives vs
the vertical
position in the
screen.

What is the next step in the
model?

Bottom Plate Model

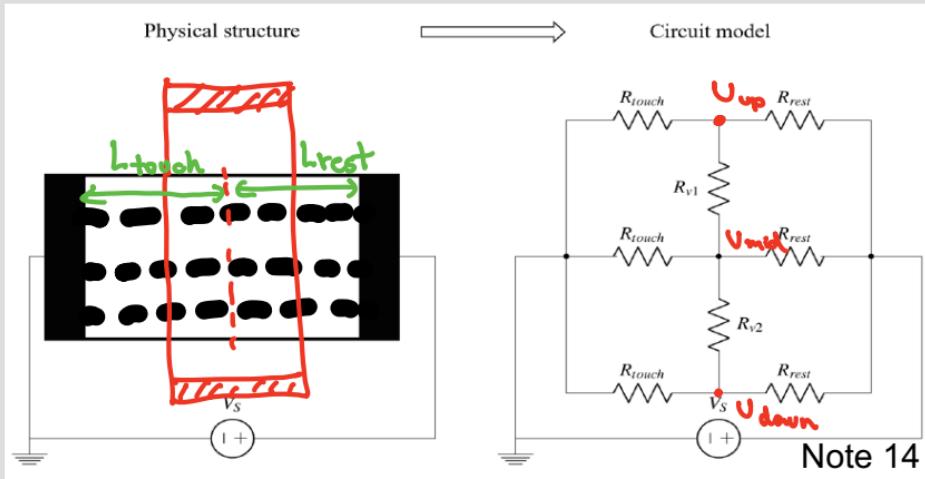

$$V_{up} = V_{mid} = V_{down}$$

$$V_{mid_H} = \frac{R_{touch_H}}{R_{rest} + R_{touch}} \cdot V_S$$

$$V_{mid_H} = \frac{L_{touch_H}}{L_H} \cdot V_S$$

L_H gives us Horizontal information