

Welcome to EECS 16A!

Designing Information Devices and Systems I





Ana Claudia Arias and Miki Lustig
Fall 2021

Module 2
Lecture 9
Operational Amplifier and Comparator
(Note 18)



Last Class...

Side view

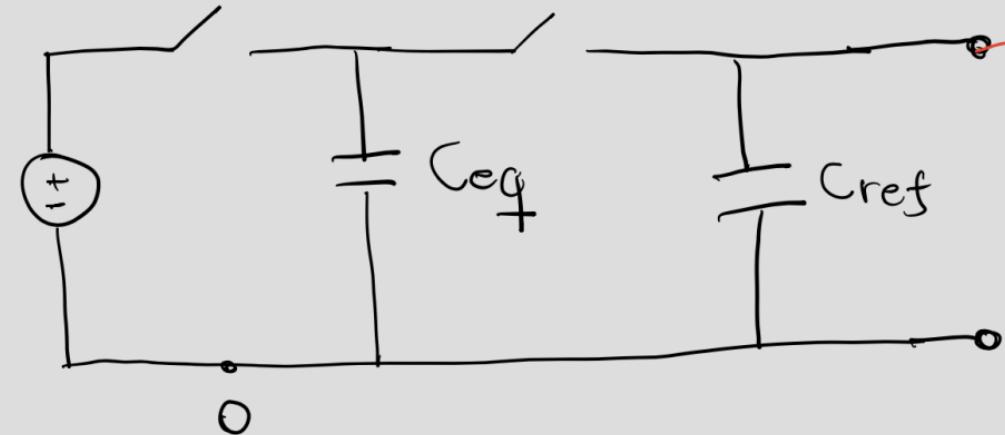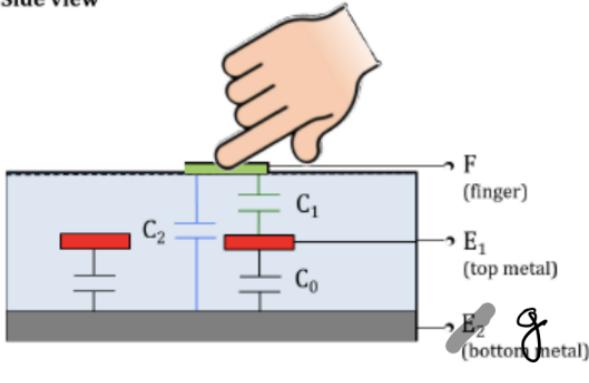


when no touch:




$$\Rightarrow V_{out} = \frac{C_0}{C_0 + C_{ref}} \cdot V_s$$

with touch:

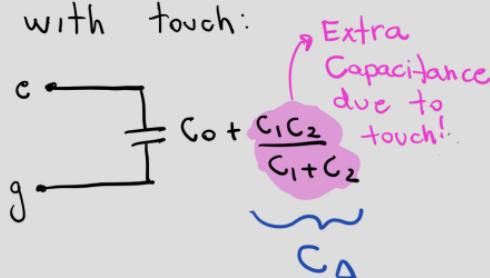

$$\Rightarrow V_{out} = \frac{(C_0 + C_\Delta)}{C_0 + C_\Delta + C_{ref}} \cdot V_s$$

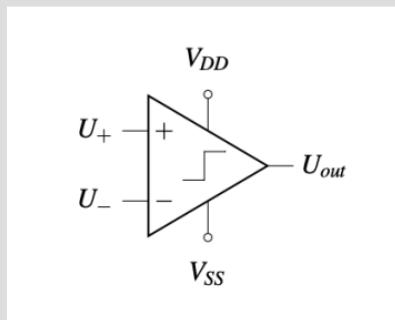How can we go from voltage measurement to binary
answer: touch or no touch?




- We need to choose a Voltage that we call : Threshold Voltage (V_{th})
- Above $V_{th} \therefore 1$ (touch)
- Below $V_{th} \therefore 0$ (no-touch)


We need to compare Voltages to determine if 1 or 0

How can we go from voltage measurement to binary
answer: touch or no touch?

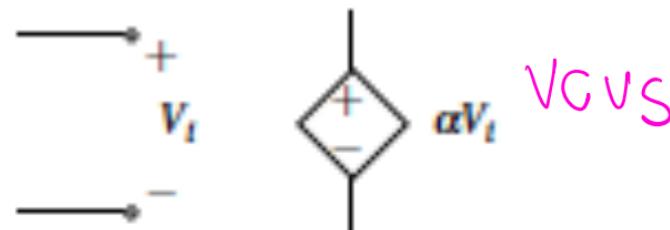
- New tools are needed – new circuit elements



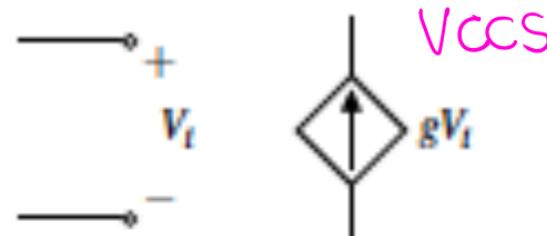
Voltage-controlled voltage source
Op - Amps



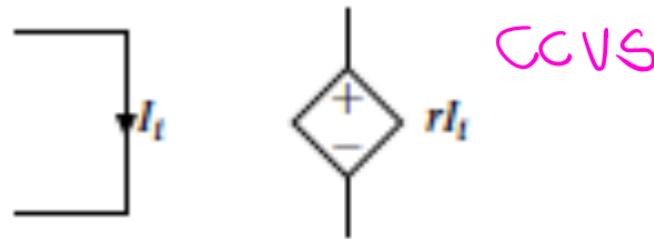Voltage-controlled current source
Transistors




Current-controlled voltage source

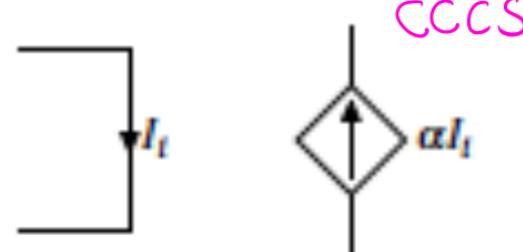


Current-controlled current source

An example of an Op-amp circuit diagram

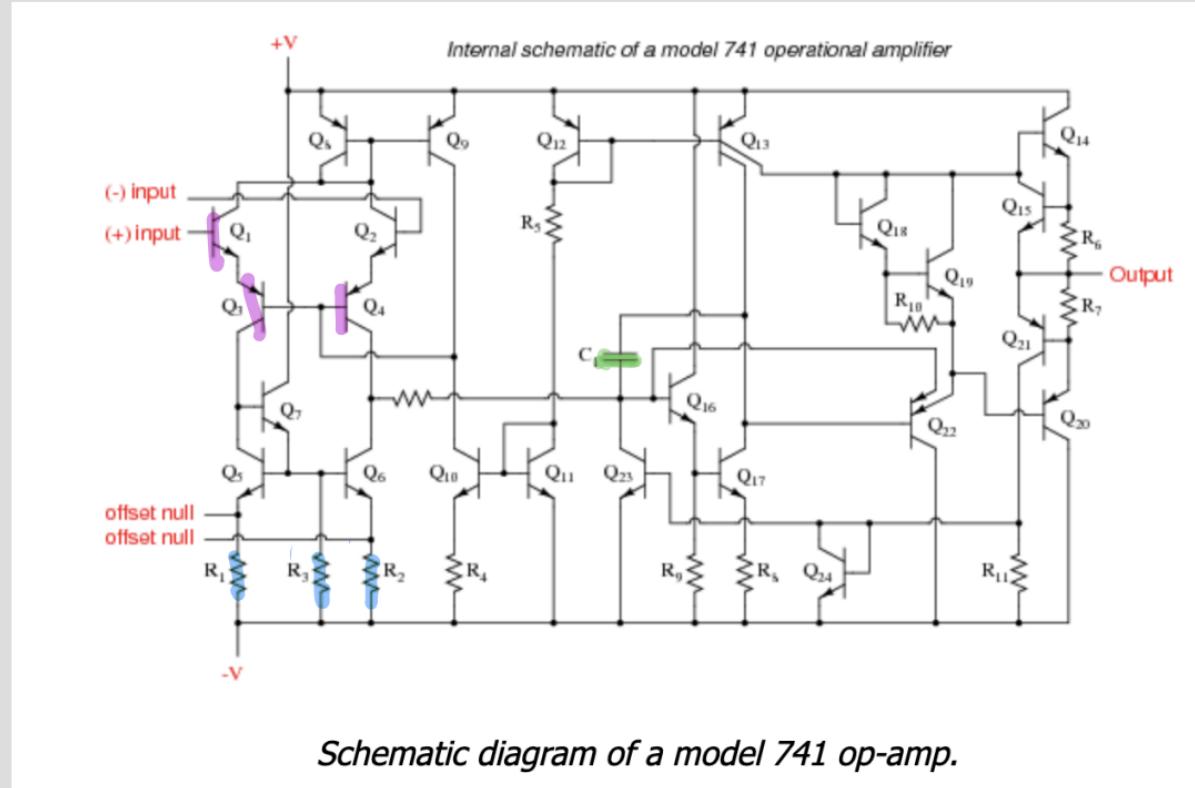


Operational Amplifier

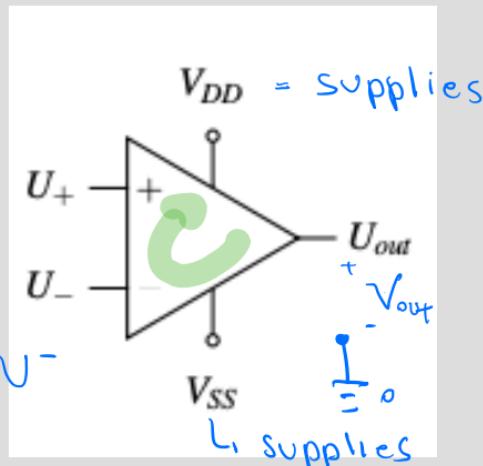An op-amp (operational amplifier) is a device that transforms a small voltage difference into a very large voltage difference.



An op-amp has two input terminals marked (+) and (-) with potentials U_+ and U_- , two power supply terminals called V_{DD} and V_{SS} , and one output terminal with potential U_{out} .

Model

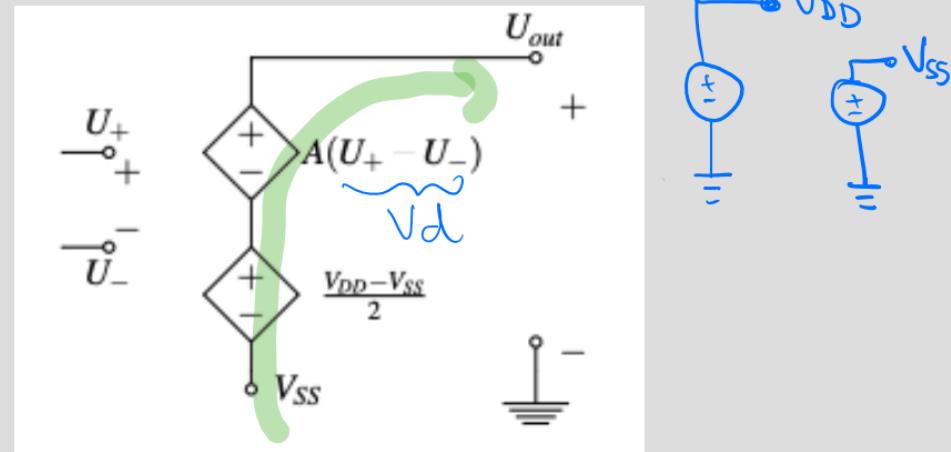


$$V_{out} = V_{ss} + \frac{V_{dd} - V_{ss}}{2} + A \cdot V_d$$

when


$$V_{ss} \leq \frac{V_{dd} - V_{ss}}{2} + A \cdot V_d \leq V_{dd}$$

Operational Amplifier

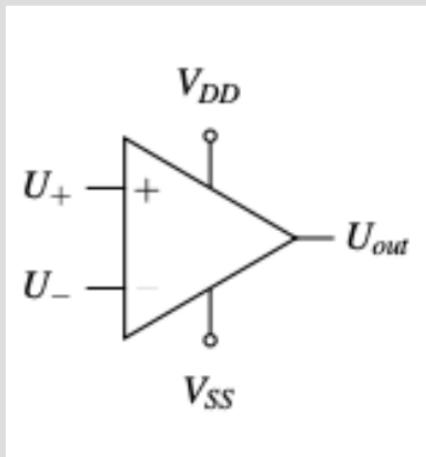An op-amp (operational amplifier) is a device that transforms a small voltage difference into a very large voltage difference.



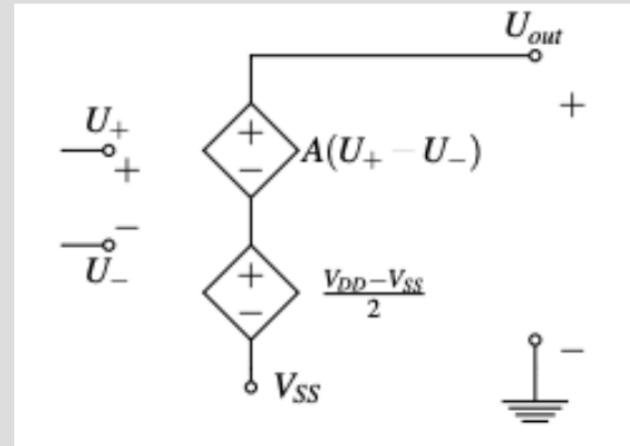An op-amp has two input terminals marked (+) and (-) with potentials U_+ and U_- , two power supply terminals called V_{DD} and V_{SS} , and one output terminal with potential U_{out} .




$$V_{out} = V_{DD} \quad \text{if} \quad V^* > V_{DD}$$

$$V_{out} = V_{SS} \quad \text{if} \quad V^* < V_{SS}$$

Can be used to compare Voltage



Comparator – optimized for binary output

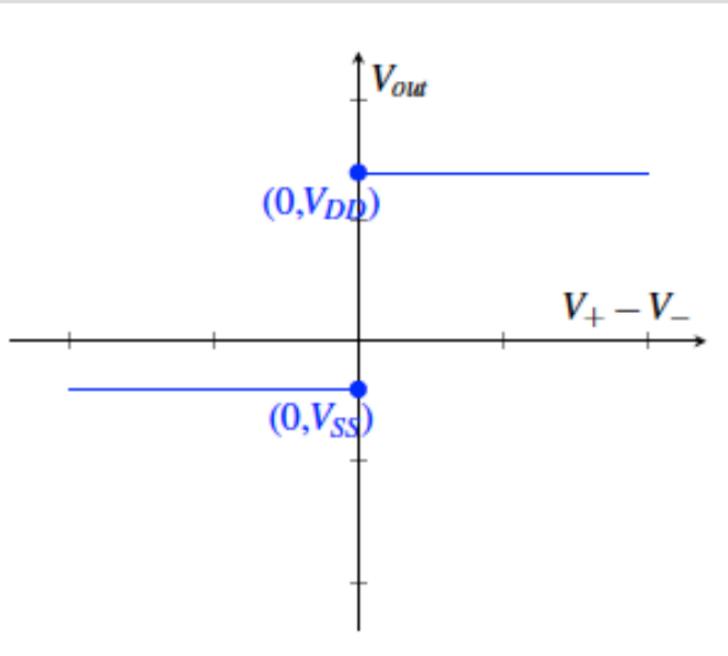

V_{DD} can be much
higher than V_{SS}
..
it amplifies the
Signal.

Comparator – optimized for binary output


Also optimized for speed

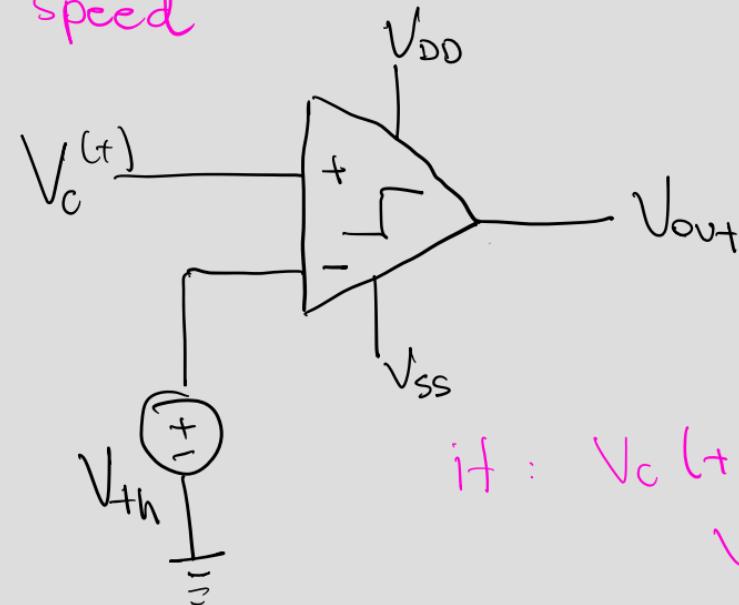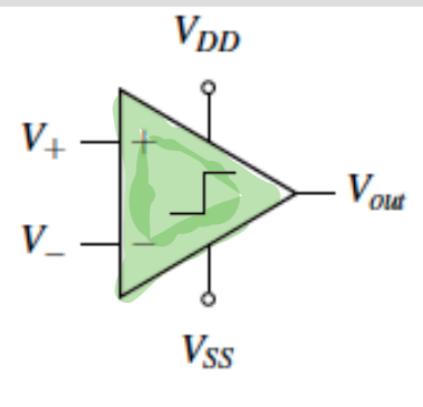


if : $V_c^{(+)} > V_{Th}$
 $V_{out} = V_{DD}$

if : $V_c^{(+)} \leq V_{Th}$
 $V_{out} = V_{SS}$

Back to our Capacitive Touchscreen

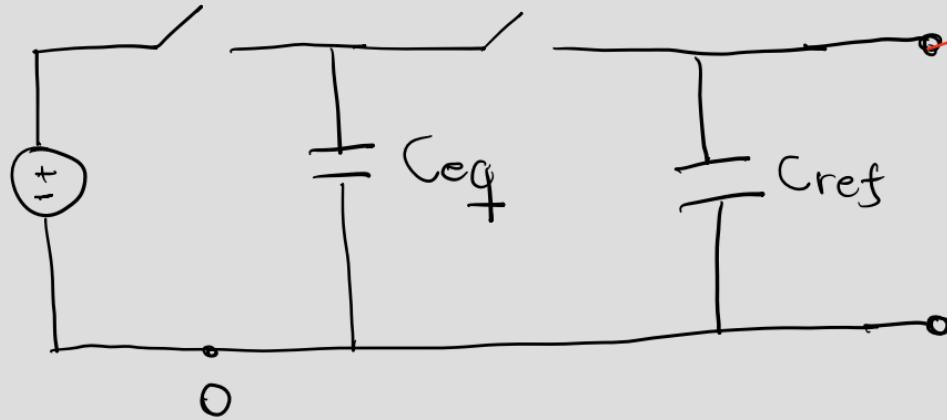


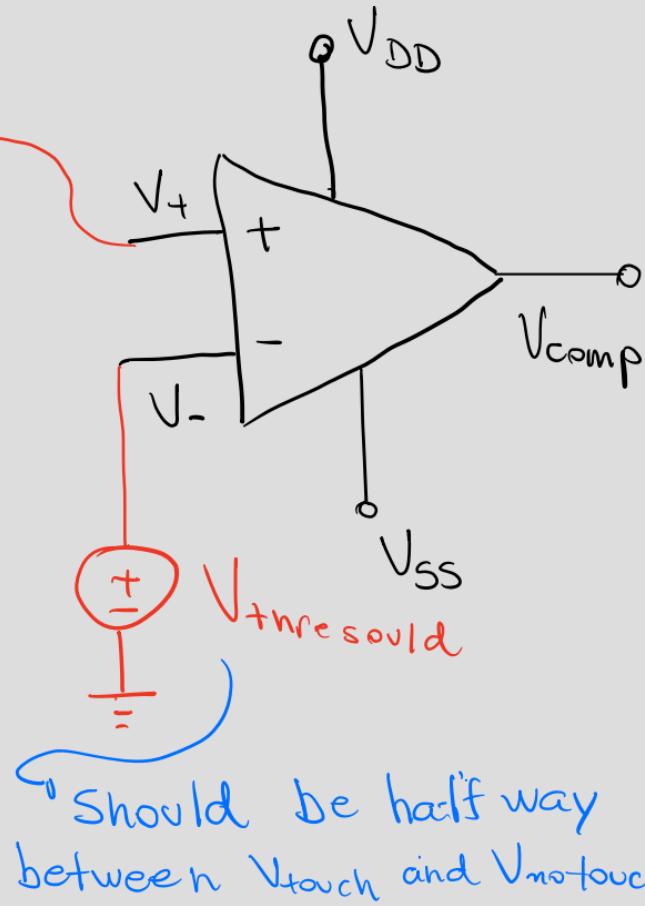$C_{eq} \Rightarrow C_0 + C_A$ - touch
 C_0 - no touch
 V_{DD} touch
notouch V_{SS}





New Design – Let's play music


* Want to play music LOUD

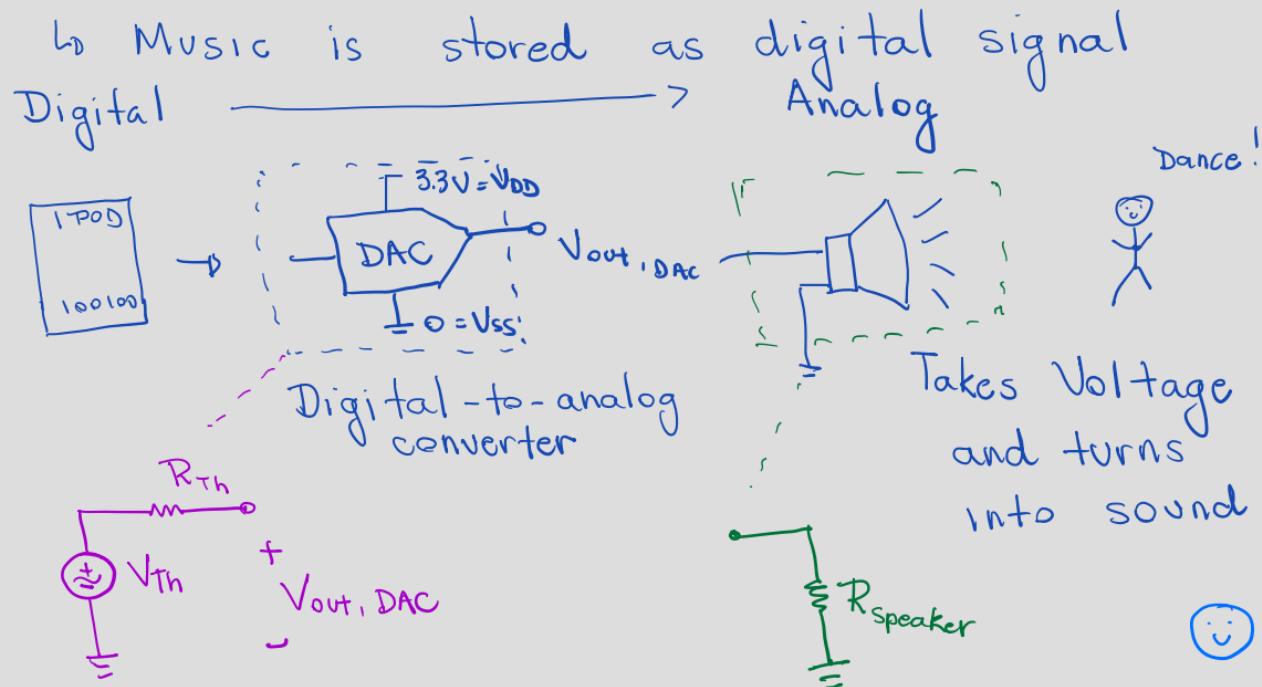

Digital to Analog Converter - DAC

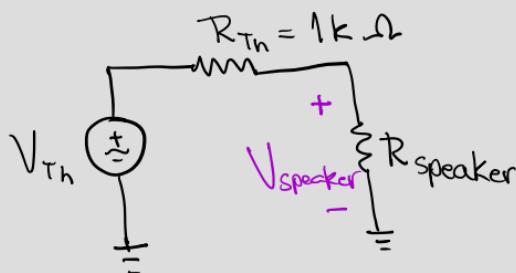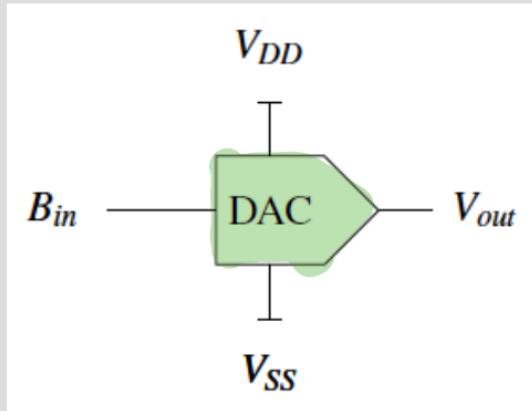

Voltage Divider

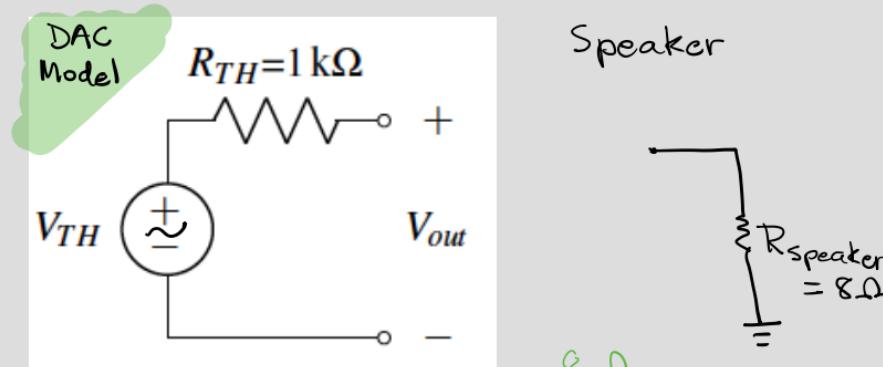

$$V_{speaker} = \frac{R_{speaker}}{R_{TH} + R_{speaker}} \cdot V_{TH}$$


$$V_{speaker} = \frac{V_{TH}}{128}$$

Not loud!
Too quiet!

Need to isolate DAC.



Digital to Analog Converter - DAC

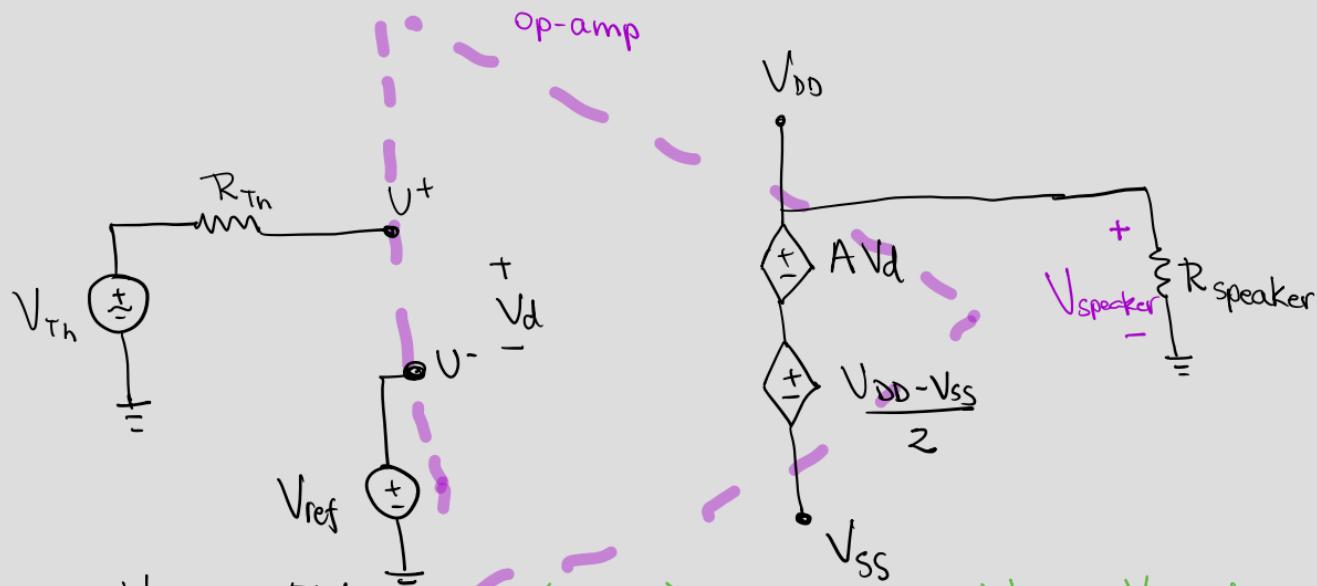


10V output
(Input)

$$V_d = U^+ - U^- = V_{Th} - V_{ref}$$


$$V_{speaker} = V_{ss} + \frac{V_{DD} - V_{ss}}{2} + AV_d = AV_d$$

~~$\frac{V_{DD} + V_{ss}}{2}$~~

when: $V_{ss} < AV_d < V_{DD}$

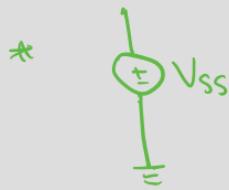

Digital to Analog Converter - DAC

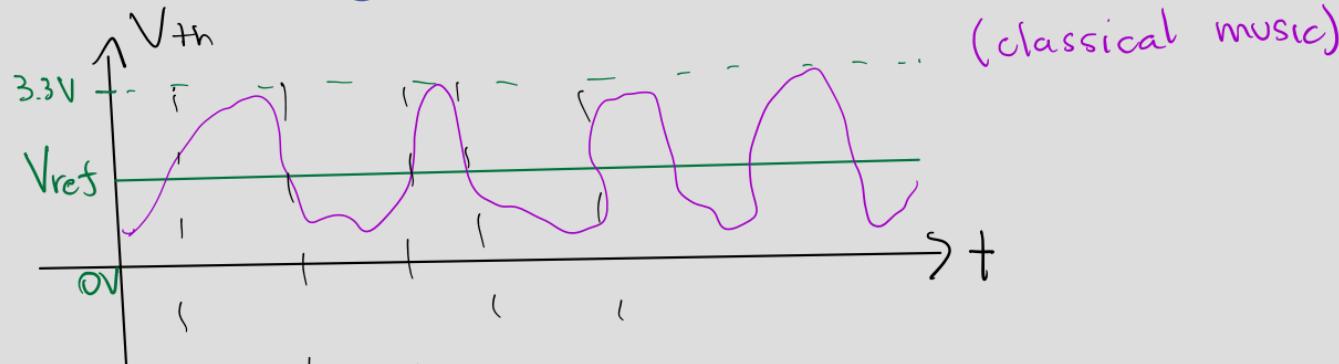

Need to isolate DAC with controllable gain!

Negative Feedback

$$S_{err} = S_{in} - S_{fb}$$


$$S_{out} = A \cdot S_{err}$$

$$S_{fb} = f \cdot S_{out}$$

$$\frac{S_{out}}{A} = S_{in} - S_{fb}$$

$$S_{out} \left(\frac{1}{A} + f \right) = S_{in}$$
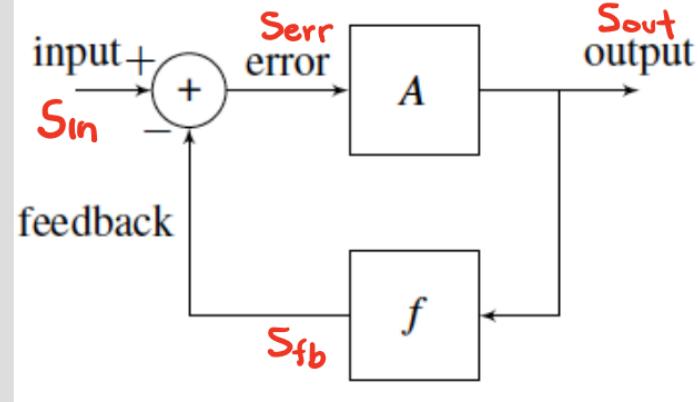
$$\frac{S_{out}}{S_{in}} = \frac{1}{\frac{1}{A} + f} = \frac{A}{1 + Af}$$



- Making small adjustments to correct output on the fly
- Basis of control theory
- Many examples in daily life:
 - Biology
 - Self-driving car
 - Human driving car
 - Hand-eye coordination
 - ...

Negative Feedback

$$\frac{S_{out}}{S_{in}} = \frac{A}{1+Af}$$

- {
- Describes the behaviour of the system - transfer function.
 - How S_{out} depends on S_{in}


$$\frac{S_{out}}{S_{in}} = \frac{1}{f} \quad A \rightarrow \infty$$

↳ We control the output via block f !


So $V_{out} = \frac{1}{f} V_{in}$ for very large gain.

↳ we can set f to get any output.
(Beautiful result) :)

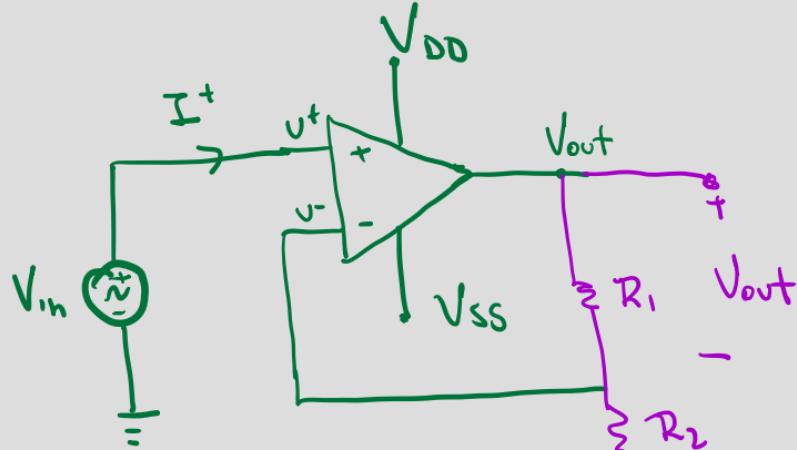Need to isolate the DAC from speaker - OP-Amp with NFB



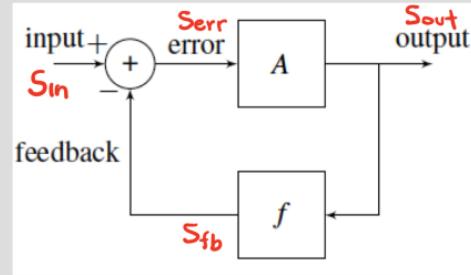- We want to measure V_{out} , take a portion of the signal and feedback as U^-



$$U^+ = S_{in}$$


$$V_{out} = S_{out}$$

$$U^- = S_{fb}$$

$$U^+ - U^- = S_{err}$$

Op-Amp in negative feedback

Non-inverting op-amp

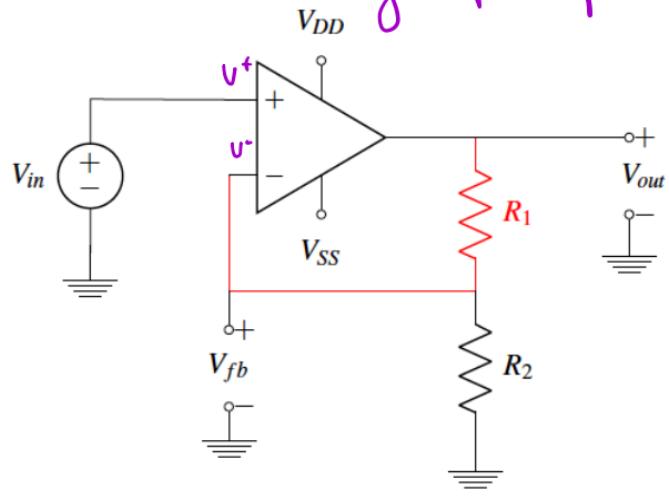


$$(1) \quad V_d = V^+ - V^- = V_{in} - V_{sb}$$

$$(2) \quad V_{out} = AV_d$$


$$(3) \quad V_{sb} = \frac{R_2}{R_1 + R_2} \cdot V_{out}$$

"BUFFER circuit"

Model:

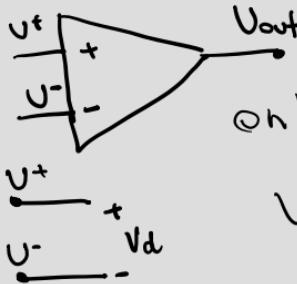

only for
 $V_{ss} < V_{out} < V_{DD}$

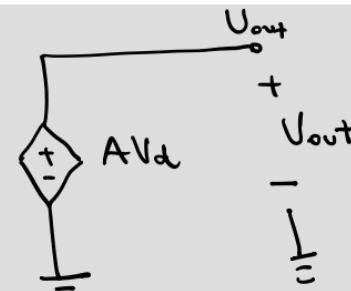

Simpler model as the second source is not "needed".

$$V_{out} = A (V_{in} - f \cdot V_{out})$$

$$V_{out} (1 + AF) = A V_{in}$$

$$A_v = \text{Gain} = \frac{V_{out}}{V_{in}} = \frac{A}{1+AF}$$

$$A_v = \frac{1}{f} \quad \text{if } A \rightarrow \infty \quad \Rightarrow \quad \frac{R_1 + R_2}{R_2} = 1 + \frac{R_1}{R_2}$$

Golden Rules of Op-Amps

For our design we want $A = 3$

$$V_d = \frac{V_{out}}{A} \quad \text{if } A \rightarrow \infty$$


$$V_d = \frac{1}{A} \cdot \frac{A}{1+A_f} V_{in} = \frac{V_{in}}{1+A_f} = 0$$

In NFB : $V^+ = V^-$ and $A \rightarrow \infty$


Rules: (Golden Rules)

(1) $I^+ = I^- = 0$ (always true)

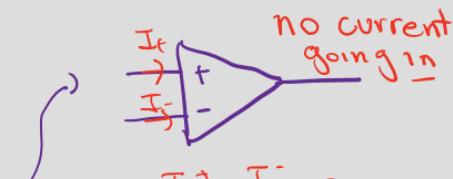(2) $V^+ = V^-$ (only in NFB & $A \rightarrow \infty$)



Let's go back to playing music

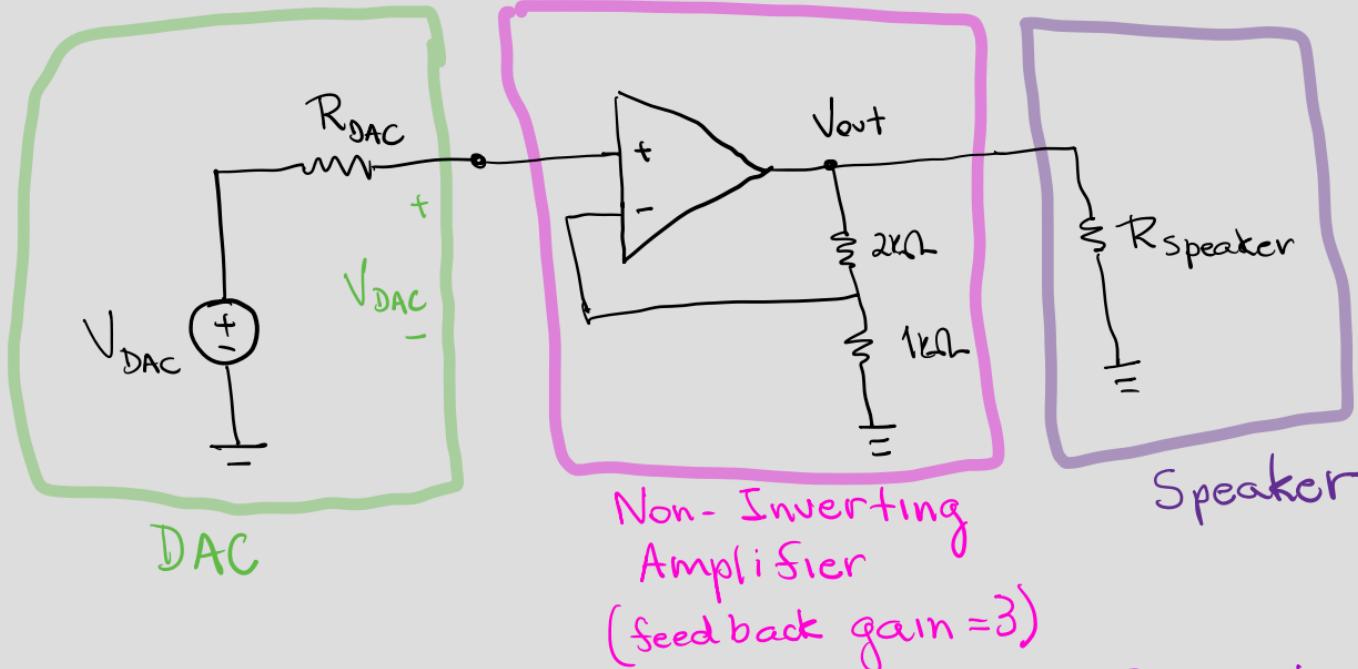

Party time!
Yay!