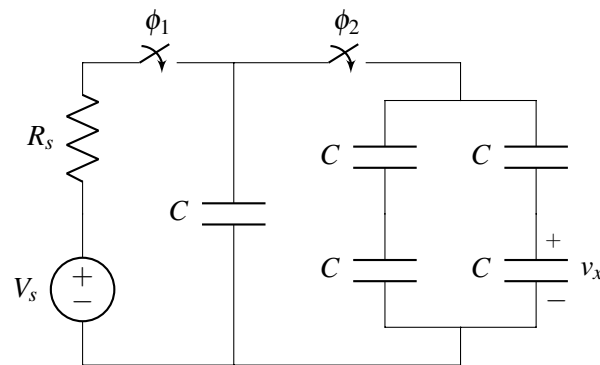


1. Module 2 Review

Optional Review Problems:

2. Charge-Sharing (Fall 2016 MT2)

Initially, all capacitors are uncharged and have the same capacitance C . For $t < 0$, the switch ϕ_1 is *closed*, ϕ_2 is *open*, and the circuit has achieved steady state. Later, at $t = 0$, ϕ_1 is *open* and ϕ_2 is *closed*; then the system is allowed to reach steady state.




What is the voltage v_x at $t \gg 0$?

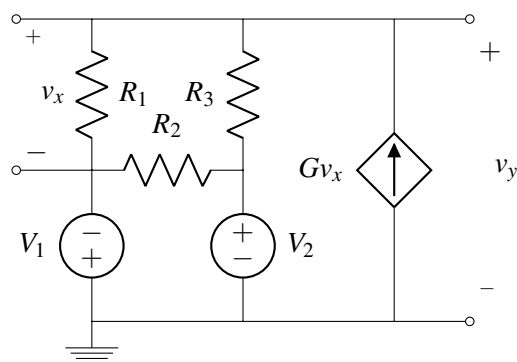
3. Take Node of the Voltage Sources (Fall 2016 MT2)

Use nodal analysis to solve for the voltages v_x and v_y . Use the following values for numerical calculations. **Note the polarity on the voltage sources.**

$$\begin{aligned} V_1 &= 5\text{ V} & R_1 &= 10\ \Omega \\ V_2 &= 5\text{ V} & R_2 &= 50\ \Omega \\ G &= \frac{1}{4}\text{ S} & R_3 &= 40\ \Omega \end{aligned}$$



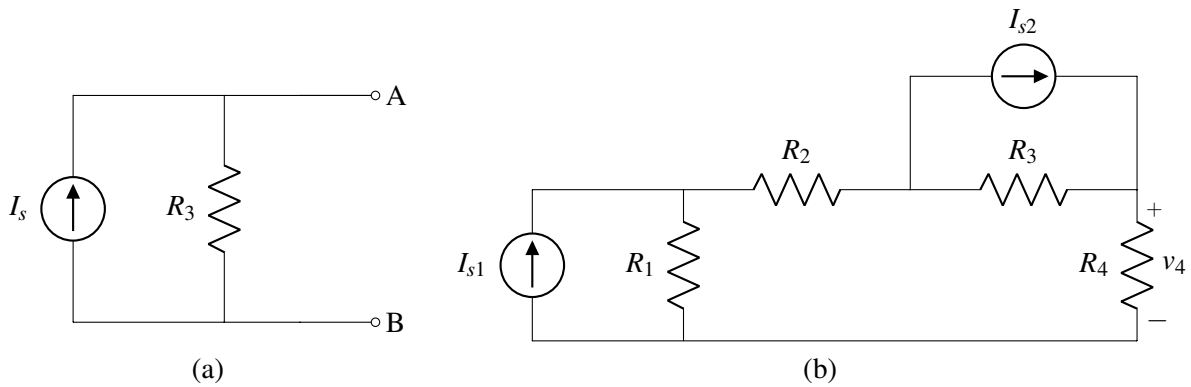4. One Norton at a Time! (Spring 2017 MT2)



- (a) Given the circuit labeled (a), draw the Thévenin equivalent circuit for $I_s = \frac{1}{5} \text{A}$ and $R_3 = 20 \Omega$ and determine V_{th} and R_{th} .
- (b) Redraw the circuit labeled (b) with the following restrictions: you must use only voltage sources and the given four resistors. Determine the value of the voltage sources given $R_1 = 30 \Omega$, $R_2 = 10 \Omega$, $R_3 = 20 \Omega$, $R_4 = 10 \Omega$, $I_{s1} = \frac{1}{3} \text{A}$, and $I_{s2} = \frac{1}{5} \text{A}$.
- (c) Calculate the voltage drop across R_4 .