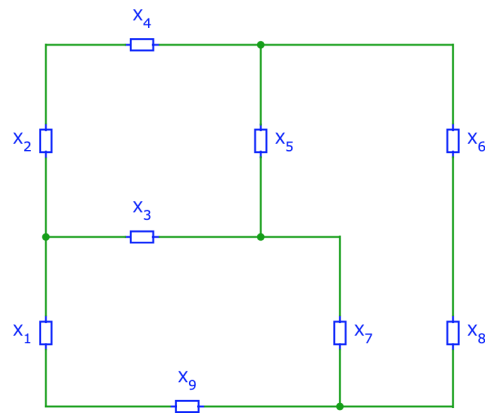


# EECS 16A Designing Information Devices and Systems I

## Summer 2020 Discussion 3A

### 1. Nodes and Branches

In the circuit shown below, label and count all nodes and branches.



**Answer:** There are seven nodes and nine branches.

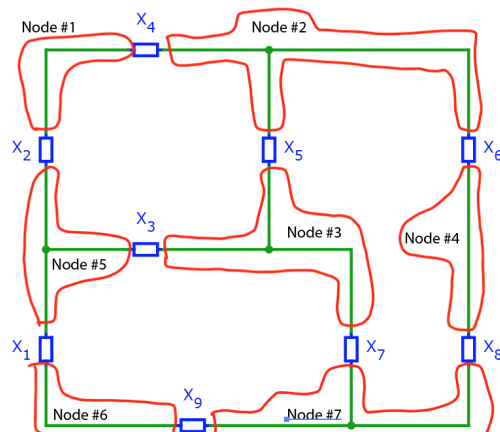


Figure 1: Labeled Nodes


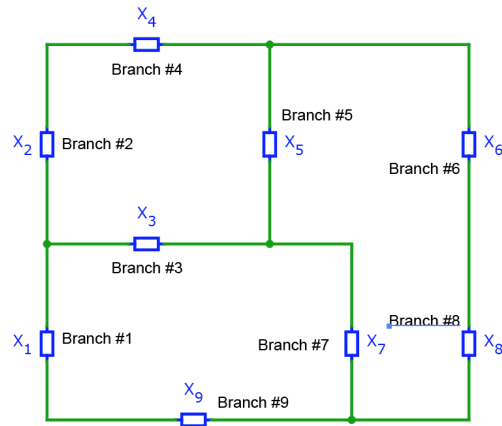


Figure 2: Labeled branches


## 2. A Simple Circuit

Use KVL and/or KCL to solve the following circuits.

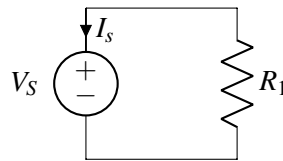- (a) For this problem assume  $V_S = 1V$  and  $R_1 = 1k\Omega$ . Find the current,  $I_s$  flowing through the voltage source.



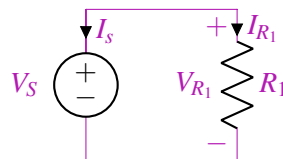**Answer:** Since this circuit has only 2 terminals we can find the current flowing through  $I_s$  without precisely following the algorithm outlined in lecture. In fact we can even not assign a ground potential. Labeling element voltages and currents we have:



Using KVL and Ohm's law we get:


$$V_S = V_{R_1} \quad (1)$$

$$I_{R_1} = \frac{V_{R_1}}{R_1} = \frac{V_S}{R_1} \quad (2)$$


Finally through KCL on the top node we obtain:

$$I_s + I_{R_1} = 0 \Rightarrow I_s = -I_{R_1} = -\frac{V_S}{R_1} = -1mA \quad (3)$$

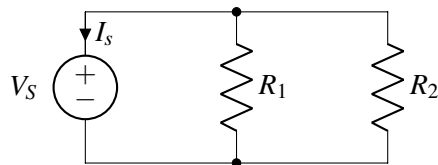- (b) For this problem assume  $V_S = 1V$ ,  $R_1 = 2k\Omega$ , and  $R_2 = 2k\Omega$ . Find the current,  $I_s$  flowing through the voltage source.



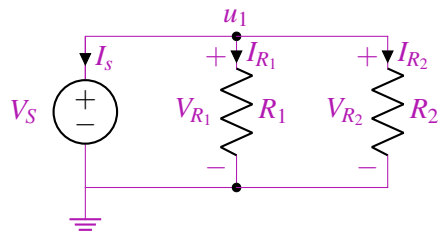**Answer:** Again we can follow the same procedure since we still have two terminals. Let's label again all element voltages and currents.



Here we have also assigned a ground node and labeled the other node of the circuit as  $u_1$ . Once again we will use KVL and Ohm's law:

$$V_S = V_{R_1} = V_{R_2} \quad (4)$$

$$I_{R_1} = \frac{V_{R_1}}{R_1} = \frac{V_S}{R_1} \quad (5)$$

$$I_{R_2} = \frac{V_{R_2}}{R_2} = \frac{V_S}{R_2} \quad (6)$$

$$(7)$$

Then writing out KCL and substituting from above we have:

$$I_{R_1} + I_{R_2} + I_S = 0 \quad (8)$$

$$\frac{V_S}{R_1} + \frac{V_S}{R_2} + I_S = 0 \Rightarrow I_S = - \left( \frac{V_S}{R_1} + \frac{V_S}{R_2} \right) \quad (9)$$


Plugging in,

$$I_S = -1mA \quad (10)$$

Notice that we did not make use of node  $u_1$  or the ground node anywhere.
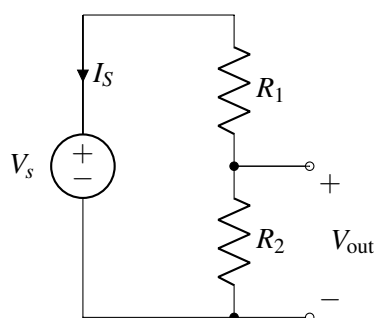
### 3. Practice: Voltage Divider


For the circuit below, find the voltage  $V_{out}$  in terms of the resistances  $R_1$ ,  $R_2$ , and  $V_S$ .




**Answer:**

In this example we will go through all the steps that we saw in lecture one-by-one.


Step 1: Select a ground node,

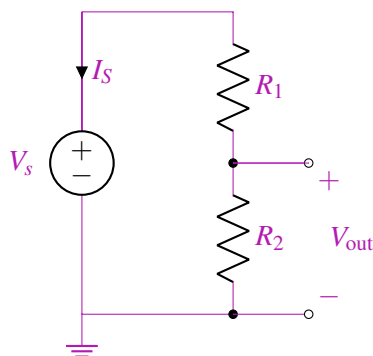

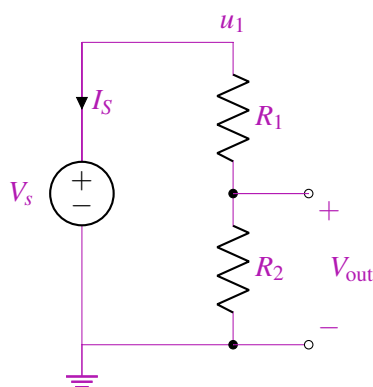
Step 2: Label all nodes with voltage set by voltage sources (denoted below as  $u_1$ ),



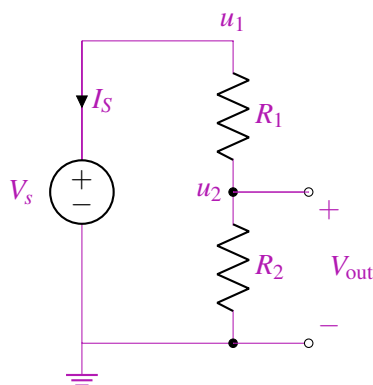Step 3: Label remaining nodes (denoted below as  $u_2$ ),



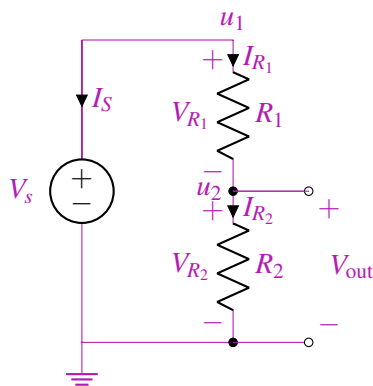Step 4: Label element voltages and currents,



Step 5: Write KCL equations for all nodes with unknown voltages (namely  $u_2$ ):

$$I_{R_2} = I_{R_1}$$

Step 6: Find expressions for all element currents in terms of element voltages and characteristics,

$$I_{R_1} = \frac{V_{R_1}}{R_1} = \frac{u_1 - u_2}{R_1} = \frac{V_s - u_2}{R_1}$$

$$I_{R_2} = \frac{V_{R_2}}{R_2} = \frac{u_2 - 0}{R_2}$$

Where we used the fact that  $u_1 = V_s$

Step 7: Substitute expressions found in 6 into the KCL equations from step 5,

$$I_{R_2} = I_{R_1}$$

$$\Rightarrow \frac{V_s - u_2}{R_1} = \frac{u_2 - 0}{R_2}$$

$$\Rightarrow (V_s - u_2)R_2 = u_2R_1$$

$$\Rightarrow u_2 = \frac{R_2}{R_1 + R_2}V_s$$

Now we have two unknowns,  $i_x$  and  $u_2$ , and two equations. We can solve them directly for  $u_2$ . Notice that  $V_{\text{out}} = u_2 - 0 = u_2$

$$V_{\text{out}} = u_2 = \frac{R_2}{R_1 + R_2}V_s$$