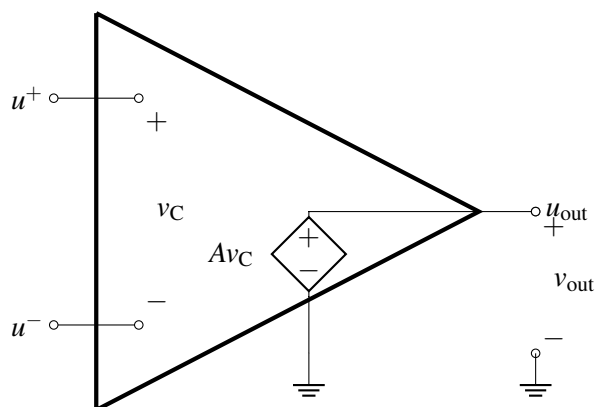


# EECS 16A Designing Information Devices and Systems I

## Summer 2020 Discussion 4D

### 1. Op-Amp Rules and Negative Feedback Rule

Here is an equivalent circuit of an op-amp (where we are assuming that  $V_{SS} = -V_{DD}$ ) for reference:



- (a) What are the currents flowing into the positive and negative terminals of the op-amp (i.e., what are  $I^+$  and  $I^-$ )? Based on this answer, what are some of the advantages of using an op-amp in your circuit designs?

**Answer:**


The  $u^+$  and  $u^-$  terminals have no closed circuit connection between them, and therefore no current can flow into or out of them. This is very good because we can connect an op-amp to any other circuit, and the op-amp will not disturb that circuit in any way because it does not load the circuit (it is an open circuit).

- (b) Suppose we add a resistor of value  $R_L$  between  $u_{out}$  and ground. What is the value of  $v_{out}$ ? Does your answer depend on  $R_L$ ? In other words, how does  $R_L$  affect  $Av_C$ ? What are the implications of this with respect to using op-amps in circuit design?

**Answer:**

Notice that  $u_{out}$  is connected directly to a controlled/dependent voltage source, and therefore  $v_{out}$  will always have to be equal to  $Av_C$  regardless of what  $R_L$  is connected to the op-amp. This is very advantageous because it means that the output of the op-amp can be connected to any other circuit (except a voltage source), and we will always get the desired/expected voltage out of the op-amp.

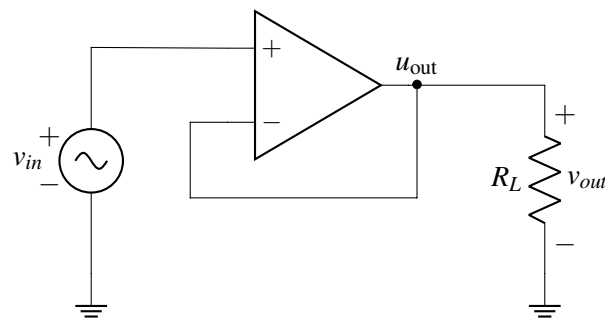**For the rest of the problem, consider the following op-amp circuit in negative feedback:**



- (c) Assuming that this is an ideal op-amp, what is  $v_{out}$ ?

**Answer:**

Recall for an ideal op-amp in negative feedback, we know from the negative feedback rule that  $u^+ = u^-$ . In this case,  $u^- = u_{out} = u^+$ .

- (d) Draw the equivalent circuit for this op-amp and calculate  $v_{out}$  in terms of  $A$ ,  $v_{in}$ , and  $R_L$  for the circuit in negative feedback. Does  $v_{out}$  depend on  $R_L$ ? What is  $v_{out}$  in the limit as  $A \rightarrow \infty$ ?

**Answer:**


Notice that the op-amp can be modeled as a voltage-controlled voltage source. Thus, we have the following equation:

$$\begin{aligned} v_{out} &= A(v_{in} - v_{out}) \\ v_{out} + Av_{out} &= Av_{in} \\ v_{out} &= v_{in} \frac{A}{1+A} \end{aligned}$$

Thus, as  $A \rightarrow \infty$ ,  $v_{out} \rightarrow v_{in}$ . This is the same as what we get after applying the op-amp rule.

Notice that output voltage does not depend on  $R$ . Thus, this circuit acts like a voltage source that provides the same voltage read at  $u^+$  without drawing any current from the terminal at  $u^+$ . This is why the circuit is often referred to as a “unity gain buffer,” “voltage follower,” or just “buffer.”

## 2. An Inverting Amplifier

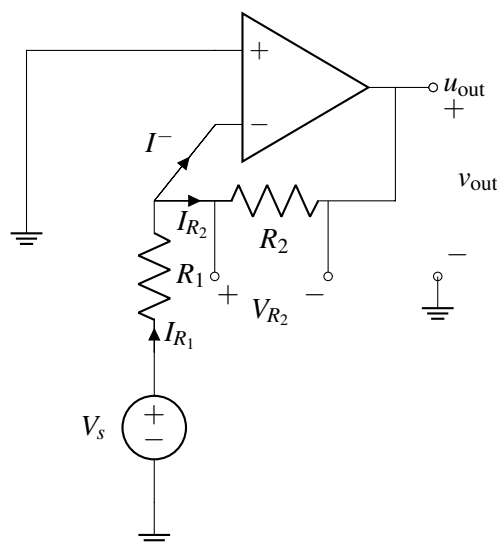

(a) Calculate  $v_{out}$  as a function of  $V_s$  and  $R_1$  and  $R_2$ .


**Answer:**

Because the op-amp is in negative feedback, we know that  $u^+ = u^- = 0\text{ V}$ . Therefore,  $v_{out} = u^- - V_{R_2} = -I_{R_2}R_2$ .

We also know that  $I^- = 0$ , so  $I_{R_1} = I_{R_2}$ . Thus,  $v_{out} = u^- - V_{R_2} = -I_{R_2}R_2 = -I_{R_1}R_2 = -V_s \frac{R_2}{R_1}$ .
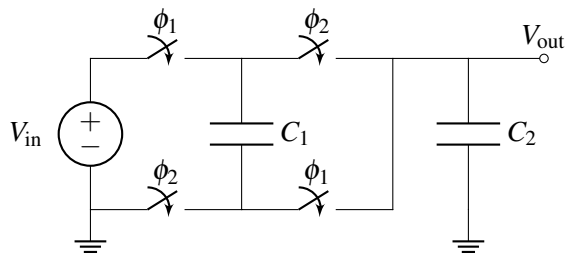
### 3. Charge Sharing


Consider the circuit shown below. In phase  $\phi_1$ , the switches labeled  $\phi_1$  are on while the switches labeled  $\phi_2$  are off. In phase  $\phi_2$ , the switches labeled  $\phi_2$  are on while the switches labeled  $\phi_1$  are off.



(a) Draw the polarity of the voltage (using + and - signs) across the two capacitors  $C_1$  and  $C_2$ . (It doesn't matter which terminal you label + or -; just remember to keep these consistent through phase 1 and 2!)

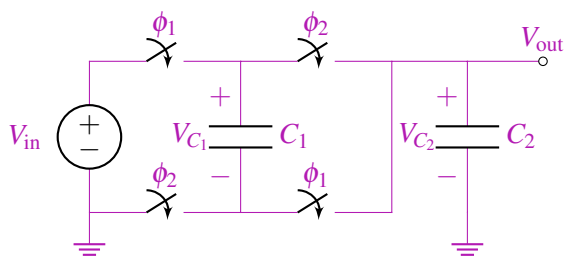**Answer:**


One way of marking the polarities is + on the top plate and - on the bottom plate of both  $C_1$  and  $C_2$ . Let's call the voltage drop across  $C_1$   $V_{C_1}$  and across  $C_2$   $V_{C_2}$ .




(b) Redraw the circuit in phase  $\phi_1$  and phase  $\phi_2$ . Keep your polarity from part (a) in mind.

**Answer:**

Phase  $\phi_1$

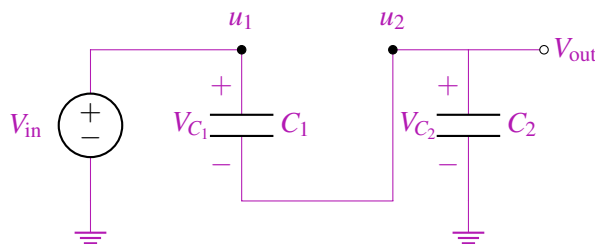

Phase  $\phi_2$

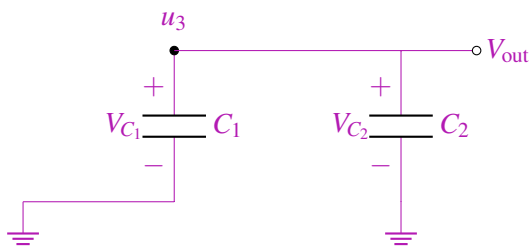

- (c) Find  $V_{\text{out}}$  in phase  $\phi_2$  as a function of  $V_{\text{in}}$ ,  $C_1$ , and  $C_2$ .

**Answer:**

First, we must identify the floating node in phase  $\phi_2$ . For this circuit, the floating node is  $u_3$ , as we can see that charge on the “+” plates of  $C_1$  and  $C_2$  cannot flow to ground.

Now that we know what plates are connected to our floating node, we must find the charge on those plates in phase  $\phi_1$ . The two capacitors in series have a total capacitance of  $C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$ . We know that there is a voltage of  $V_{\text{in}}$  across this capacitor and thus  $Q_{C_{eq}} = V_{\text{in}} \frac{C_1 C_2}{C_1 + C_2}$  charge. Because they’re in series, we know that the charge across the equivalent capacitance is the same as a charge across each individual capacitor. Since we are looking for the charge on the “+” terminals of those capacitors it will be:

$$\begin{aligned} Q_{u_3}^{\phi_1} &= Q_{C_1} + Q_{C_2} \\ &= 2Q_{C_{eq}} \\ &= 2V_{\text{in}} \frac{C_1 C_2}{C_1 + C_2} \end{aligned}$$

Similarly, we must find the charge on those plates in phase  $\phi_2$ .

$$\begin{aligned} Q_{u_3}^{\phi_2} &= V_{C_1} C_1 + V_{C_2} C_2 \\ &= (u_3 - 0)C_1 + (u_3 - 0)C_2 \\ &= (V_{\text{out}} - 0)C_1 + (V_{\text{out}} - 0)C_2 \\ &= V_{\text{out}}(C_1 + C_2) \end{aligned}$$

Because of the conservation of charge, we can equate the total charge in phase  $\phi_1$  and phase  $\phi_2$ .

$$\begin{aligned} Q_{u_3}^{\phi_1} &= Q_{u_3}^{\phi_2} \\ 2V_{\text{in}} \frac{C_1 C_2}{C_1 + C_2} &= V_{\text{out}}(C_1 + C_2) \\ V_{\text{out}} &= 2 \frac{C_1 C_2}{(C_1 + C_2)^2} V_{\text{in}} \end{aligned}$$

- (d) How will the charges be distributed in phase  $\phi_2$  if we assume  $C_1 \gg C_2$ ?

**Answer:**

We know that the capacitors are in parallel in phase  $\phi_2$ , so the voltage across both capacitors is the same. Considering that  $Q = CV$ , if  $C_1 \gg C_2$ , then  $Q_1 \gg Q_2$ .