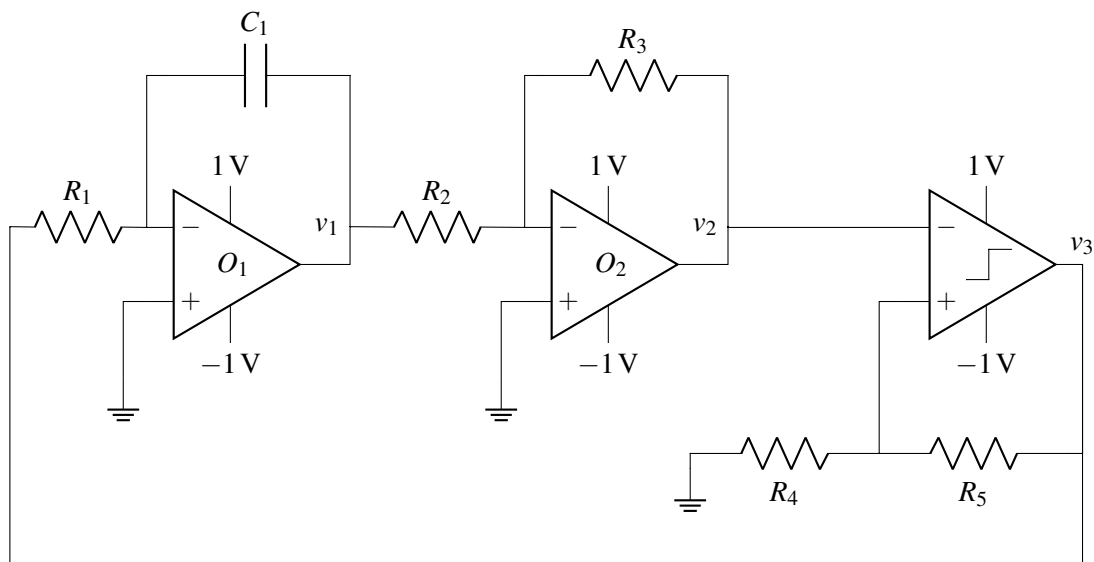


EECS 16A Designing Information Devices and Systems I

Summer 2020 Discussion 5C

1. Timer Circuit

In this problem, we will walk through another useful, real-world circuit, the timer circuit. The circuit is shown below. All resistors have a resistance of $1\text{ k}\Omega$ and $C_1 = 1\text{ }\mu\text{F}$.



- (a) Find the current through the capacitor C_1 in terms of the voltage V_3 and the resistor R_1 .

Answer:

For an op-amp, no current flows into the input terminals. Therefore, all the current through R_1 must flow through C_1 . Applying the Golden Rules, we know that $v_+ = v_- = 0\text{ V}$.

$$i_{R_1} = i_{C_1} = \frac{v_3}{R_1}$$

- (b) Suppose that at time $t = 0$, C_1 is uncharged. Find the voltage v_1 in terms of t , v_3 , and R_1 . What is the maximum $|v_1|$ could be?

Answer:

Recall the voltage across a capacitor is related to the charge on the capacitor, that is $Q = CV$. Current is related to charge with the equation $I = \frac{dQ}{dt}$.

$$v_{C_1} = \frac{Q}{C_1} = \frac{It}{C_1} = \frac{v_3}{R_1 C_1} t = \frac{v_3}{1\text{ ms}} t$$

Note that a ΩF is a second. Using the formula for v_{C_1} from above and the fact that $v_- = v_+ = 0$, the voltage at node v_1 can be calculated as:

$$v_{C_1} = 0 - v_1 \implies v_1 = -\frac{v_3}{1\text{ ms}} t$$

The maximum or minimum for v_1 is the top or bottom supply rail, so either $+1\text{ V}$ or -1 V . Therefore, the maximum $|v_1| = 1\text{ V}$.

- (c) How is v_2 related to v_1 ? What is the voltage v_2 ?

Answer:

O_2 is an inverting amplifier. The output voltage v_2 is equal to $-v_1$.

$$v_2 = \frac{v_3}{1\text{ ms}}t$$

Now, let's independently analyze the circuit in the two possible outputs of the comparator, when $v_3 = 1\text{ V}$ and when $v_3 = -1\text{ V}$.

- (d) Assume that the output of the comparator v_3 has railed to the top rail. With this value of v_3 , what is v_2 as a function of time? What is the voltage at the positive input of the comparator? At what time will the two inputs of the comparator be equal?

Answer:

With v_3 at the top rail, v_2 is $\frac{t}{1\text{ ms}}\text{ V}$. The voltage at the positive input of the comparator is 0.5 V because of R_5 and R_4 . Therefore, when $t = 0.5\text{ ms}$, $v_2 = 0.5\text{ V}$.

- (e) Now assume that the reverse occurs, that is, the output of the comparator has railed to the bottom rail. Repeat part (d) with this value of v_3 .


Answer:

With v_3 at the bottom rail, v_2 is $-\frac{t}{1\text{ ms}}\text{ V}$. Similar to part (d), the voltage at the positive input is -0.5 V . Therefore, when $t = 0.5\text{ ms}$, $v_2 = -0.5\text{ V}$.

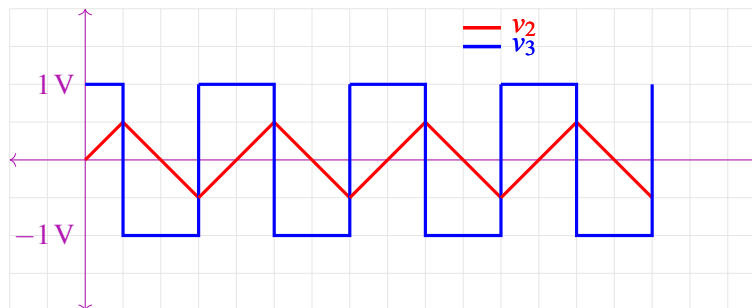- (f) What is v_3 as a function of time? Draw a graph of v_3 and v_2 . Since the graph is periodic, find its period and frequency.

Answer:

Notice that in each of the above cases, once v_2 was equal to v_+ , the output of the comparator would flip. This leads to a periodic function, where v_3 is either $+1\text{ V}$ or -1 V . The period of this function is $T = 2\text{ ms}$. Notice that in each of the above cases we analyzed, we always assumed that the capacitor was initially uncharged. However, when v_3 switches, the capacitor will already have some charge built up on it, so it must first be drained. This is why the period is twice what we expect.



- (g) Suppose that we changed the value of C_1 to be $2\mu\text{F}$? What is the new period? Suppose that we change R_5 to be $2\text{ k}\Omega$. What is the new period? What if we change R_5 to be 0Ω ? Will this circuit still operate?

Answer:


Notice above we got the constant 1 ms by multiplying R_1 and C_1 together. If we double C_1 , the effective period would double because it would take longer to charge C_1 to the same voltage with the same current.

Changing R_5 affects the “flip” threshold because v_+ is at a different voltage. Increasing R_5 decreases the voltage at v_+ , so we would expect the flip voltage to decrease. In fact, the new period is $\frac{4}{3}$ ms.

The circuit would not operate if $R_5 = 0\Omega$. The inverting input needs to be able to go above and below the non-inverting input, which is not possible if the non-inverting input is constant at the rail.

2. Practice: Dividers for Days

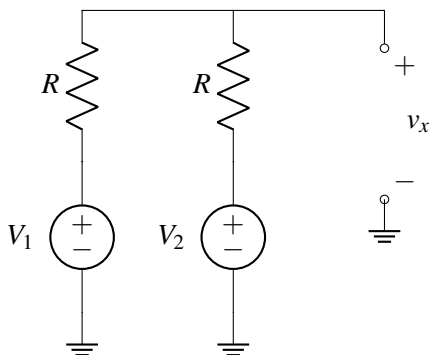- (a) Solve the following circuit for v_x .




Answer:

$$v_x = \frac{1}{2}V_1 + \frac{1}{2}V_2$$

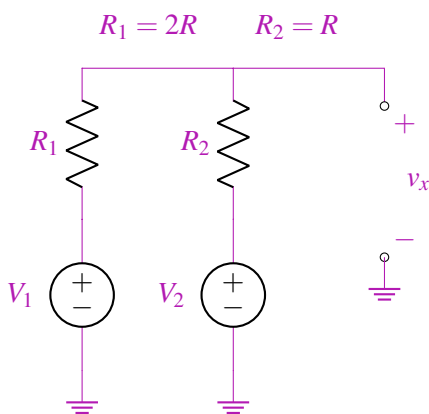- (b) You have access to two voltage sources, V_1 and V_2 . You can use two resistors (as long as $0 \leq R < \infty$). How would you design a circuit that produces a voltage $v_x = \frac{1}{3}V_1 + \frac{2}{3}V_2$?

Answer:


Use superposition. Even if you know the voltage summer, make sure you know the analysis with KVL/KCL. Using any nonzero values for R :



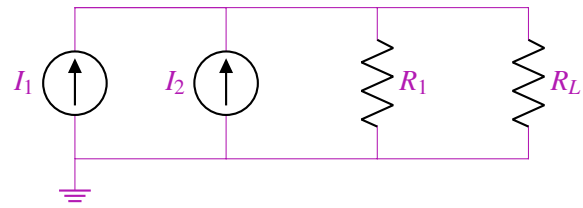- (c) You have two current sources I_1 and I_2 . You also have a load resistor $R_L = 6\text{k}\Omega$. Similar to the first part, you can use whatever resistors you want (as long as they are finite integer values). How would you design a circuit such that the current running through R_L is $I_L = \frac{2}{5}(I_1 + I_2)$?

Answer:

Use superposition, so think of the two currents as one summed current. Use KCL to determine how to divide the currents.



$$R_L = 6\text{k}\Omega, R_1 = 4\text{k}\Omega$$