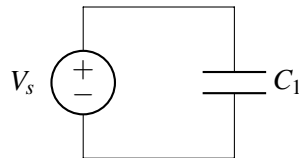

EECS 16A Designing Information Devices and Systems I
 Summer 2020 Discussion 4B


1. Voltages Across Capacitors

For the circuits given below, calculate the voltage across the capacitors. For parts (a) and (b) only, also calculate the charge and energy stored in each capacitor. Let $C_1 = 1\ \mu\text{F}$, $C_2 = 3\ \mu\text{F}$, $V_s = 1\ \text{V}$, and $I_s = 2\ \text{mA}$.

(a)




(b)

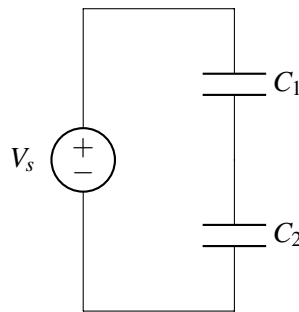


2. Current Sources And Capacitors

For the circuits given below, give an expression for $v_{\text{out}}(t)$ in terms of I_s , C_1 , C_2 , and t . Assume that all capacitors are initially uncharged, i.e. the initial voltage across each capacitor is $0\ \text{V}$.

(a)

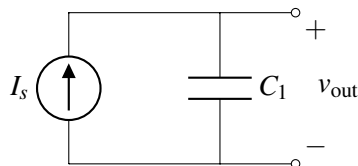


(b)

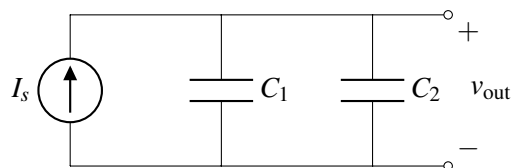


3. Practice: Series And Parallel CapacitorsDerive C_{eq} for the following circuits.

(a)

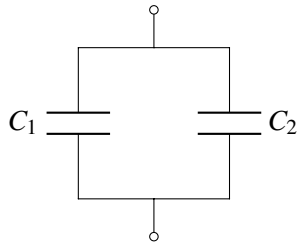

(b)

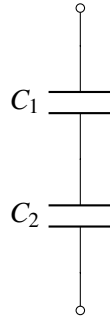

(c)

