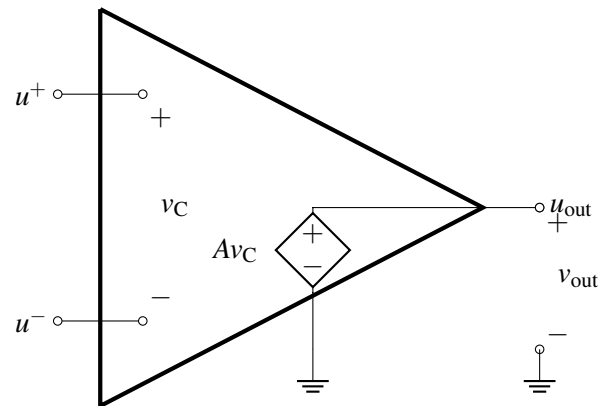


# EECS 16A Designing Information Devices and Systems I

## Summer 2020 Discussion 4D


### 1. Op-Amp Rules and Negative Feedback Rule

Here is an equivalent circuit of an op-amp (where we are assuming that  $V_{SS} = -V_{DD}$ ) for reference:




- What are the currents flowing into the positive and negative terminals of the op-amp (i.e., what are  $I^+$  and  $I^-$ )? Based on this answer, what are some of the advantages of using an op-amp in your circuit designs?
- Suppose we add a resistor of value  $R_L$  between  $u_{out}$  and ground. What is the value of  $v_{out}$ ? Does your answer depend on  $R_L$ ? In other words, how does  $R_L$  affect  $Av_C$ ? What are the implications of this with respect to using op-amps in circuit design?

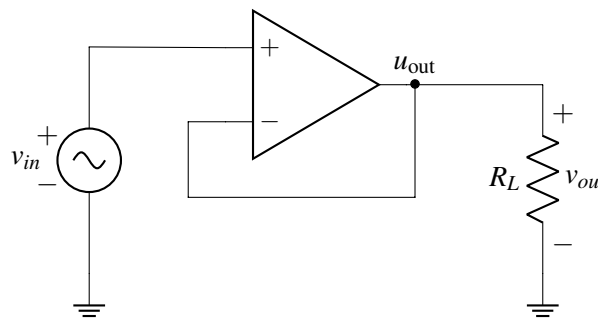**For the rest of the problem, consider the following op-amp circuit in negative feedback:**



- Assuming that this is an ideal op-amp, what is  $v_{out}$ ?
- Draw the equivalent circuit for this op-amp and calculate  $v_{out}$  in terms of  $A$ ,  $v_{in}$ , and  $R_L$  for the circuit in negative feedback. Does  $v_{out}$  depend on  $R_L$ ? What is  $v_{out}$  in the limit as  $A \rightarrow \infty$ ?


### 2. An Inverting Amplifier

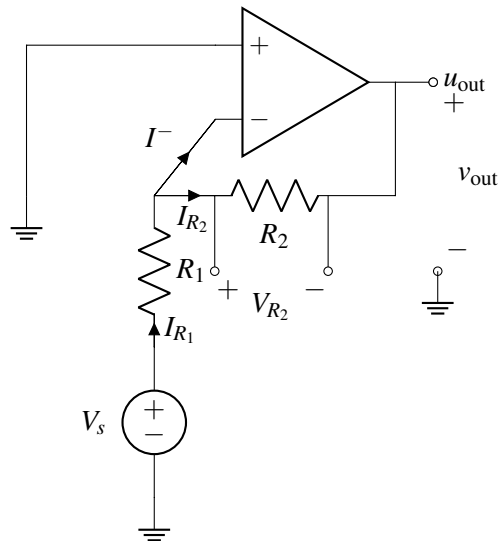

(a) Calculate  $v_{out}$  as a function of  $V_s$  and  $R_1$  and  $R_2$ .
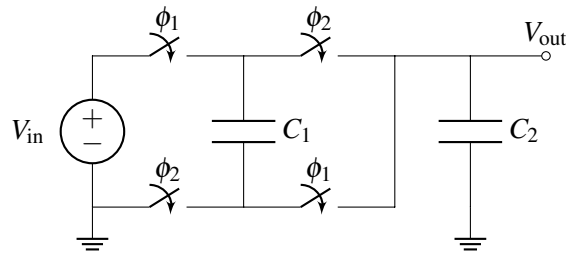
### 3. Charge Sharing

Consider the circuit shown below. In phase  $\phi_1$ , the switches labeled  $\phi_1$  are on while the switches labeled  $\phi_2$  are off. In phase  $\phi_2$ , the switches labeled  $\phi_2$  are on while the switches labeled  $\phi_1$  are off.



- Draw the polarity of the voltage (using + and - signs) across the two capacitors  $C_1$  and  $C_2$ . (It doesn't matter which terminal you label + or -; just remember to keep these consistent through phase 1 and 2!)
- Redraw the circuit in phase  $\phi_1$  and phase  $\phi_2$ . Keep your polarity from part (a) in mind.
- Find  $V_{out}$  in phase  $\phi_2$  as a function of  $V_{in}$ ,  $C_1$ , and  $C_2$ .
- How will the charges be distributed in phase  $\phi_2$  if we assume  $C_1 \gg C_2$ ?