
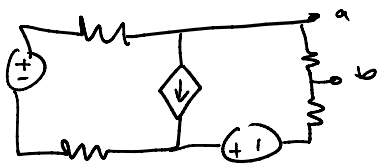




complex circuit

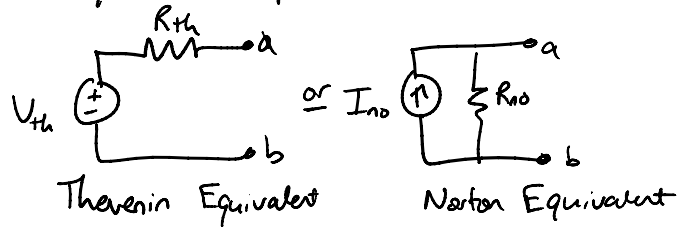

equivalent simpler circuit









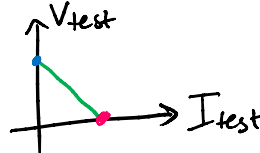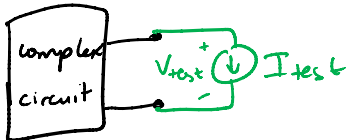\* 2 circuits are equivalent if they have the same I-V relationship



when  $V_{test} = 0$   
 → no voltage drop  
 → short circuit current  $I_{test} = I_{sc}$

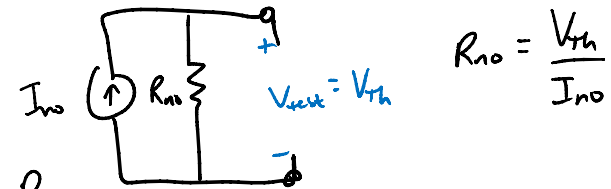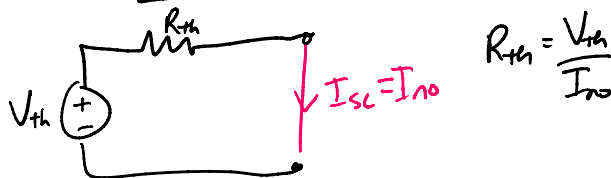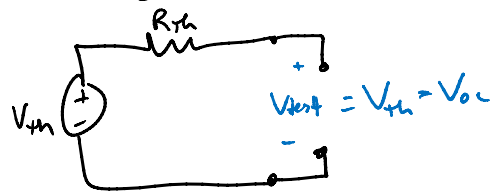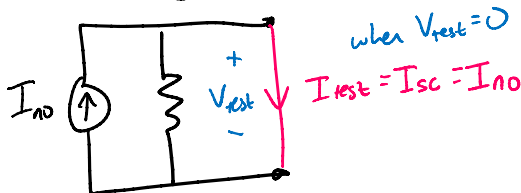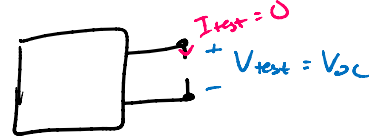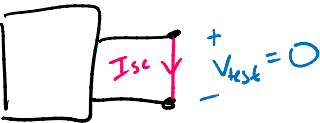when  $I_{test} = 0$   
 → no current flowing  
 → open circuit voltage  $V_{test} = V_{oc}$



$R_{th} = R_{no}$

Finding Thevenin and Norton Equivalents

- 1)  $V_{th} = V_{oc}$  - NVA or Superposition
- 2)  $I_{no} = I_{sc}$  - NVA or Superposition

3)  $R_{th}, R_{no}$


a)  $R_{th} = R_{no} = \frac{V_{th}}{I_{no}} = \frac{V_{oc}}{I_{sc}}$  (only works if  $V_{th} \neq 0, I_{no} \neq 0$ )

b) turn off independent sources, find  $R_{eq}$   
 (only works if all sources turn off) \*quickest

c) turn off independent sources, excite output w/ test source  $R_{th} = R_{no} = \frac{V_{test}}{I_{test}}$  \*slowest  
 (always works)

Sp 18 MT2 Q7


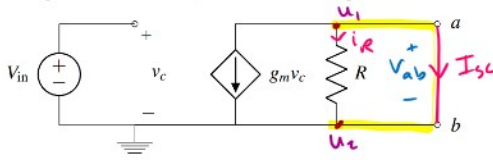
(b) (6 points) Find and draw the Norton equivalent circuit between terminals  $a$  and  $b$  in the circuit below. Clearly label the Norton equivalent current,  $I_{no}$ , and the Norton equivalent resistance  $R_{no}$ .



① find  $I_{no} = I_{sc}$   
 $u_1 = u_2 \quad V_{ab} = u_1 - u_2 = i_R R = 0$

KCL @  $u_1$ :  $g_m V_c + i_R + I_{sc} = 0 \rightarrow i_R = 0$   
 $I_{sc} = -g_m V_{in}$

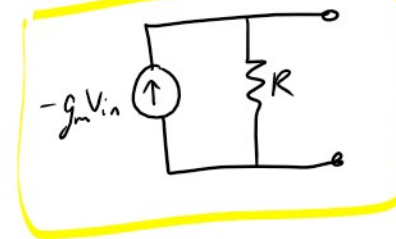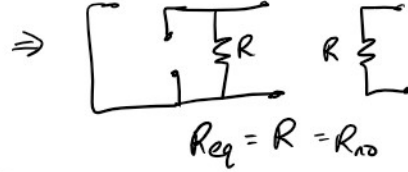
② find  $R_{no}$  → which methods can we use? a) b) c)




Sp 20 MT2 Q9

9. Thévenin Equivalence (12 points)

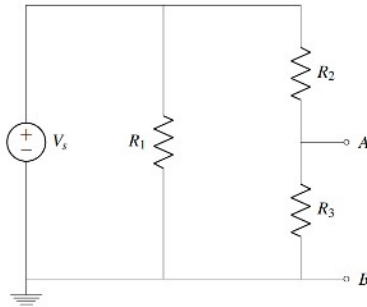(a) Find the Thévenin resistance  $R_{th}$  of the circuit shown below, with respect to its terminals  $A$  and  $B$ . Assume that  $R_1 = 4R$ ,  $R_2 = R$  and  $R_3 = 9R$ .



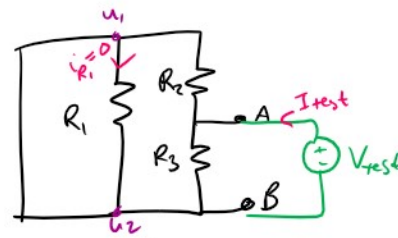could use a) b) & c)  
 but let's use b) because it's the easiest




$u_1 = u_2$   
 $V_{R_1} = u_1 - u_2 = i_{R_1} R_1 = 0$   
 $i_{R_1} = 0$


$R_{th} = R_2 || R_3$



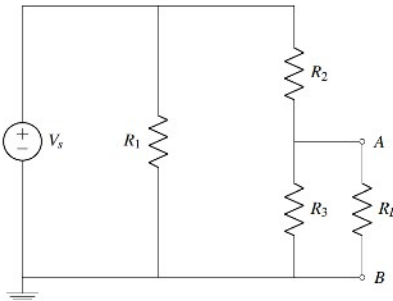(b) Now a load resistor,  $R_L = 9R$ , is connected across terminals  $A$  and  $B$  as shown in the circuit below. Find the supply voltage,  $V_s$ , such that 1 mW is dissipated across the load resistor. Let  $R = 36k\Omega$ .




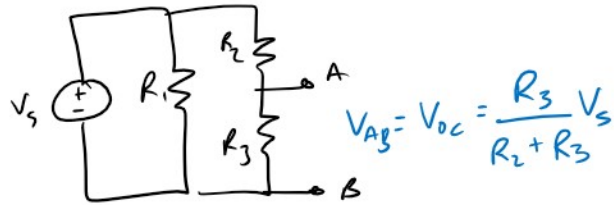Want to find Thévenin equiv → find  $V_{th}$



$V_{AB} = V_{oc} = \frac{R_3}{R_2 + R_3} V_s$


Thévenin equiv

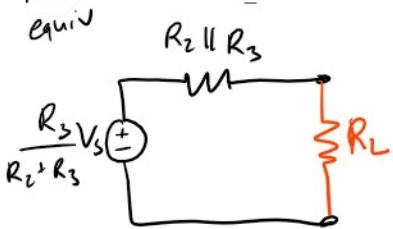

$V_{R_L} = \frac{R_L}{R_{th} + R_L} V_{th} = \frac{R_L}{R_2 || R_3 + R_L} \frac{R_3}{R_2 + R_3} V_s$


$P_{R_L} = I_{R_L} V_{R_L} = \frac{V_{R_L}^2}{R_L} \rightarrow \text{solve for } V_s$

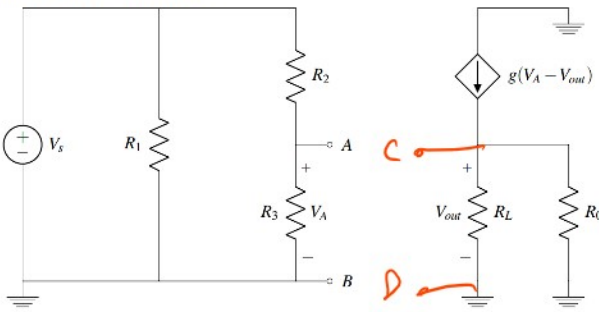(c) We modify the circuit as shown below:





Find a symbolic expression for  $V_{out}$  as a function of  $V_s$ .

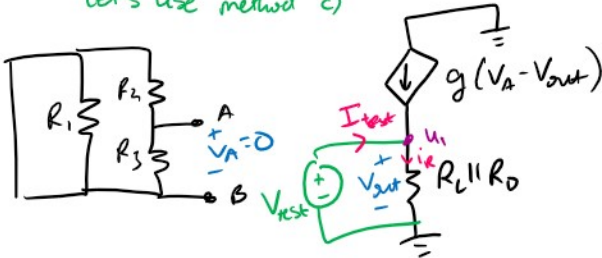Let's also find  $R_{th}$  w.r.t. C and D  
 Which methods can we use? not b)  
 Let's use method c)



\*  $i_R = \frac{V_{out}}{R_L \parallel R_0}$

$V_{out} = V_{test}$

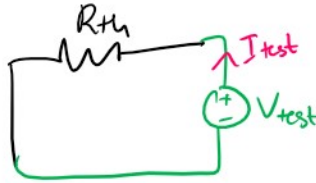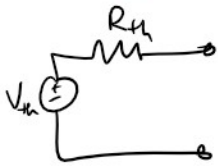

$R_{th} = \frac{V_{test}}{I_{test}} = \frac{V_{test}}{(\frac{1}{R_L \parallel R_0} + g)V_{test}}$

$R_{th} = \frac{1}{\frac{1}{R_L \parallel R_0} + g}$

*(This equation is highlighted in yellow in the original image)*

KCL @  $u_1$ :  $I_{test} + g(V_A - V_{out}) - i_R = 0$

$I_{test} = i_R + gV_{out} = i_R + gV_{test}$


$= \frac{V_{test}}{R_L \parallel R_0} + gV_{test} = (\frac{1}{R_L \parallel R_0} + g)V_{test}$

*(This equation is highlighted in yellow in the original image)*

\* Didn't get to this problem but wrote out the solutions

Fall 16 MTZ Q5

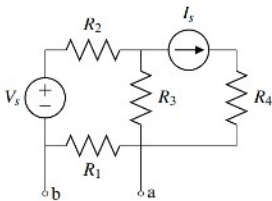5. Thévenin and Norton Equivalence (10 points)







$I_{test} = \frac{V_{test}}{R_{eq}}$       $R_{th} = \frac{V_{test}}{I_{test}} = R_{eq}$

$R_{th} = \frac{R_1(R_2 + R_3)}{R_1 + R_2 + R_3}$

*(This equation is highlighted in yellow in the original image)*




(a) (4 points) Redraw the circuit with all sources nulled, then calculate  $R_{th}$  between terminals a and b.

let's use method c) \* could've used b)

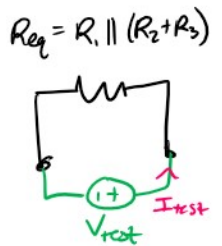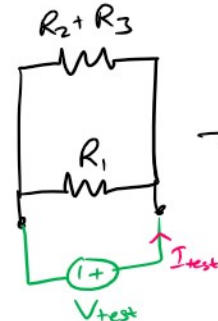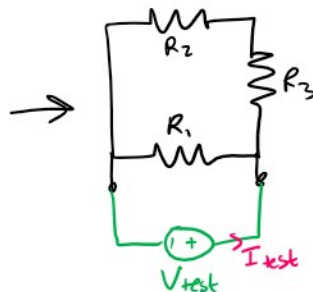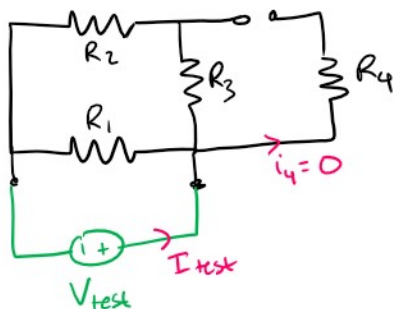


(b) (6 points) Find the Thévenin voltage between the terminals  $a$  and  $b$ . Hint: superposition may be useful.

only  $V_s$  on

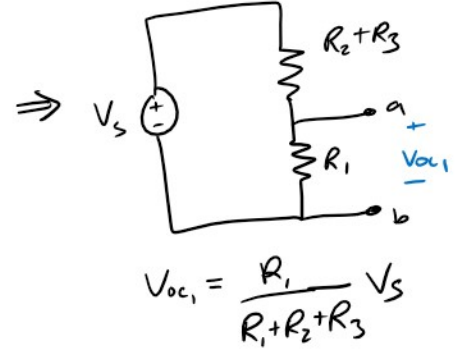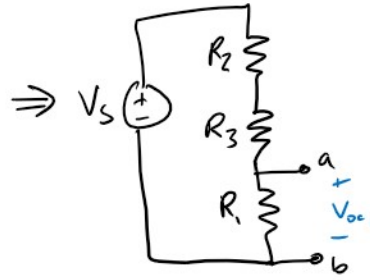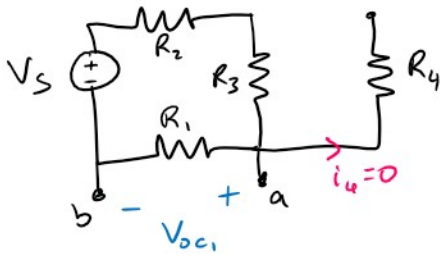

only  $I_s$  on

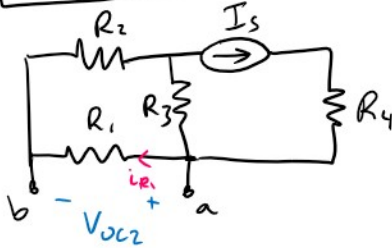


\* Recall current divider:



$$I_{R_1} = \frac{R_2}{R_1 + R_2} I_s$$

$$I_{R_2} = \frac{R_1}{R_1 + R_2} I_s$$

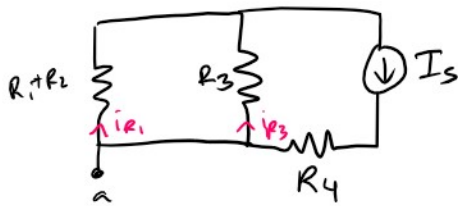

$$i_{R_1} = \frac{R_3}{R_1 + R_2 + R_3} I_s$$

$$V_{oc2} = i_{R_1} R_1 = \frac{R_3 R_1}{R_1 + R_2 + R_3} I_s$$

$$V_{oc} = V_{oc1} + V_{oc2} = \frac{R_1}{R_1 + R_2 + R_3} V_s + \frac{R_3 R_1}{R_1 + R_2 + R_3} I_s = V_{th}$$