

EECS16 DIS 3A (First Circuits Discussion)



What is a circuit made of?

Nodes - junction of connections between "highways" for charge

Branches - highways for charge (electrical elements wires/openers)
 (paths/links between nodes)

Charge - \oplus (voltages & currents are a result of charge)

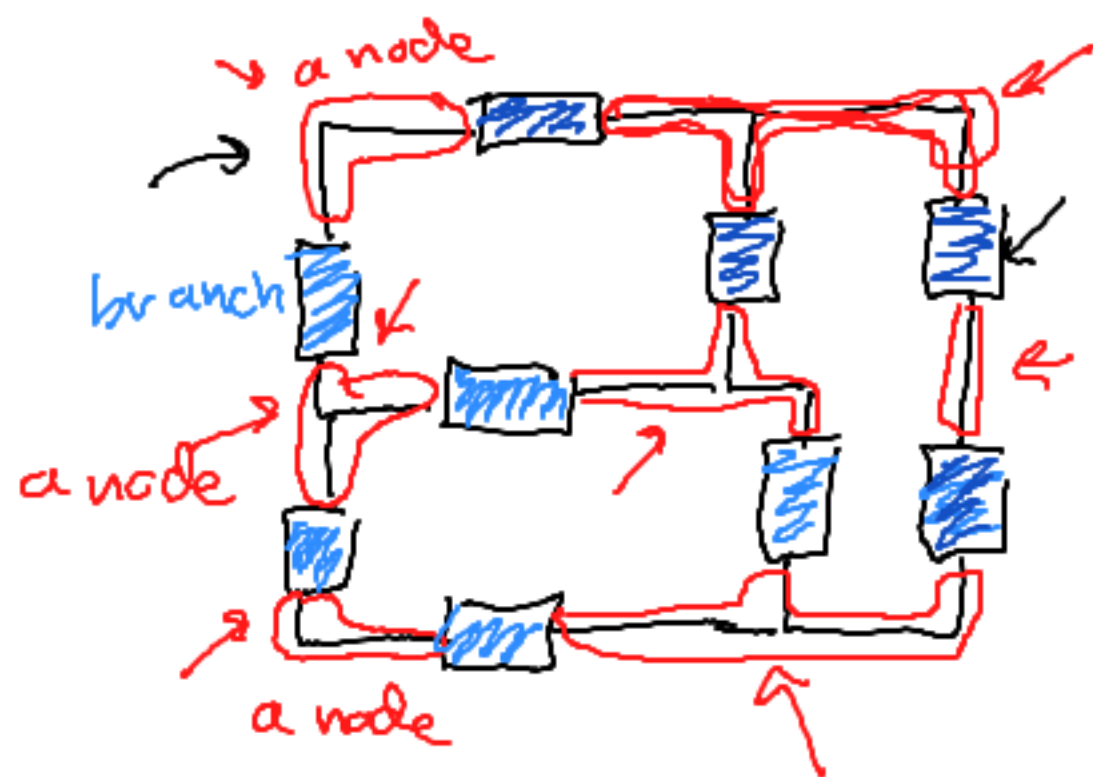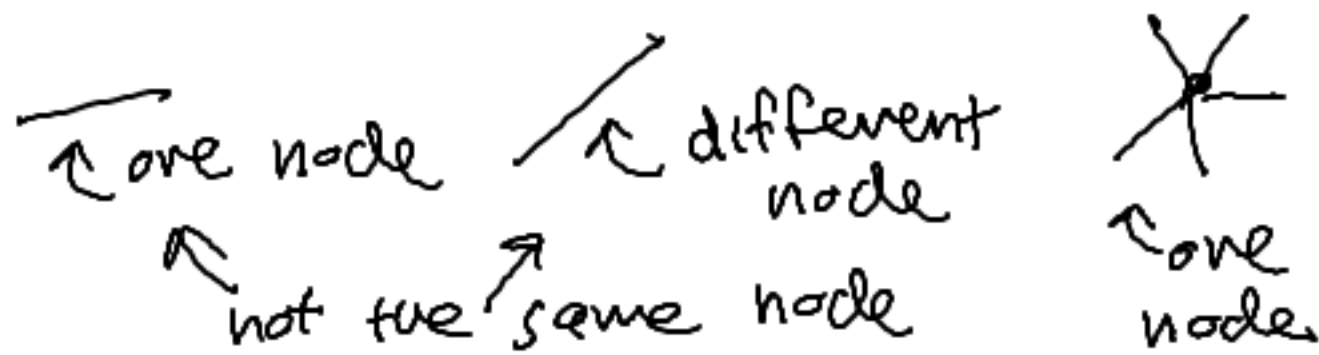
Node - connected/continuous piece of wire



Branches:
Quantities

Branch Voltages
label on a branch $+V_i$

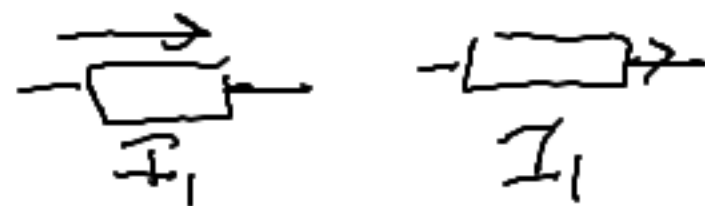Branch currents
amount of charge flowing/time
through a branch



Nodes


Node voltage

"Elevation" relative to some reference height

~~Node current~~


to some reference height

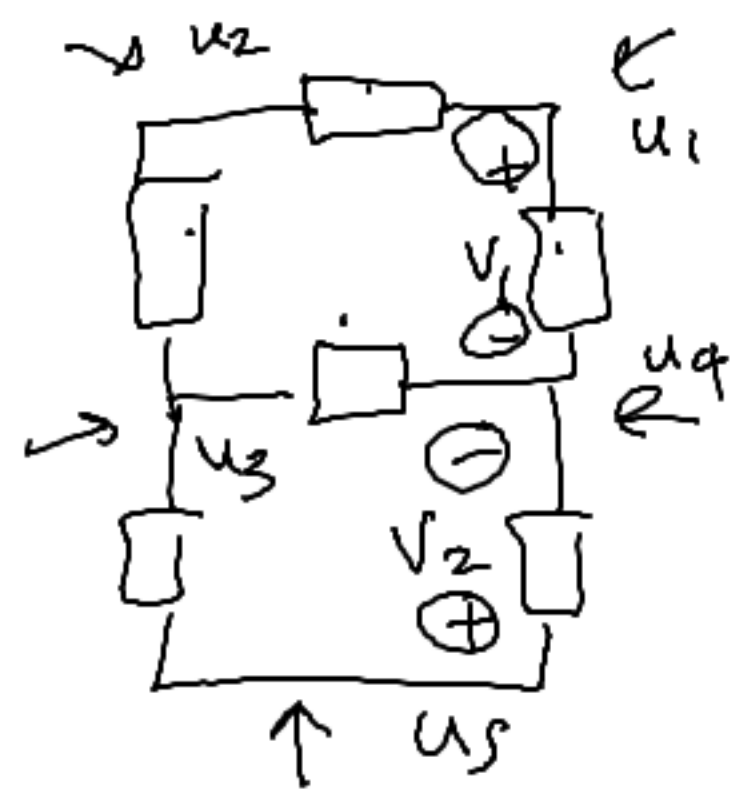A relationship between branch voltages & node voltages




$$V_1 = u_1 - u_4$$

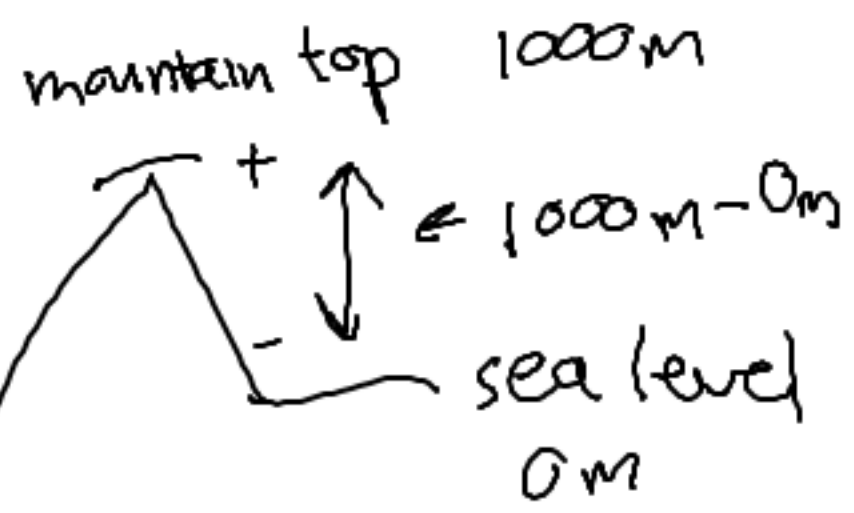branch voltage \equiv node voltage on (+) terminal - node voltage on (-) terminal



$$V_2 = u_5 - u_4 \quad \checkmark$$

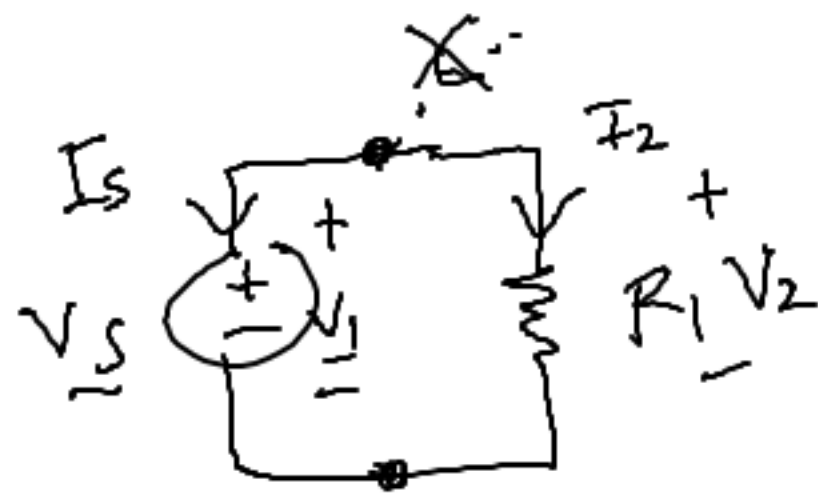

Find I_S
 given $V_S = 1V, R_1 = \Omega$

$$V_1 = V_S \Leftarrow$$

Using KCL, KVL, Ohm's law

KCL: at a node, the currents coming in from branches is the same as currents going out on branches

$$0 = I_S + I_2 \quad \checkmark$$

KVL: for a loop of branches the sum of branch voltages will be zero



$$-V_S + V_2 = 0$$

$$V_2 = V_1 = V_S \quad \checkmark$$

Ohm's law: relates branch current + branch voltage for a resistor

Convention regarding
 branch voltages }
 branch currents }

: Passive sign convention

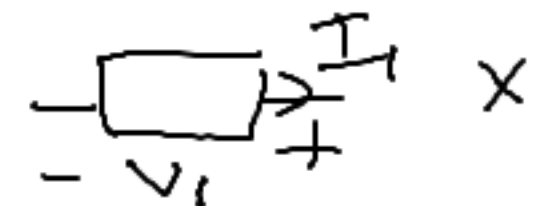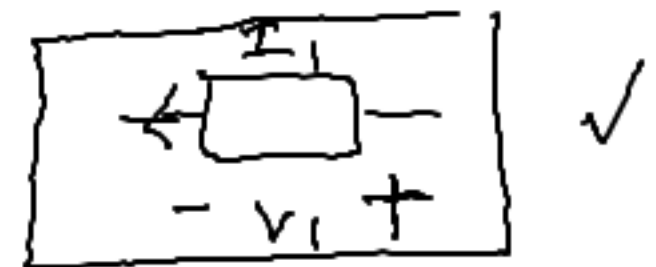



$$\begin{aligned} \textcircled{1} \quad 0 &= \underline{I_s} + I_2 \\ \textcircled{2} \quad V_1 &= V_2 = V_s \leftarrow \\ \textcircled{3} \quad V_2 &= R_1 I_2 \end{aligned}$$

$$\begin{aligned} V_s &= 1V \\ R_1 &= 1k\Omega \end{aligned}$$

Ohm's law:

$$V_B = R I_B$$

V_B : branch voltage of R

I_B : branch current of R


$$\boxed{V_2 = R_1 I_2}$$

$$\begin{aligned} \textcircled{1} \rightarrow \textcircled{1} \quad I_s &= -I_2 \\ \textcircled{2} \rightarrow \textcircled{3} \rightarrow V_s &= R_1 I_2 \\ \frac{V_s}{R_1} &= I_2 \end{aligned} \quad \rightarrow \quad I_s = -\frac{V_s}{R_1} = \frac{-1V}{1k\Omega} = \boxed{-1mA}$$


kilo = $\times 1000$

milli = $\times \frac{1}{1000}$

What do negative currents mean?

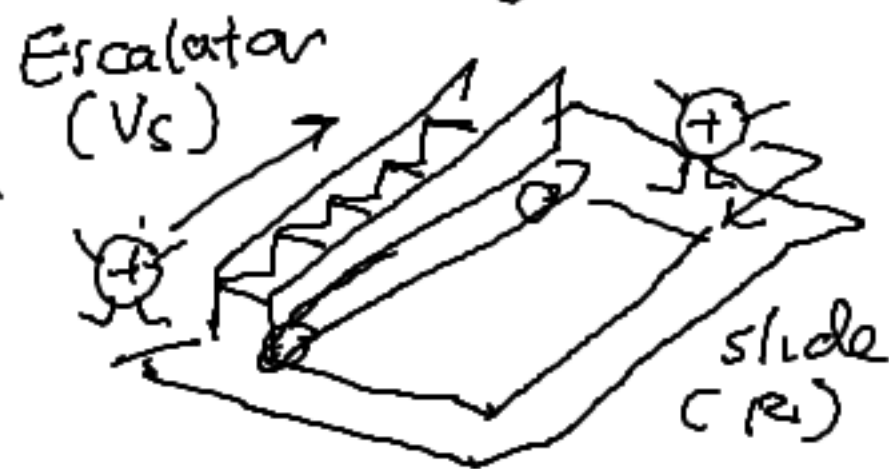

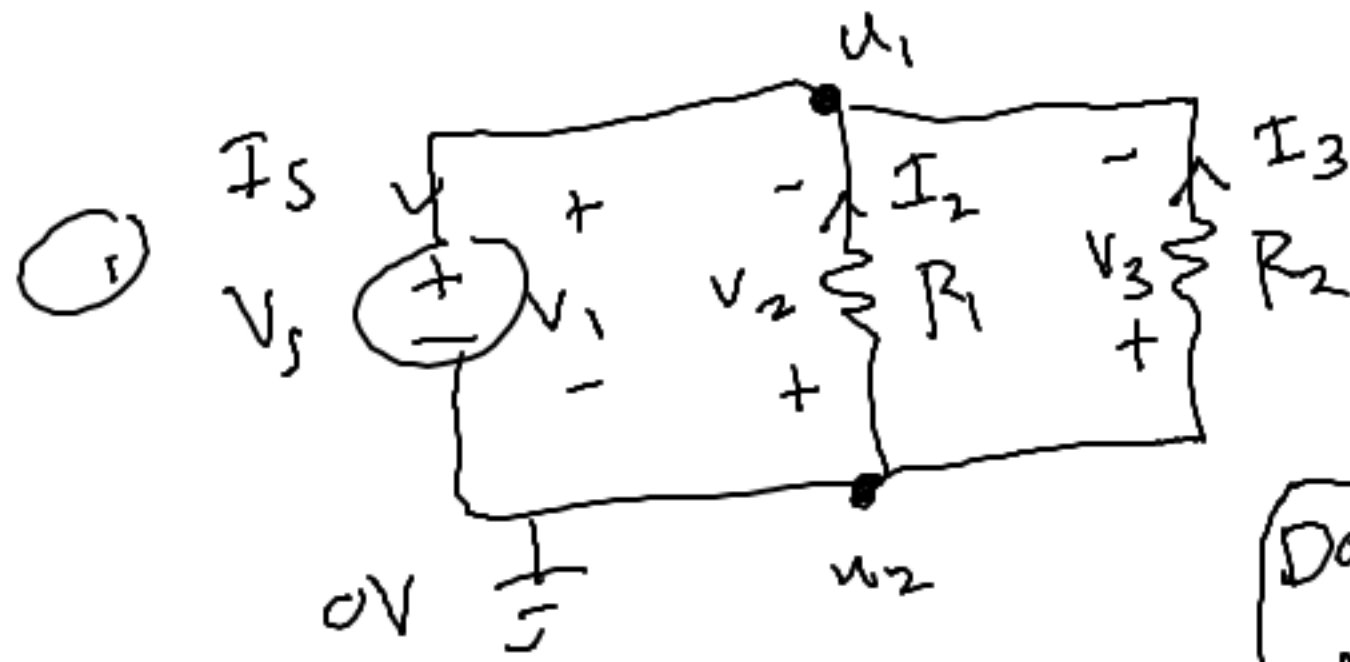\hookrightarrow Our assumed direction of movement for positive charges was wrong, they move the opposite way.



$V_s = 1V$
 $R_1 = 2k\Omega$
 $R_2 = 2k\Omega$

Node voltage analysis (NVA)
(aka Nodal analysis)

- ① Labeling circuit
- ② Write KCL eqns
- ③ Substitute Ohm's law in terms of node voltages
- ④ Solve for node voltages (couldn't apply)

Don't write KCL for nodes w/ voltage sources if using NVA

$u_2 = 0V$
 $V_1 = V_s$

② KCL (a) u_1 node:
 $I_s = I_2 + I_3$
 $I_s - I_2 - I_3 = 0$
 $-I_s + I_2 + I_3 = 0$

take your pick

③ Ohm's law:
 $V_2 = I_2 R_1$
 ~~$V_1 = I_1 R_1$~~
 $V_3 = I_3 R_2$


Node voltages
 $V_2 = 0 - u_1$
 $V_1 = V_s = u_1 - 0$
 $V_3 = 0 - u_1$

Substitute into KCL

$-\frac{u_1}{R_1} = I_2$
 $V_s = u_1$
 $I_3 = \frac{-u_1}{R_2}$

$$\begin{aligned}
 I_s &= -\frac{u_1}{R_1} + \left(\frac{-u_1}{R_2}\right) \\
 &= -\left(\frac{V_s}{R_1} + \frac{V_s}{R_2}\right) \\
 &= -\left(\frac{1V}{2k\Omega} + \frac{1V}{2k\Omega}\right) \\
 &= \boxed{-1mA}
 \end{aligned}$$

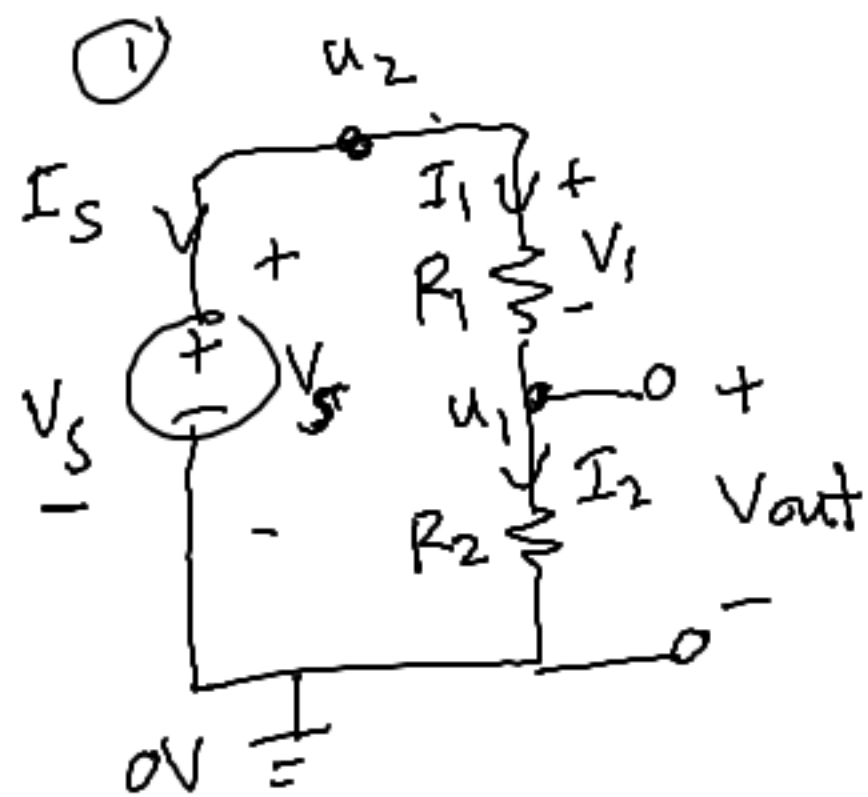Goal of NVA: a system of eqns in terms of node voltage



Find V_{out} in terms of R_1, R_2, V_S

② KCL @ non V_S nodes

③ u_1 $I_1 = I_2$
(in) (out)

③ Sub. Ohm's law

$$\left. \begin{aligned} V_1 = R_1 I_1 = u_2 - u_1 \\ \rightarrow V_{out} = R_2 I_2 = u_1 - 0V \end{aligned} \right\} \Rightarrow \begin{cases} I_1 = \frac{V_S - u_1}{R_1} \\ I_2 = \frac{u_1}{R_2} \end{cases} \Rightarrow \boxed{\frac{V_S - u_1}{R_1} = \frac{u_1}{R_2}}$$

$$\underline{V_S = u_2 - 0V}$$

④ Solve for u_1 (node voltages)

$$\frac{V_S}{R_1} = \frac{u_1}{R_1} + \frac{u_1}{R_2} \Rightarrow u_1 = \frac{V_S}{\frac{1}{R_1} + \frac{1}{R_2}}$$

$$u_1 = \frac{R_2}{R_1 + R_2} V_S$$

* ⑤ What are solving for?

$$\boxed{V_{out} = \frac{R_2}{R_1 + R_2} V_S}$$