

EECS 16A DIS 3B


Today's Topics

- ① Move NVA/Nodal analysis
- ② Current Divider derivation
- ③ Current Divider demo
- ④ If time leftover: DIS3BQ3

Some notes from DIS3A

"Element voltages" ←
"Branch voltages" ← same thing

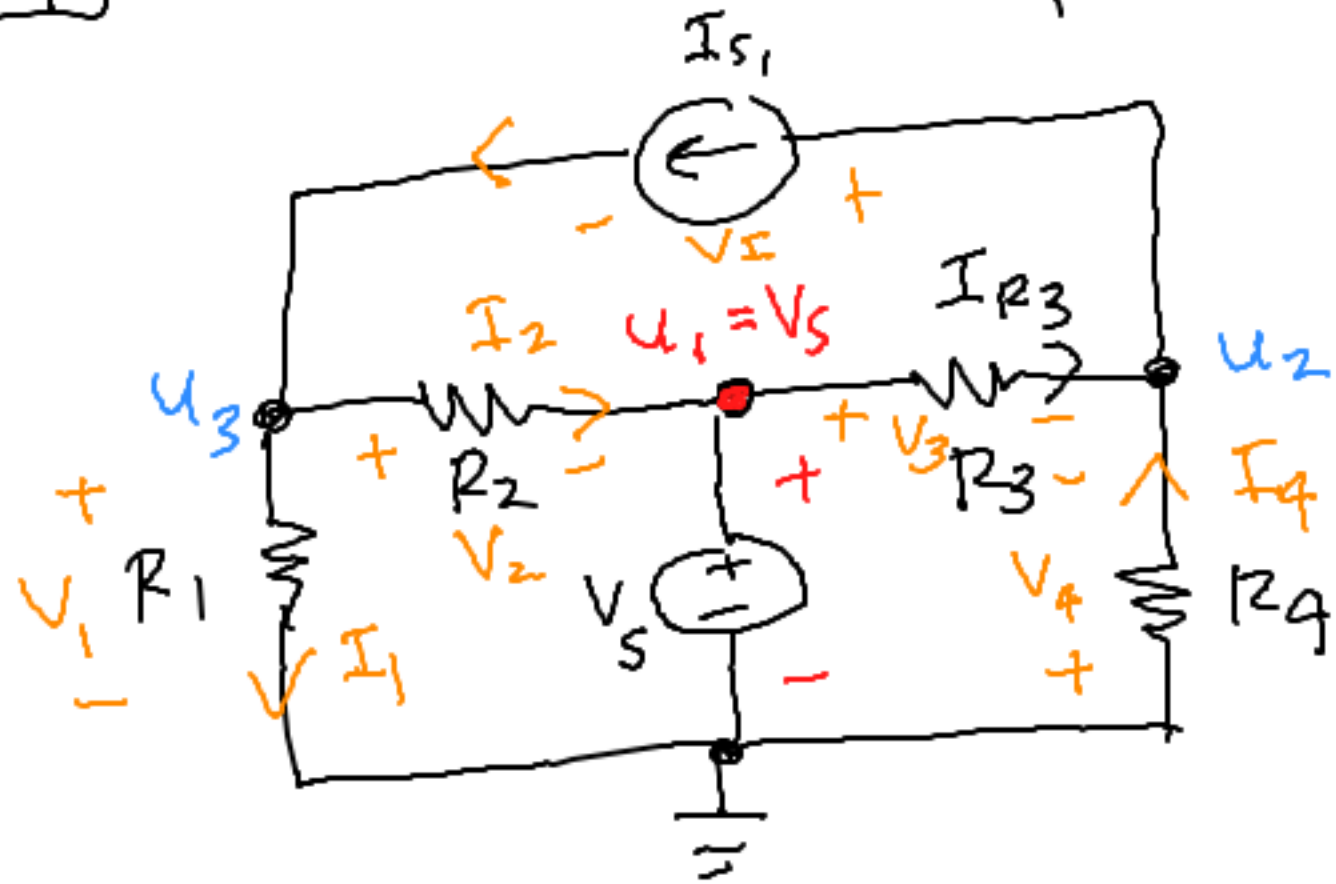□ Use nodal analysis to find all node voltages



- ✓ (1) Pick and label ground
- ✓ (2) Label all nodes w/ voltages set by voltage sources

$$V_5 = u_1 - 0$$

(branch v)

- ✓ (3) Label remaining nodes u_3, u_2
- ✓ (4) Label branch/element I 's V 's according to passive sign convention

$$\text{KCL @ } u_2 : I_{R3} + I_4 = I_{S1}$$

$$\text{KCL @ } u_3 : I_{S1} = I_1 + I_2$$

$$V_1 = R_1 I_1, \quad V_2 = R_2 I_2, \quad V_3 = R_3 I_{R3}, \quad V_4 = I_4 R_4$$

$$I_1 = \frac{u_3 - 0}{R_1}, \quad I_2 = \frac{u_3 - V_5}{R_2}, \quad I_{R3} = \frac{V_5 - u_2}{R_3}$$

$$I_4 = \frac{0 - u_2}{R_4}$$

- ✓ (5) KCL eqns. (write only for unk. nodes)
- ✓ (6) Element I 's \rightarrow Element V 's (ohm's)
- ✓ (7) Write Element V 's \rightarrow node V 's
- Ⓢ (8) Sub. into KCL, solve.

✓ ⑧ Sub. into KCL (and solve for node V's)

$$I_{R_3} + I_4 = I_{S_1} \Leftrightarrow \begin{cases} I_1 = \frac{u_3}{R_1} & I_2 = \frac{u_3 - V_S}{R_2} \\ I_{R_3} = \frac{V_S - u_2}{R_3} & I_4 = \frac{-u_2}{R_4} \end{cases}$$
$$I_{S_1} = I_1 + I_2$$

$$\left\{ \begin{array}{l} \frac{V_S - u_2}{R_3} + \frac{-u_2}{R_4} = I_{S_1}, \quad I_{S_1} = \frac{u_3}{R_1} + \frac{u_3 - V_S}{R_2} \end{array} \right\}$$

system of eqns.
in u_2, u_3

$$-I_{S_1} + \frac{u_2}{R_3} + \frac{u_2}{R_4} = I_{S_1} + \frac{u_2}{R_3} + \frac{u_2}{R_4}$$


$$\frac{V_S}{R_3} - I_{S_1} = u_2 \left(\frac{1}{R_3} + \frac{1}{R_4} \right)$$

$$I_{S_1} + \frac{V_S}{R_2} = u_3 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \rightarrow$$

u_2, u_3
can be found

⑥ Find: $I_{R_3} = \frac{V_S - u_2}{R_3}$ $\rightarrow u_2 = \frac{R_4}{R_3 + R_4} V_S - \frac{R_3 R_4}{R_3 + R_4} I_{S_1}$ ✓

2

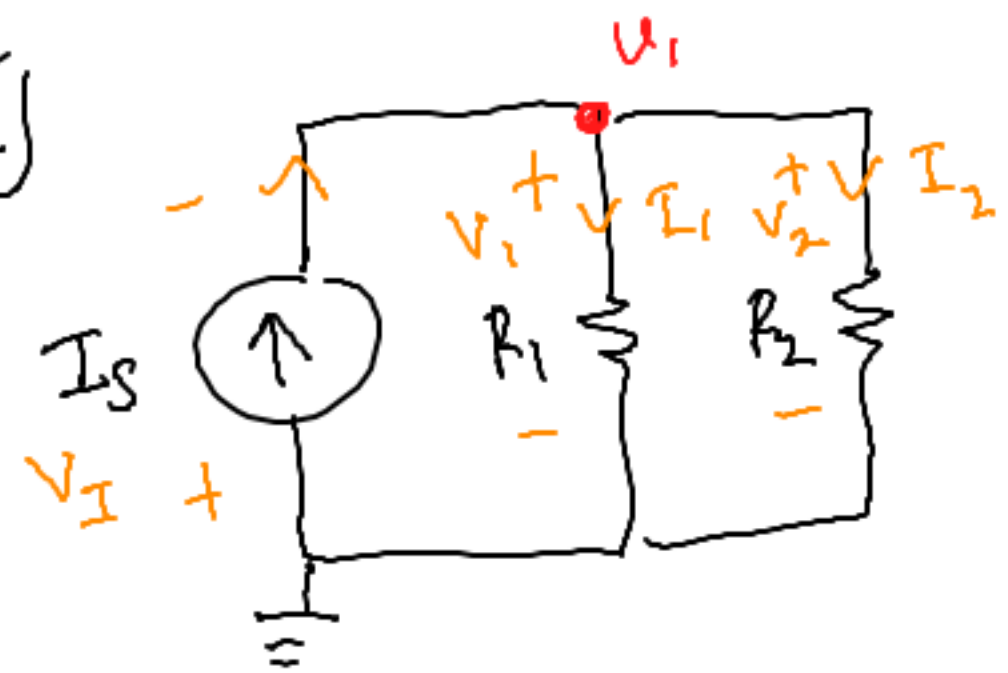

Current divider "splits up current" into two paths

What is I_1 and I_2 ?

KCL @ u_1 : $I_s = I_1 + I_2$

Branch I / Branch V relations: $V_1 = R_1 I_1$
 $V_2 = R_2 I_2$

Note voltages ~ I's : $I_1 = \frac{u_1 - 0}{R_1}$
 $I_2 = \frac{u_1 - 0}{R_2}$

Sub, solve:

$$I_s = \frac{u_1}{R_1} + \frac{u_1}{R_2}$$

$$u_1 = \frac{R_1 R_2 \cdot I_s}{R_1 R_2 \frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_2 + R_1} I_s$$

$$I_1 = \frac{u_1}{R_1} = \frac{1}{R_1} \left(\frac{R_1 R_2}{R_1 + R_2} I_s \right)$$

$$I_1 = \frac{R_2}{R_1 + R_2} I_s$$

$$I_2 = \frac{R_1}{R_1 + R_2} I_s$$

Case 1: $R_1 \gg R_2$

$$\frac{R_1}{R_1 + R_2} \sim 1 \quad \frac{R_2}{R_1 + R_2} \sim 0$$

$$I_2 \approx I_s \quad I_1 \approx 0$$

"current takes path of least resistance"

$$\boxed{3} \quad R = \rho \frac{L}{A}$$



ρ : material property

L : length of resistor

A : cross sectional