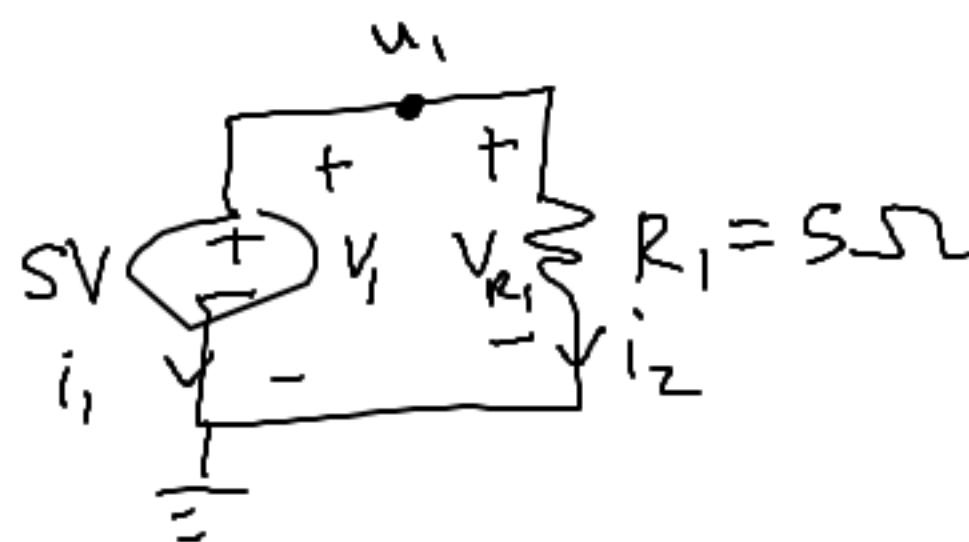


EECS16A DIS3C

Topics

- ① What's the relationship between passive sign convention 3 power
- ② Composing Circuits



$$P_{VS} = i_1 \cdot V_1$$

$$= (-1A)(SV) = \boxed{-5W}$$

$$KCL: i_1 + i_2 = 0$$

$$\Rightarrow i_1 = -i_2 = -1A$$

$$SV = u_1 - 0 = V_{R_1} \Rightarrow i_2 = \frac{V_{R_1}}{R_1} = \frac{SV}{5\Omega} = 1A$$

Q: Find power supplied/dissipated by
volt. source, resistor

$$P = I \cdot V$$

(power of an element)

branch current

branch voltage

$[W = \frac{J \cdot V}{s}]$

For any element

Resistors by Ohm's law

$$V = IR$$

$$P = I^2 R, P = \frac{V^2}{R}$$

Resistors only!

$$P_R = V_{R_1} \cdot i_2$$

$$= (SV)(1A)$$

$$= \boxed{+5W}$$

The resistor dissipates positive power



(b) Find P_{VS} , P_R

$$P_{VS} = (-SV)(1A) = \boxed{-SW}$$

$$P_R = (SV)(1A) = \boxed{SW}$$

$$V_2 = SV \text{ (because of } V_S)$$

$$I_2 = \frac{V_2}{R_2} = 1A$$

What's i_1 ?

$$KCL @ u_1 : i_1 = i_2 = 1A$$

What's V_1 ?

$$V_1 = -SV$$

(why? $= -V_S$)
flipped


Conclusion: Using passive sign convention will tell you which elements absorb/dissipate energy by having positive power no matter the directions/ or polarity you start w/

* Comment: • Power is conserved $\sum P_i = 0$

- Sources do not always supply power


- Resistors always dissipate (passive elements)

Exercise

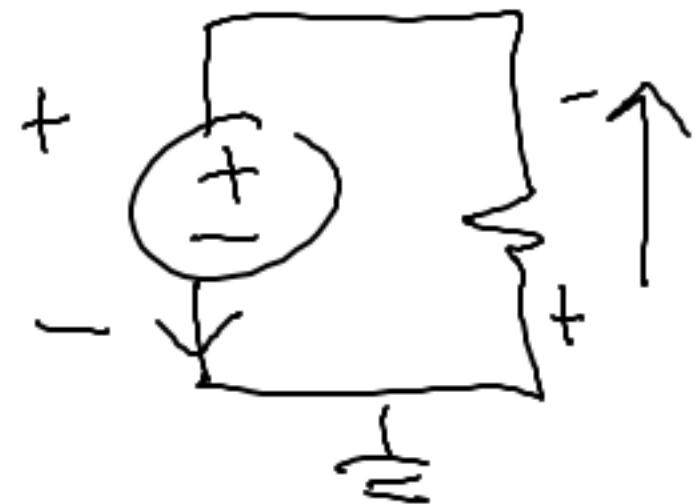

Also the same power?

When might a source not supply power?

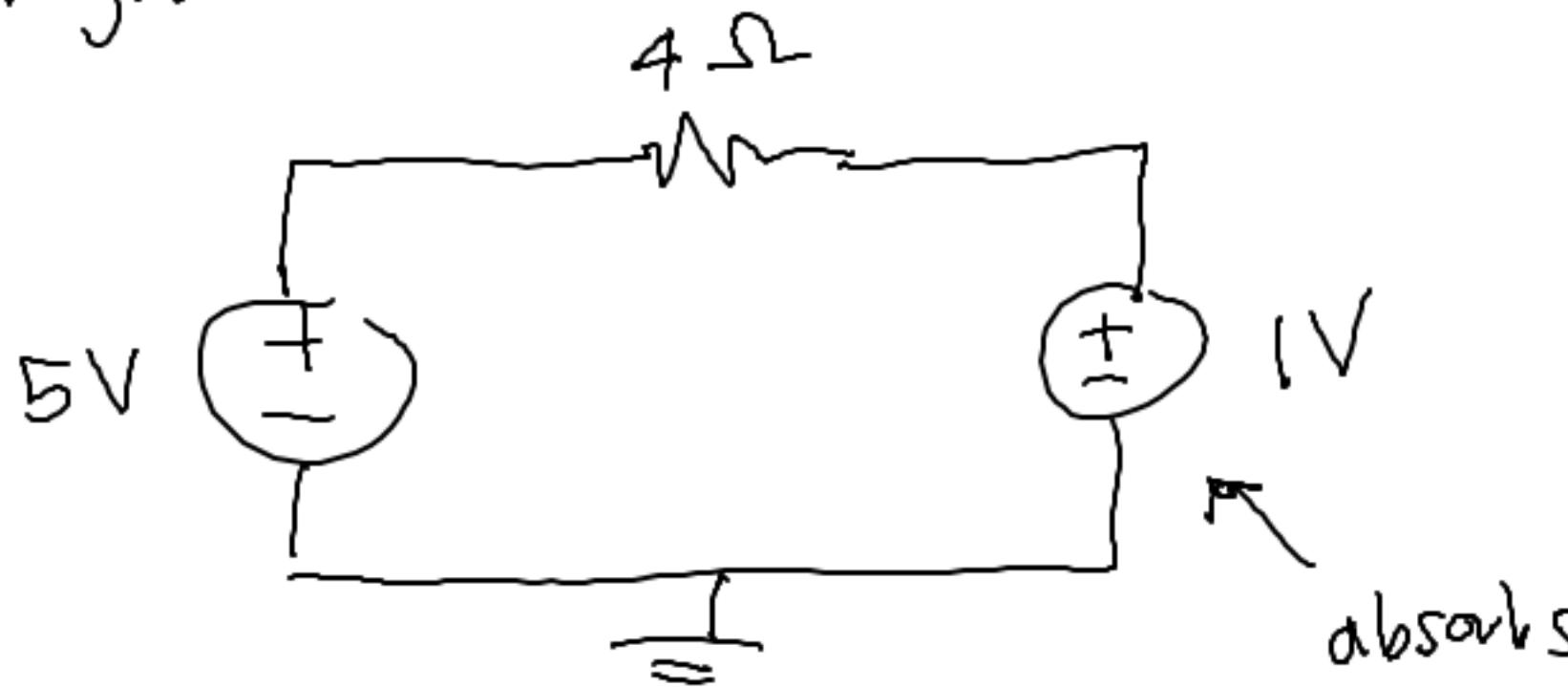

$$P_{SV} < 0 \text{ (supplies)}$$

$$P_{4\Omega} > 0 \text{ (dissipate)}$$

$$P_{IV} > 0 \text{ (dissipate)}$$


absorbs
power

2) Design Procedure

- ① Think of a circuit that might do the job
- ② Calculate how the circuit's behavior depends on choice of components/parameters
- ③ Choose values to get behavior you want
- ④ If it doesn't work, modify go back to step ①.

Good things to memorize

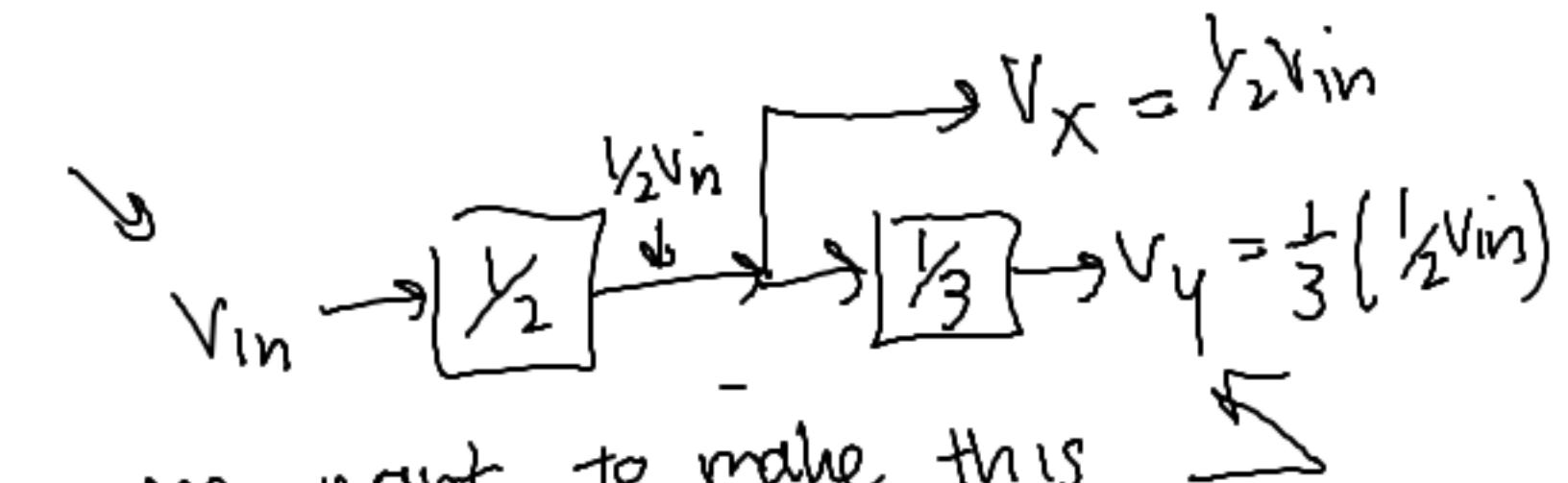- ① Voltage dividers
- ② Current dividers




we want to make this

How?



takes V_{in} , outputs $\frac{1}{2}V_{in}$

$$V_{out} = \frac{1}{2}V_{in}$$

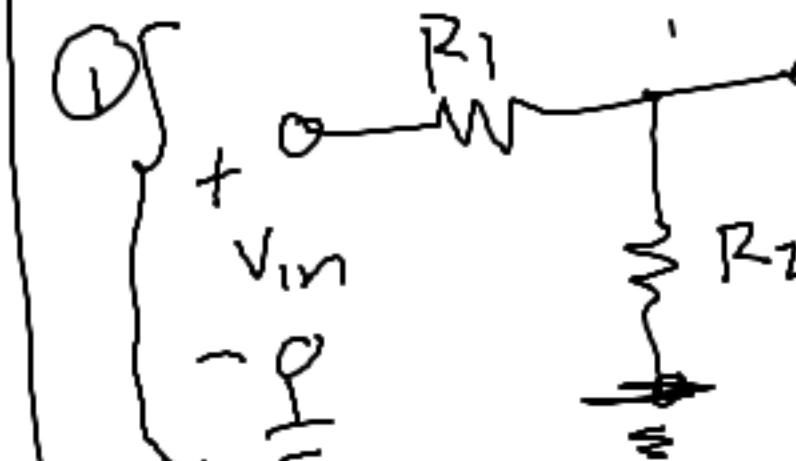


$$\textcircled{2} \quad V_{out} = \frac{R_2}{R_1 + R_2} V_{in}$$


$$\textcircled{3} \quad \frac{1}{2} = \frac{R_2}{R_1 + R_2}$$

$$\downarrow$$

$$R_1 = R_2$$

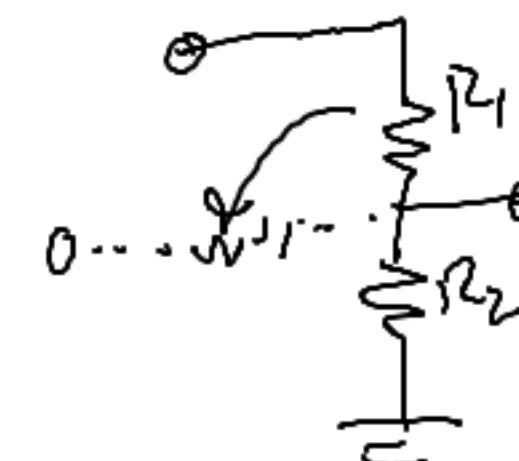

$$\textcircled{2} \quad \boxed{V_3}$$

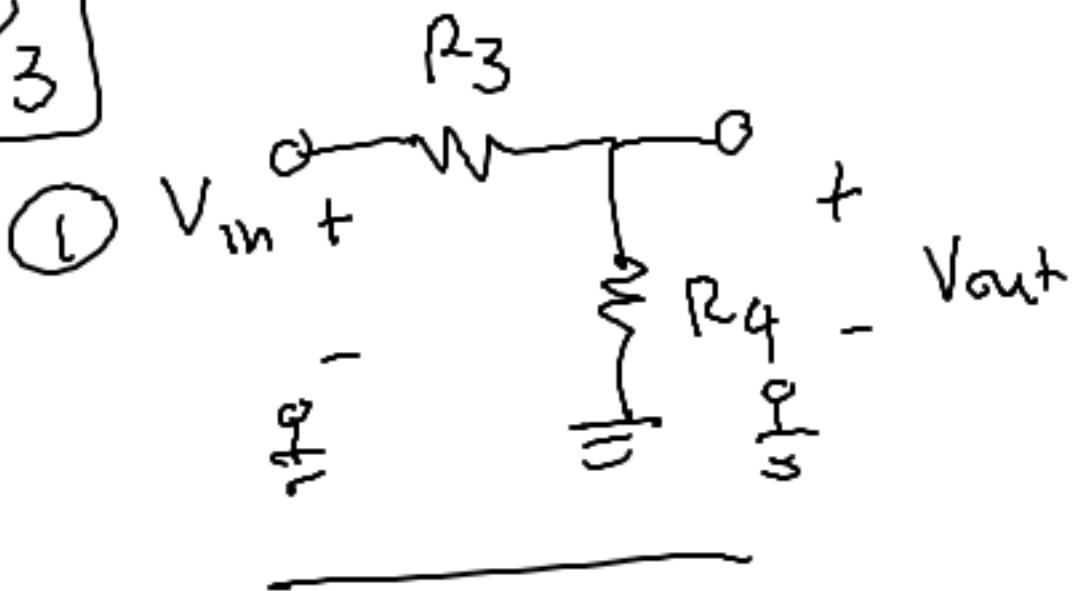


$$V_{out} = \frac{1}{3} V_{in}$$

$$\textcircled{2} \quad V_{out} = \frac{R_4}{R_3 + R_4} V_{in}$$

$$\textcircled{3} \quad \frac{R_4}{R_3 + R_4} = \frac{1}{3} \Rightarrow 3R_4 = R_3 + R_4$$

$$2R_4 = R_3$$

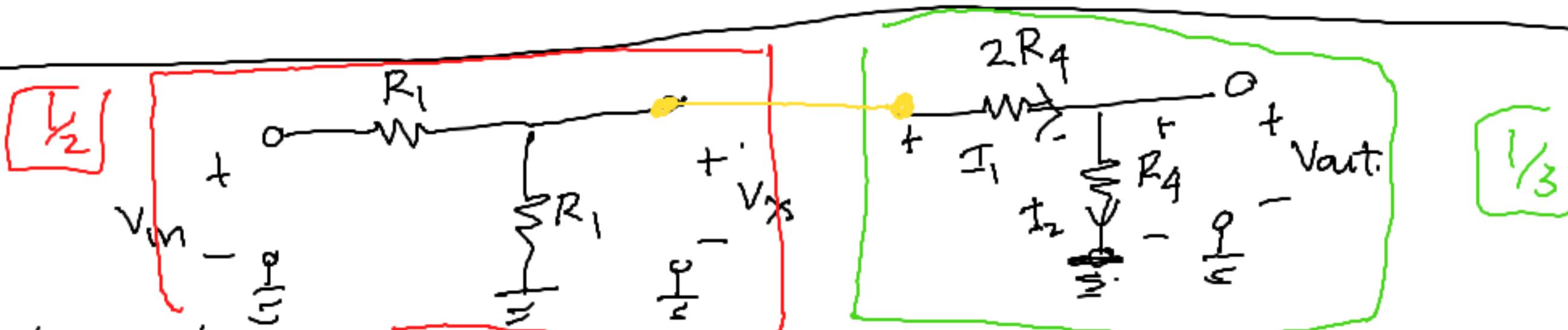

Does $V_{out} = \frac{1}{6} V_{in}$?


and does $V_{out} = \frac{1}{3} V_x$?

KCL @ V_{out} : $I_1 = I_2 \Rightarrow \frac{V_x - V_{out}}{2R_4} = \frac{V_{out}}{R_4}$

$$I_1 = \frac{V_x - V_{out}}{2R_4}$$

$$\Rightarrow V_{out} = \frac{1}{3} V_x \checkmark$$

$$I_2 = \frac{V_{out} - 0}{R_4}$$

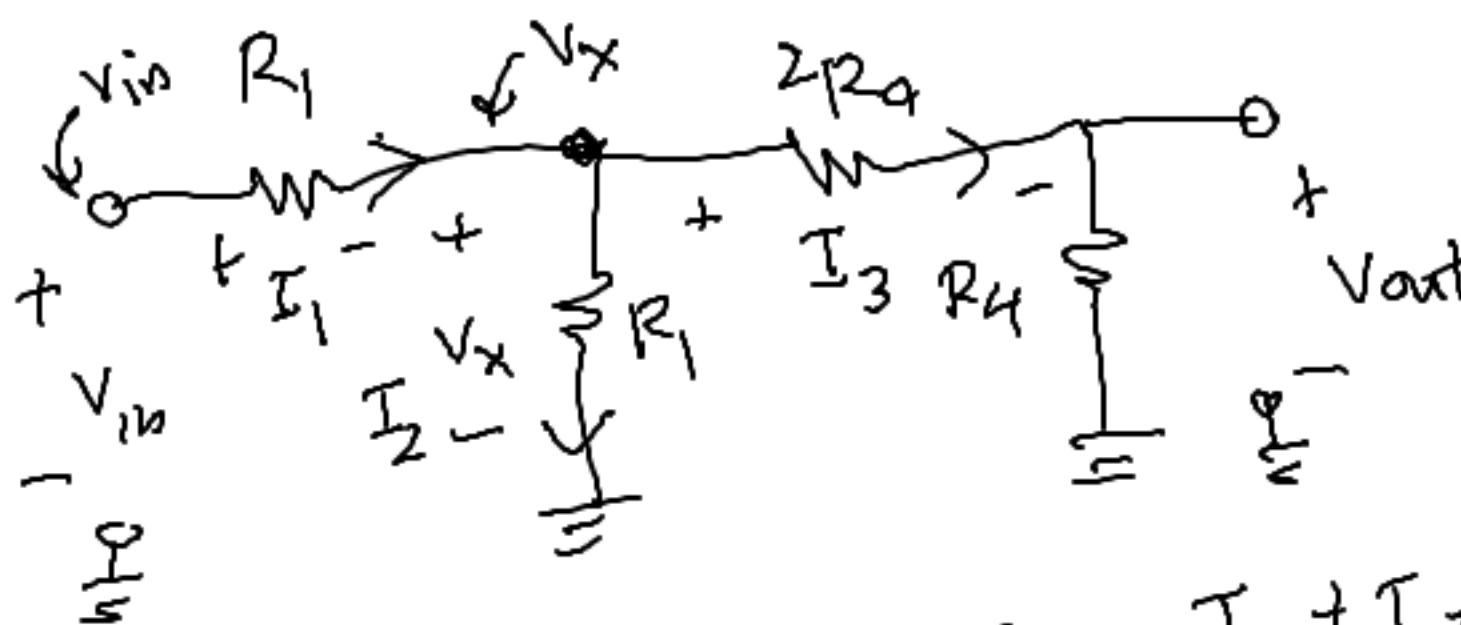

$$V_{\text{out}} = \frac{2R_4}{R_1} V_{\text{in}} - \frac{12R_4}{2+R_1} V_{\text{out}}$$

↙ Not Y_6 .

KCL @ V_x node:

$$I_1 = I_2 + I_3 \quad (\text{Find } V_{\text{out}})$$

(in) (out)

$$I_1 = \frac{V_{\text{in}} - V_x}{R_1}$$

$$I_2 = \frac{V_x - 0}{R_1}$$

$$I_3 = \frac{V_x - V_{\text{out}}}{2R_4}$$

$$\frac{V_{\text{in}} - V_x}{R_1} = \frac{V_x}{R_1} + \frac{V_x - V_{\text{out}}}{2R_4}$$

$$\frac{V_{\text{in}}}{R_1} - \frac{V_x}{R_1} - \frac{V_x}{2R_4} - \frac{V_x}{2R_4} = -\frac{V_{\text{out}}}{2R_4}$$

$$(V_{\text{out}} = \frac{1}{3}V_x)$$

$$\frac{2R_4}{R_1} V_{\text{in}} - \frac{4R_4}{R_1} V_x - V_x = -V_{\text{out}}$$

$$\frac{2R_4}{R_1} V_{\text{in}} - \left(\frac{4R_4}{R_1} + 1\right)(3V_{\text{out}}) = -V_{\text{out}}$$

$$\frac{2R_4}{R_1} V_{\text{in}} = 2V_{\text{out}} + \frac{12R_4}{R_1} V_{\text{out}}$$

Tideway: Can't just stick two circuits together
Composition doesn't work (yet)

Extra demo! + Some notes on problem 3 (practice)



Can't just stick circuits together and expect perfect behavior

Partial sol: Choose resistors relative to resistors in the previous block (R_i)
resistor values/magnitudes to infinity

Consequence: Increase

Is there a solution? Yes (later lectures)

Prob [3]: Power units, power transfer

$$\Rightarrow [V] = \left[\frac{J}{C} \right] \quad [W] = \left[\frac{J}{S} \right] \quad [A] = \left[\frac{C}{S} \right]$$

Q: Under what conditions do we transfer the most power?