


EECS DIS 3D

① Power: Example of a case where sources can absorb power ←

② How to model 2-D touchscreens
→ How to translate physical models into a schematic

③ If time: Resistor equivalence (Practice)

Objective: Find power of each element

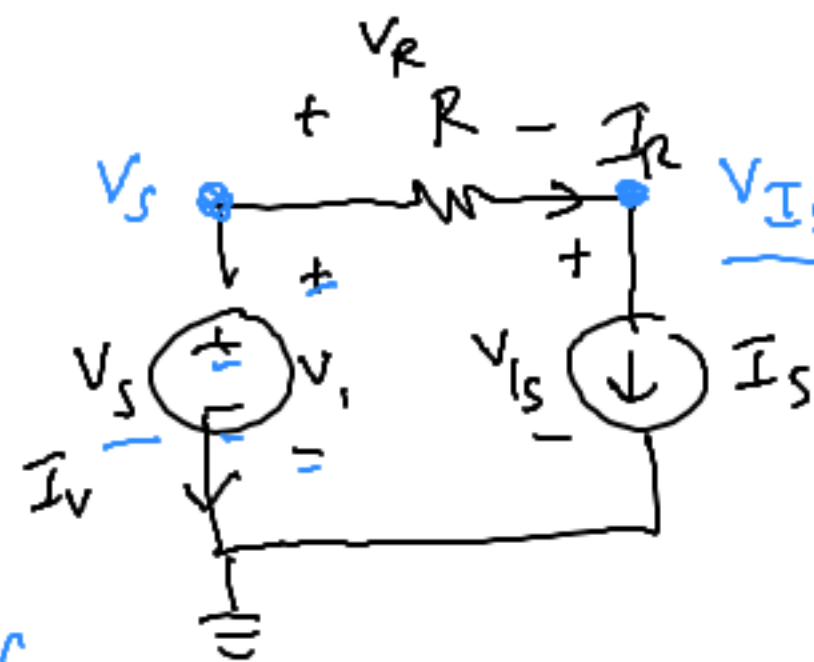

$V_{I_s} = ?$ KVL $-V_1 + V_R + V_{I_s} = 0$

$V_{I_s} = V_1 - V_R$
 $= V_s - I_R R = \underline{V_s} - \underline{I_s} R$

✓ $I_R = I_s$? (KCL) at node top right
 $5V - \frac{1}{2}A \cdot 5\Omega$

$V_{I_s} = 2.5V$ ✓

$V_R = 2.5V$

$V_1 = 5V$

$I_s = \frac{1}{2}A$

$I_R = \frac{1}{2}A$

$I_v = -\frac{1}{2}A$

(KCL @ left node)
 $I_v + I_R = 0$

$V_s = 5V$
 $R = 5\Omega$

$I_s = \frac{1}{2}A$

$P_{V_s} = -2.5W$
(V_1)(I_v)

$P_R = 1.25W$
(V_R)(I_R)

$P_{I_s} = \underline{1.25W} > 0$
(V_{I_s})(I_s)

2D Touchscreen: How to translate physical models to circuit diagram




$$R = \rho \frac{L}{A}$$

↑ resistivity


$$\frac{R_x}{R_y} \leftarrow$$

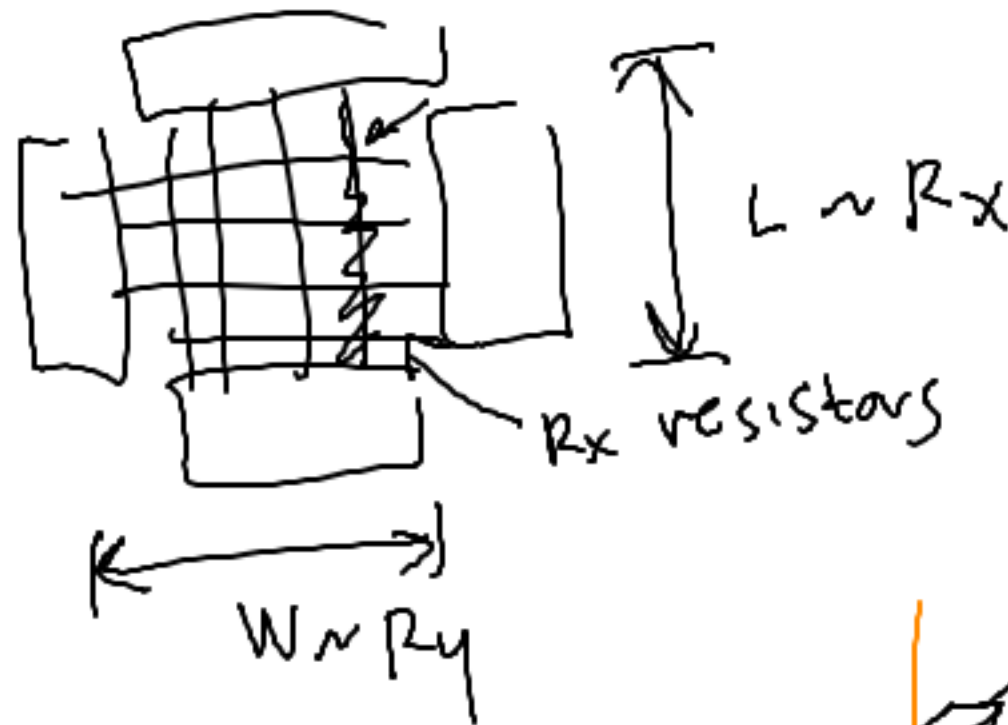
Does R_x go vertically or horizontally?
 $R_y \rightarrow$ horizontally




$$R_x = \rho_x \frac{L}{A}$$

$$R_y = \rho_y \frac{W}{A} \leftarrow$$

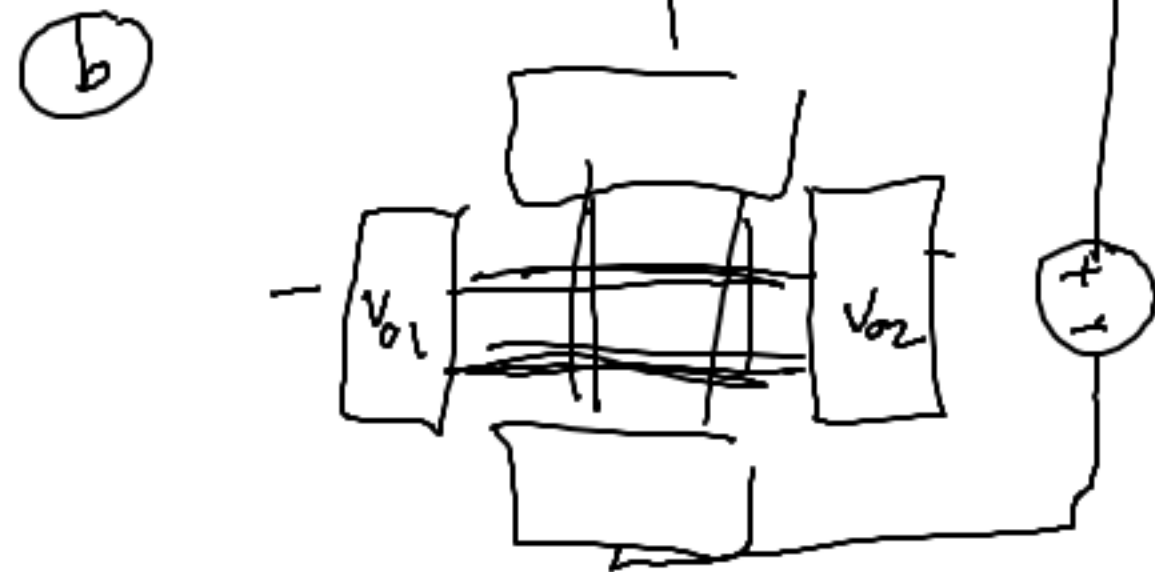

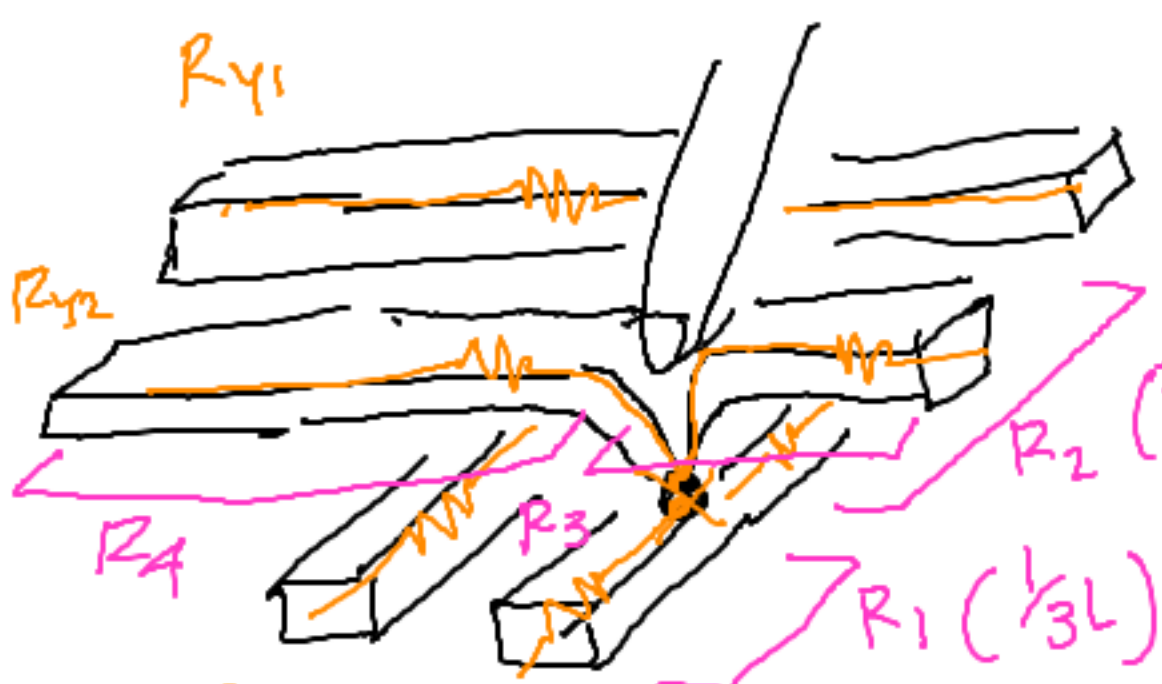

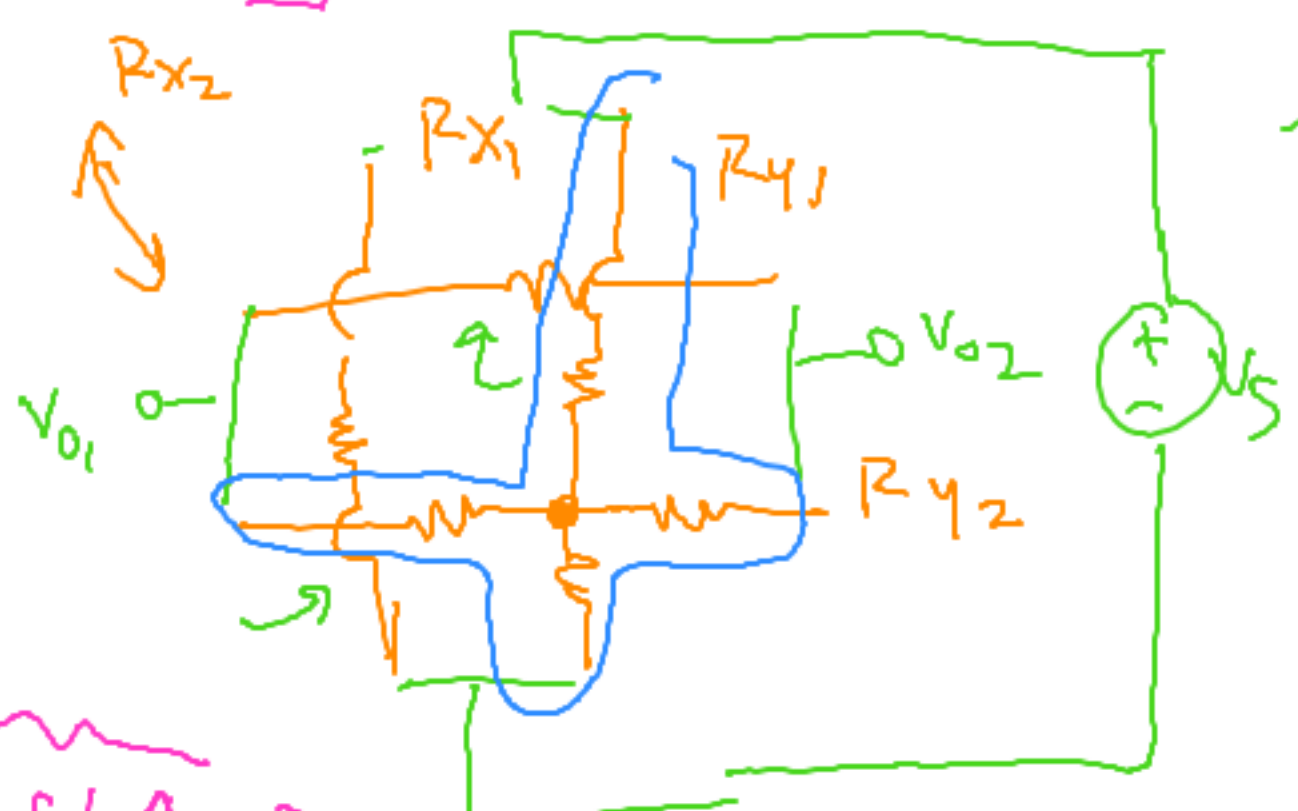R_{y1} - not affected, single R_y
 R_{x1} - not affected, single R_x
 R_{y2}, R_{x2} - break up into two



$R_x = R_y = 2k\Omega$




R_{y1} - doesn't matter
 no current
 R_{x1} - doesn't matter
 → doesn't change voltage drop

$$R_1 = \rho \times \frac{L/3}{A} = \frac{1}{3} R_x$$

$$R_2 = \rho \times \frac{2/3 L}{A} = \frac{2}{3} R_x$$

$$R_3 = \rho \times \frac{1/3 W}{A} = \frac{1}{3} R_y$$
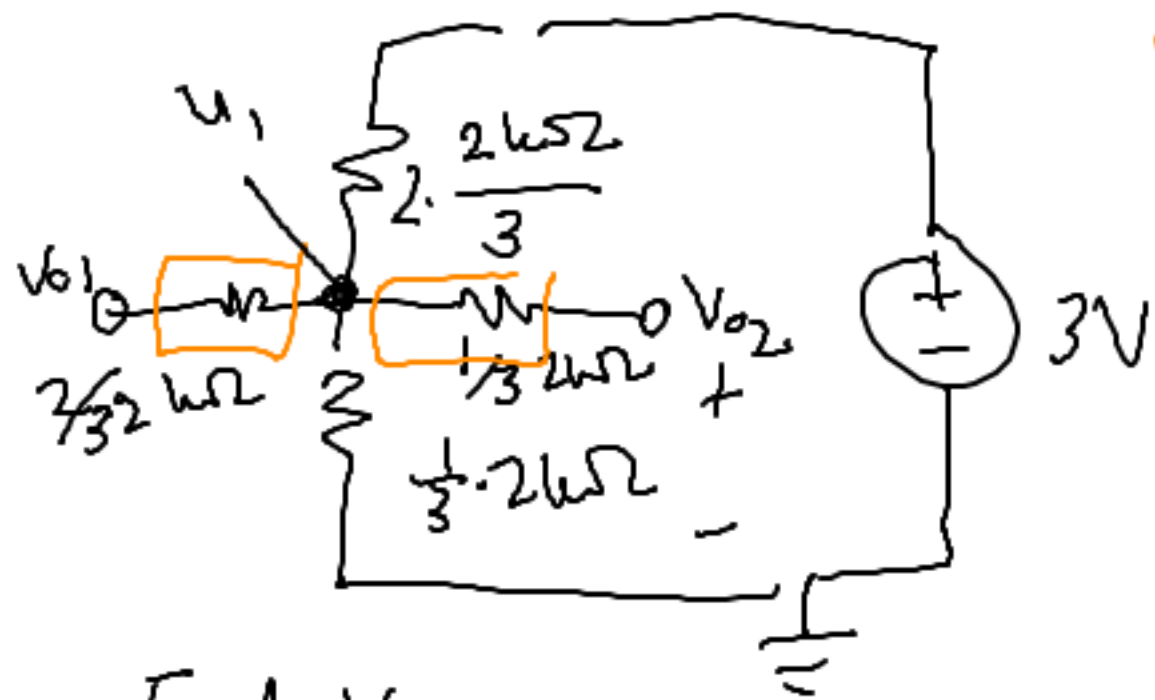
$$R_4 = \rho \times \frac{2/3 W}{A} = \frac{2}{3} R_y$$



Find V_{02}

Current through these?

→ No current
 → Open circuits (no path from V_{01}, V_{02} to other location)


$$u_1 - V_{02} = \underline{I} R \quad (R = \frac{1}{3} \cdot 2k\Omega)$$

$$I = 0$$

$$u_1 - V_{02} = 0$$

$$u_1 = V_{02}$$

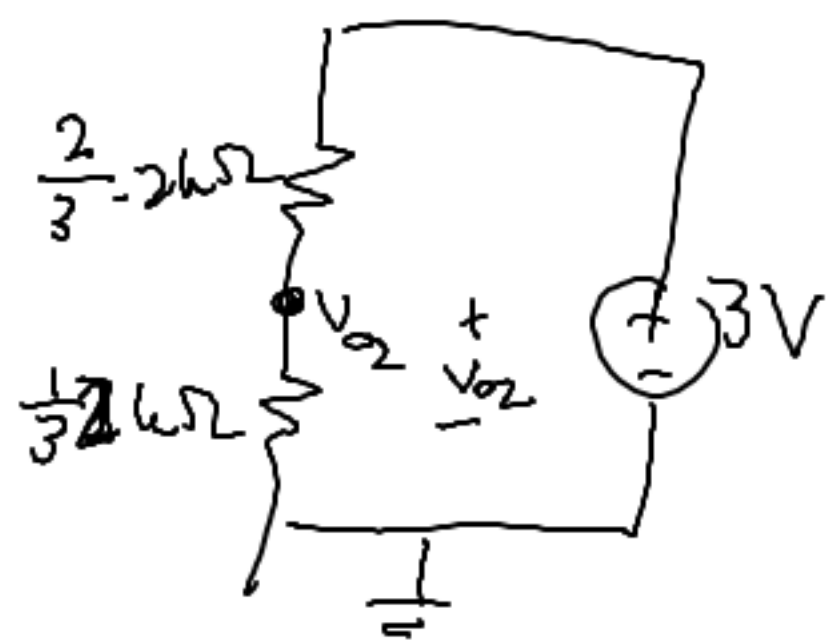(right $\frac{1}{3} k\Omega$ resistor is a dangling resistor)



$$V_{02} = \frac{R_{bot}}{R_{bot} + R_{top}} V_S$$



$$= \frac{\frac{1}{3} 2k\Omega}{\frac{1}{3} 2k\Omega + \frac{2}{3} 2k\Omega} 3V$$

$$= \frac{1}{3} 3V = 1V \checkmark$$

If you touch @ a diff. location, schematic are same?

No: diff. touch point \rightarrow different lengths,
different resistors involved
connected in different ways

1D - vs - 2D touchscreen (Extra)

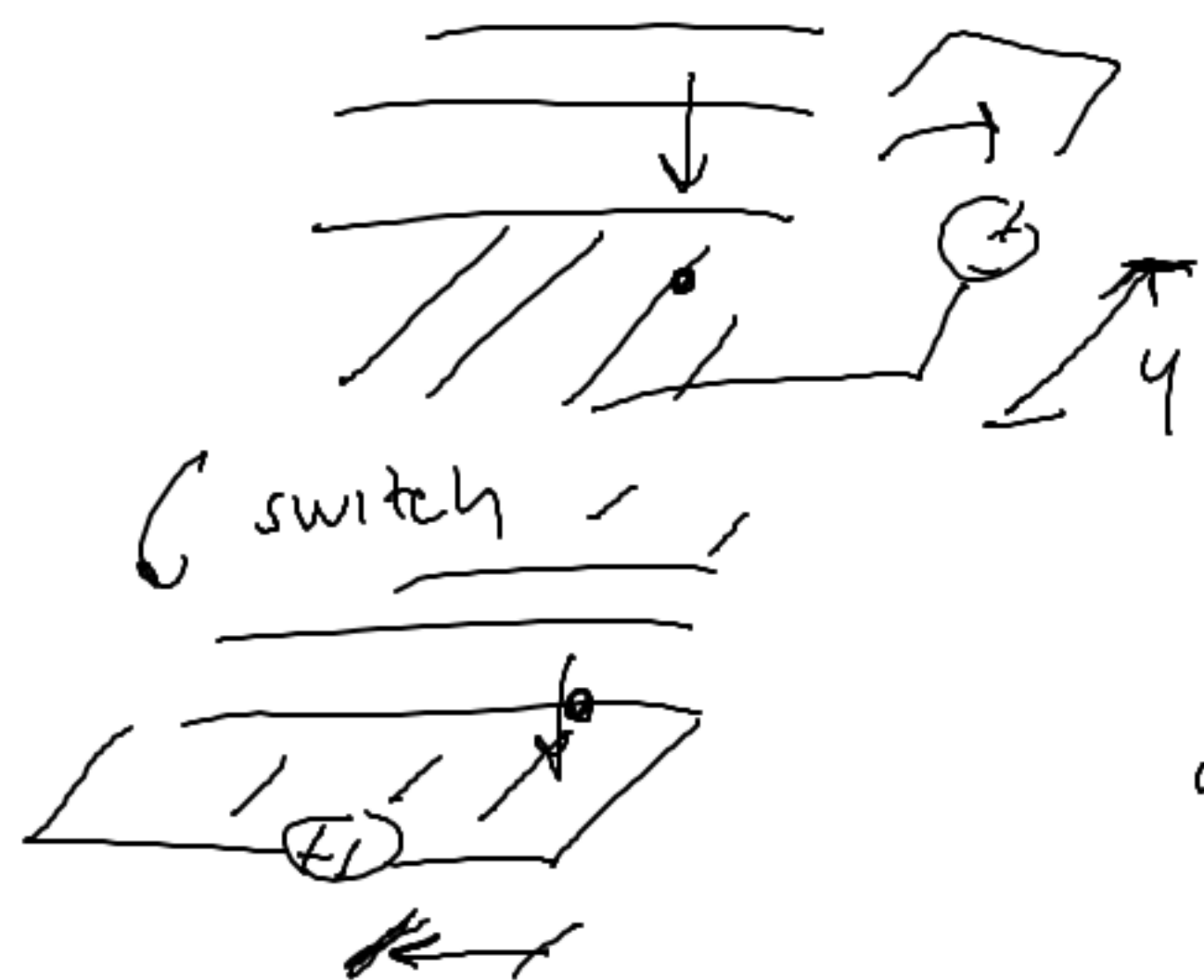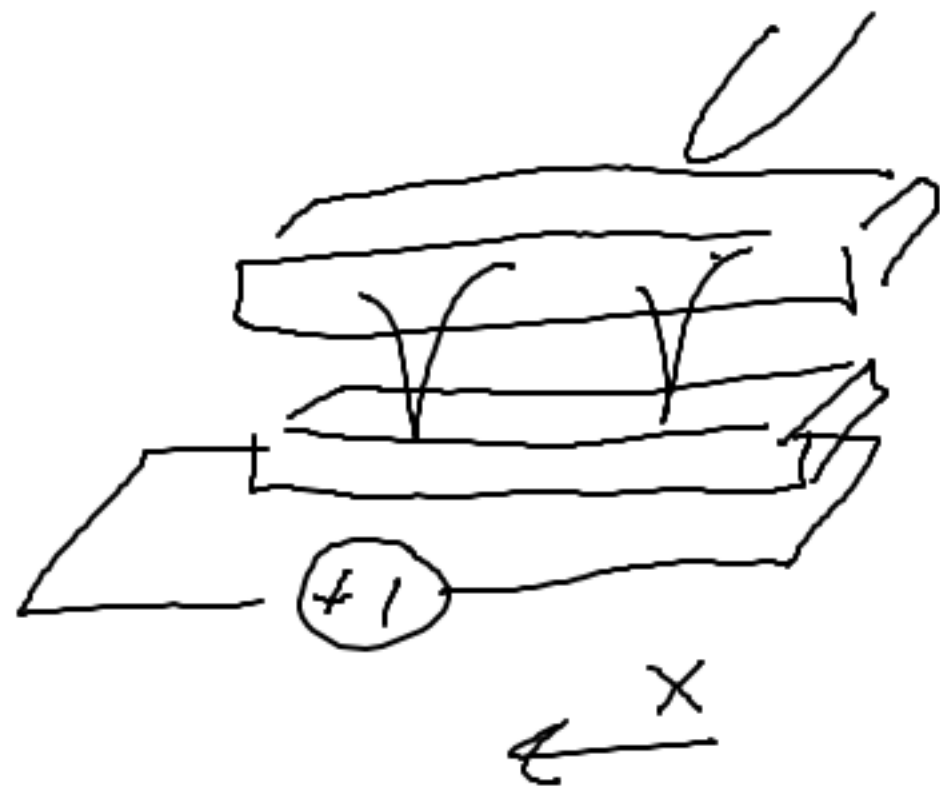

2D touchscreens
are just
1D along x ,
1D along y ,
rapidly
switch
between
 \rightarrow measure
 (x, y) before
our finger is
lifted

Q: What is the difference
between 1-D TS & 2-D TS
if both give us a
voltage divider?