


DIS 4A

- 1) Examples for superposition
- 2) Techniques for finding Thevenin & Norton equivalent circuits (23 methods)
- 3) How to identify series and parallel resistors
↳ How to redraw circuits

Midsemester survey → fill this out

Superposition: method for finding voltages & currents

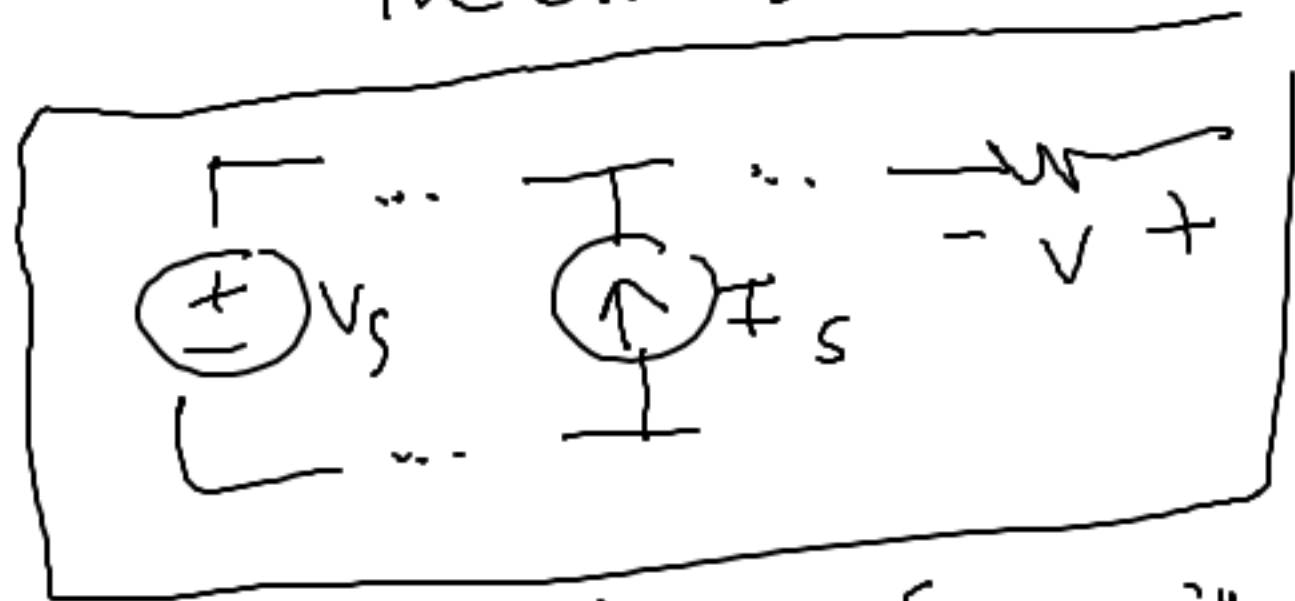Consider a voltage or current to be the sum of the effects of all sources acting independently



V_s and I_s work together to produce V
but if calculate effects of V_s & I_s separately, we can add to find V


$$\left. \begin{aligned} \underline{V} &= R \underline{I} \\ \underline{I} &= \frac{\underline{V}}{R} \end{aligned} \right\} \text{linearity}$$

Superposition can't calculate power

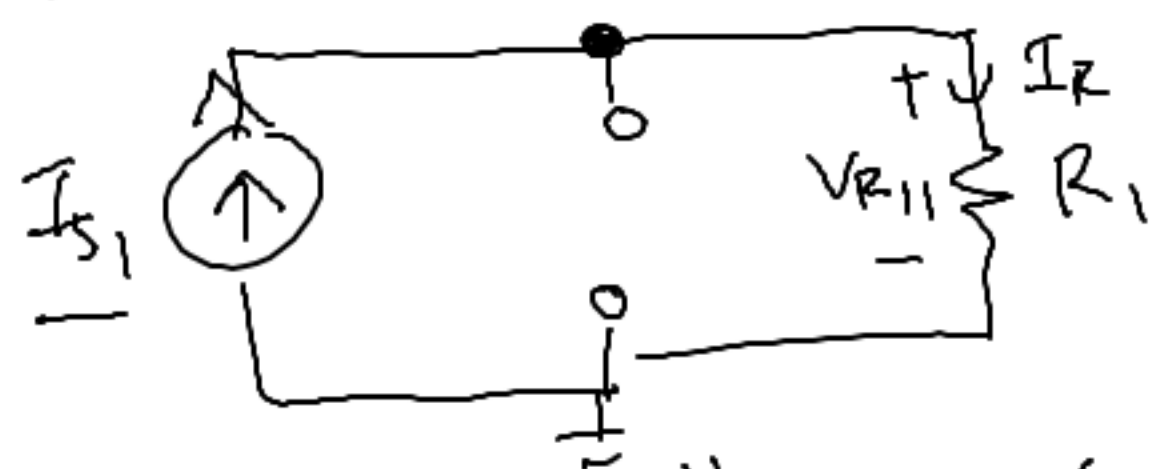i) Use superposition to find V_{R_i} (voltages across resistors)



First: turn off all sources except I_{s1} (current source off \Leftrightarrow open)




$$I_{s1} = I_R$$

$$\Rightarrow V_{R11} = I_{s1} R_1$$

Second: turn off all sources except I_{s2}

$$I_{s2} + I_R = 0$$

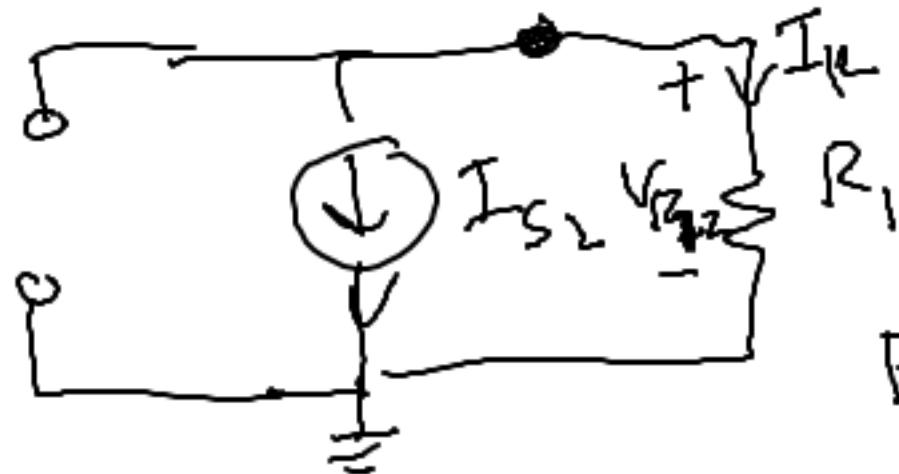

$$I_{s2} = -I_R$$

$$\Rightarrow V_{R12} = -I_{s2} R_1$$


Note: maintain the same polarity/direction of desired quantities
desired

By superposition $V_{R1} = V_{R11} + V_{R12} = (I_{s1} - I_{s2}) R_1$

For the ii) parts: power of all elements sum to 0


- ① Turn on one source at a time
- ② calculate value for subcircuit
- ③ add

⑥ ①

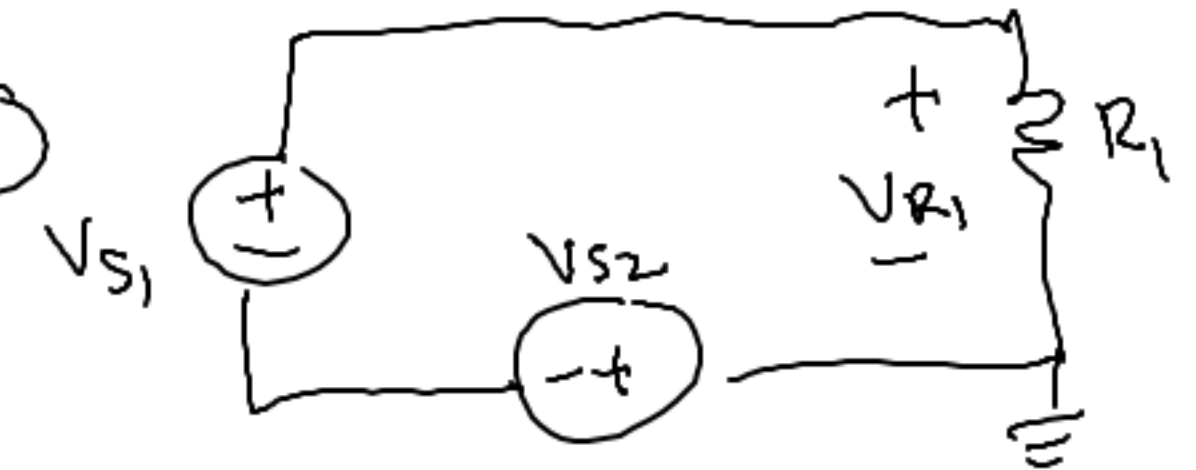

Find V_{R1}

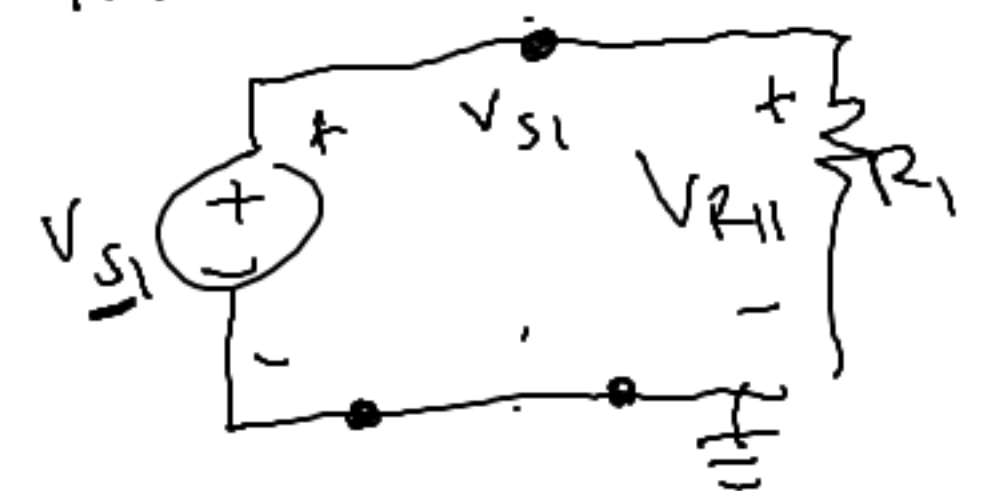① Turn off all sources except V_{S1} (turning off voltage source \rightarrow short/wire)




$$V_{R11} = V_{S1} - 0$$

$$\boxed{V_{R11} = V_{S1}}$$

By superposition

② Turn off all sources except V_{S2}

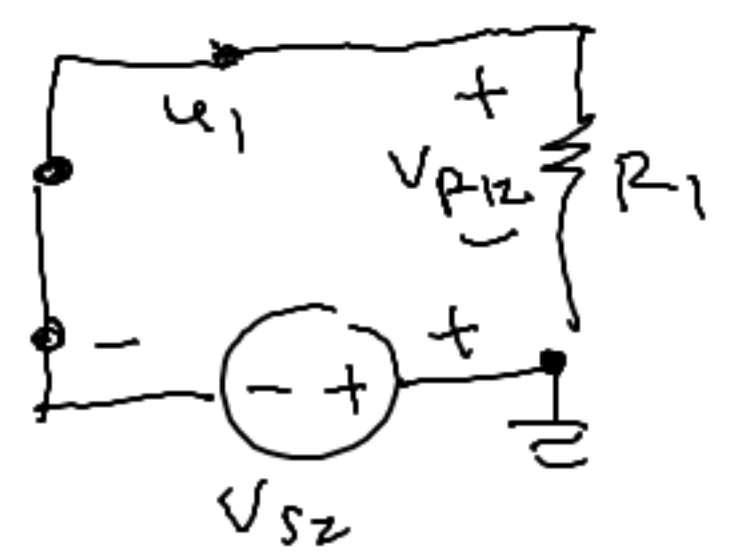


$$0V - u_1 = V_{S2}$$

$$V_{R12} = u_1 - 0$$

$$\boxed{V_{R12} = -V_{S2}}$$


$$V_{R1} = V_{R11} + V_{R12}$$

$$= \boxed{V_{S1} - V_{S2}}$$

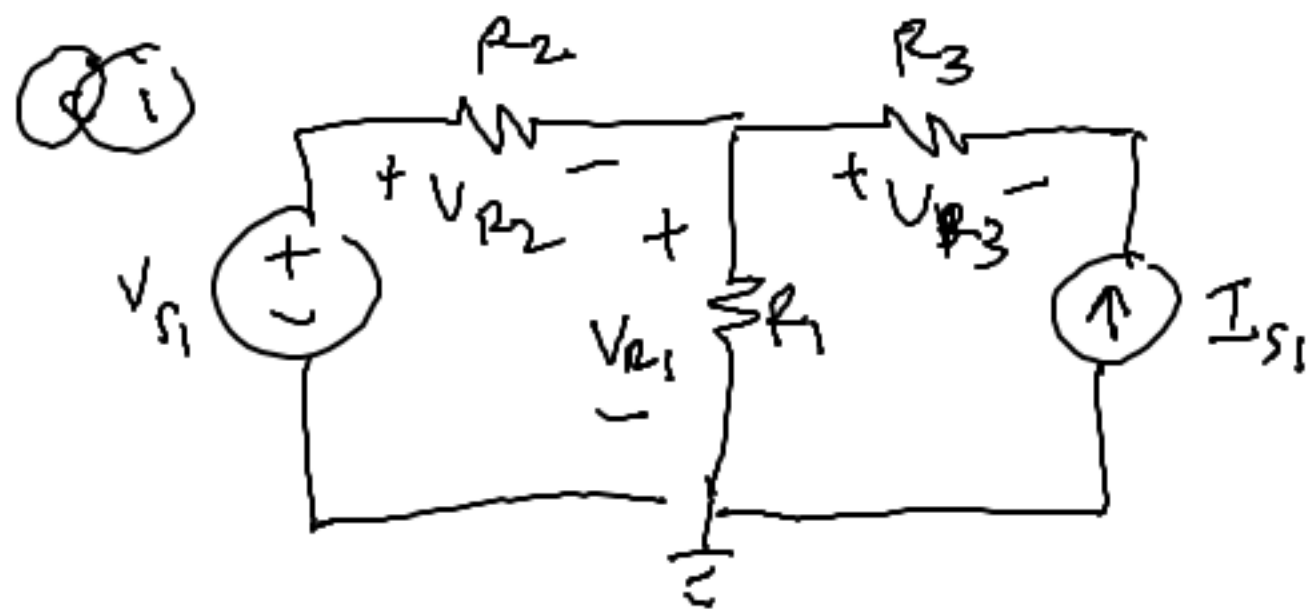

Find V_{R1}, V_{R2}, V_{R3}

Turn off I_{S1} , keep V_{S1} on

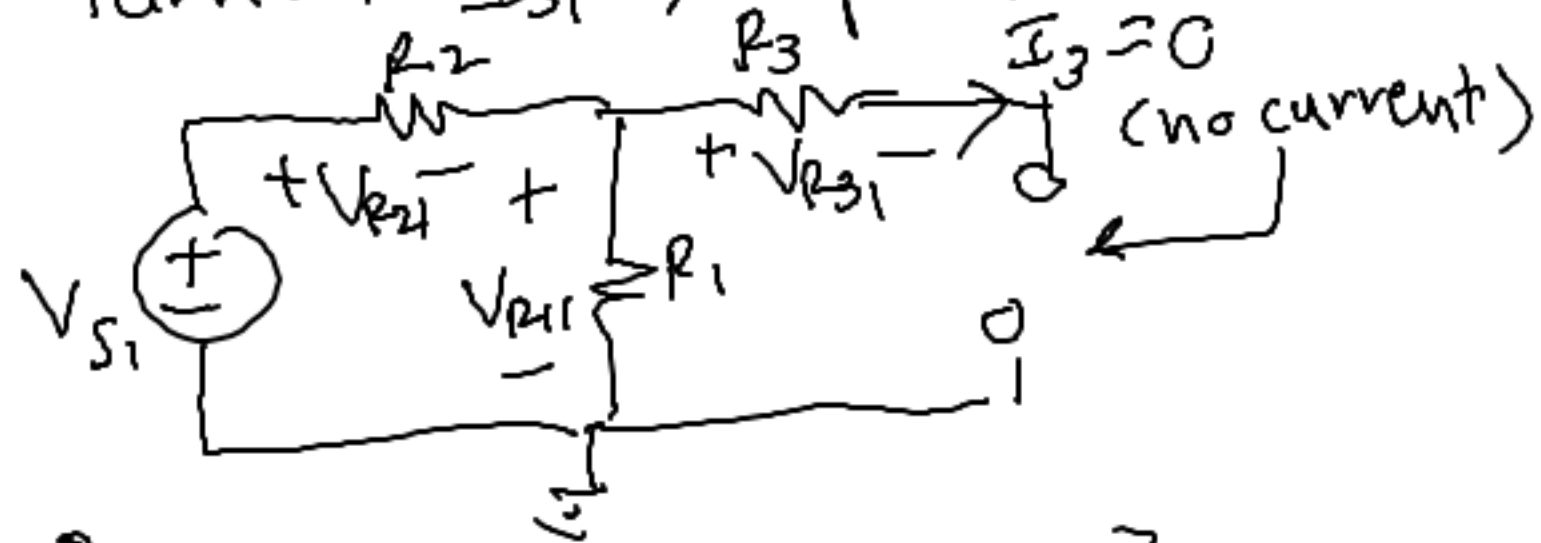


$$V_{R31} = R_3 I_3 = 0V$$

$$V_{R11} = \frac{R_1}{R_1 + R_2} V_{S1}$$

$$V_{R21} = \frac{R_2}{R_1 + R_2} V_{S1}$$

When applying formulas, check your assumption

Turn off V_{S1} , keep I_{S1} on

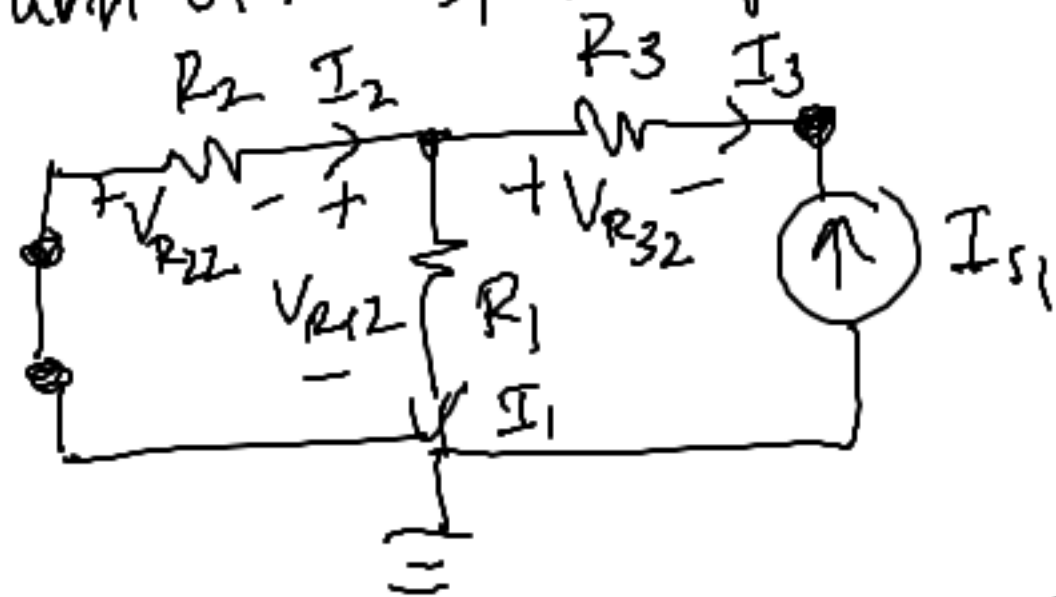

Current divider

$$I_3 + I_{S1} = 0 \Rightarrow I_3 = -I_{S1}$$

$$V_{R32} = R_3 I_3 = -R_3 I_{S1} \checkmark$$

$$V_{R12} = R_1 I_1 = \frac{R_1 R_2}{R_1 + R_2} I_{S1}$$

$$I_1 = \frac{R_2}{R_1 + R_2} I_{S1}$$

$$V_{R22} = R_2 I_2 = -\frac{R_1 R_2}{R_1 + R_2} I_{S1}$$


$$I_2 = \frac{R_1}{R_1 + R_2} I_{S1}$$

By superposition

$$V_{R_1} = V_{R_{11}} + V_{R_{12}} = \frac{R_1}{R_1 + R_2} V_{S_1} + \frac{R_1 R_2}{R_1 + R_2} I_{S_1} \quad \checkmark$$




$$V_{R_2} = V_{R_{21}} + V_{R_{22}} = \frac{R_2}{R_1 + R_2} V_{S_1} + \left(-\frac{R_1 R_2}{R_1 + R_2} I_{S_1} \right) \quad \checkmark$$
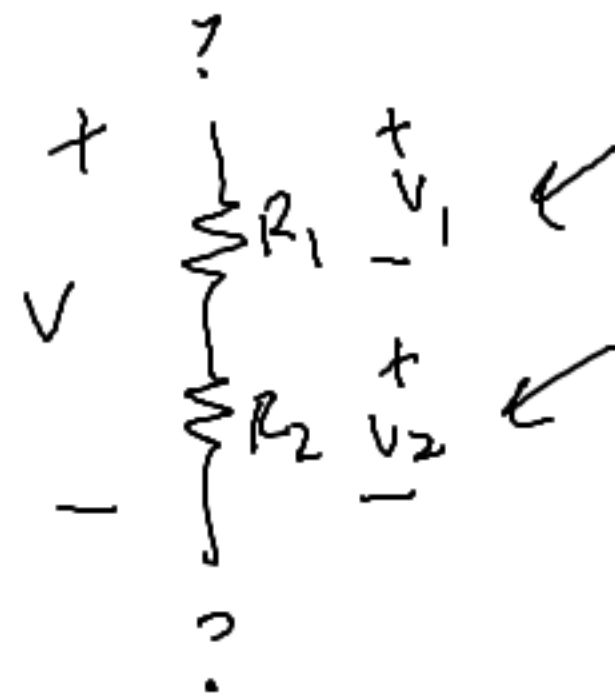
$$V_{R_3} = V_{R_{31}} + V_{R_{32}} = 0V + (-R_3 I_{S_1}) \quad \checkmark$$



Theremin $\frac{1}{3}$ Norton equivalent

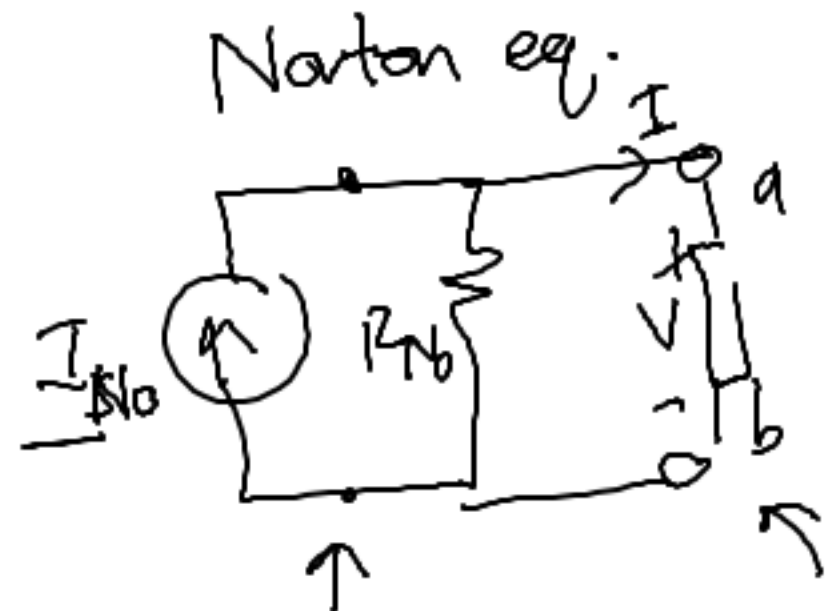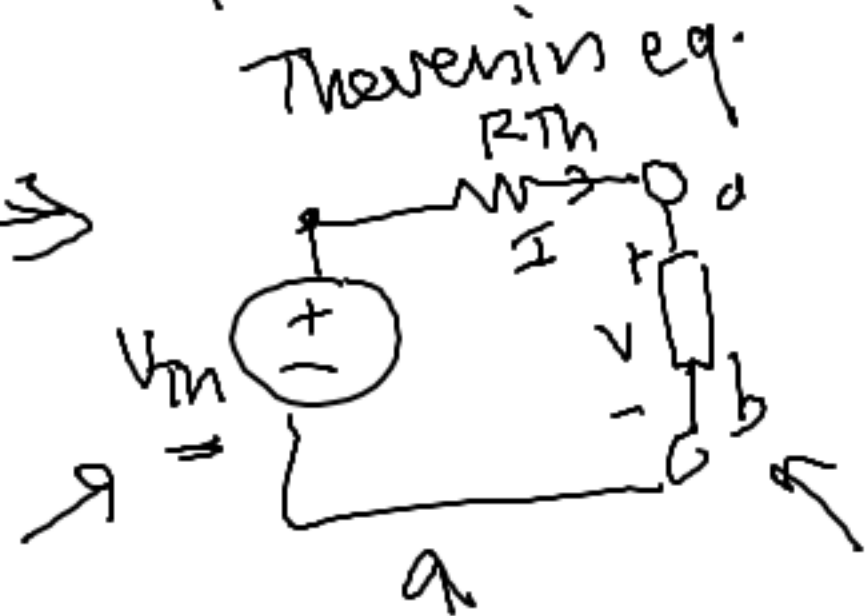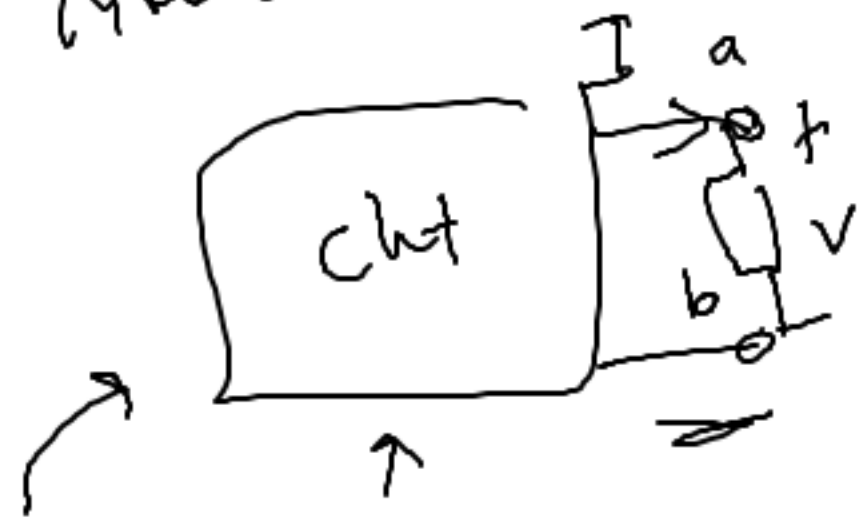- Take a complicated ckt. made of V_s , I_s , and R 's
- Simplify to a model of a single source + single resistor
- Model behaves the same way in terms of V, I





How to find? (Just find 2/3 below)

- 1 $V_{oc} = V_{th}$ (NVA)
- 2 $I_{sc} = I_{No}$ (NVA)



→ 3 $R_{th} = R_{No} = \frac{V_{th}}{I_{No}}$

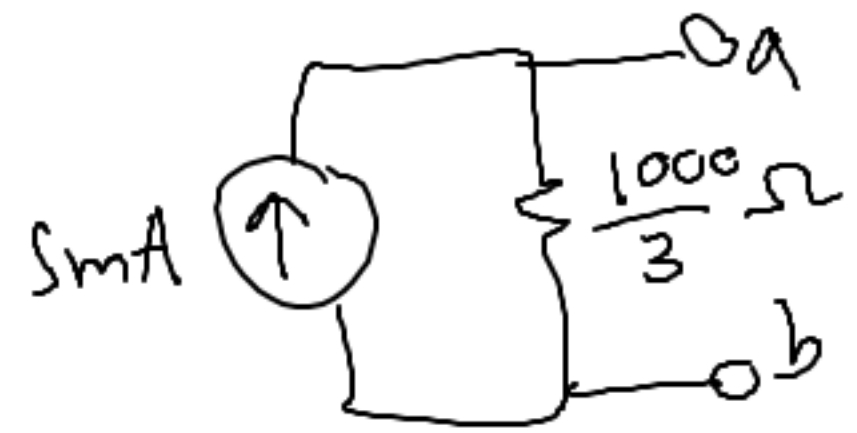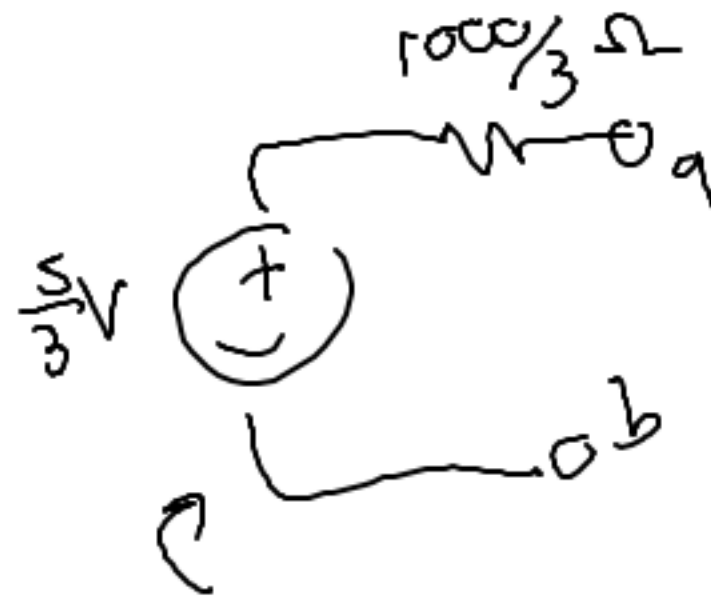- 3(i) Find eq. resistance w/ all sources in ckt. off
 - 3(ii) Find test current + test voltage w/ all independent sources off
- $R_{Th} = R_{No} = V_{test}/I_{test}$**



1) $V_{oc} = V_{th}$

$$V_{oc} = \frac{\frac{1}{2}k\Omega}{\frac{1}{2}k\Omega + 1k\Omega} 5V = \boxed{\frac{5}{3}V = V_{th}}$$


3) $R_{th} = R_{No} = \frac{V_{th}}{I_{No}} = \frac{\frac{5}{3}V}{5mA}$

$$= \boxed{\frac{1000}{3}\Omega}$$

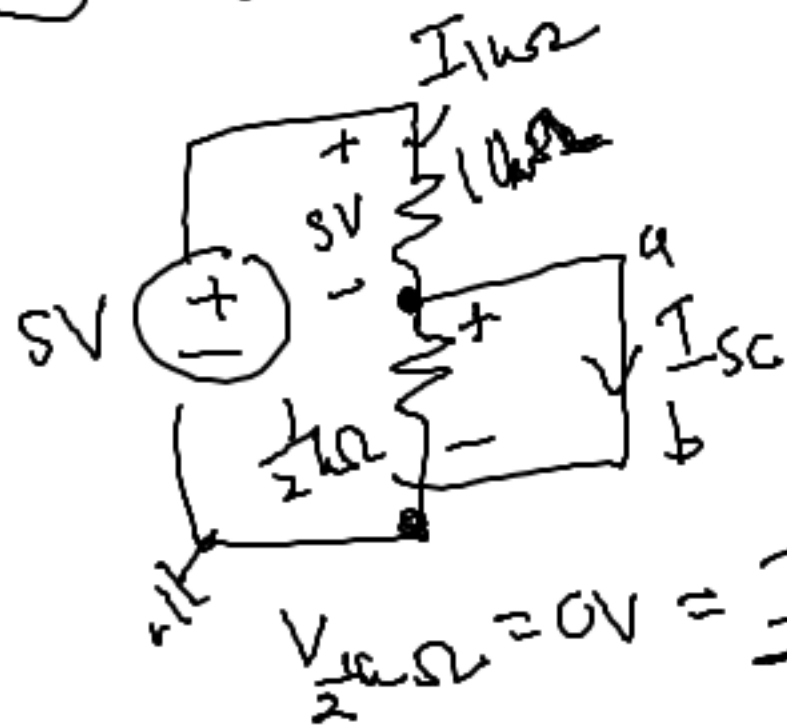2) $I_{sc} = I_{No}$

$$I_{1k\Omega} = 0 + I_{sc}$$

$$I_{sc} = I_{1k\Omega} = \frac{5V}{1k\Omega} = \boxed{5mA}$$





3 i




$$R_{th} = R_{eq} = 1k\Omega \parallel \frac{1}{2}k\Omega = \frac{1000}{3}\Omega$$

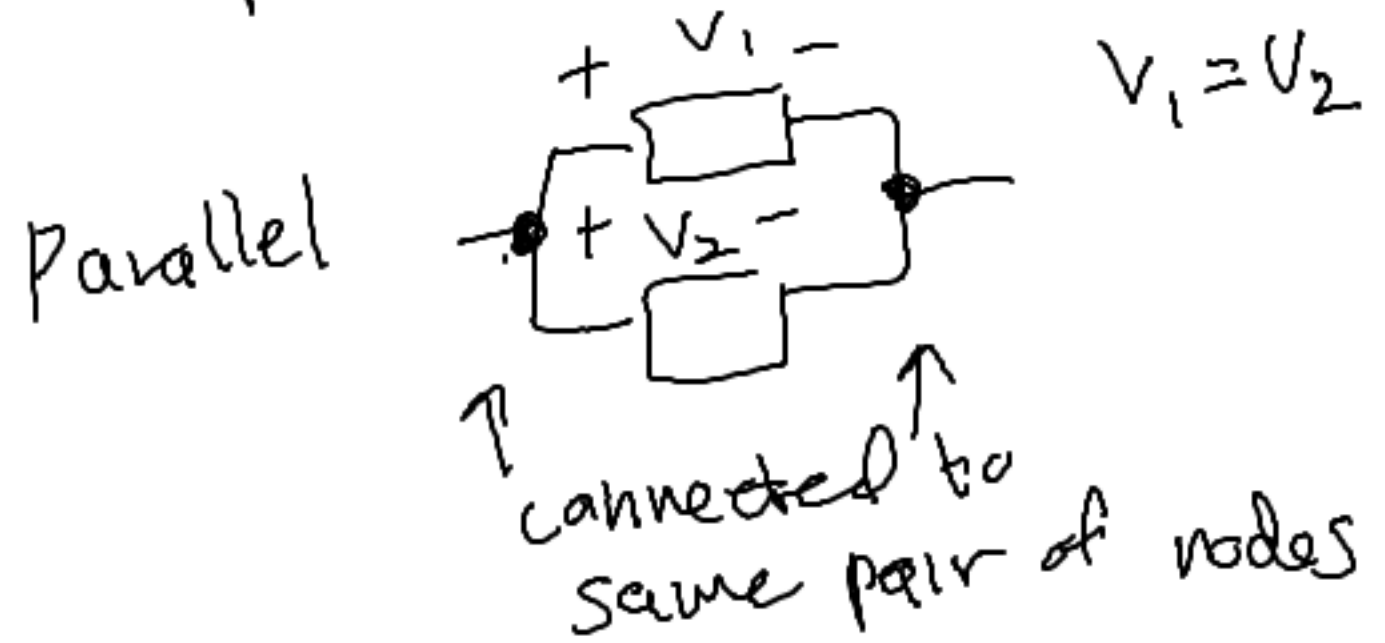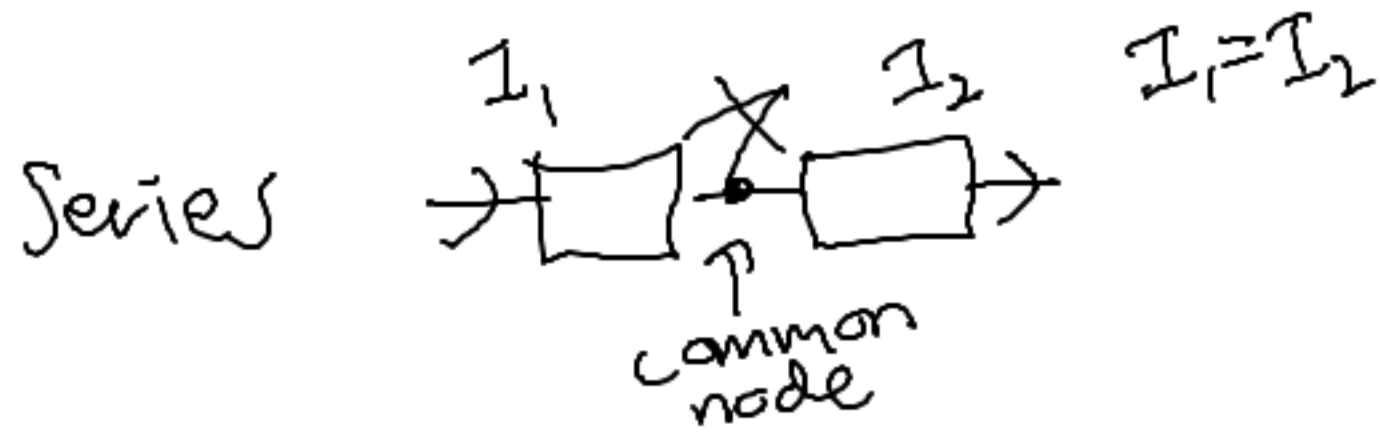3) Series - two elements are in series if they share a node with nothing else on it.


Parallel - two elements share a pair of nodes



Series resistor equivalents

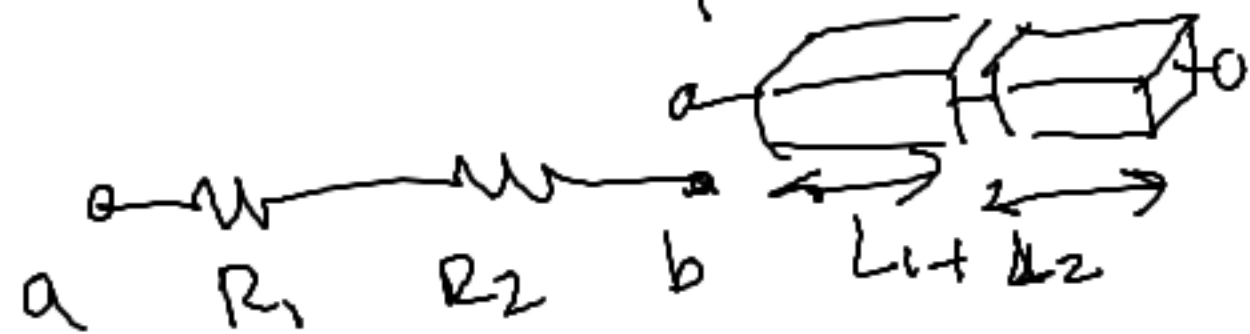


Parallel resistor equivalents

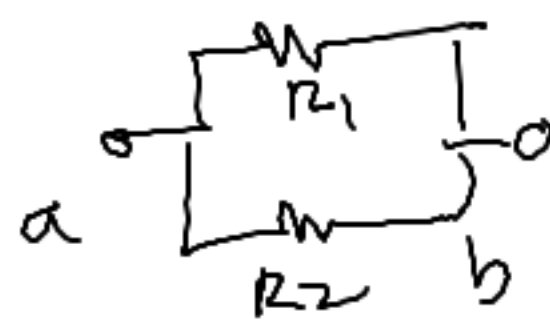


$$\underline{R_1 \parallel R_2} = \frac{R_1 R_2}{R_1 + R_2}$$
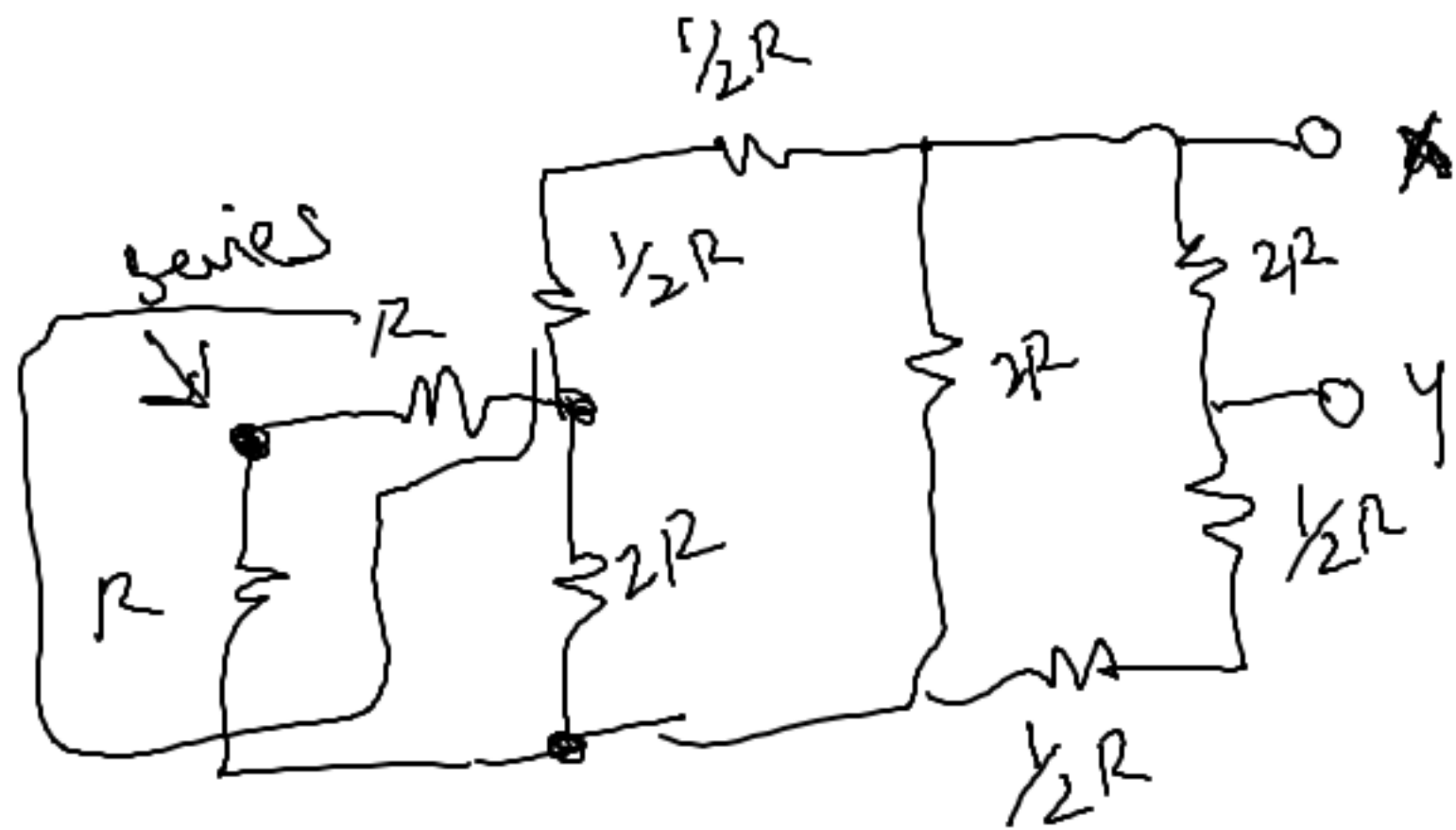
$$= \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$




Steps

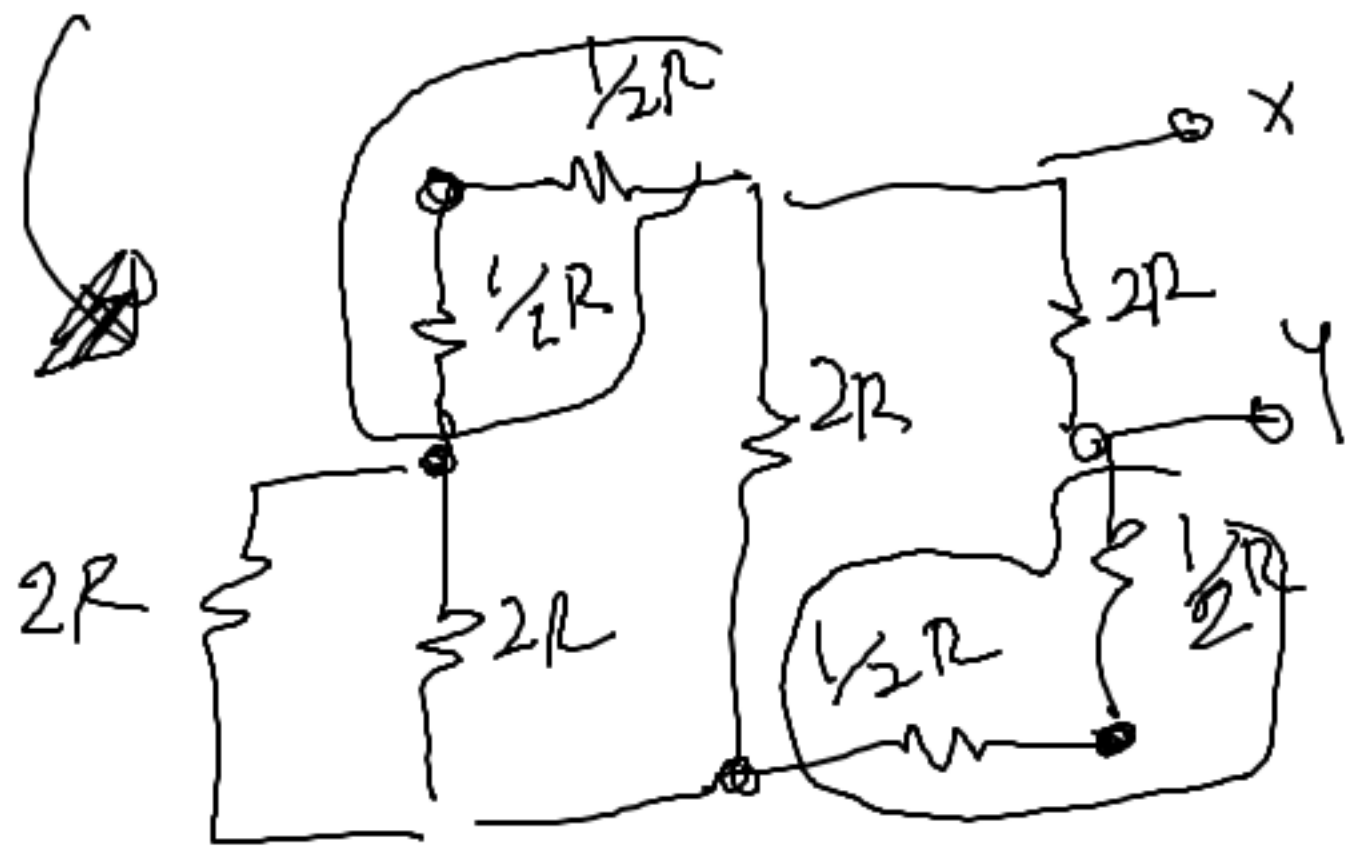- ① Choose a pair of resistors check if series/parallel
- ② If so, combine, calculate
- ③ Redraw ckt.
- ④ Repeat until simplified



$2R || 2R = R$

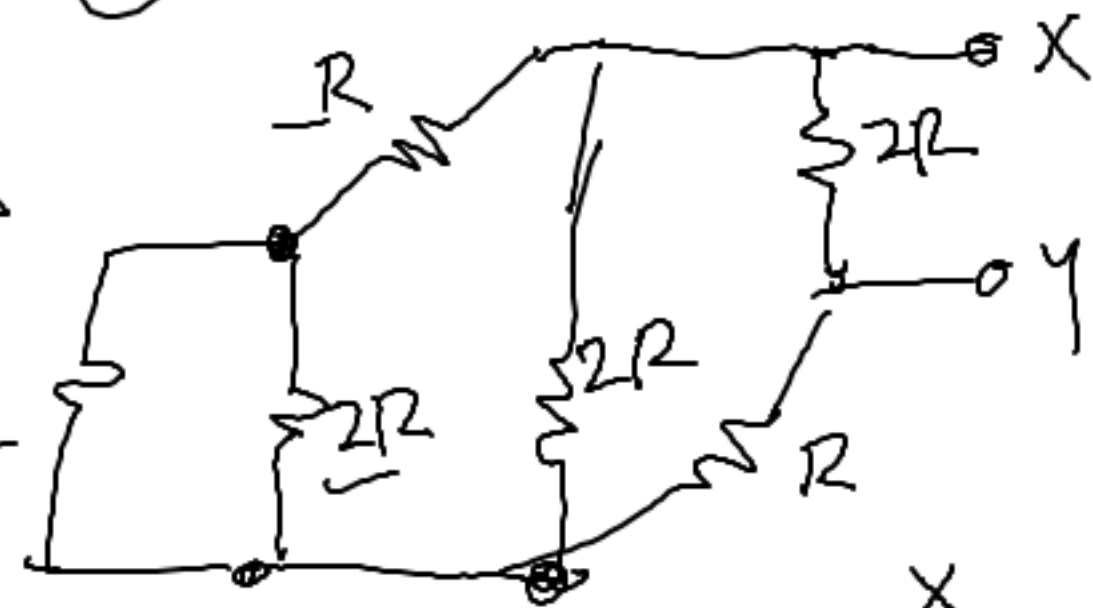

keep iterating until simplified