


EECS 16A DIS 4B

* Don't forget, there's a checkoff today

Today's topics

- 1 Capacitor Review (voltage, current, charge, energy)
- 2 Time dependent behavior of a charging capacitor
- 3 If time: Capacitor Equivalence derivations + practice
↳ Appeared in lecture yesterday

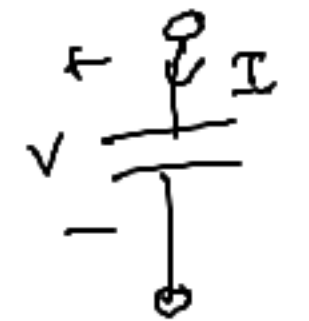I-V relation / I-V characteristic / Branch-Branch relationship



$Q = CV$

$i = \frac{dQ}{dt}$

Assuming a constant C

$i = \frac{dQ}{dt} = \frac{d}{dt}(CV) = C \frac{dV}{dt}$

$i = C \frac{dV}{dt}$

C - Capacitance [Farads]


Energy (stored in the capacitor)

$E = \frac{1}{2} CV^2$

$= \frac{1}{2} \frac{Q^2}{C}$

$= \frac{1}{2} QV$ [C][$\frac{J}{C}$]

$\rightarrow [J]$

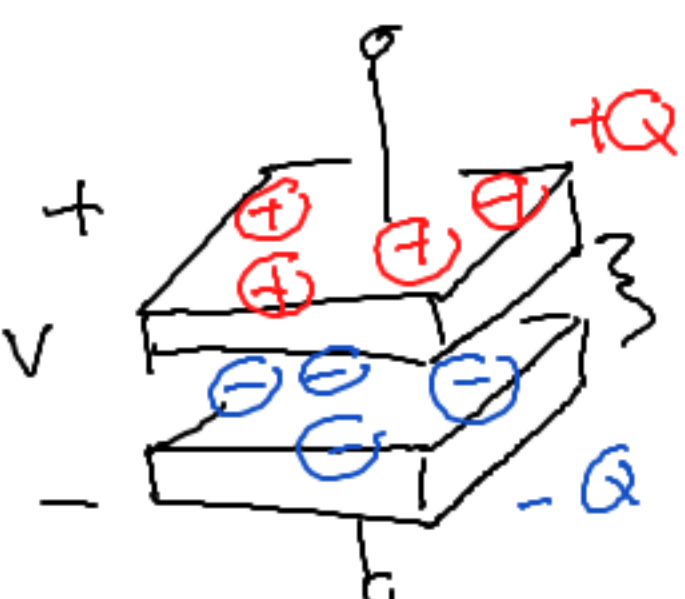

1 a



What is the charge + energy?

$$Q_1 = C_1 V_1$$

$$[F][V] = [C] \text{ coulombs, unit of charge}$$

$$V_s = 1V$$

$$V_1 = V_s \checkmark$$

$$C_1 = 1\mu F$$

$$Q_1 = (1\mu F)(1V) = \boxed{1\mu C}$$

Q: How do SI prefixes combine?

$$10^{-3} \text{ milli}[A] \times \text{milli}[B] = 10^{-3} \times 10^{-3} [AB] = 10^{-6} [AB] = \text{micro}[AB]$$

$$\text{milli}[A] \times [B] = 10^{-3} [AB] = \text{milli}[AB]$$


$$E = \frac{1}{2} CV^2 = \frac{1}{2} (1\mu F)(1V)^2 = \boxed{\frac{1}{2} \mu J}$$

$$[F][V]^2 \\ [C][V] \\ [J]$$

$$[V] = \left[\frac{J}{C} \right]$$

1 5

After capacitors have had time to charge

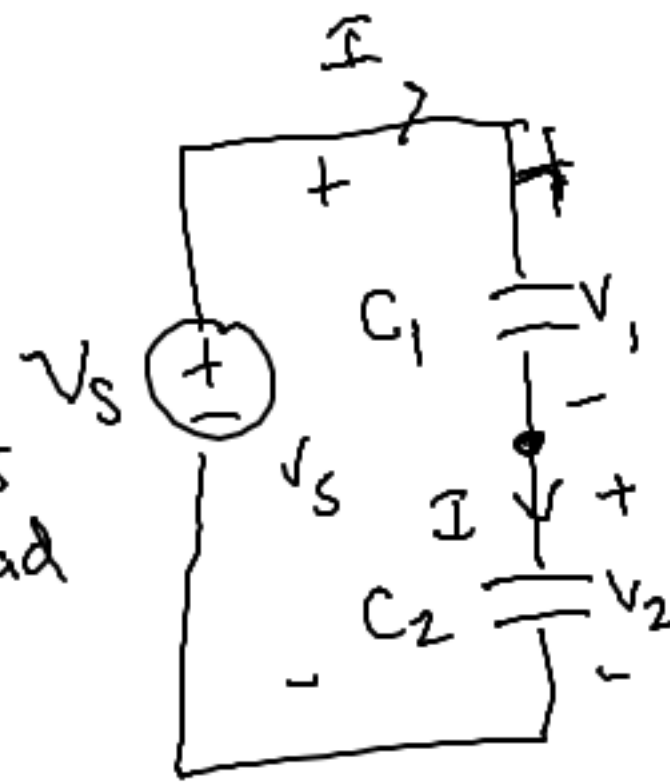


$V_s = 1V$
 $C_1 = 1\mu F$
 $C_2 = 3\mu F$

Find Q_1, Q_2 & E_1, E_2
 (charge on each cap.)
 (energy stored in each cap.)

Method 1

$V_s = V_1 + V_2$ (true after charging)
 $= \frac{Q_1}{C_1} + \frac{Q_2}{C_2}$
 $V_s = \frac{Q}{C_1} + \frac{Q}{C_2}$

We've assuming both caps unchanged @ start

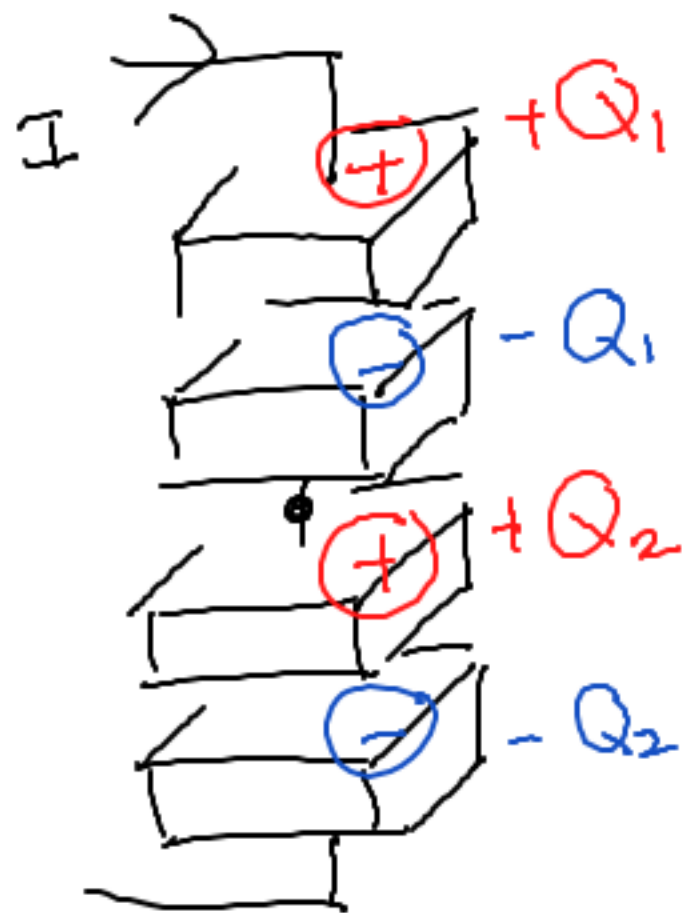

Method 1: (true even during charging)
 load at both caps charges
 $Q_1 = Q_2 = Q$
 Method 2: Use equivalence

$Q = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} V_s = \frac{C_1 C_2}{C_1 + C_2} V_s = \frac{1\mu F \cdot 3\mu F}{1\mu F + 3\mu F} \cdot 1V = \frac{3}{4} \mu C = Q_1 = Q_2$


Using method 2

$Q = (C_1 || C_2) V_s$

$E_1 = \frac{1}{2} Q_1 V_1 = \frac{1}{2} \frac{Q_1^2}{C_1} = \frac{1}{2} \frac{(\frac{3}{4} \mu C)^2}{1\mu F} = \frac{9}{16} \mu J$
 $E_2 = \frac{1}{2} \frac{Q_2^2}{C_2} = \frac{1}{2} \frac{(\frac{3}{4} \mu C)^2}{3\mu F} = \frac{3}{32} \mu J$

I didn't calc. V_1

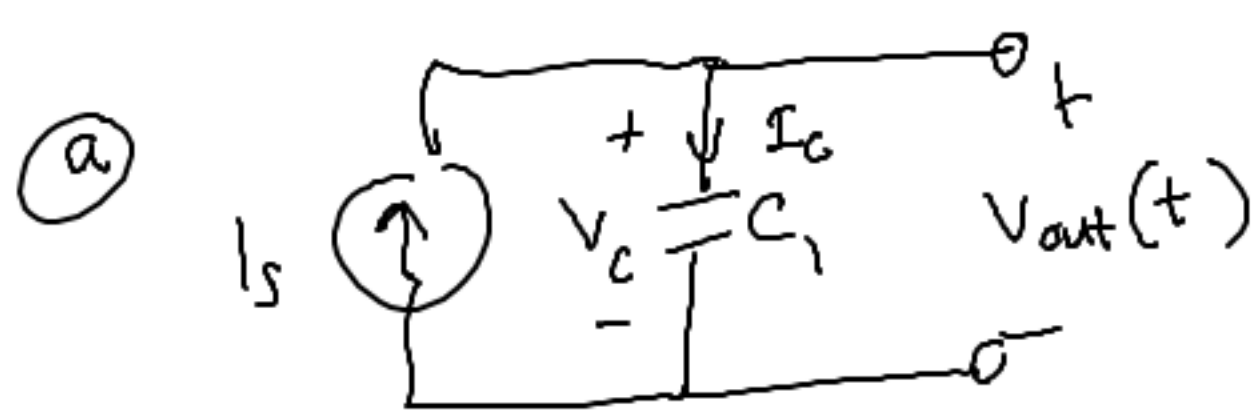2] How capacitors behave (with time) when charged by a constant current source.



Find $V_{out}(t)$ in terms of C_1, I_s, t (time)

$$\begin{cases} Q = CV & \textcircled{1} \\ i = C \frac{dV}{dt} & \textcircled{2} \leftarrow \end{cases}$$

$$I_c = I_s \text{ (KCL @ top)}$$

$$C_1 \frac{dV_c}{dt} = I_s \quad V_c(t) = V_{out}(t)$$

$$\frac{dV_{out}}{dt} = \frac{I_s}{C_1}$$

$$\int_{V_{out}(0)}^{V_{out}(t)} dV_{out} = \int_{t=0}^{t=t} \frac{I_s}{C_1} dt$$

$$V_{out} \Big|_{V_{out}(0)}^{V_{out}(t)} = \frac{I_s}{C_1} t \Big|_0^t$$

$$V_{out}(t) - V_{out}(0) = \frac{I_s}{C_1} (t - 0)$$



$$V_{out}(t) = \underbrace{V_{out}(0)} + \underbrace{\frac{I_s}{C_1} t} \Rightarrow$$

$$V_{out}(0) = 0V$$

$$V_{out}(t) = \frac{I_s}{C_1} t$$

constant current leads to constantly increasing (linearly) voltage

6

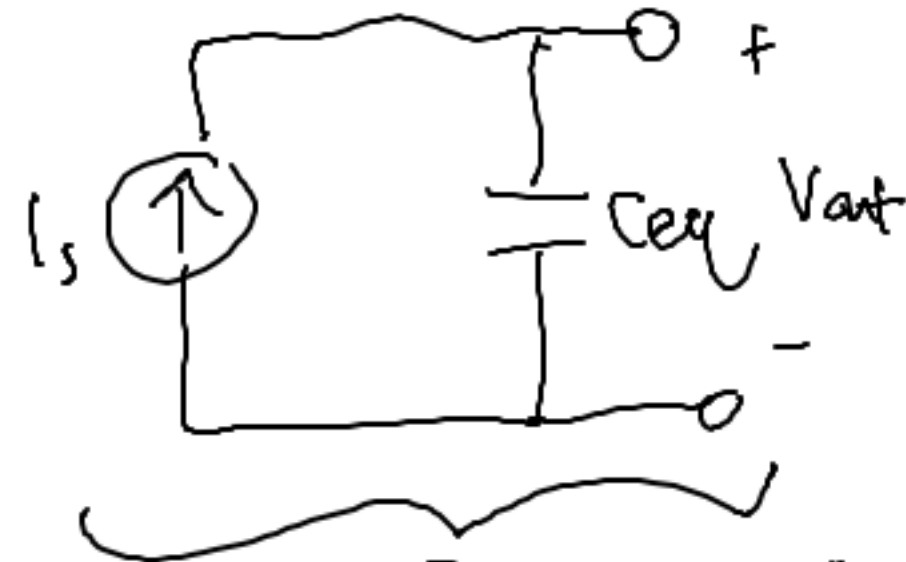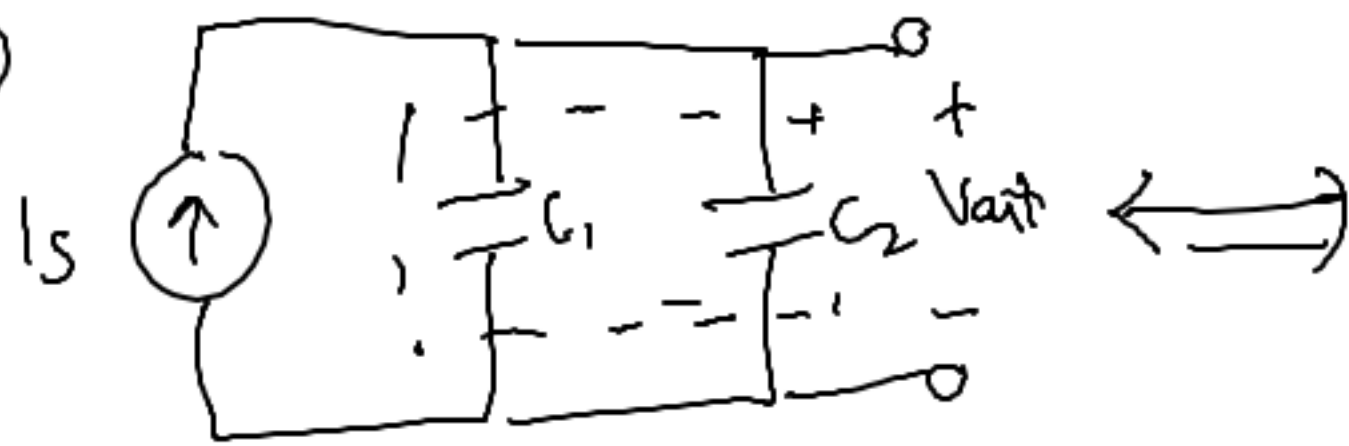

Using
cap.
equivalence

$$C_{eq} = C_1 + C_2$$

(parallel caps add)


$$V_{out}(t) = \frac{I_s}{C_{eq}} t = \boxed{\frac{I_s}{C_1 + C_2} t}$$

- 3 (a) Deriving Parallel equivalent capacitance
 (b) Deriving series " "
 (c) Practising using equivalence

$$i = C \frac{dV}{dt}$$

in lecture this was used

$$Q = CV$$

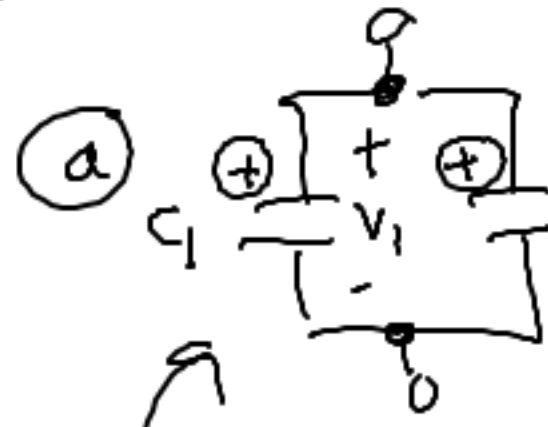

$$V_{eq} = V_1 = V_2 \text{ (parallel)}$$

$$Q_1, Q_2$$

$$Q_{eq} = Q_1 + Q_2$$

$$V_{eq} \sim Q_{eq} ?$$

$$Q_{eq} = C_1 V_{eq} + C_2 V_{eq}$$


$$Q_1 = C_1 V_1 = C_1 V_{eq}$$

$$Q_2 = C_2 V_2 = C_2 V_{eq}$$

$$i_{eq} = C_1 \frac{dV_1}{dt} + C_2 \frac{dV_2}{dt}$$

$$Q_{eq} = C_{eq} V_{eq} = (C_1 + C_2) V_{eq}$$
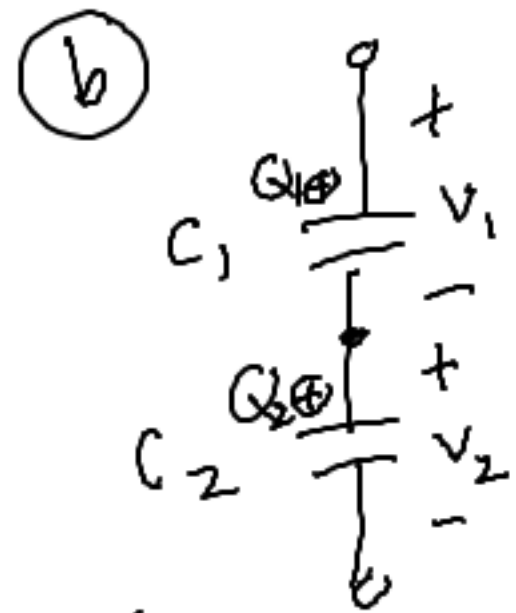
$$C_{eq} = C_1 + C_2 \text{ (in parallel)}$$



Series eq. C : Assumption: both start uncharged
 both start with the same amount of charge

$$Q_{eq} = Q_1 = Q_2$$

(series, same current
 dumps same charge)

$$V_{eq} = V_1 + V_2$$

$$V_{eq} = \frac{Q_{eq}}{C_1} + \frac{Q_{eq}}{C_2} = \left(\frac{1}{C_1} + \frac{1}{C_2} \right) Q_{eq}$$

$$Q_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} V_{eq} = \underbrace{\frac{C_1 C_2}{C_1 + C_2}}_{C_1 || C_2} V_{eq}$$

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$


(series eq.)

$A || B = \frac{AB}{A+B}$
 operation, not
 shape of circuit



Extra: Not covered, but here for your use/learning/checking

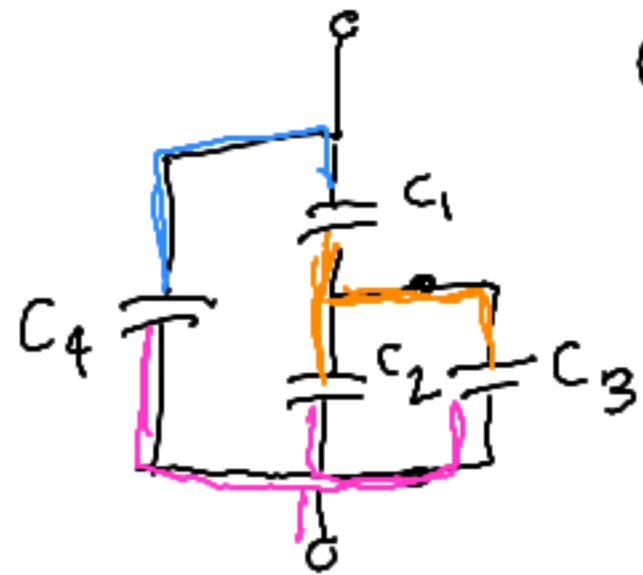3 (c) Practice using series and parallel equivalence to reduce to a single equivalent



1 Check series & parallel for pairs


✗ $C_1 \parallel C_2$? No, neither (bc of C_3 , not series, bc of C_4 not parallel)

✗ $C_4 \parallel C_2$? also Neither

✔ $C_2 \parallel C_3$? Yes! Parallel

2 Calculate value
 $C_{eq} = C_2 + C_3$

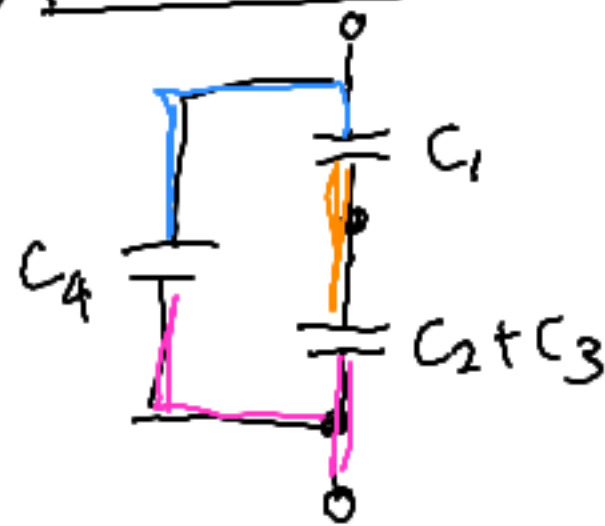
3 Redraw with substitution: The equivalent should be connected to the same pair of nodes (●, ●)



4 Iterate!

1 $C_1 \parallel C_2 + C_3$ series

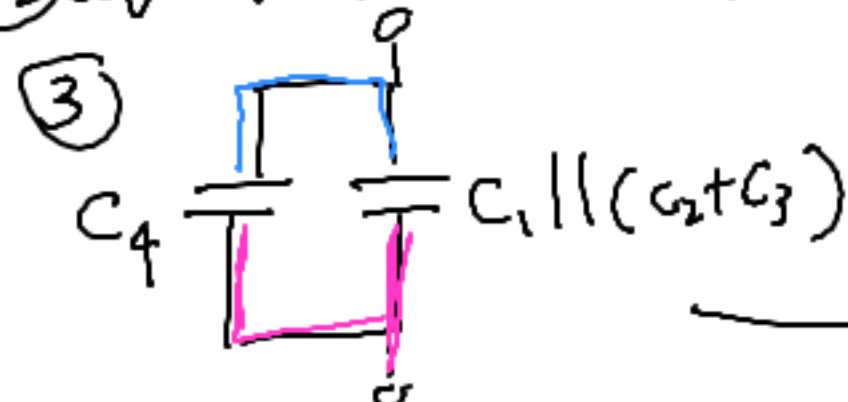2 $C_{eq} = C_1 \parallel (C_2 + C_3)$ (parallel operator doesn't distribute)



(●, ●)

4



$$C_{eq} = C_4 + C_1 \parallel (C_2 + C_3)$$

Extra: not covered during discussion but here for your use/learning

Q: Why is equivalence useful?

So far, we have learned of 4 kinds of equivalence

- Norton
- Resistor
- Thevenin
- Capacitor



A: Equivalence is actually useful to analysis (finding voltages + currents)

Q: How?

Hard problem: Find I_S

Easier problem: Find I_S

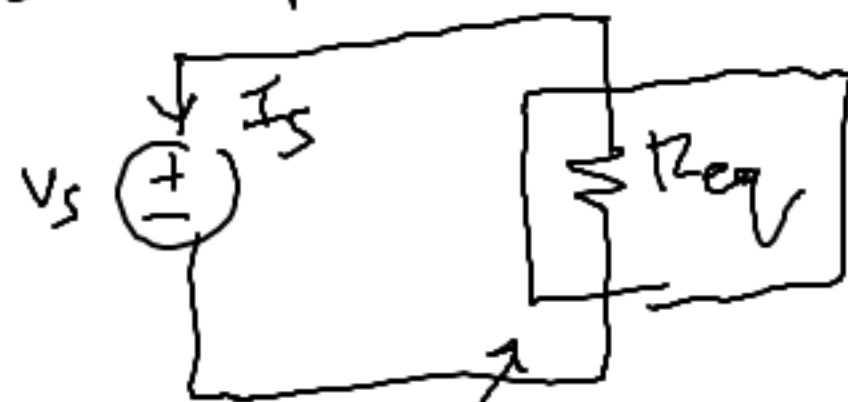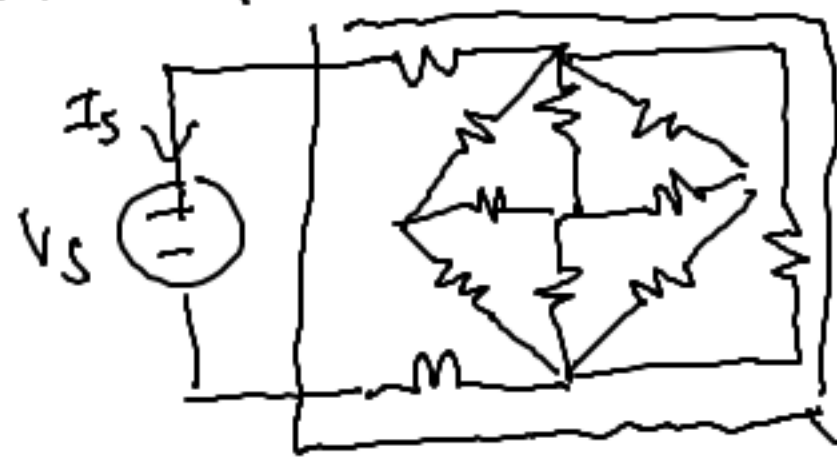A: It converts hard problems into easier problems with the same behavior




Calculate R_{eq}

Q: How to use it then? Here is a rough procedure

- A:
- ① Reduce some subpart of a circuit to its equivalent (redraw the circuit)
 - ② Calculate a voltage/current in the easier circuit
 - ③ Go back to unreduced circuit / unwind the simplification you made
 - ④ Use new quantity you know to iterate, apply value

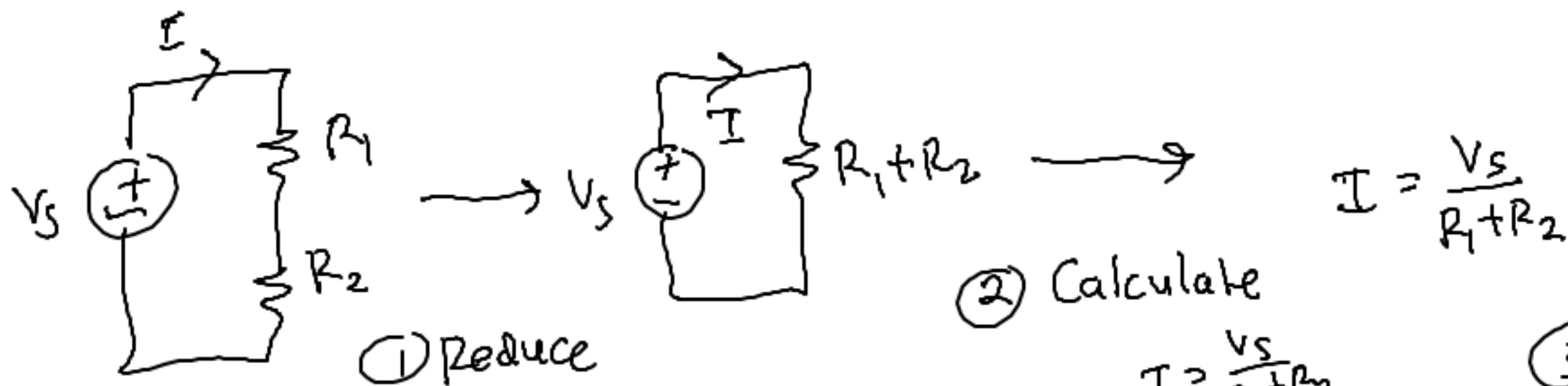Examples:

Deriving
Voltage
divider
using
equivalence



$$I_{R_1} = I$$


$$I_{R_2} = I$$

$$\Rightarrow V_{R_1} = R_1 I = R_1 \left(\frac{V_s}{R_1 + R_2} \right)$$

$$V_{R_2} = R_2 I = R_2 \left(\frac{V_s}{R_1 + R_2} \right)$$


Tada! Very
succinct!

④ apply

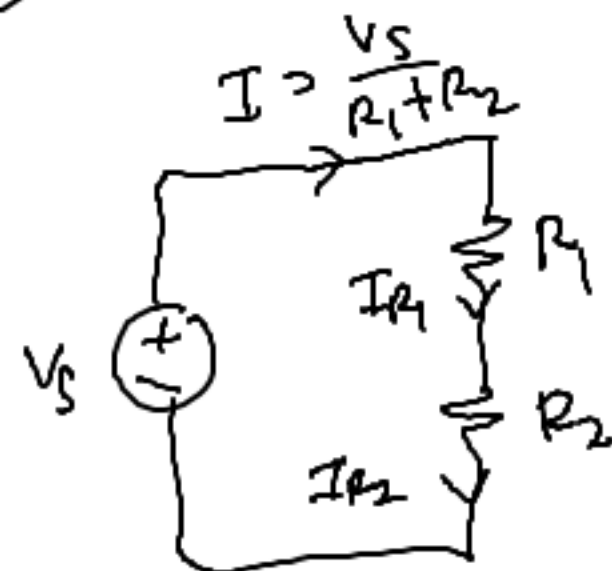

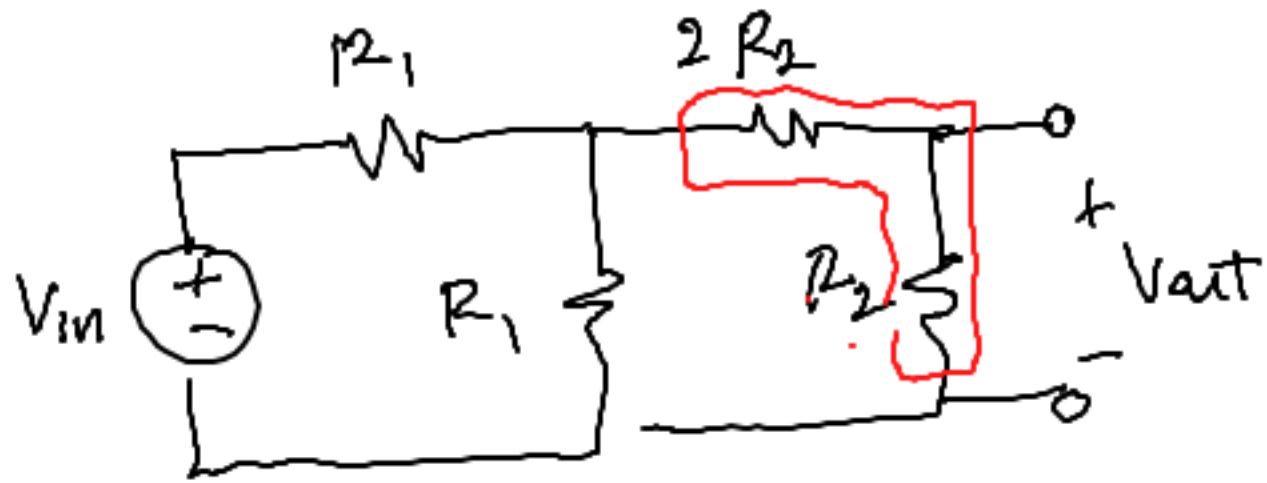
Examples:

DIS 3C
Analyzing
composed
voltage
dividers



Objective: find V_{out} in terms of V_{in}

① Reduce: $2R_2$ & R_2 in series

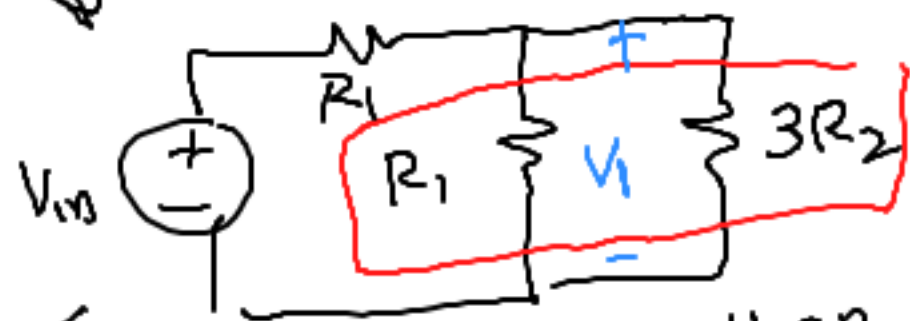

V_{out} no longer here!
that's okay though, will see later

① Reduce: $R_1 \parallel 3R_2$





② Calculate!
Use voltage division to find V_1

$$V_1 = \frac{R_1 \parallel 3R_2}{R_1 + R_1 \parallel 3R_2} V_{in}$$

③ Rewind! $\times 2 \rightarrow$

④ Apply: Use voltage divider again

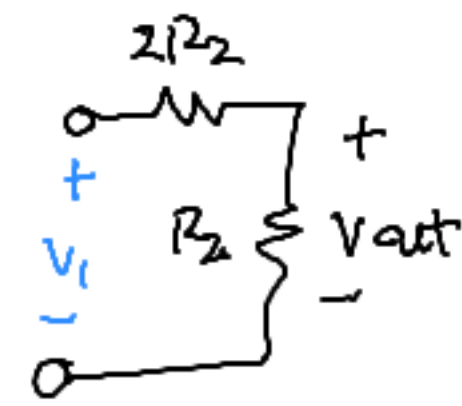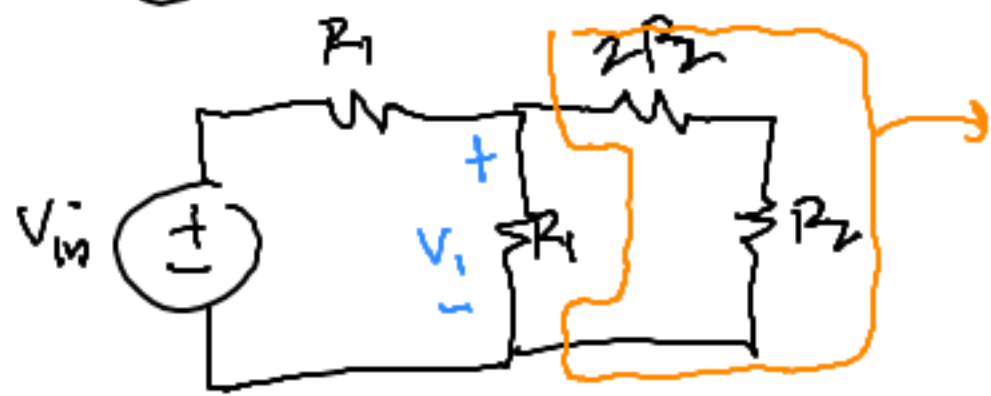

$$\begin{aligned} V_{out} &= \frac{R_2}{2R_2 + R_2} V_1 \\ &= \frac{1}{3} V_1 \\ &= \dots \end{aligned}$$


Final answer:

$$V_{out} = \frac{1}{3} \frac{R_1 \parallel 3R_2}{R_1 + R_1 \parallel 3R_2} V_{in}$$

Note: compute $R_1 \parallel 3R_2$, compare to previous notes


Exercise: Try using Thevenin/Norton on previous example

Hint:

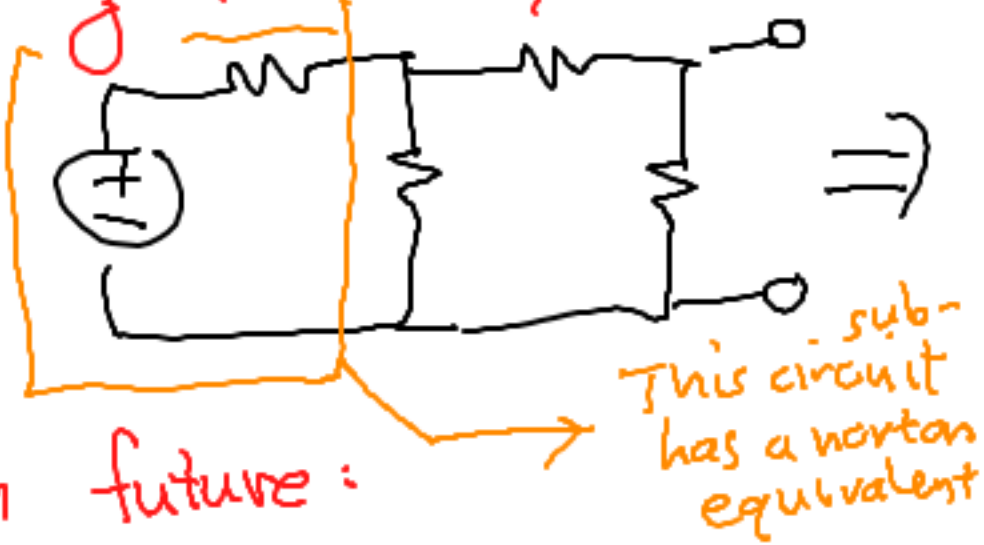

Thing to look for in future:

Example:

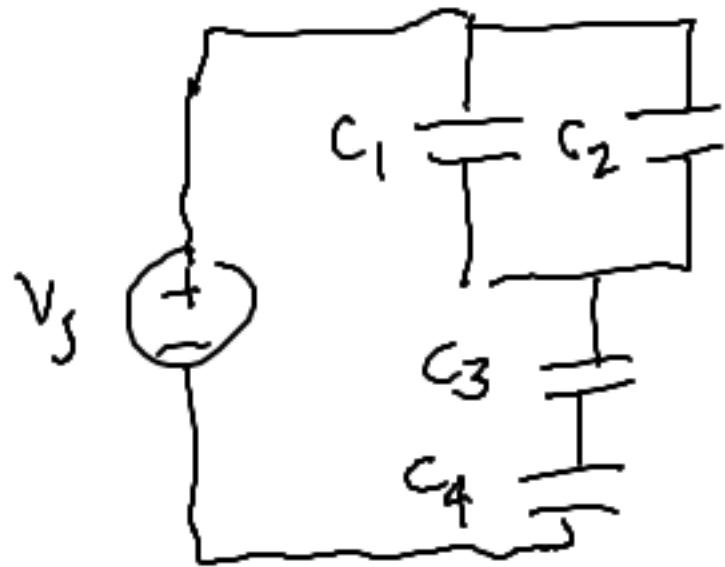

Calculate Q on C_1, C_2, C_3, C_4