

EECS16A DIS 4C

Topics for today

[1] Charge conservation and when and where it applies

(Definition of floating nodes)

[2] Charge sharing algorithm

(algorithm for analyzing voltages in a switch capacitor ckt)

Useful for analyzing switch capacitor ckt's

In circuits we have positive charges \oplus
negative charges \ominus

physics - can't destroy
- energy
- mass
- charge

Charge is only conserved when we have a closed system where it can't leave


↳ nodes from which charge can't leave

→ there are no conductive paths from this node to elsewhere

→ no resistors, no wires to other nodes

→ no batteries/voltages, no current sources

this is a Floating node
what is called a

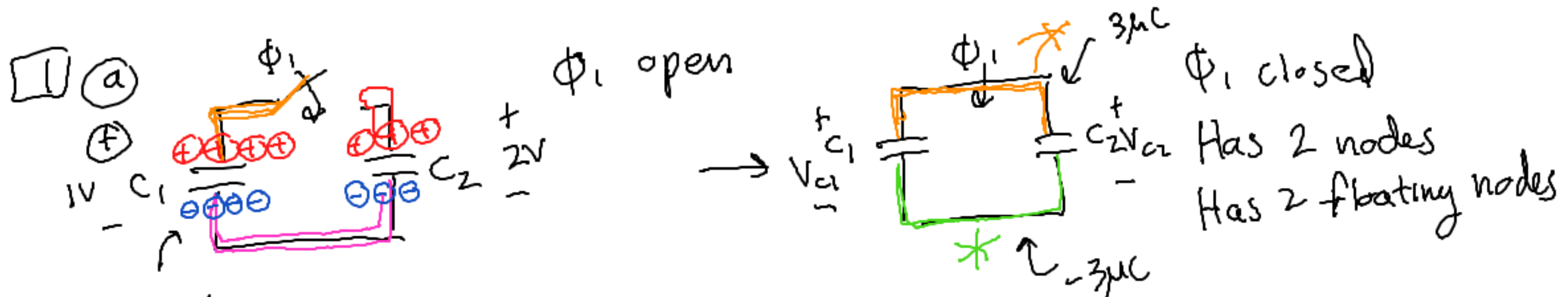

$C_1 = C_2 = 1 \mu F$

- Q: What is the charge on C_1, C_2
- Q: What nodes do we have before ϕ_1 closed?
3 nodes, they are floating nodes

$Q = CV$

$Q_1 = (1 \mu F)(1V) = 1 \mu C$

↳ Positive top left charge (+ + + +)
Negative bottom left charge (- - - -)
↳ $-1 \mu C$

$Q_2 = 1 \mu F \cdot 2V = 2 \mu C$
↳ Positive top right (+ + +)

⑥ When ϕ_1 closed
what is V_{C1} and V_{C2} ?
 $V_{C1} = V_{C2}$
 $Q_{top} = Q_1 + Q_2 = 3 \mu C$
 $Q_{bottom} = -(Q_1 + Q_2) = -3 \mu C$

What does Q_{top} } Q_{bottom} tell us about V_{c1} , V_{c2} and Q_1 } Q_2 (on each cap when the switch is closed?)

$$Q_{top} = 3 \mu C, \quad Q_{bot} = -3 \mu C$$



$$Q_1^{\phi_1} = C_1 V_{c1} = C_1 V$$

$$Q_2^{\phi_1} = C_2 V_{c2} = C_2 V$$




$$Q_{top} = Q_1^{\phi_1} + Q_2^{\phi_1}$$

$$3 \mu C = C_1 V + C_2 V \rightarrow$$

$$3 \mu C = (1 \mu F + 1 \mu F) V \Rightarrow V = \frac{3 \mu C}{2 \mu F} = \boxed{1.5 V}$$

$$Q_1^{\phi_1} = \underline{C_1} V = 1 \mu F \cdot 1.5 V = \boxed{1.5 \mu C}$$
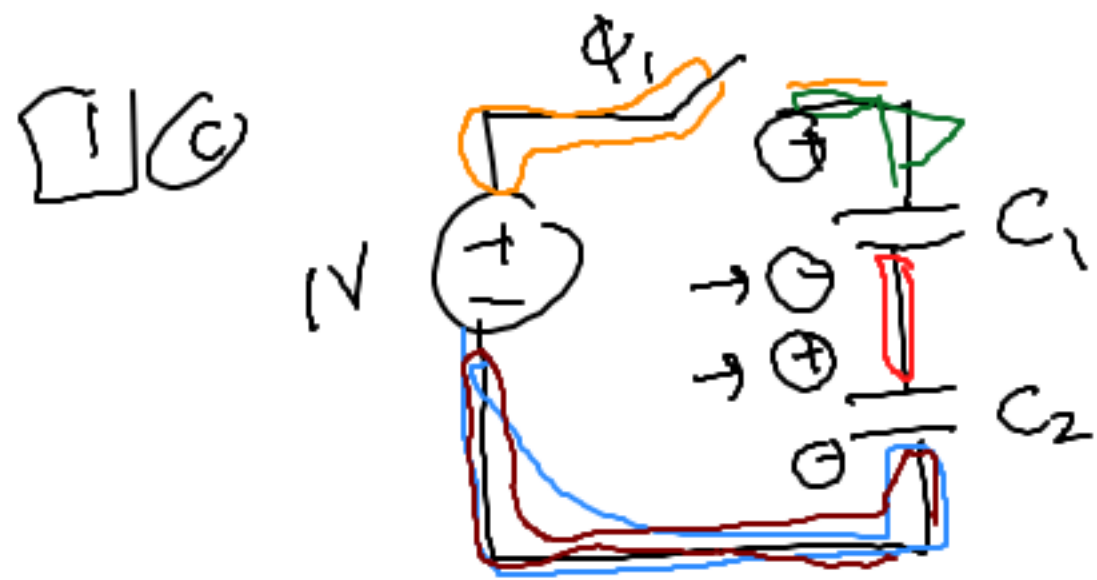
$$Q_2^{\phi_1} = \underline{C_2} V = 1 \mu F \cdot 1.5 V = \boxed{1.5 \mu C}$$




$$C_1 = 1 \mu F$$

$$C_2 = 3 \mu F$$

$$V_{C_1}(\phi_1 \text{ open}) = 0V \quad (\text{No charge on plates})$$


$$V_{C_2}(\phi_1 \text{ open}) = 0V \quad (\text{No charge on plates})$$

But when ϕ_1 closes

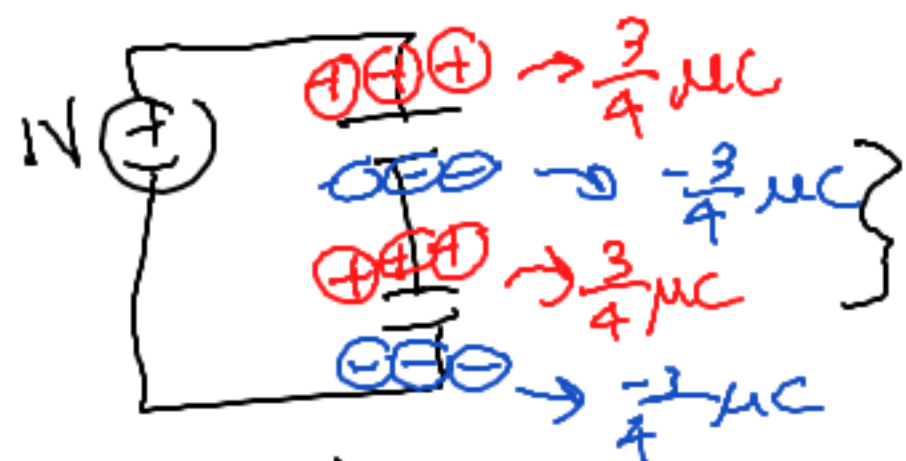

Q: Which are floating nodes? A: ● ● (also, 4 nodes total)

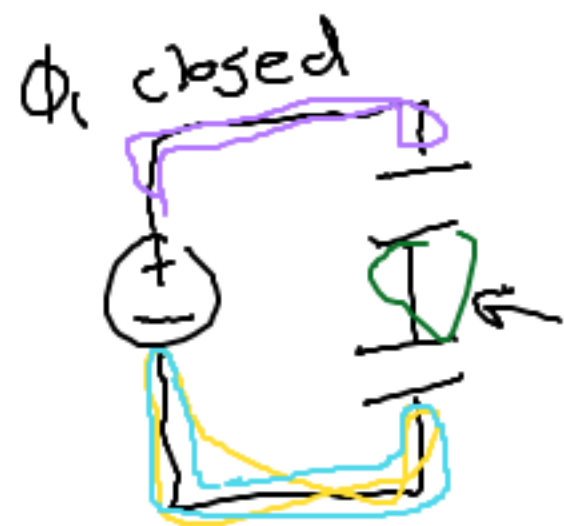Q: How much charge is on red node? 0nC
(charge is conserved here)



Q: Which are floating nodes? A: ●


→ 3 nodes ● ● ●

→ 1 floating node

Q: How much charge is on green node? 0nC
(charge is conserved here)

$$\left. \begin{matrix} 3 \mu C \\ - \frac{3}{4} \mu C \end{matrix} \right\}$$

2 Charge Sharing Algo.

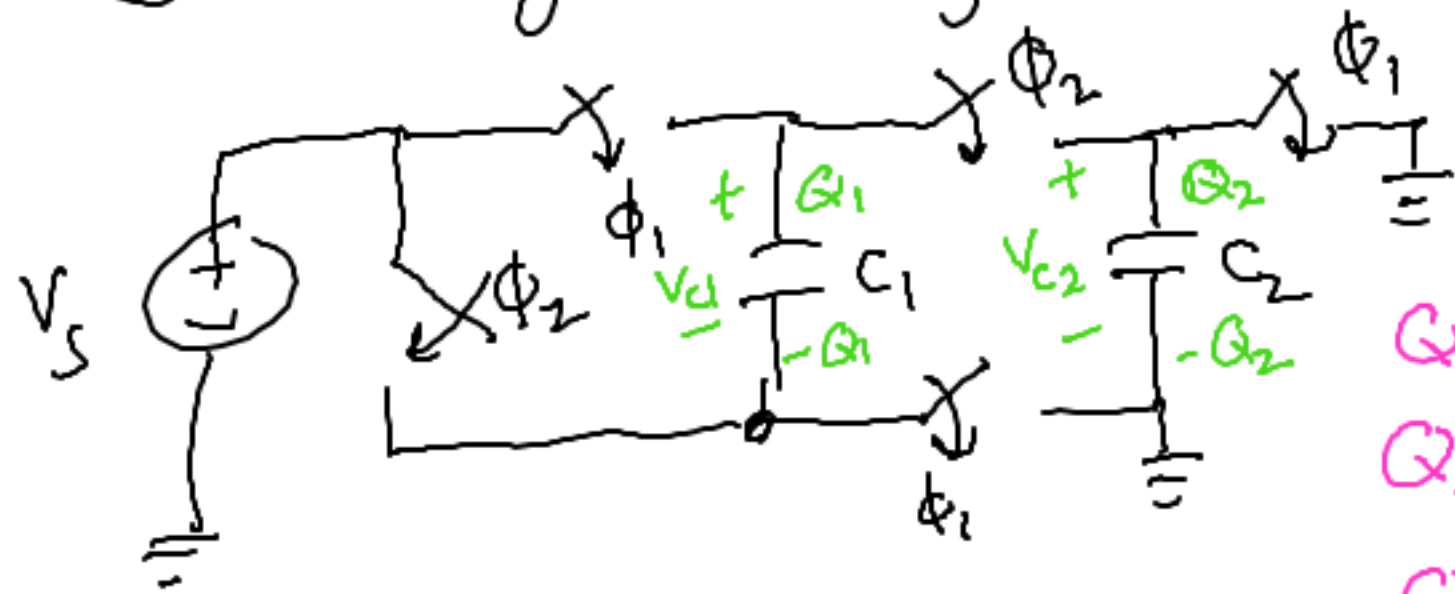

Q: Calculate all node voltages at the end of phase 2 as a function of V_s, C_1, C_2 (when ϕ_2 open)

Charge Sharing Algo.

- 1 Label voltages + charges in circuit
- 2 Draw equivalent circuits for each phase (label voltages + charges)
- 3 Identify floating nodes in second phase
- 4 Apply charge conservation at each floating node


$$Q_1^{\phi_1} = C_1 V_s$$

$$Q_2^{\phi_1} = C_2 \cdot 0$$


$$Q_1^{\phi_2} = C_1 (u - V_s)$$

$$Q_2^{\phi_2} = C_2 (u - 0)$$

When ϕ_1 switches are closed

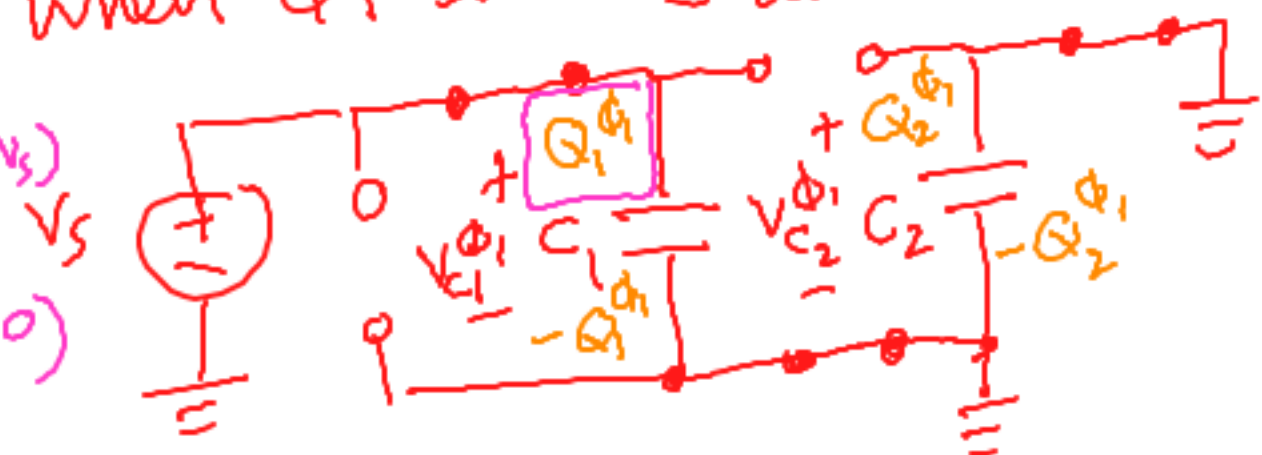

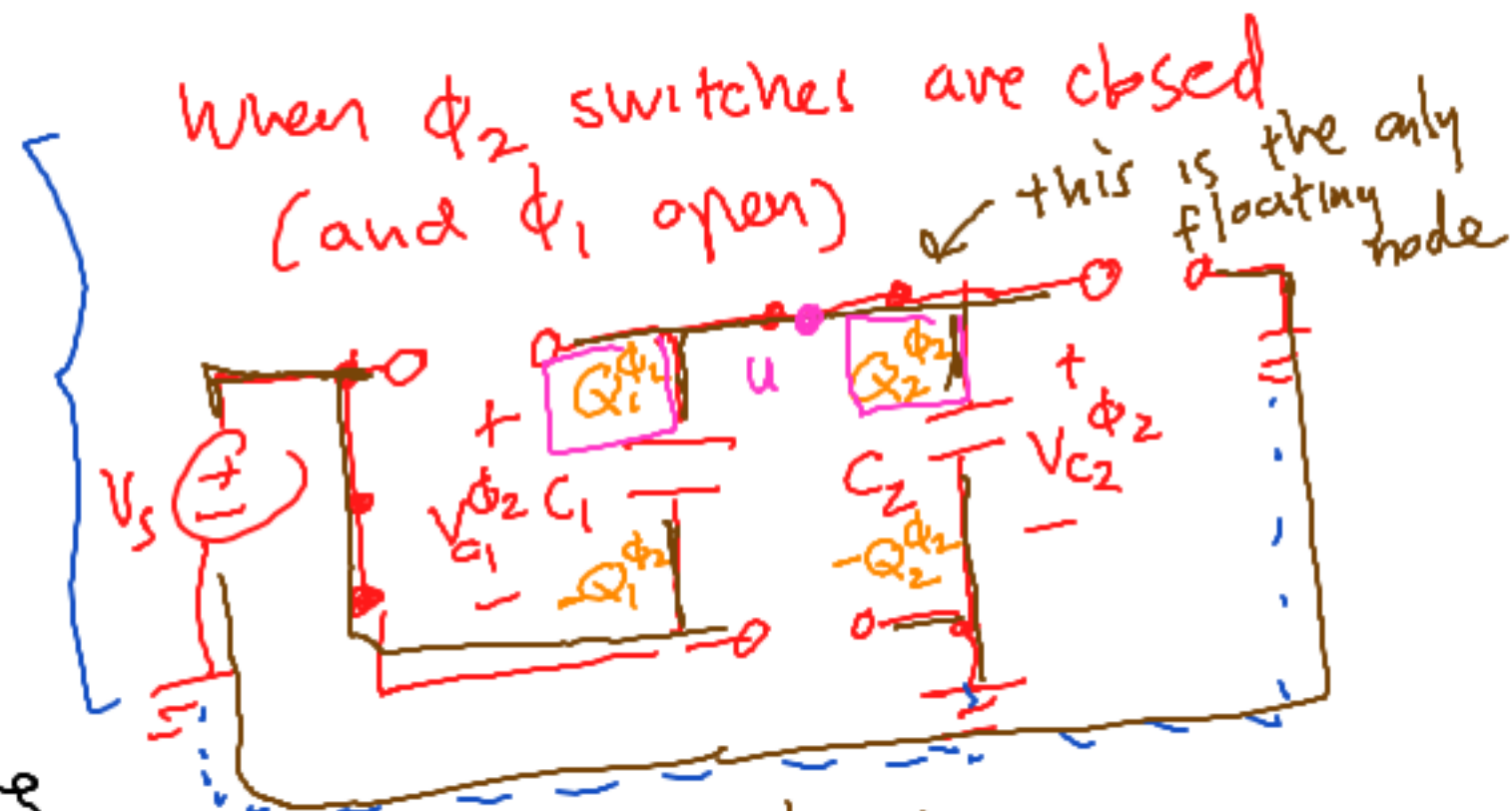When ϕ_2 switches are closed (and ϕ_1 open)



$$Q_1^{\phi_1} + Q_2^{\phi_1} = Q_1^{\phi_2} + Q_2^{\phi_2}$$

$$C_1 V_s + 0 = C_1 (u - V_s) + C_2 u \rightarrow \text{solve for } u = \frac{2C_1}{C_1 + C_2} V_s$$

3 nodes in brown