

EECS16A DIS4D

* Don't forget: Discussion checkoff form today (#10)


Today's topics

- 1] Op amps: What are they and what do they do?
- 2] Introduction to the inverting amplifier (and also, buffer)


Op. amp: Operational Amplifier
Mathematical operations circuit element that amplifies voltages & currents

- • Addition and subtraction of voltages
- Integration & differentiation " "
- • Multiply a voltage by a constant (amplification when multiplier > 1)
- • Linear combination of voltages
- Multiplication of voltages (nonlinear)
↳ out of scope / not in focus

Symbol

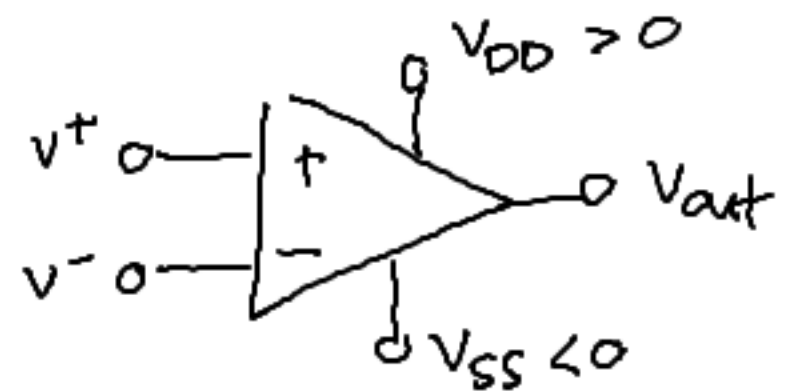

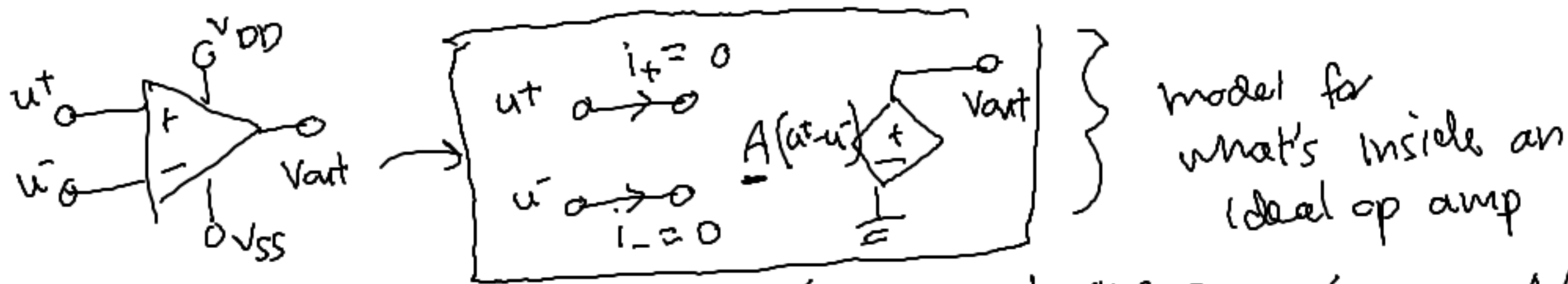$V_{DD} \neq V_{SS}$ are sources / power supplies



1) G.R. #1: Currents going into $+/-$ terminals are zero

2) G.R. #2: $V^+ = V^-$ if NFB, $A = \infty$ (ideal)

(Def) Gain: the scaling factor of an input voltage (quantity) to an output voltage (quantity)

output voltage $\rightarrow V_{out} = A(u^+ - u^-) \leftarrow$ "input voltage"
 \uparrow gain of an op amp (without FB)

$A_v \leftarrow$ gain of an op amp clt w/ FB

$$V_{out} = A(u^+ - u^-)$$

$$A = \infty$$


$V_{out} = V_{DD} \geq 0$
 if the value of $A(u^+ - u^-)$ is too high

$V_{out} = V_{SS} \leq 0$
 if the value of $A(u^+ - u^-)$ is too low

In DIS 3C: Saw that sticking two voltage dividers together did not behave how we wanted (loading)


Loading: the phenomenon where a voltage in a circuit changes due to connecting another clt on its output

$\sim 4.5\text{mA}$

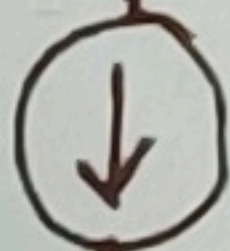

Current divider demo from DIS3B with current divider implemented with "magic element"

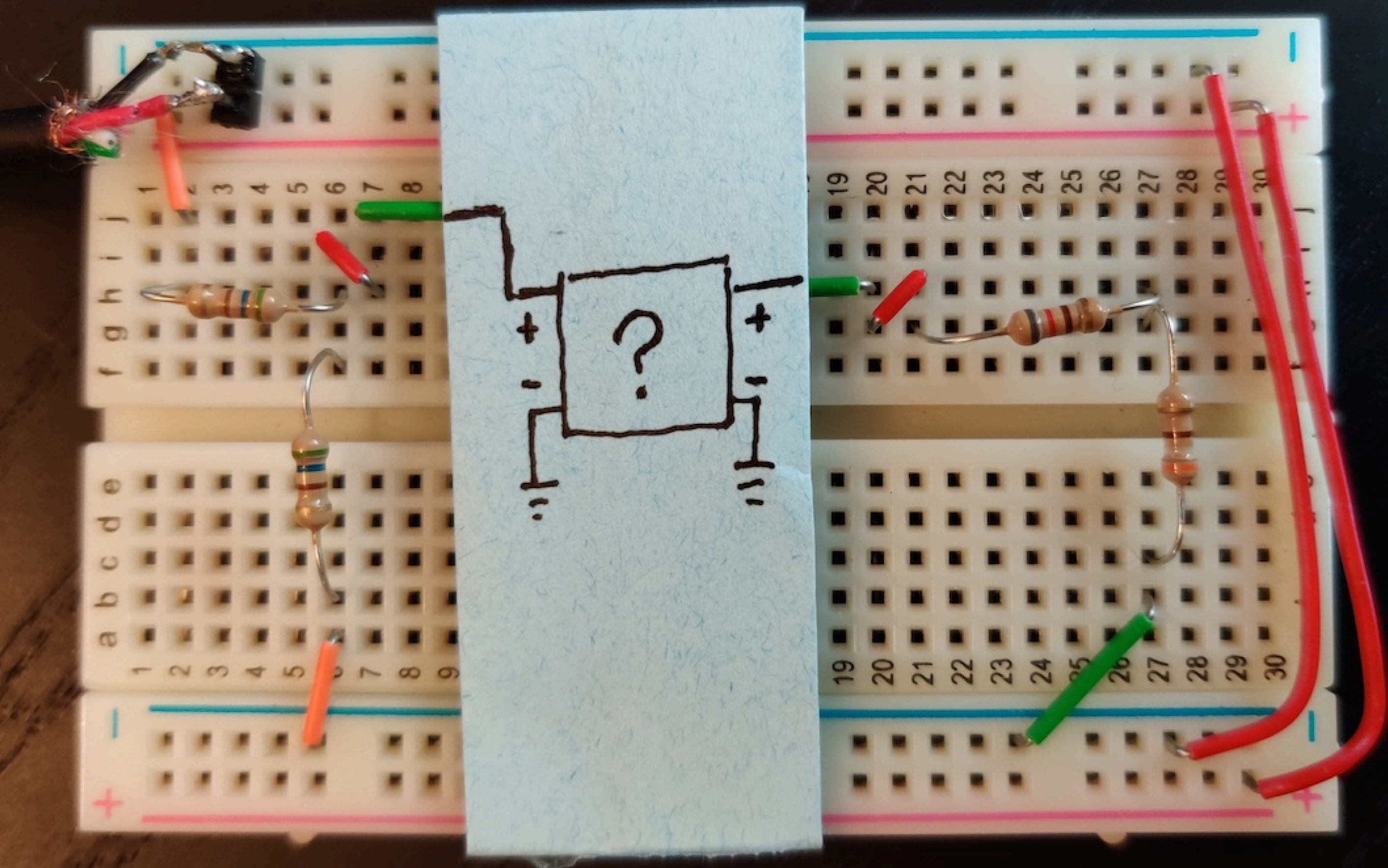
Circuit from DIS3C Extra Demo with “magic element”



Benefit of op amps (magically)

- Solves loading problem (DIS 3C Q2)
- Build a current source

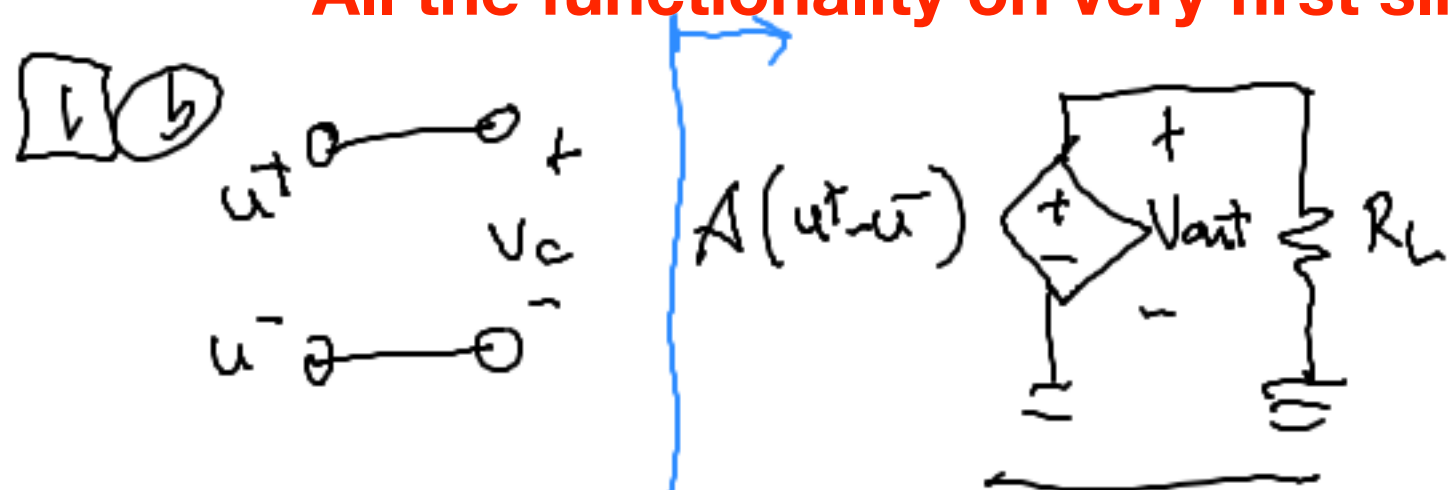***All the functionality on very first slide**




$V_{out} = ?$
 $\equiv AV_c$
 $= A(u^+ - u^-)$

$R_L = 100 \Omega$ $R_L = 10k \Omega$

$V_{out} = AV_c$ $V_{out} = AV_c$

why the same? : R_L is in parallel w/ AV_c ,

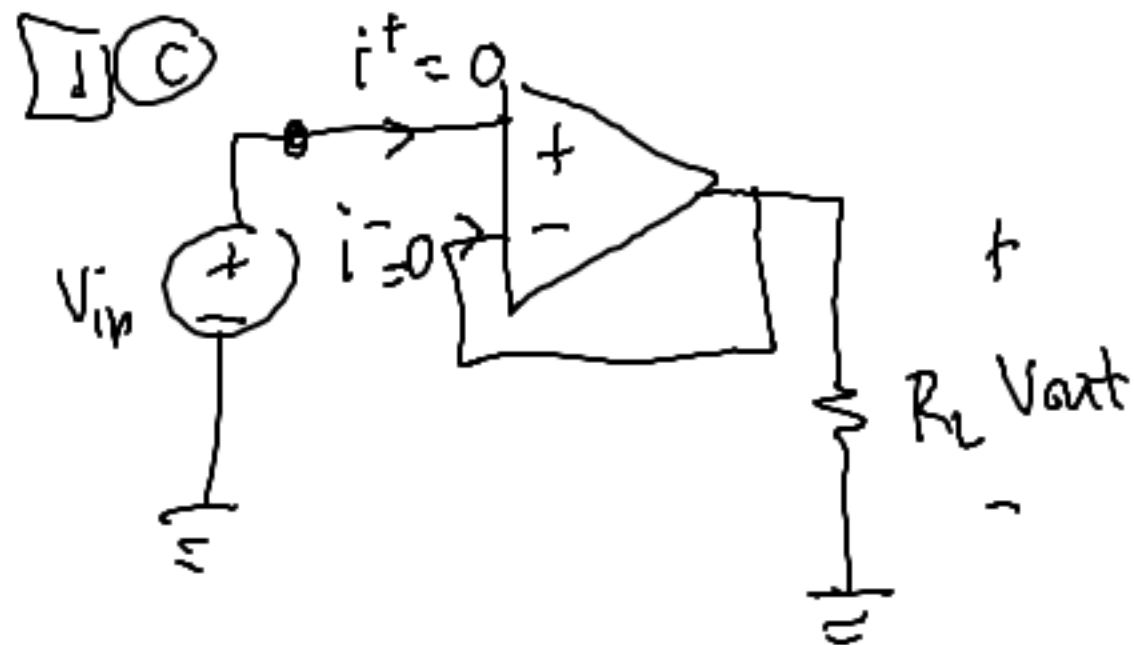$V_{out} = AV_c$ only dependent on u^+, u^-



Let's apply GR


1) $i^+ = i^- = 0$

$[u^+ = V_{in}] \rightarrow$ Not a GR

2) If NFB, $u^+ = u^-$. Check \checkmark

Check NFB

2a) Turn off sources

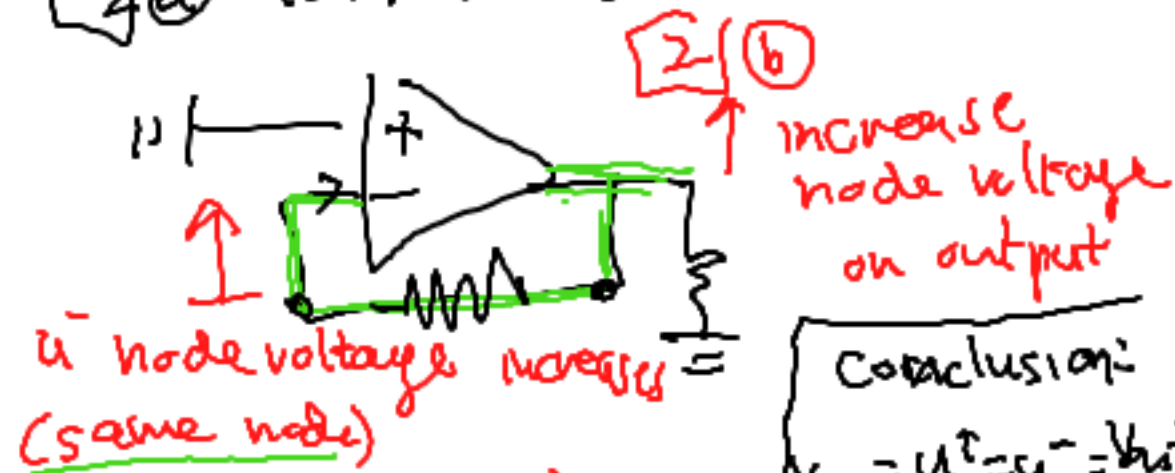

u^- node voltage increases = (same node)

$V_{out} = A(u^+ - u^-)$
 \downarrow dec \uparrow inc.

Conclusion:
 $V_{in} = u^+ = u^- = V_{out}$



This circuit takes V_{in} and makes $V_{out} = V_{in}$

Unity gain buffer

"1" $A_v =$ multiplier for feedback


$$V_{out} = A_v V_{in}$$

$$\frac{V_{out}}{V_{in}} = A_v = 1$$

Memorize the block above


↳ thing that goes in between circuits helps connect/moderate

Q: Is $V_{in} = u^+ - u^-$. no Why?

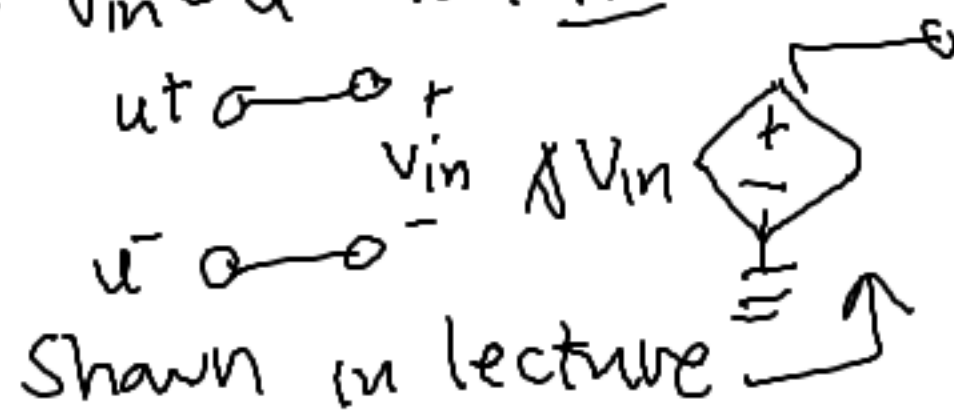

V_{in} here refers to source on (+) terminal

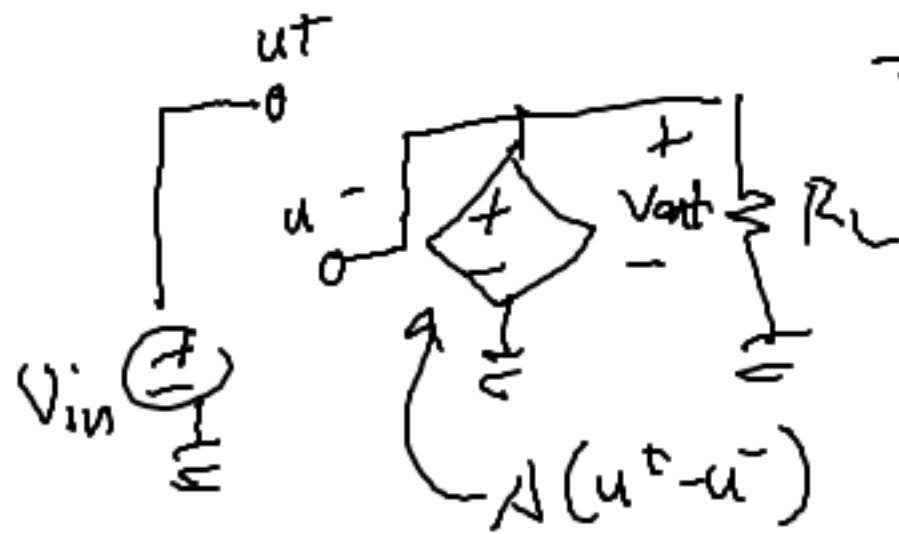1 d In ideal case R_L does not make V_{out} change.



$$\rightarrow V_{out} = A(u^+ - u^-)$$


$$V_{out} = A(V_{in} - V_{out})$$

$$V_{out} + AV_{out} = AV_{in}$$

$$V_{out} = \frac{A}{1+A} V_{in}$$

$$A \rightarrow \infty \quad V_{out} = V_{in}$$

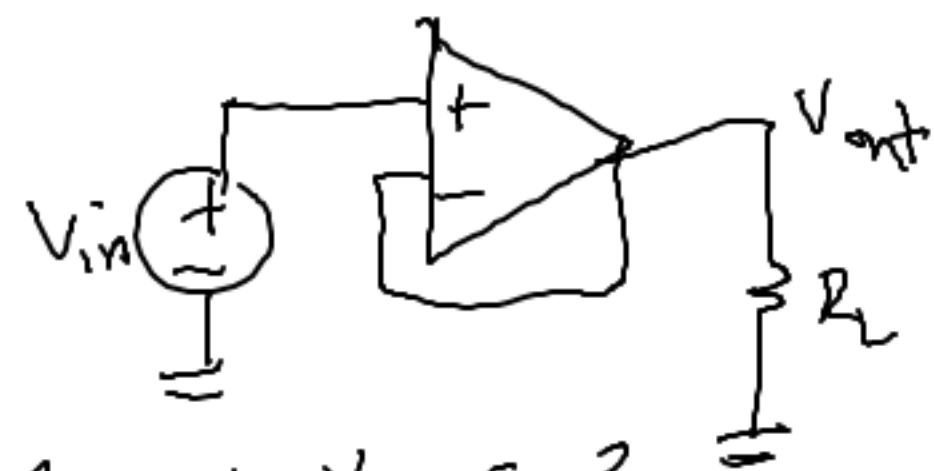When A is not infinite R_L still doesn't affect V_{out}



Q: What's I_{R_L} ?
When $A = \infty$

$$V_{out} = V_{in}$$

$$I_{R_L} = \frac{V_{out}}{R_L} \neq 0$$

When $A \neq \infty$

$$V_{out} = \frac{A}{1+A} V_{in}$$

$$I_{R_L} = \frac{V_{out}}{R_L} \neq 0$$


[2] Inverting Amplifier

Derive V_{out} as a function of V_{in} (Use NVA)



Don't choose to write KCL @ output bc

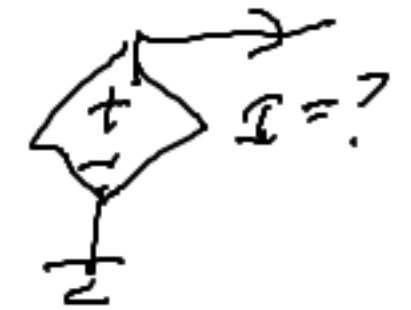(a) u^- KCL: $I_1 = i^- + I_2$
 $I_1 = I_2$ (GR#1)



Why 0?
 $u^- = u^+ \rightarrow 0 - V_{in} = \frac{V_{out} - 0}{R_2}$
 $= 0V$
 NFB (GR#2)

$$V_{out} = -\frac{R_2}{R_1} V_{in}$$

$A_v = -\frac{R_2}{R_1}$ (negative)
 ↪ gain w/ FB


Extra Notes / Questions

URL for circuit sim of inverting amplifier: tinyurl.com/y45fb625

Q: Does the unity gain buffer use an ideal op amp?
↳ We'll assume op amps are ideal in this course, so yes.

Q: Are A_v and A different?
↳ Yes. A_v - gain $\left(\frac{V_{out}}{V_{in}}\right)$ with feedback (determined by circuit around op amp)
 A - gain $\left(\frac{V_{out}}{V_{in}}\right)$ without feedback (intrinsic to op amp)

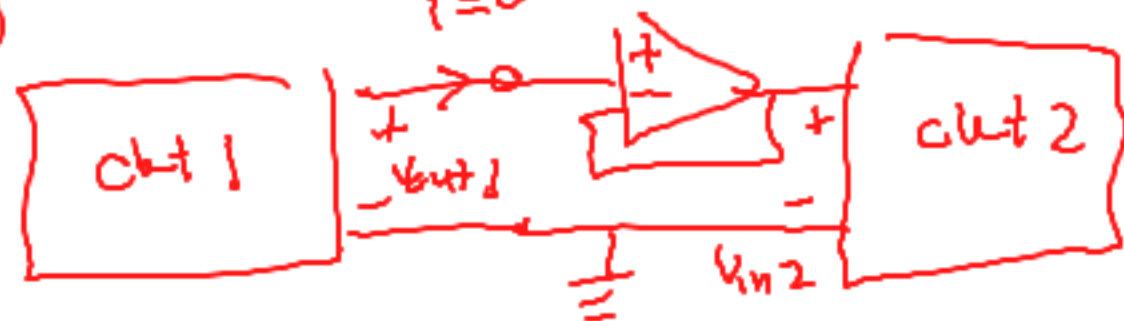Q: What's the purpose of the unity gain buffer?
↳ Prevents loading, let's us connect circuit 1 to circuit 2 without affecting circuit 1. $i = 0$



$$V_{out1} = V_{in2}$$