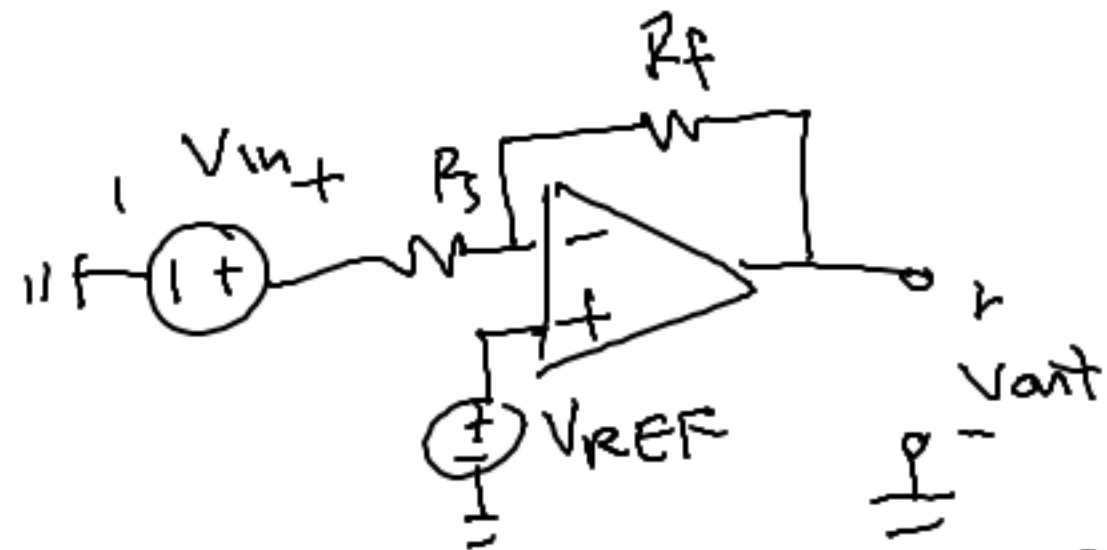


EECS16A DIS 5A

Topics for today

- ① Some reference designs/topologies
- ② How to combine circuits and deal with loading



$$V_{out} = V_{in} \left(-\frac{R_F}{R_S} \right) + V_{REF} \left(\frac{R_F}{R_S} + 1 \right)$$

Choose $\frac{R_F}{R_S}$. Do we get to

choose the coefficients separately?

$$\frac{R_F}{R_S} = 3$$

$5V_{ref}$?


No, we can't
can't do
 $\sim 10V_{in} + 2V_{ref}$

Not possible

Term: (circuit) topology:
refers to a specific
circuit

Ex: (inverting op amp)
topology

voltage summer


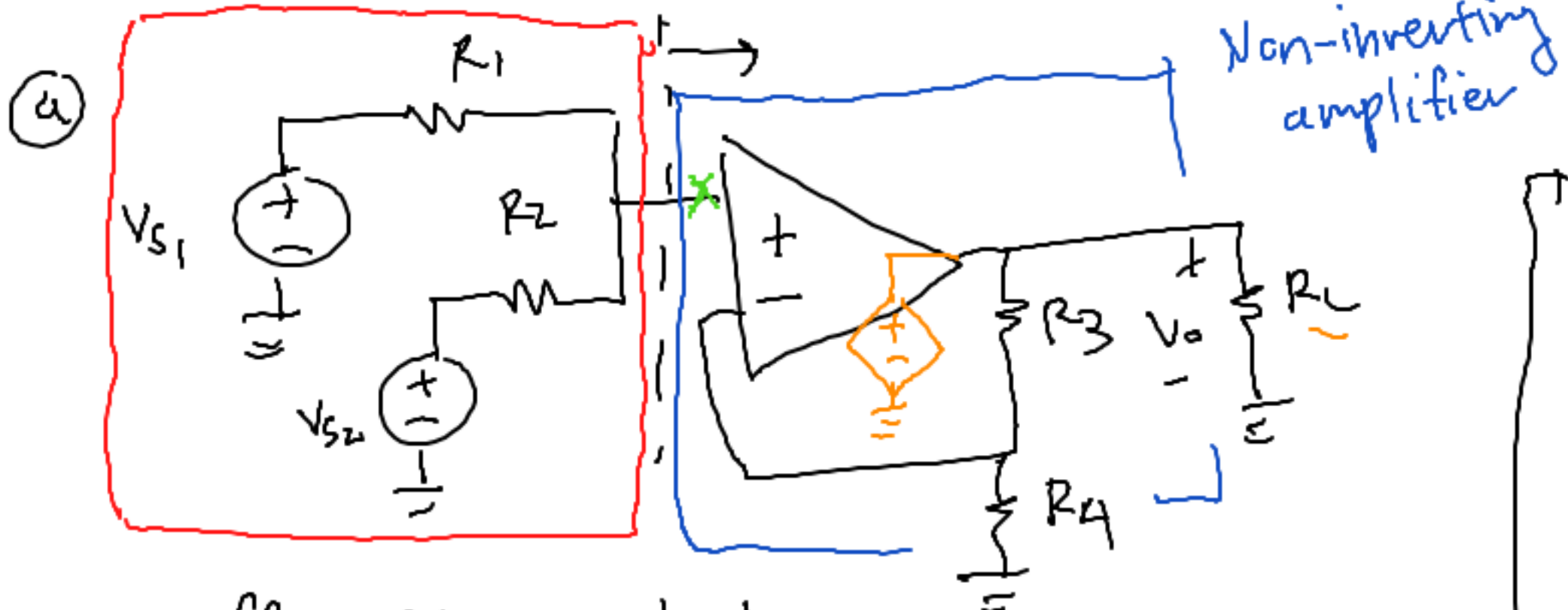


$$U^+ = \frac{R_2}{R_1 + R_2} V_{S1} + \frac{R_1}{R_1 + R_2} V_{S2}$$

Looks like voltage summer equations

Turn off a source, check for how it influences a quantity

Look at u_+

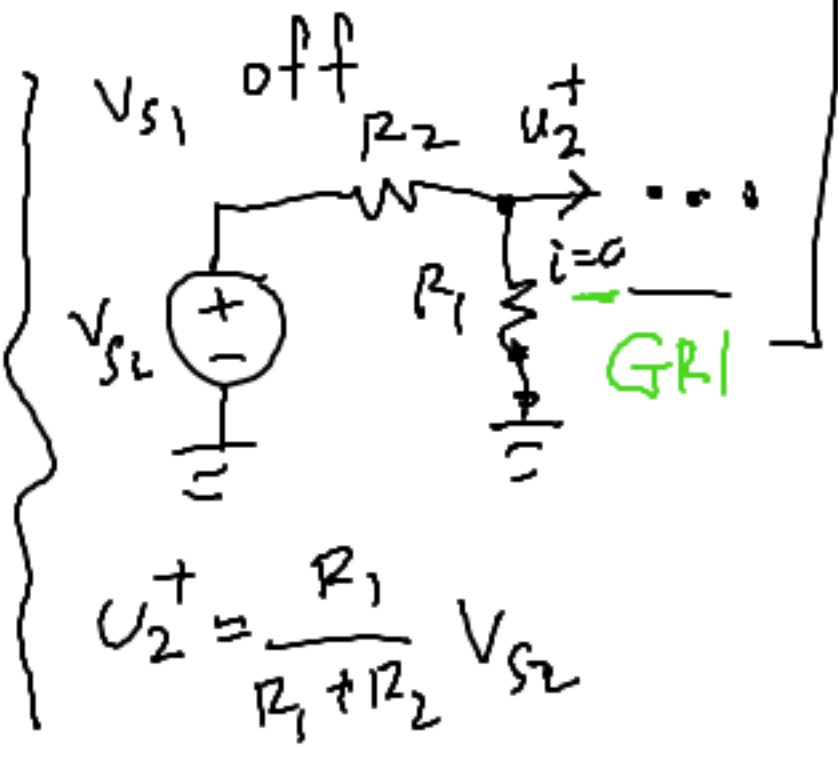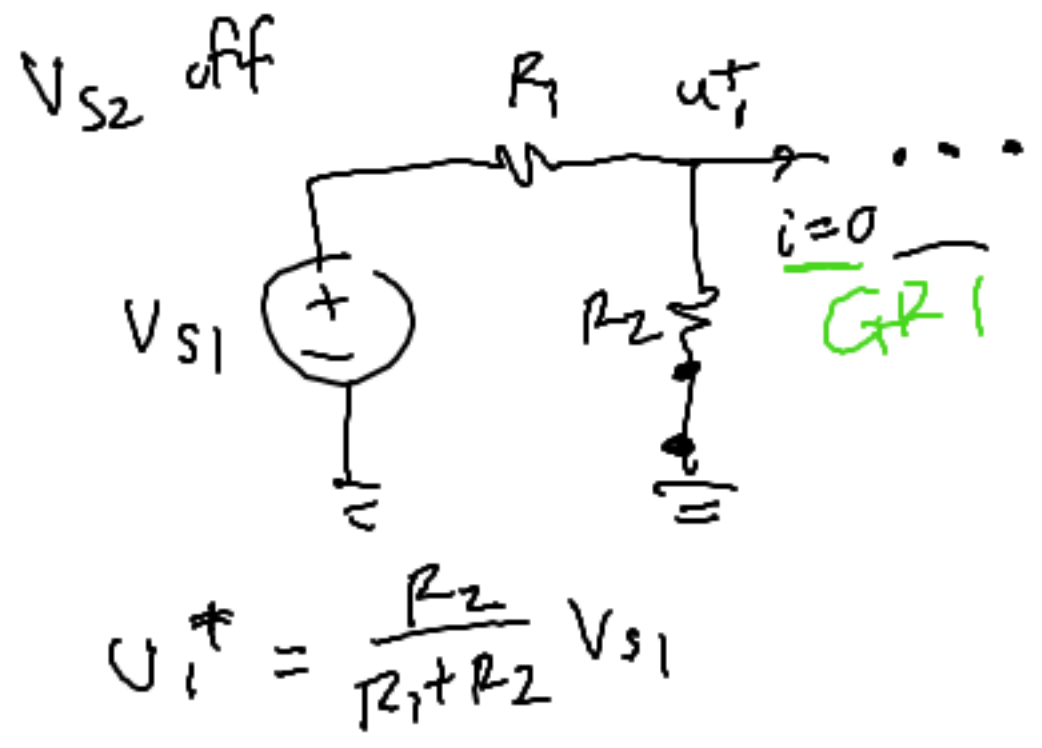

$$V_{out} = V_{in} \left(1 + \frac{R_{top}}{R_{bot}} \right)$$

? ?

$$V_{in} = U^+$$

$$R_{top} = R_3$$

$$R_{bot} = R_4$$

$$V_{out} = V_o$$

$$V_o = \left(\frac{R_2}{R_1 + R_2} V_{S1} + \frac{R_1}{R_1 + R_2} V_{S2} \right) \left(1 + \frac{R_3}{R_4} \right)$$

Does R_L influence things? **No**

Does R_1, R_2 matter for the input? **No**

(no loading)

⑥ Say that V_{s1} and V_{s2} capture data/information (numbers)

$$V_o = \left(\frac{R_2}{R_1 + R_2} V_{s1} + \frac{R_1}{R_1 + R_2} V_{s2} \right) \left(1 + \frac{R_3}{R_4} \right) \approx \text{non inverting amp}$$

can only have multiplier ≥ 1

$$\approx V_{s1} + V_{s2} ?$$

Voltage summer

$$\left\{ \begin{array}{l} \alpha V_{s1} + (1-\alpha) V_{s2} \\ \frac{1}{2} V_{s1} + \frac{1}{2} V_{s2} \\ 2 \cdot \frac{1}{2} (V_{s1} + V_{s2}) \end{array} \right.$$

Can we choose α to get $\alpha = 1$
 $1 - \alpha = 1$?

$$\alpha = (1 - \alpha)$$

$$\Rightarrow \alpha = \frac{1}{2}$$


$$\Rightarrow \boxed{R_1 = R_2 = R_3 = R_4}$$

$$\frac{R_2}{R_1 + R_2} = \frac{1}{2}$$


$$\frac{R_1}{R_1 + R_2} = \frac{1}{2}$$

$$\left(1 + \frac{R_3}{R_4} \right) = 1 + 1 = 2$$


2

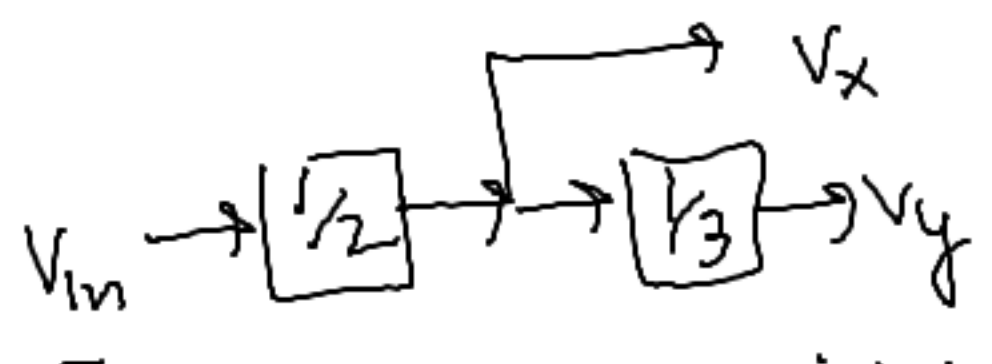


Tried two voltage dividers

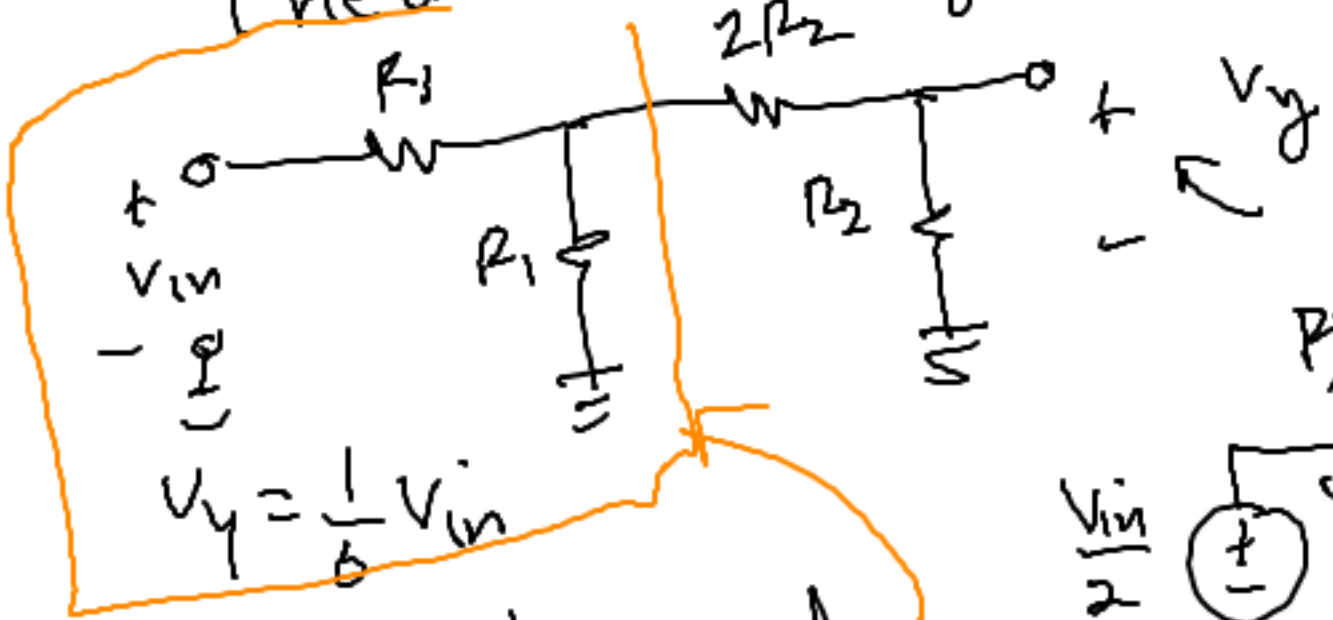

Loading happened

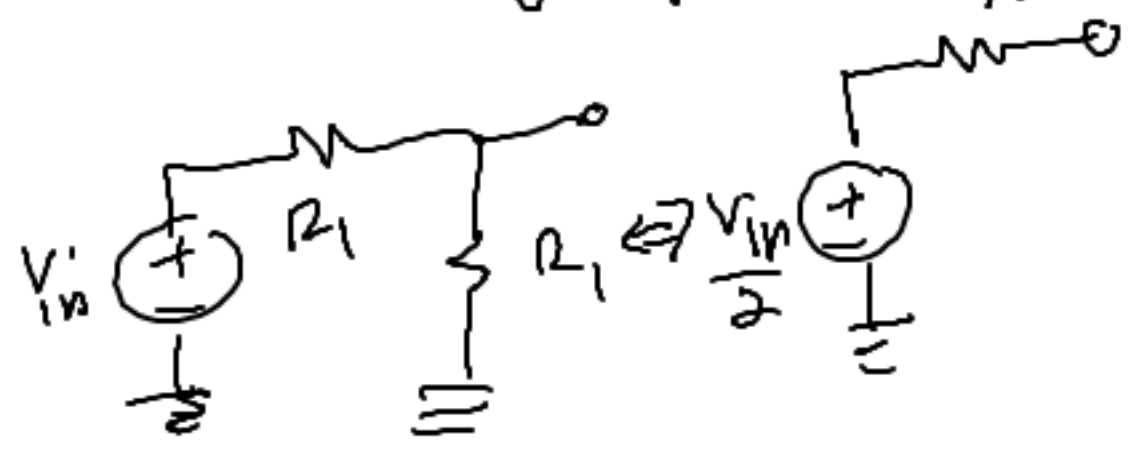

$R_1/2$ is causing the issue

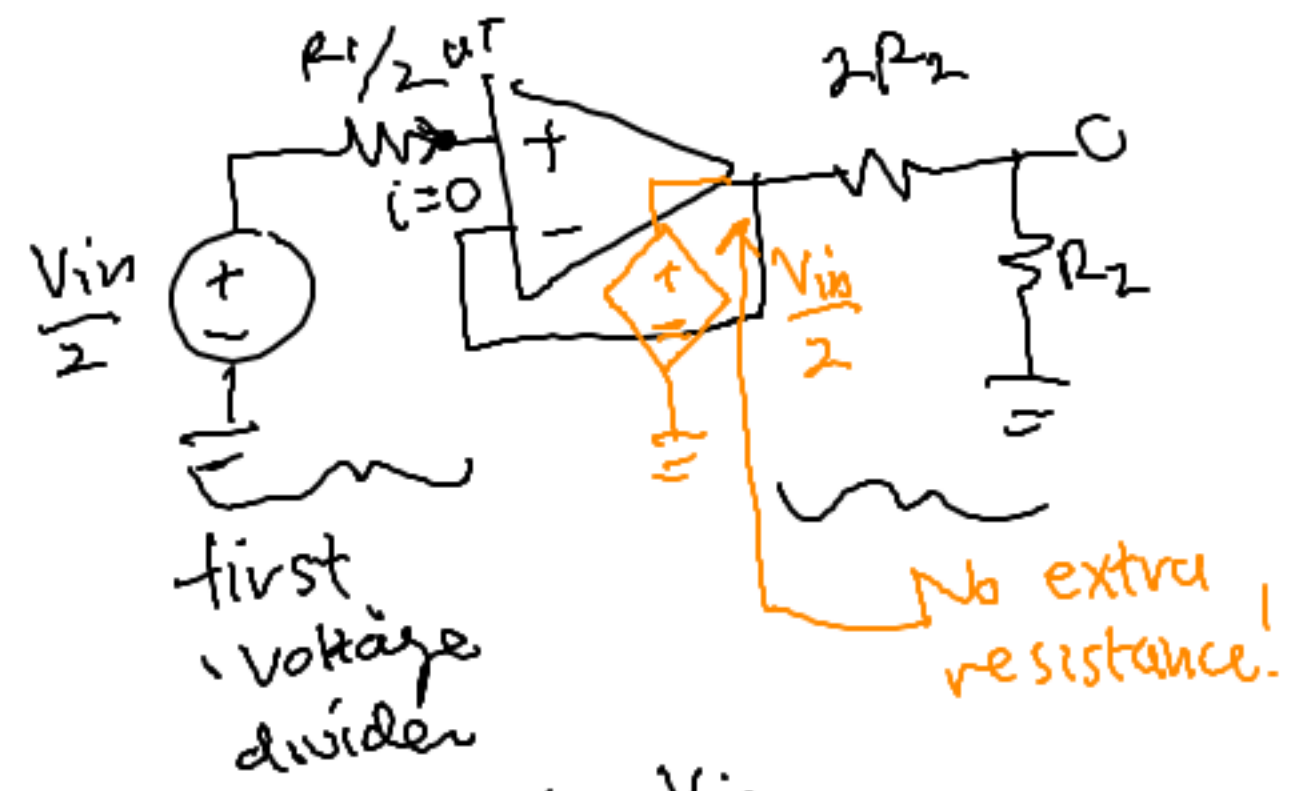


first voltage divider

$$U^+ = \frac{V_{in}}{2}$$

$$G \approx 2 \Rightarrow U^- = U^+ = \frac{V_{in}}{2}$$

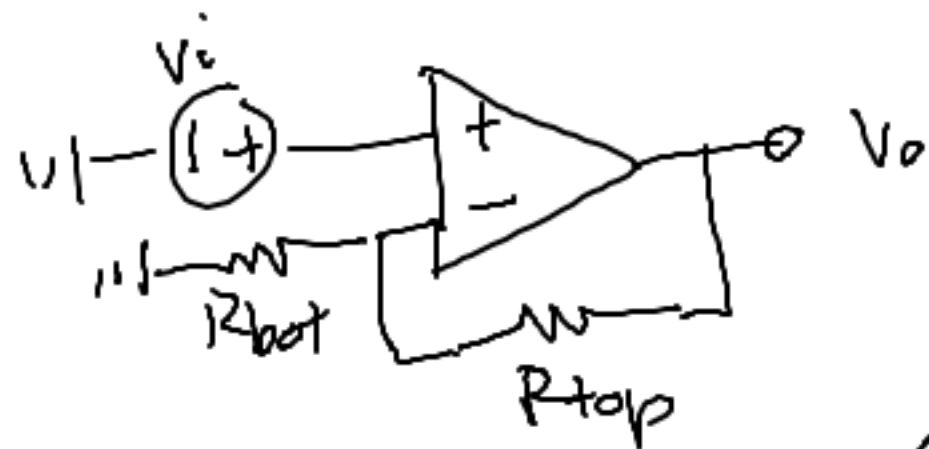(i) How to get $V_o = 5V_i$
 Non-inverting amp
 $R_{top} = 4R$, $R_{bot} = R$ (x2)



$$V_o = \left(1 + \frac{R_{top}}{R_{bot}}\right) V_i = \left(1 + \frac{4R}{R}\right) V_i = 5V_i \checkmark$$

(ii) $V_o = -2V_i$
 Inverting amp (x4)
 $R_f = 2R$, $R_s = R$
 $R_f = 2k\Omega$, $R_s = 1k\Omega$
 $R_f = 4$, $R_s = 2$
 $\frac{R_f}{R_i} = 2$




$$V_o = -\frac{R_f}{R_s} V_i$$

$$-\frac{2R}{R} V_i = -2V_i \checkmark$$

$$-\frac{2k\Omega}{1k\Omega} V_i = -2V_i$$

Inverting amp:

$$I = \frac{V_{in} - 0}{R_s} \neq 0$$

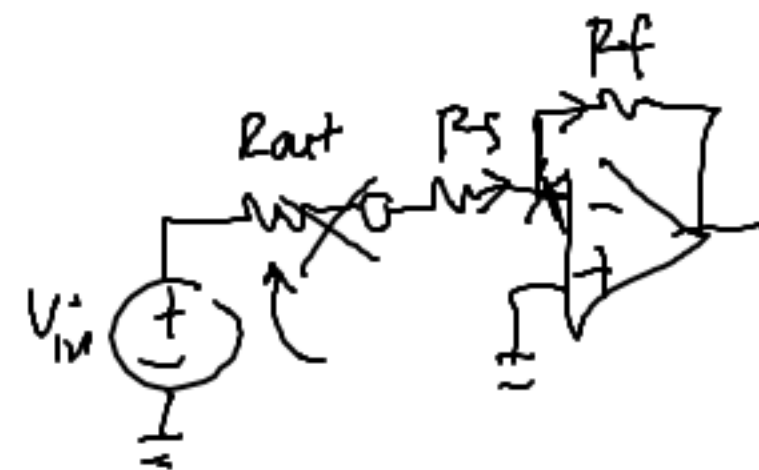

Inverting amp behaves like it has a resistance on the input \rightarrow it can load because of

(ii)


Implement $V_o = V_{i1} + V_{i2}$

→ Voltage summer (2x)


→ [Need more?]

→ Op amp?

→ Use I (a) / (b)

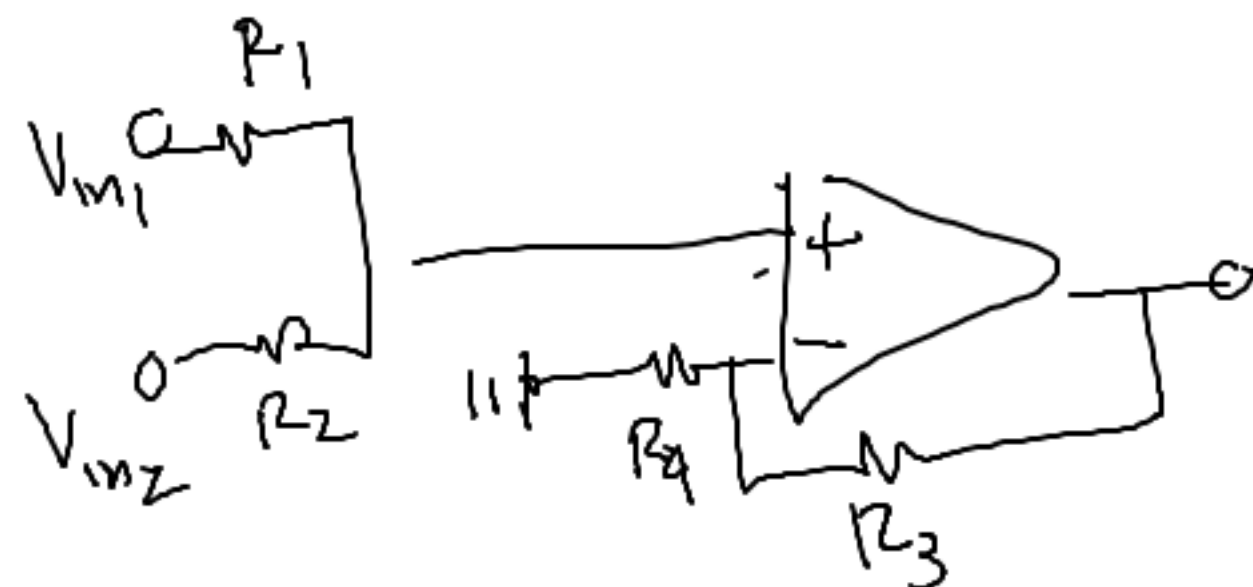

$$R_1 = R_2 = R_3 = R_4$$

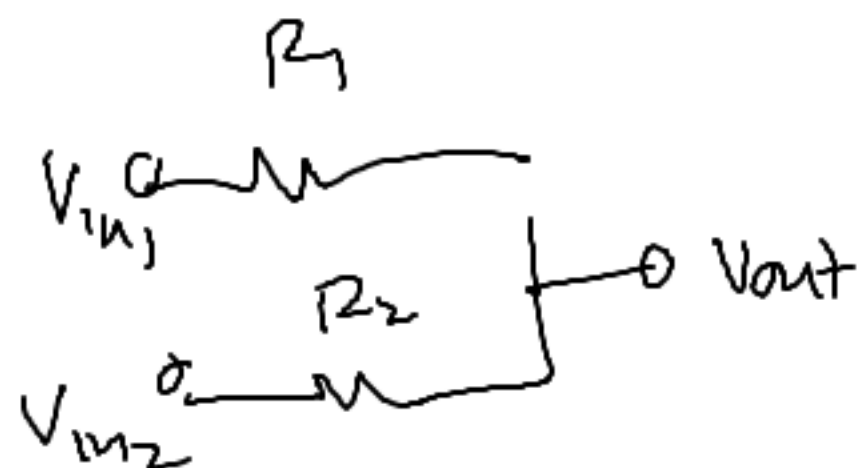

Need an amplifier to scale
things back up non-inverting
amp

$$V_{out} = \underbrace{\left(\frac{R_2}{R_1 + R_2} \right)}_{< 1} V_{i1} + \underbrace{\left(\frac{R_1}{R_1 + R_2} \right)}_{< 1} V_{i2}$$