

DIS 63 In depth example of a design problem

Design? What is it \rightarrow Choosing/a circuit to accomplish a goal
making

goal/behavior \rightarrow ckt.


Analysis: ckt \rightarrow behavior (volts/currents)

- ① Understand behavior/goal we want to achieve
- ② Formulate this as block diagrams/math
- ③ Think about limitations and constraints
- ④ Choose circuits and modify them

Noise cancelling headphones

- 1 (a) → How to get music signal to headphones
- 1 (b) → How to also add noise cancelling on top

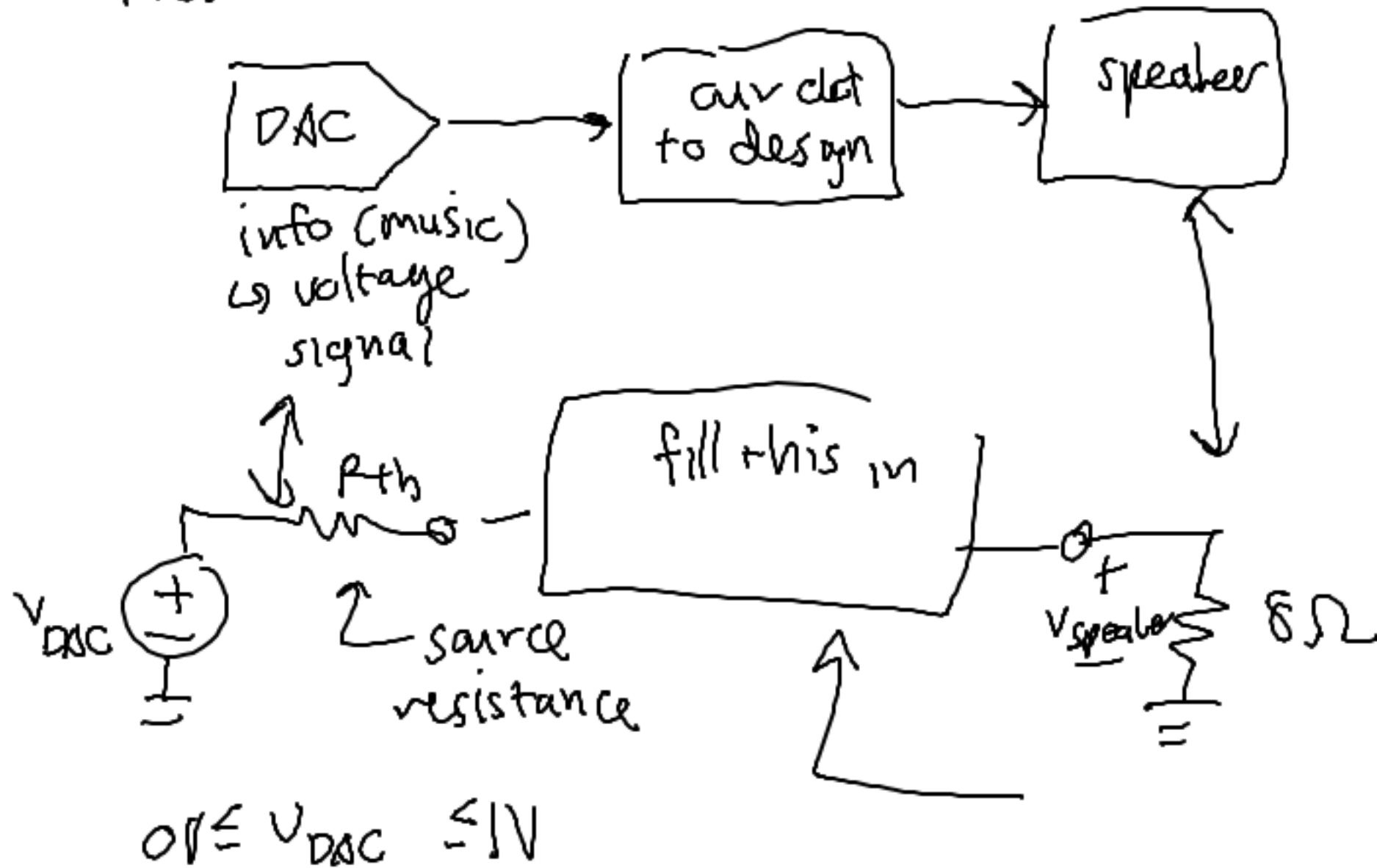Source resistance?
Thévenin model of a dkt



Goals

$$-1.5V \leq V_{speaker} \leq 1.5V$$


What do we have?

- Op amps (∞)
- Voltage sources ($-1.5V$ to $1.5V$)
- Resistors (∞)

$$0V \leq V_{DAC} \leq 1V \rightarrow \text{centered @ } \frac{1}{2}V$$

$$-1.5V \leq V_{\text{speaker}} \leq 1.5V \rightarrow \text{centered @ } 0V$$



max/min are source voltages



$$-\frac{1}{2}V \leq V_{DAC} - \frac{1}{2}V \leq \frac{1}{2}V$$

$$-\frac{3}{2}V \leq 3(V_{DAC} - \frac{1}{2}V) \leq \frac{3}{2}V$$
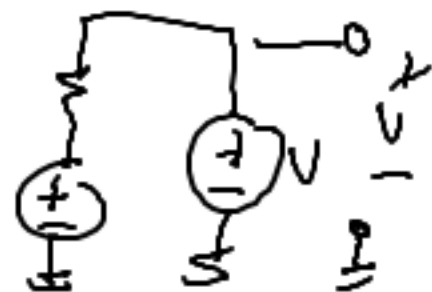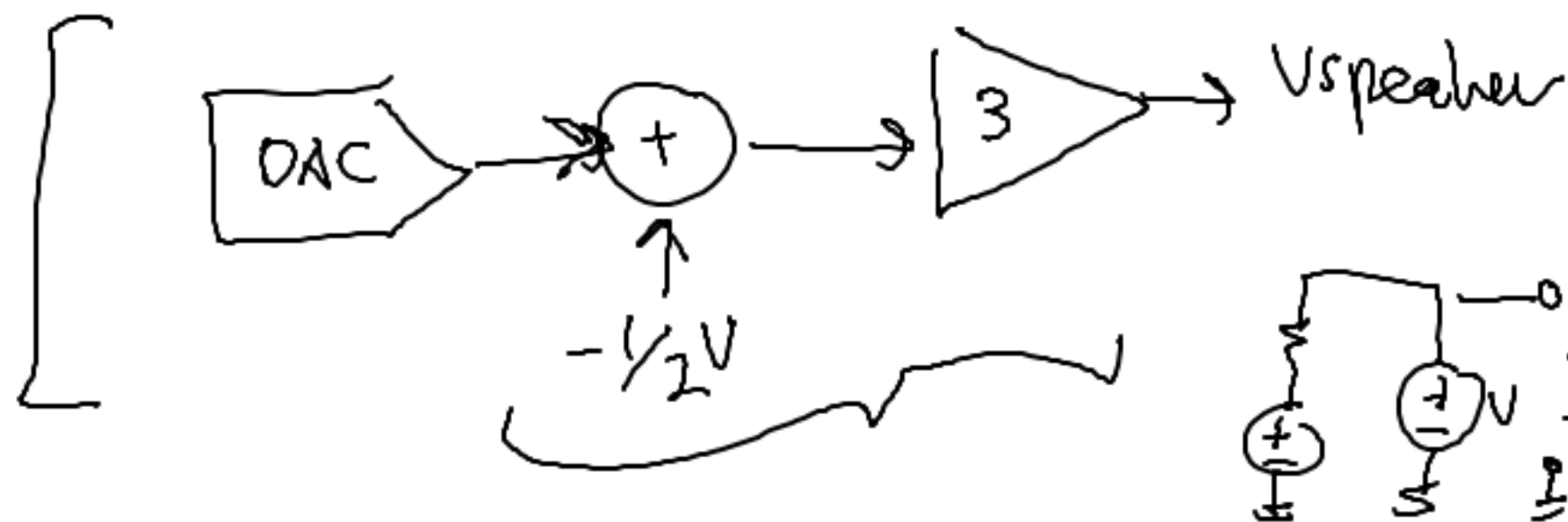
$$V_{\text{speaker}} = 3(V_{DAC} - \frac{1}{2}V)$$



Can't make R_1 or $R_2 = 0$ if we want it to be useful

- ① "Do the math"
- ② Make a block diagram
- ③ Cuts for each block

Candidates for $-\frac{1}{2}V$ shift

- op amp
- tran resistance \times current + volt.
- non invert amp limitation
- voltage summer

$$\frac{R_2}{R_1 + R_2} = 1?$$

$$\textcircled{1} \quad 3(V_{DAC} - \frac{1}{2}V) \iff \textcircled{2} \quad 3V_{DAC} - \frac{3}{2}V$$

Implement $\textcircled{1}$ or $\textcircled{2}$

Design 1

- subtract $\frac{1}{2}V$
- mult. by 3

Design 2


- Multiply by 3 \leftarrow
- subtract $\frac{3}{2}$

Not feasible

Why?: Can't output higher than 1.5V

$$0V \leq V_{DAC} \leq 1V$$

$$0V \leq 3V_{DAC} \leq \underline{3V}$$

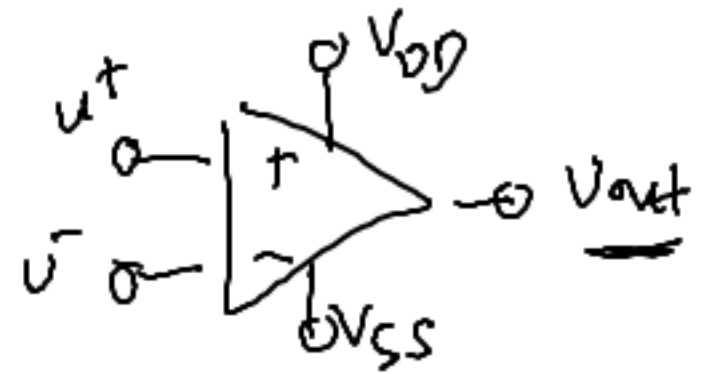

$$V_{DD} = 1.5V, \quad V_{SS} = -1.5V$$



$$V_{out} = \underbrace{\left(\frac{R_2}{R_1 + R_2}\right)}_{\alpha} V_1 + \underbrace{\left(\frac{R_1}{R_1 + R_2}\right)}_{(1-\alpha)} V_2$$

$$0 < \alpha < 1$$





$$0 = \frac{1}{2}\alpha - \frac{3}{2} + \frac{3}{2}\alpha$$

$$\frac{3}{2} = 2\alpha \Rightarrow \alpha = \frac{3}{4}$$

$$-\frac{1}{2} \leq V_{DAC} - \frac{1}{2}V \leq \frac{1}{2}$$

$$V_1 = V_{DAC}$$

$R_{th} = 50 \Omega$ (source resistance)

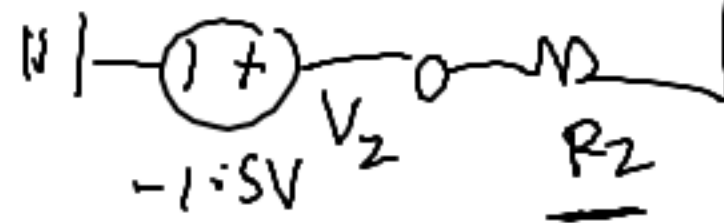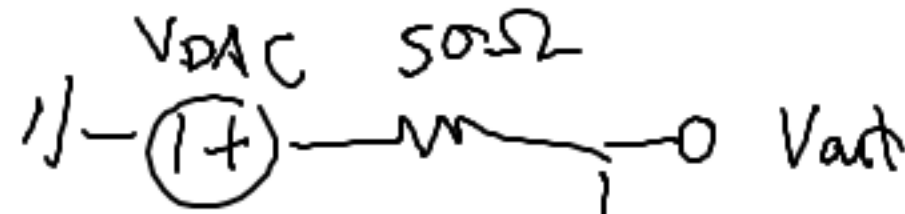

Make $V_2 = -1.5V$

Subgoal: Find R_2 to center voltage



$$V_{out} = V_{DAC} \alpha + \left(-\frac{3}{2}V\right)(1-\alpha)$$

want to center @ zero to not damage speaker

output $V_{out} = 0V$ when $V_{DAC} = \frac{1}{2}V$

$\rightarrow \frac{1}{2}V$ is the middle of V_{DAC} 's range
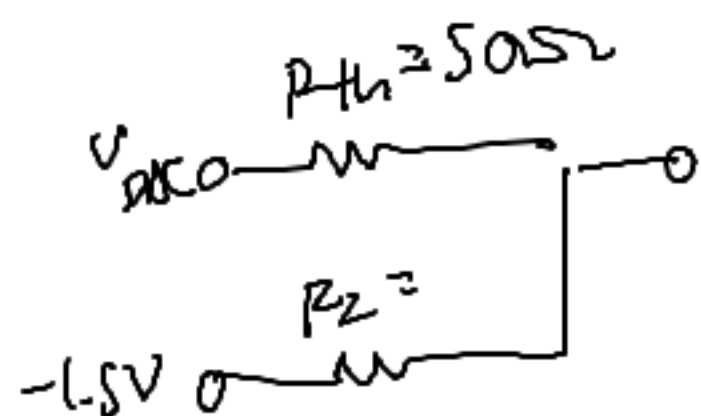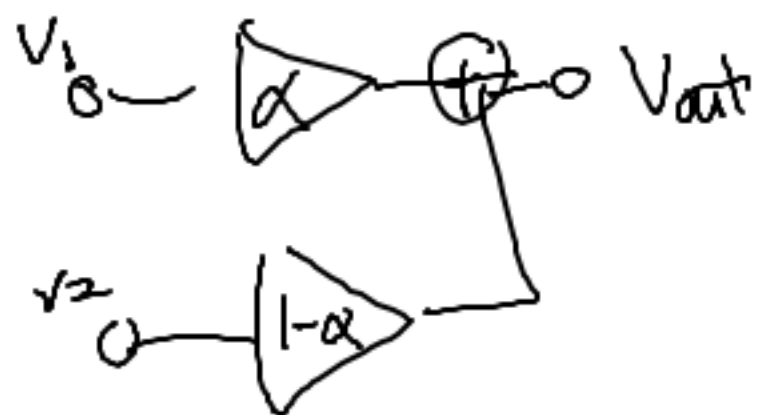
$$0V = \frac{1}{2}V \alpha + \left(-\frac{3}{2}V\right)(1-\alpha) \Rightarrow \underline{\alpha = \frac{3}{4}}$$



$$\alpha = \frac{3}{4}$$

$$\frac{3}{4} = \alpha = \frac{R_2}{R_2 + R_{th}} = \frac{R_2}{R_2 + 50\Omega}$$

$$\boxed{R_2 = 150\Omega}$$

$$\frac{150\Omega}{200\Omega} = \frac{3}{4} V$$



$$- \frac{1}{2} V \leq V_{DAC} - \frac{1}{2} \leq \frac{1}{2} V$$

$$\hookrightarrow - ? \leq V_{out} \leq ?$$

$$V_{DAC} = 1V \quad V_{out} = \alpha V_{DAC} + (1-\alpha)(-1.5V)$$

$$= \frac{1.5V}{4} = \underline{\underline{\frac{3}{8} V}}$$



$$V_{DAC} = 0V \quad V_{out} = \frac{3}{4} \cdot 0V + \frac{1}{4}(-1.5V)$$

$$= \underline{\underline{-\frac{3}{8} V}}$$

X Amplify by 3. ($\frac{1}{2} \rightarrow \frac{3}{2}$)

\Rightarrow Amplify by 4 ($\frac{3}{8} \rightarrow \frac{3}{2}$)


Amplify by 4

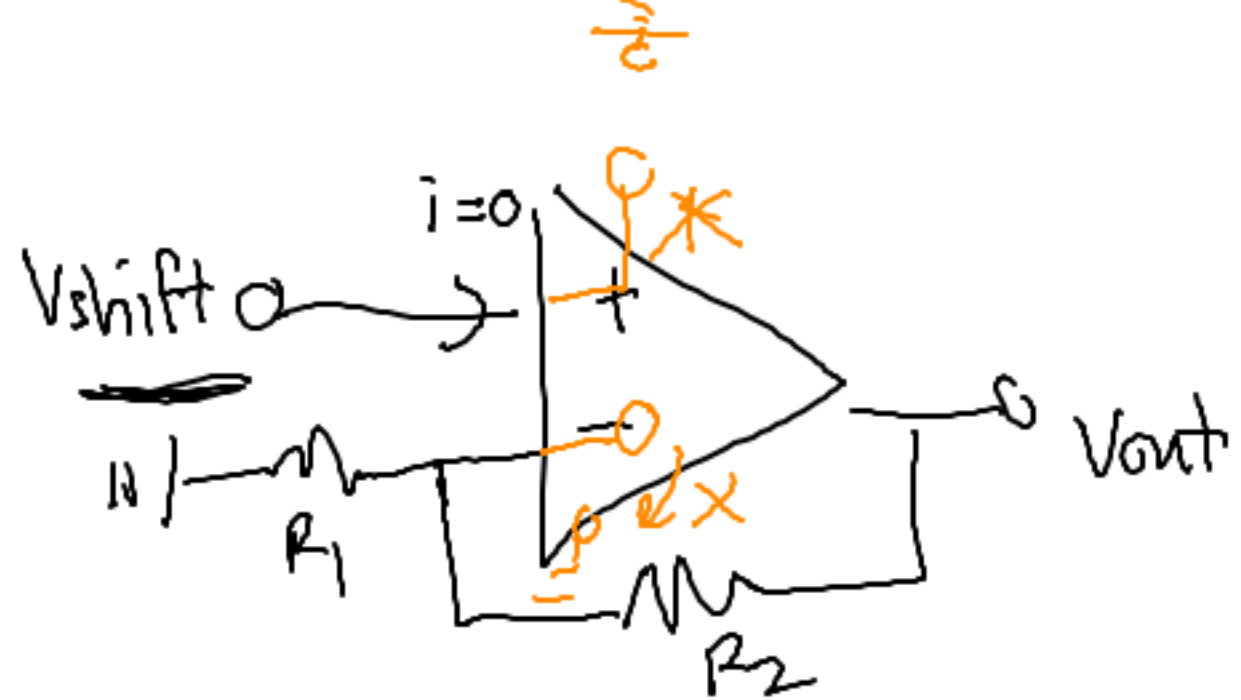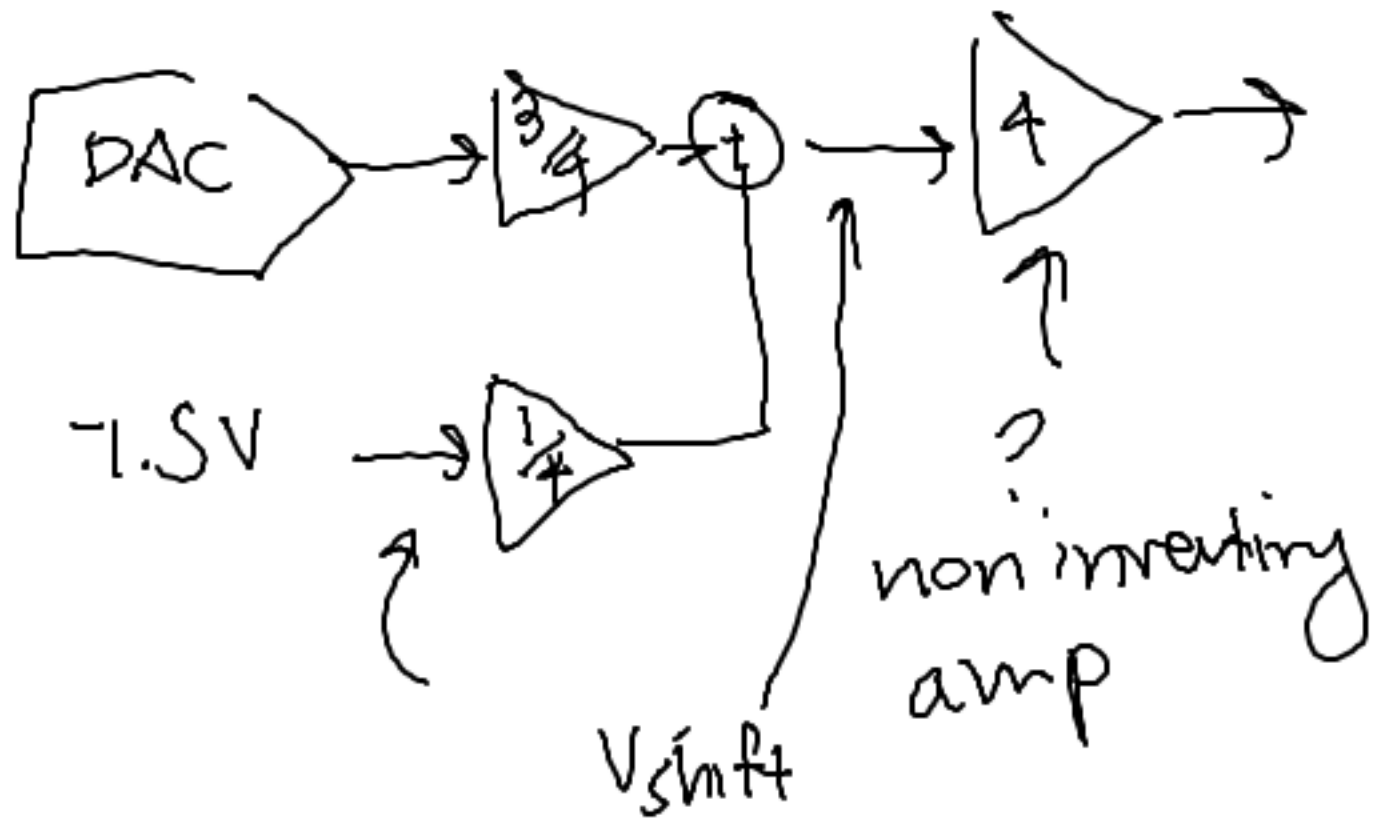


$$V_{out} = \underbrace{\left(1 + \frac{R_2}{R_1}\right)}_4 V_{shift}$$

Choose $R_2 = 3R_1$ $\left. \begin{array}{l} R_1 = 1k\Omega \\ R_2 = 3k\Omega \end{array} \right\}$

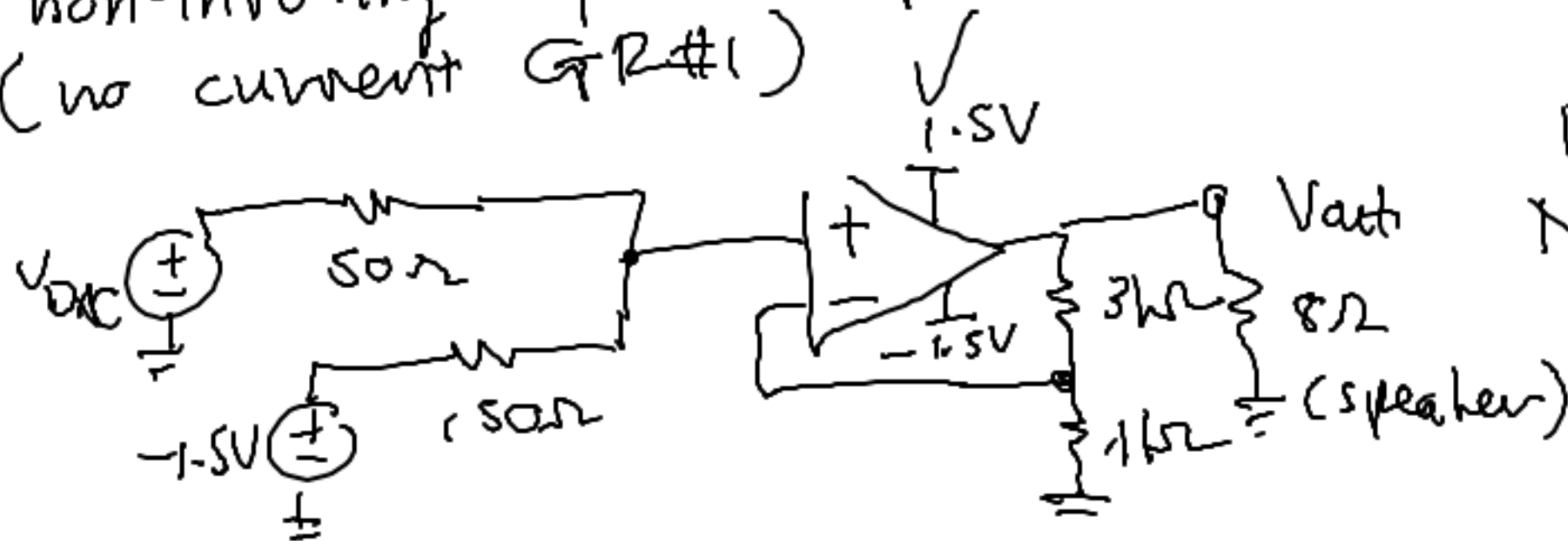No loading: + input terminal of non-inverting amp is an open (no current through R_1)



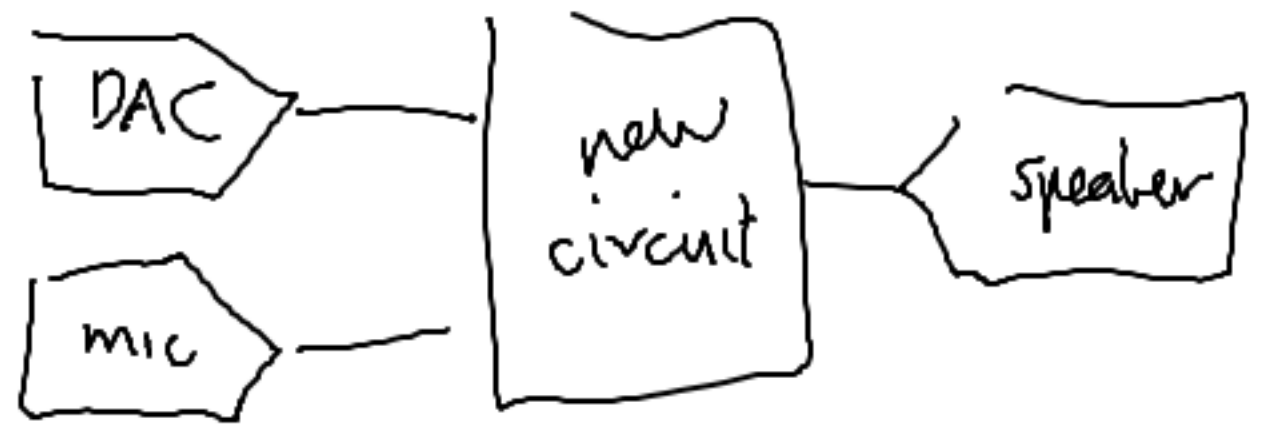Design done
No issues from source limitations




mic - outside signal

Designs goal



heard = music + cancel + outside

⇒ want, cancel = -outside

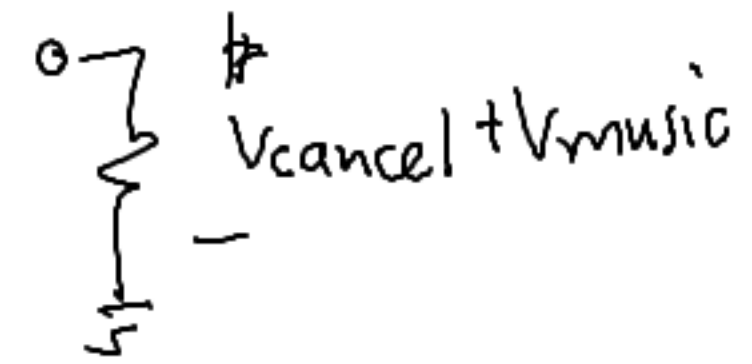


$$0 \leq V_{mic} \leq 1$$

$$-\frac{1}{8}V \leq V_{cancel} \leq \frac{1}{8}V$$

$$-\frac{1}{2} \leq V_{mic} - \frac{1}{2}V \leq \frac{1}{2}$$
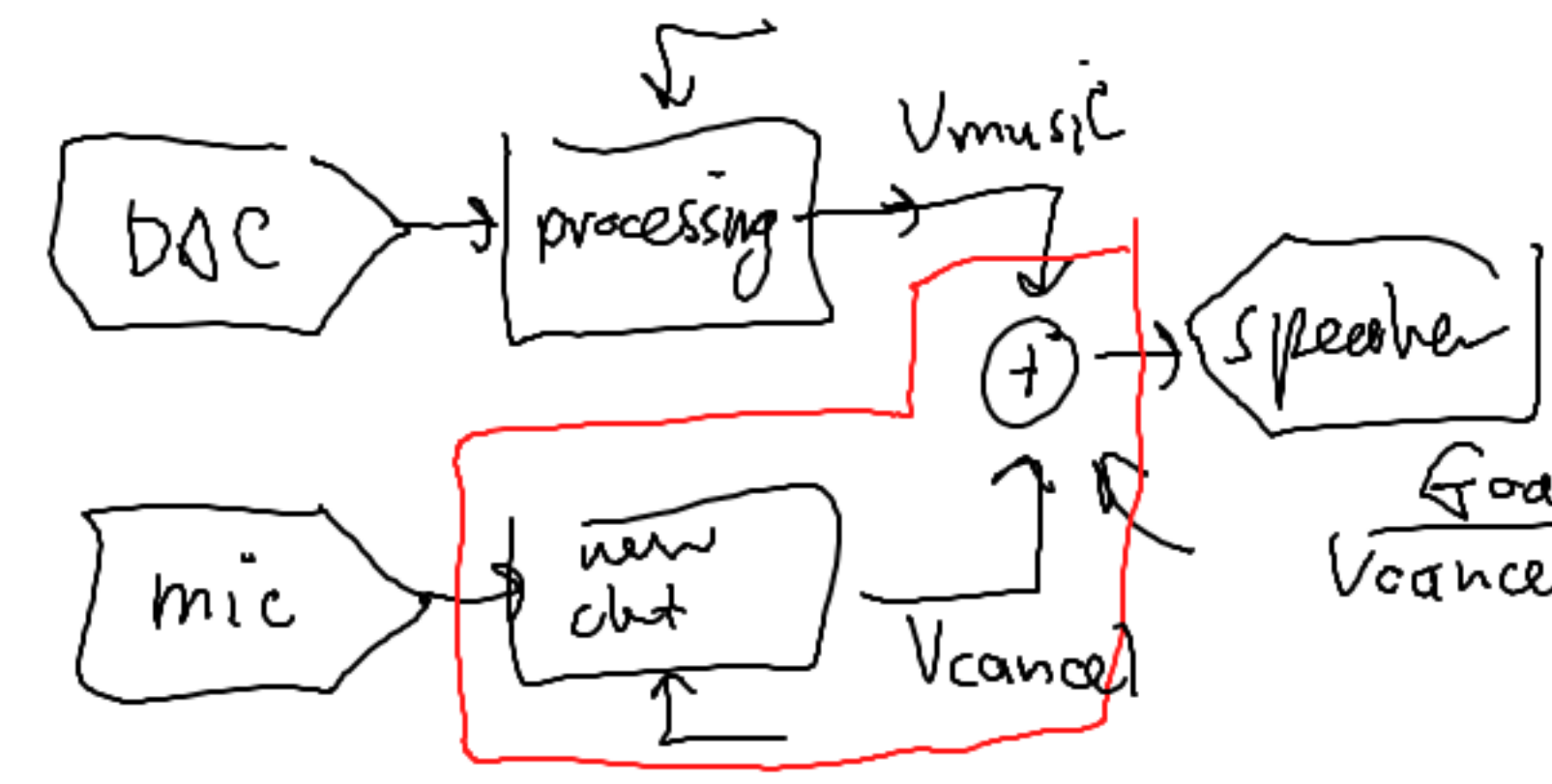
$$-\frac{1}{8} \leq -\frac{1}{4} \left(V_{mic} - \frac{1}{2}V \right) \leq \frac{1}{8}$$




Goal

$$V_{cancel} = -\frac{1}{4} \left(V_{mic} - \frac{1}{2}V \right)$$

$$V_{\text{cancel}} = -\frac{1}{4} \left(V_{\text{mic}} - \frac{1}{2}V \right)$$



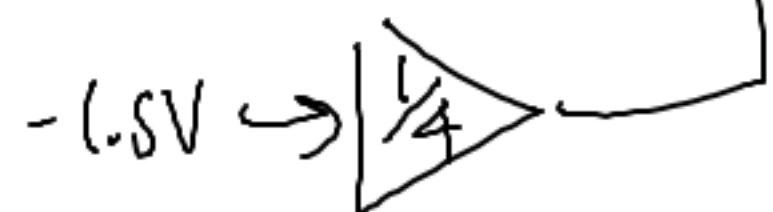
$$-\frac{1}{8}V \text{ to } \frac{1}{8}V$$



Implement


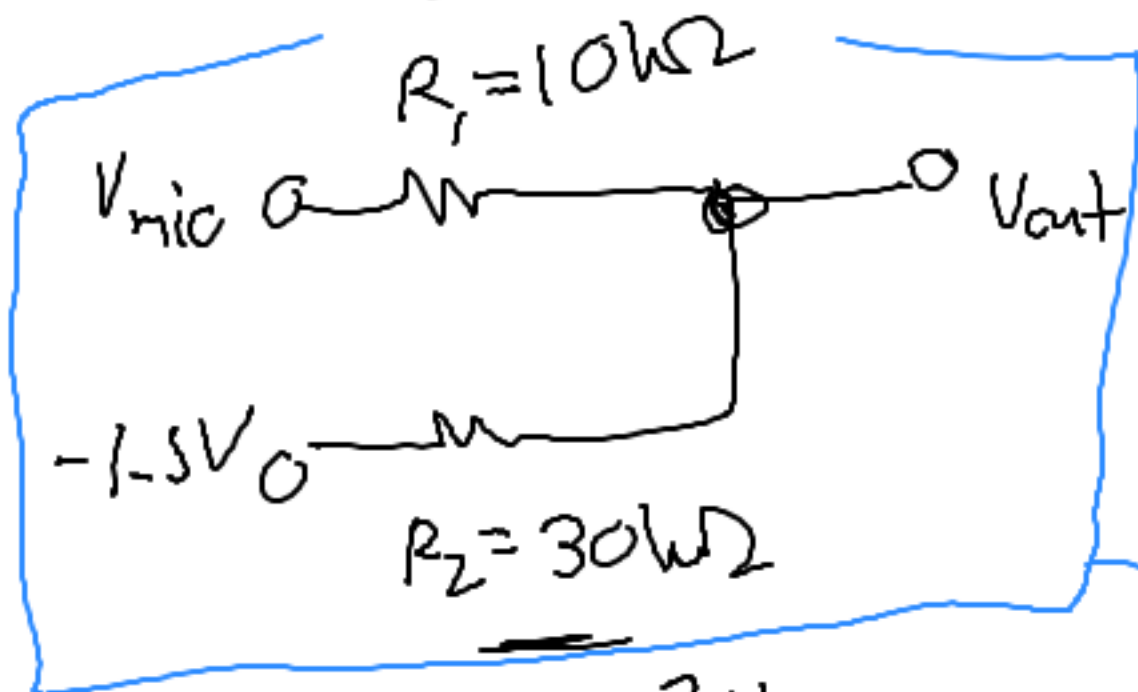
$$V_{\text{out}} = -\frac{R_2}{R_1} V_{\text{in}}$$



$$\alpha = \frac{R_2}{R_1 + R_2} = \frac{30k}{40k} = \frac{3}{4} V$$



Can't just connect,
need something
Need a buffer.

