

# EECS16A 5B

## \* Discussion checkoff

### Skills

- Identify nodes & branches in ckt's
- How to apply passive sign convention
- Redraw circuits

### Analysis (solving for voltages & currents)

- NVA
- Superposition
- Equivalence
  - ↳ Thevenin/Norton (source-resistor)<sup>ckts</sup>
  - ↳ Resistors/Capacitors
- Charge sharing algorithms

### Equations

- KCL, KVL
- Golden rules
- I-V relations
  - ↳ C ( $i_c = C \frac{dv_c}{dt}$ )
  - ↳ R (Ohm's law)

- Power  $P = IV$
- Constitutive eq:  
 $R = \rho \frac{L}{A}$ ,  $C = \epsilon \frac{A}{d}$

### Functional Blocks

- Dividers (V, I), Voltage summer
- Op Amps
  - ↳ inverting amp
  - ↳ non-inverting amp
  - ↳ Unity gain buffer
  - ↳ Transresistance amp

# Modeling


Touchscreen

↳ R

↳ C

Timer clkt

(Design ex. from lecture)

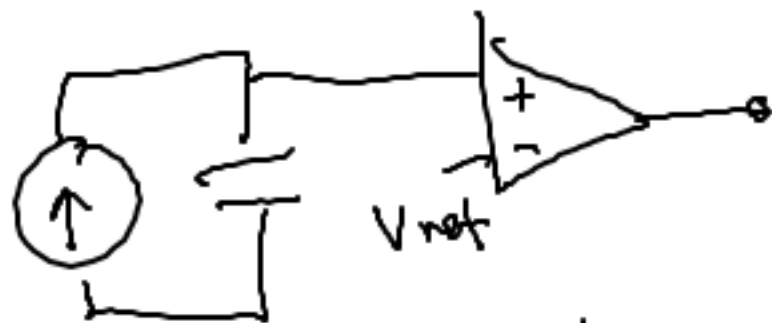

(changing cap triggers event)

## Problems

→ Noise filtering

→ Audio to speaker

# Design


Procedure  
↳ Specification (words) goal in

↳ Strategy (abstracting goal as block diagram + math)


↳ Implementation (drawing clkt)

↳ Verification (analyzing to check)

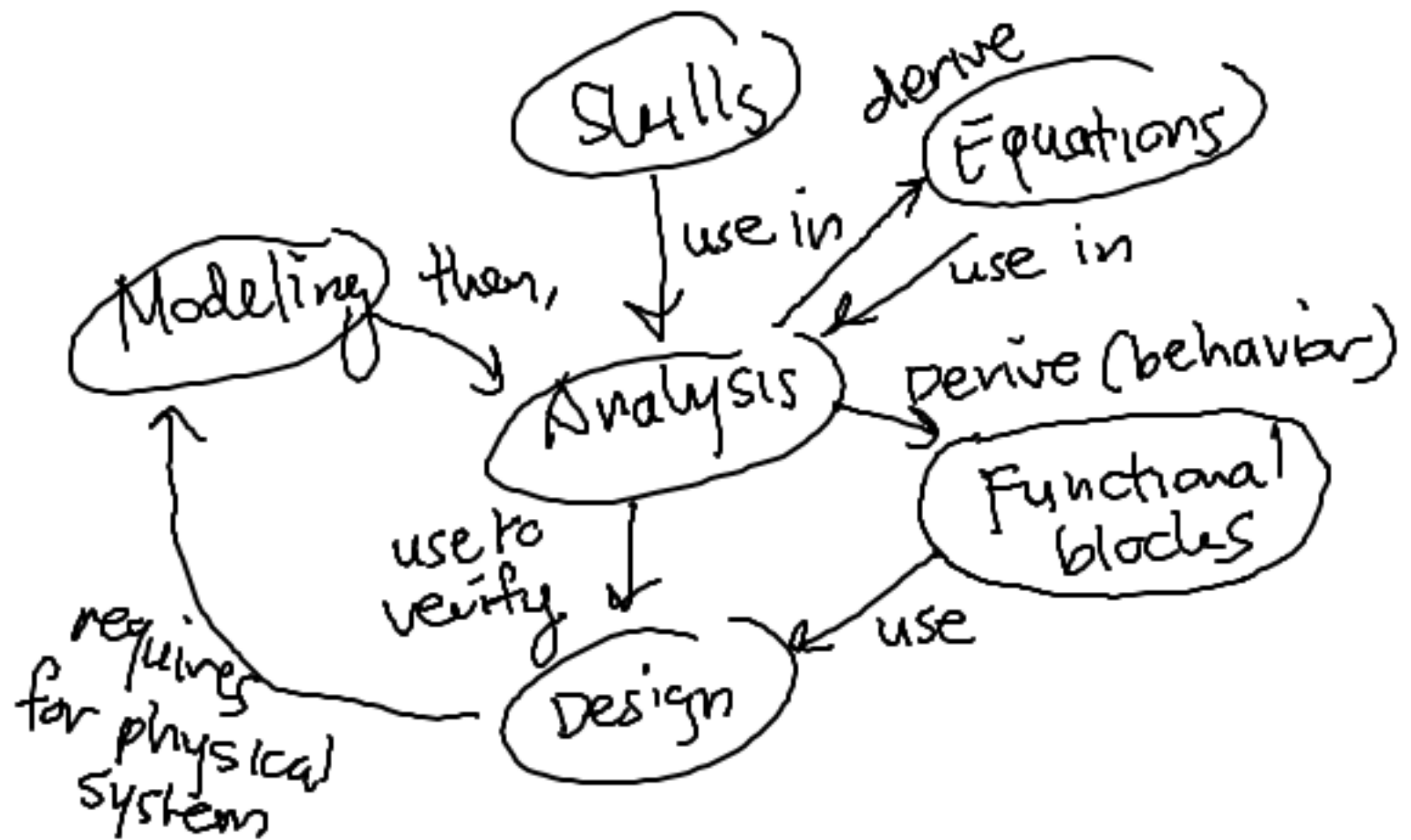composition & loading  
↳ how to identify loading




1(a)

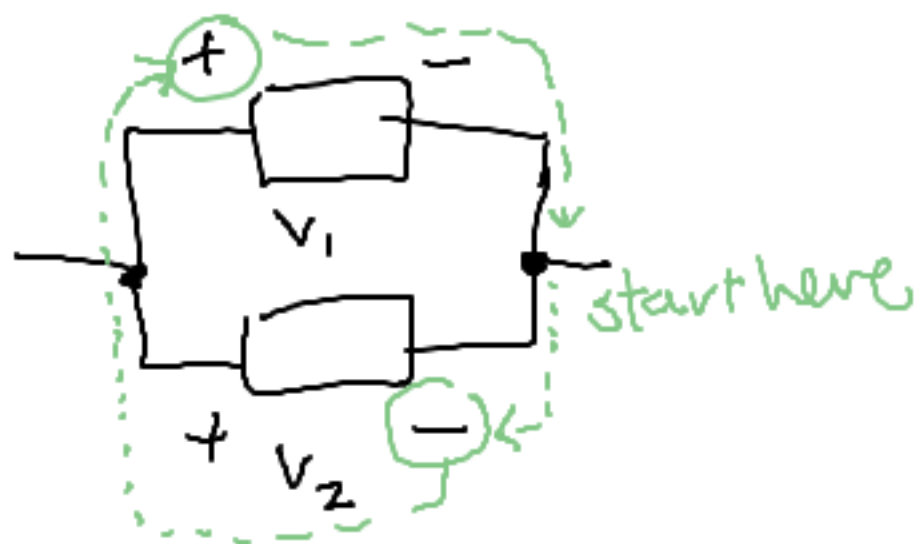


KVL:  $-V_2 + V_1 = 0$   
 $V_1 = V_2$

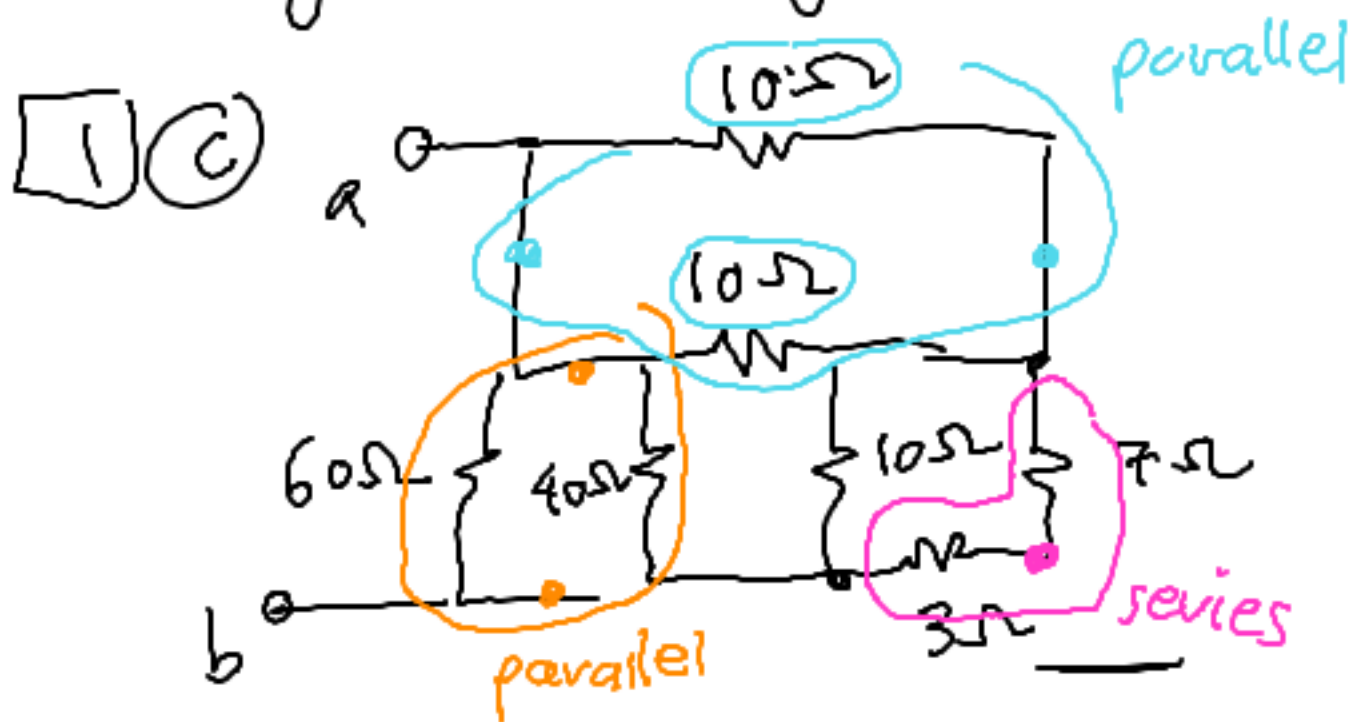Whenever in parallel, same branch voltage (assuming same labeling)





1(b)


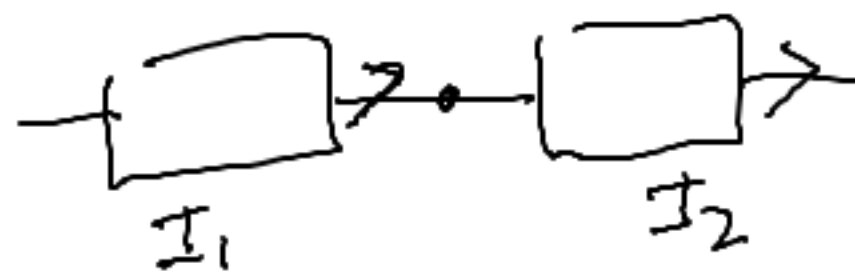


KCL:  $I_1 = I_2$

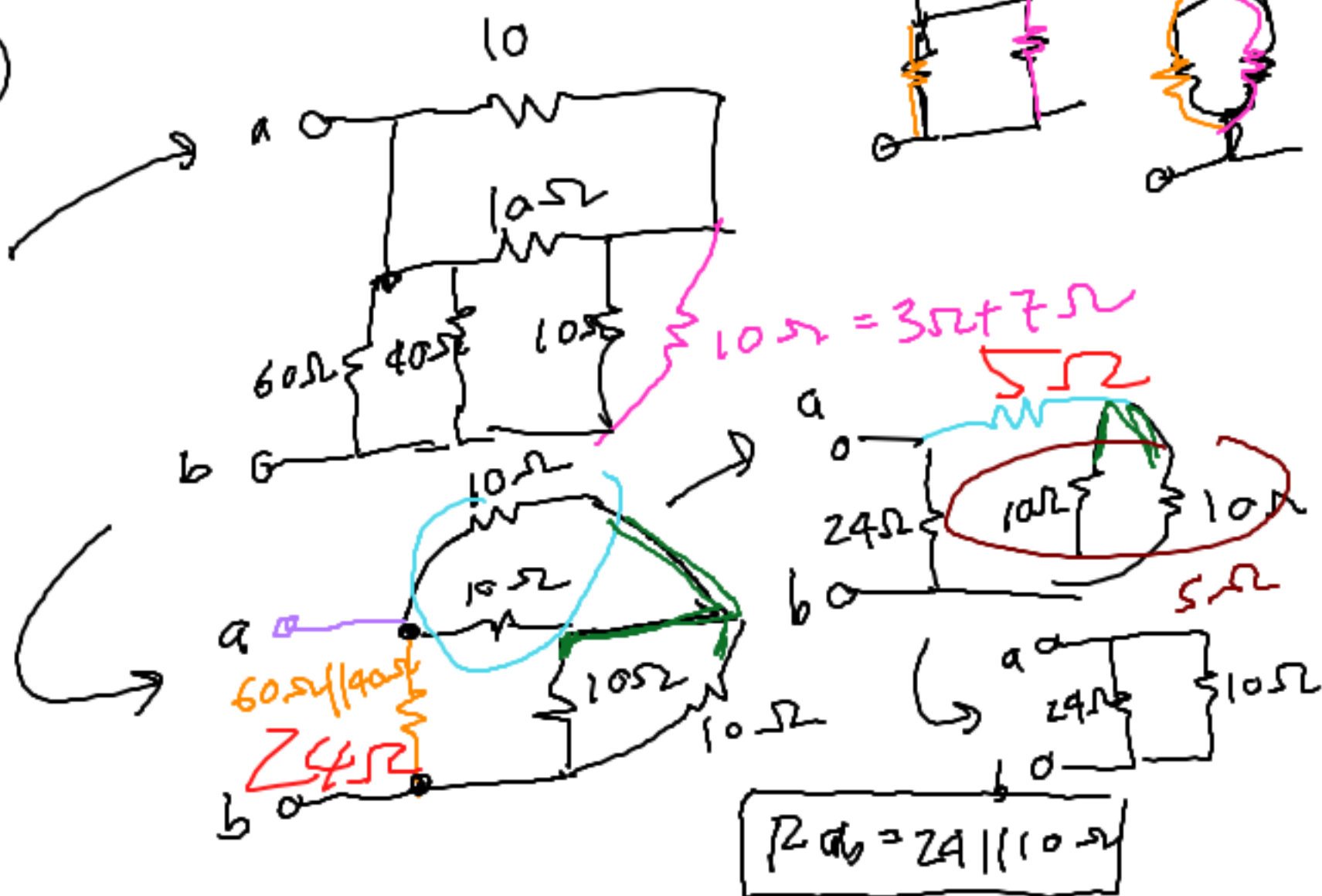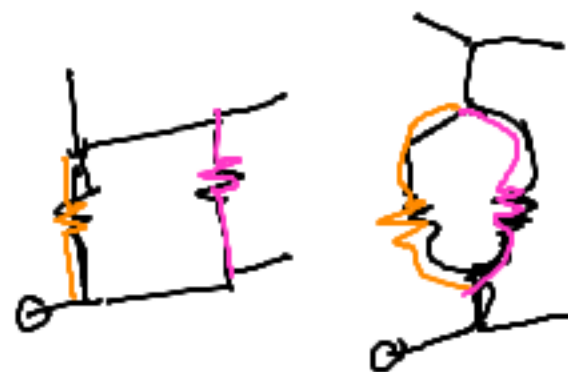Whenever in series, same current (branch)



114

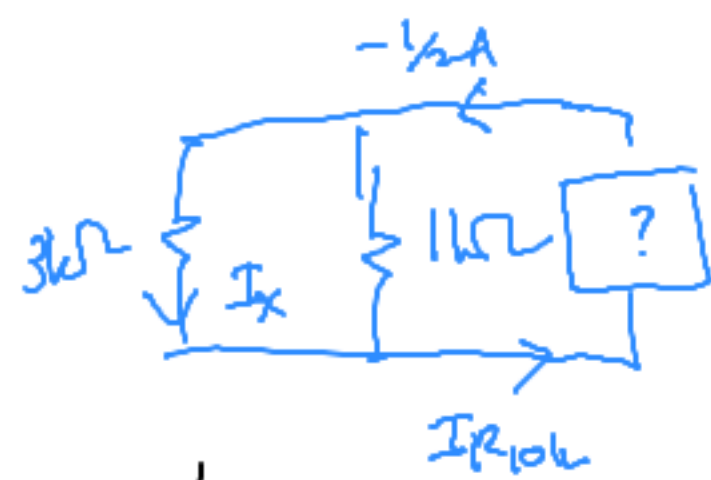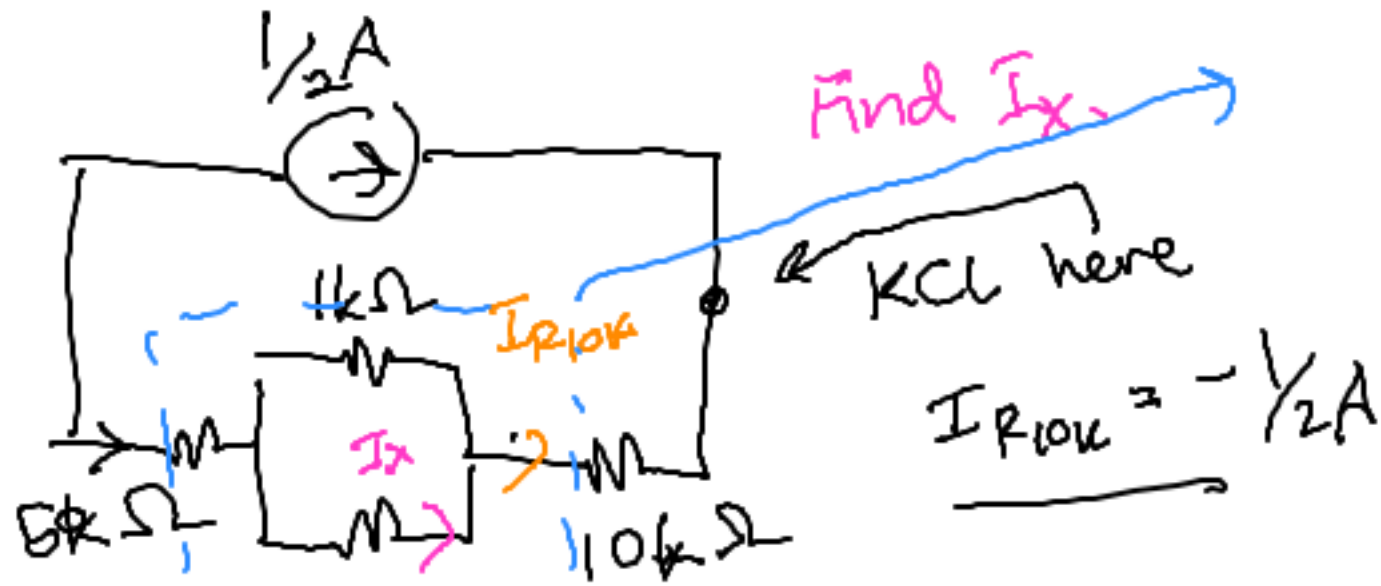

- Options:
- $I_x = -\frac{3}{4} I_{R_{10k}}$  ? X
  - $I_x = -\frac{1}{4} I_s$  ? ✓
  - $I_x = -\frac{1}{8} A$  ? ✓
  - $I_x = \frac{3}{8} A$  X


$$I_x = \frac{3}{4} (-\frac{1}{2} A) \times$$

Why? other resistor

$$I_x = \frac{1k\Omega}{3k\Omega + 1k\Omega} (-\frac{1}{2} A)$$

$$= -\frac{1}{8} A$$

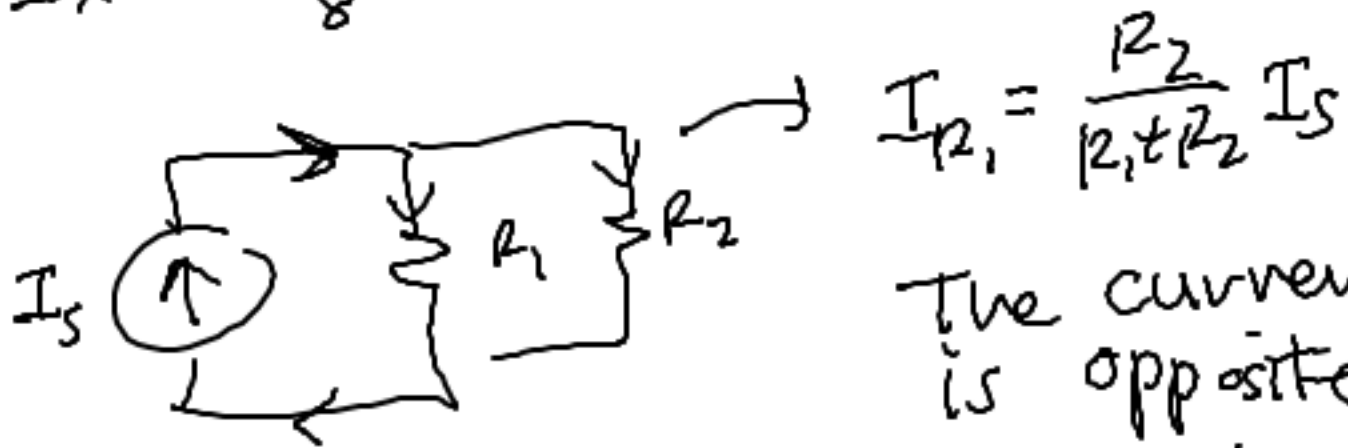
Reminder: intuitive check  
 → Current takes path of least resistance



$$I_{R_2} = \frac{R_1}{R_1 + R_2} I_s$$

The current direction for  $I_x$  is opposite to the one assumed in the derivation → negative

2

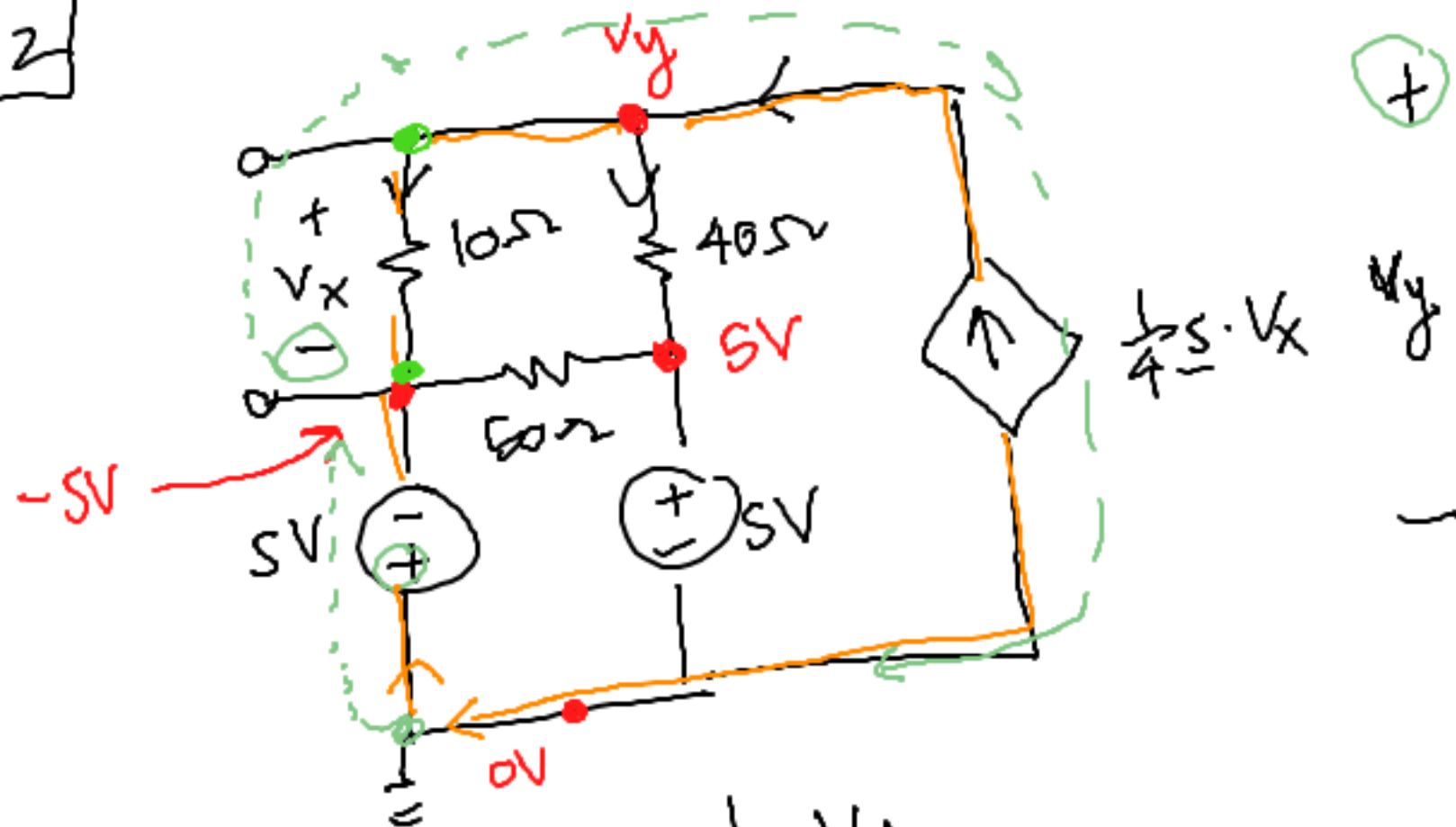

$[S]$  (siemens) =  $\left[\frac{1}{\Omega}\right]$   
 $\hookrightarrow$  conductivity

find  $V_x$  &  $V_y$

KCL (a) node  $V_y$

$$\rightarrow \frac{1}{4\Omega} V_x = \frac{V_y - 5V}{40\Omega} + \frac{V_y - (-5V)}{10\Omega}$$

(Branch)

$V_x = V_y - (-5V)$  (KVL)

$+5V - V_x + V_y = 0$  (path)

$$10V_x = V_y - 5V + 4V_y + 20V$$

$$\rightarrow V_x = V_y + 5V$$

$$10V_y + 50V = 5V_y + 15V$$

$$5V_y = -35V$$

$$V_y = -7V$$



$$V_x = (-7V) + 5V = -2V$$

Can always use NVA + KVL eqns to solve. Superposition works too (is essentially NVA)

3
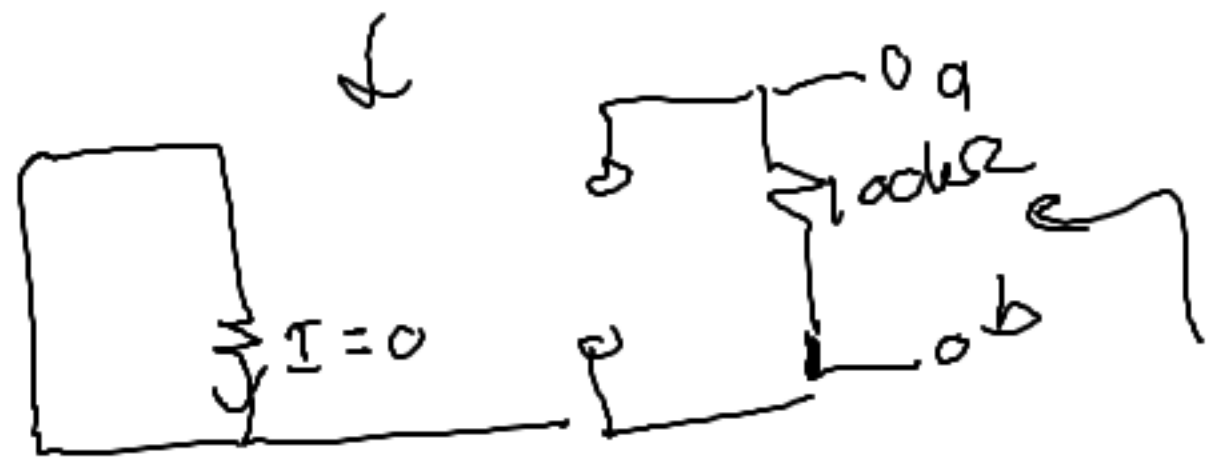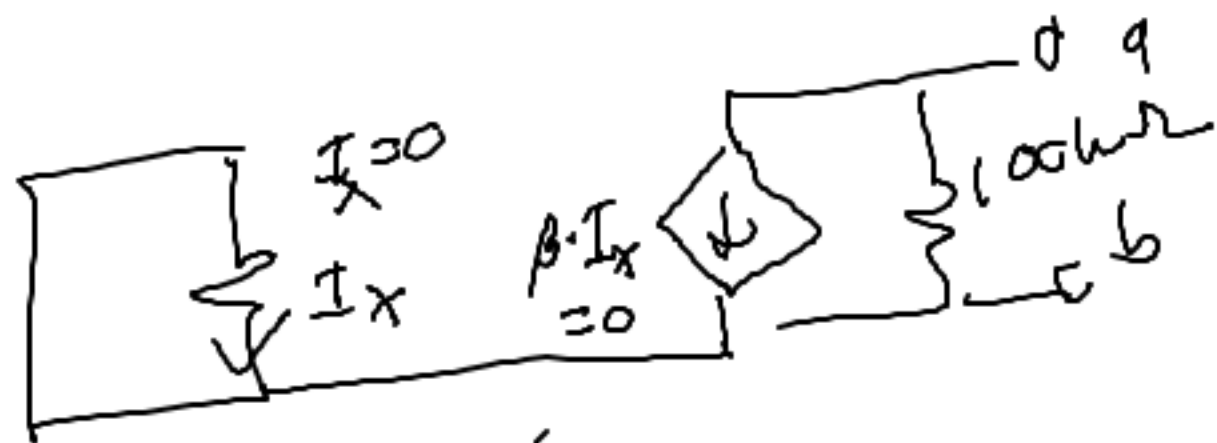
### Takeaway for equivalence (Thevenin/Norton eq)


- Dependent sources don't always require a test source on output
- If dependent source depends on a quantity that goes to zero when independent sources turn off  $\rightarrow$  also turn off dependent source



$R_{ab}$  (when sources are off)  $= R_{th} = R_N$   
 $= \underline{\underline{100\Omega}}$


Q: When to use NVA vs. Superposition? (Rule for when one is faster?)  
 Typically dependent more on which you've practiced or like better.

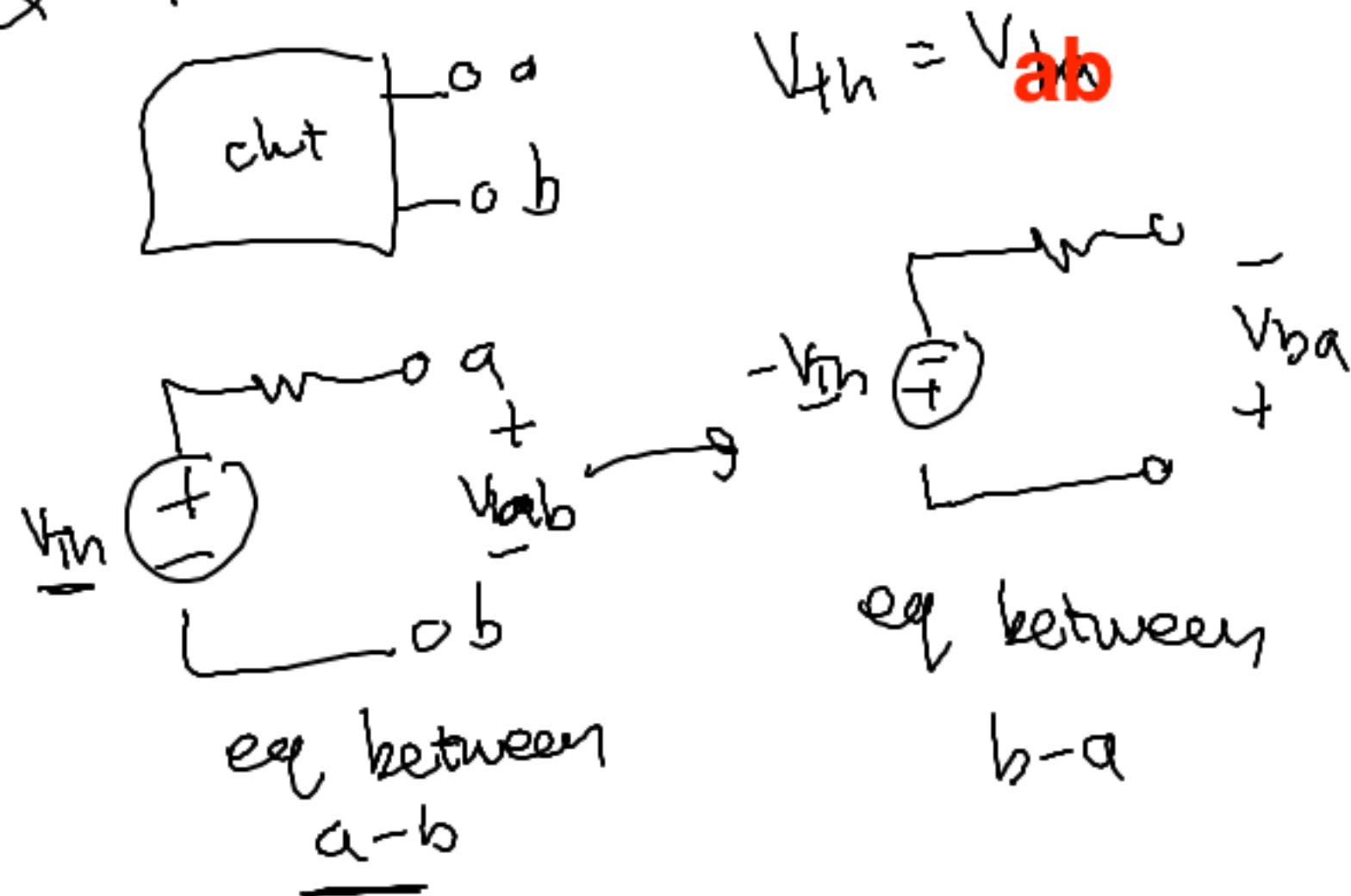Q: Thevenin/Norton eq, between a-b or b-a?



↳ Typically asking about this.

### 3 Finding $V_{th}$

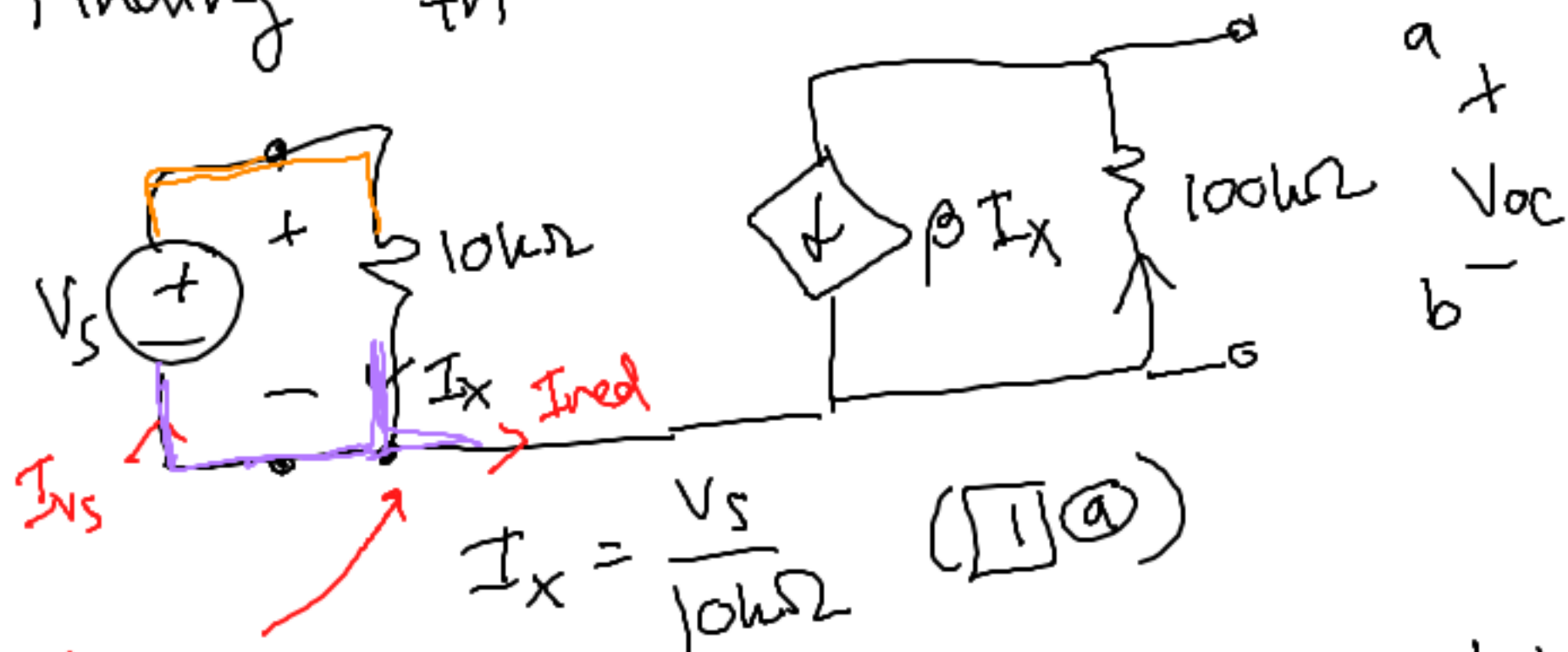

$$I_x = \frac{V_s}{10k\Omega} \quad (1a)$$

Q: any red current?

A: No


KCL:  $I_x = I_{Vs} + I_{red}$

(top)  $I_{Vs} = I_x$   
 $0 = I_{red}$

$$V_{oc} = -\beta I_x \cdot 100k\Omega \quad (\text{ohm's law})$$

$$= -\beta \frac{V_s}{10k\Omega} \cdot 100k\Omega$$

$$= -10\beta V_s$$

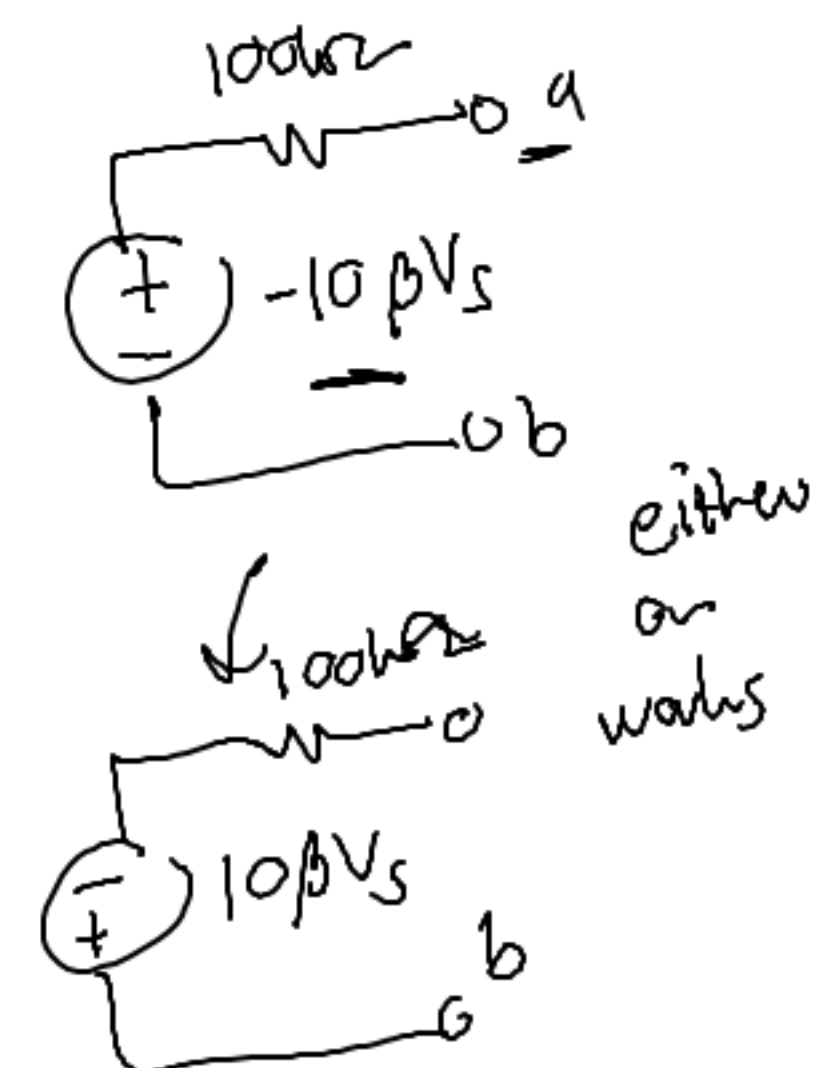

Norton eq

$$I_{No} = \frac{V_{th}}{R_{th}} = \frac{-10\beta V_s}{100k\Omega}$$

$$= -\frac{\beta V_s}{10k\Omega}$$

