

Last time:

- * Key Elements I-V
- * KCL, KVL
- * Passive Sign Convention
- * Intro to NVA


} Note 11

Today:


- * Review NVA (voltage divider)
- * Touchscreen Construction
- * "16A" Physics
- * Modeling
- * Analysis & Modeling: Putting it All Together

} Note 12


NVA Review: Voltage Divider

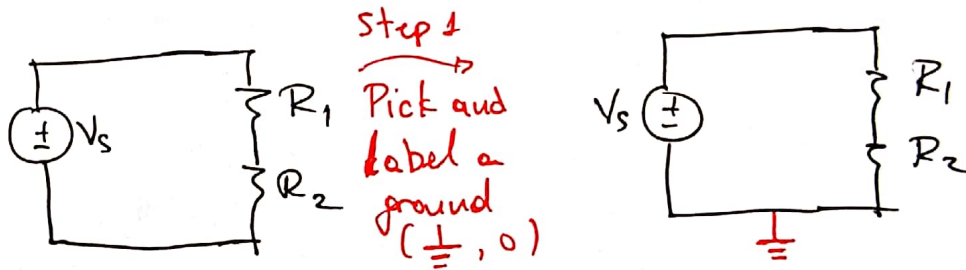

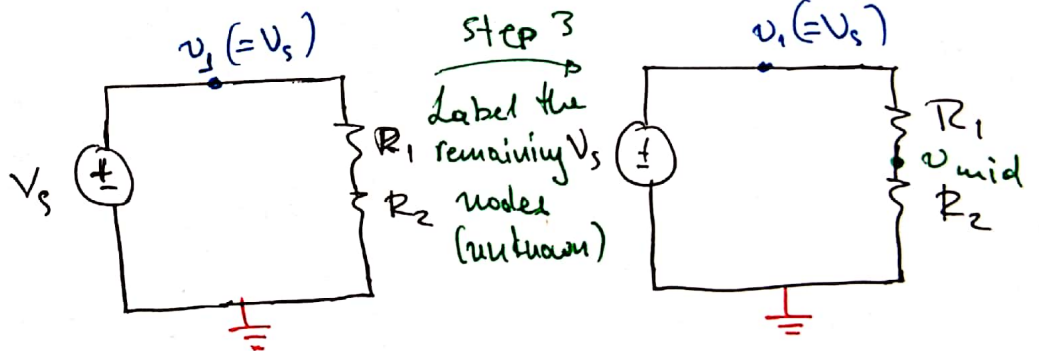Step 2
Label all nodes w/ voltages set by voltage sources



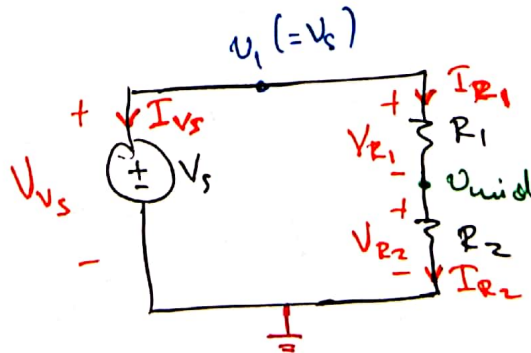Step 4
Label element current and voltages according to passive sign convention!



(P2) Step 5: KCL equation (only for unknown nodes)

$$I_{R_1} = I_{R_2}$$

Step 6: Element currents $\xrightarrow{\text{Ohm's Law}}$ element voltages + component characteristics

$$I_{R_1} = \frac{V_{R_1}}{R_1}$$

$$I_{R_2} = \frac{V_{R_2}}{R_2}$$

Step 7: Element voltages \rightarrow node voltages

$$I_{R_1} = \frac{V_{R_1}}{R_1} = \frac{V_1 - v_{mid}}{R_1} = \frac{V_s - v_{mid}}{R_1}$$



$$I_{R_2} = \frac{V_{R_2}}{R_2} = \frac{v_{mid} - 0}{R_2} = \frac{v_{mid}}{R_2}$$

Step 8: Substitute Step 7 \rightarrow Step 5 and solve for the unknown node voltages.

$$I_{R_1} = I_{R_2} \Rightarrow \frac{V_s - v_{mid}}{R_1} = \frac{v_{mid}}{R_2} \Rightarrow$$

$$\boxed{v_{mid} = \frac{R_2}{R_1 + R_2} \cdot V_s} \quad \text{voltage divider}$$

Resistive Touchscreen

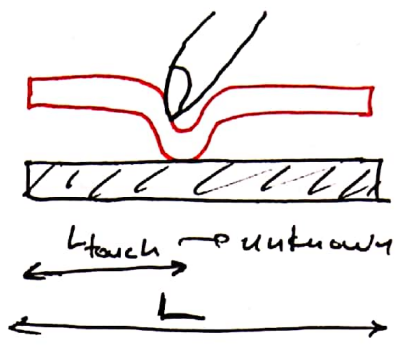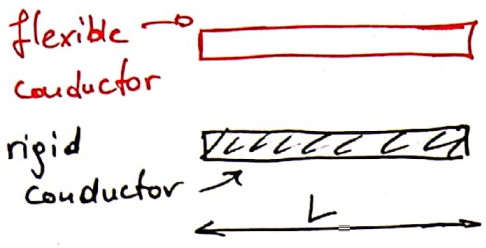

Want to measure $\frac{L_{touch}}{L}$

Need to convert length (position) to an electrical quantity (V, I)

"JGA" Physics

* Charge - Can be either positive or negative
 Basic quantity of electrical flow (e.g. electron)
 Unit: Coulomb [C]

* Current - Net amount of charge that passes through some cross-sectional area over some period of time.

$I = \frac{dq}{dt}$
 [A] ← [C] / [s]

Always do unit checks!
 $I_C = I_A \cdot I_s$

* Voltage - Represents the energy spent to move a positive unit charge from one point A to another point B.

$V = \frac{dE}{dq}$
 [V] ← [J] / [C]


particle
V_{AB}
A → B

Q4

* Resistance - Real pieces of metal require some amount of energy to allow charges to flow through them.

$V = I \cdot R$
[V] ← [A] → [Ω]

Modeling a Resistor

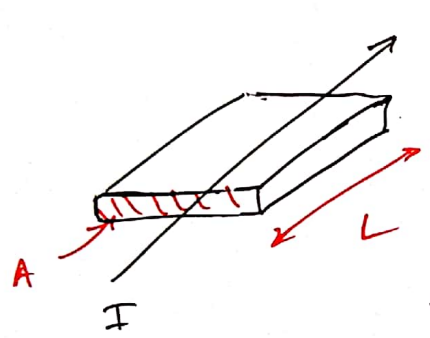

$R = \rho \frac{L}{A}$
[Ω] [Ω·m] [m] [m²]

Resistance value depends on:


- 1) Geometry of the structure
- 2) Properties of the material

Conductor → $\rho_{\text{copper}} = 1.7 \cdot 10^{-8} \Omega \cdot m$
semiconductor → $\rho_{\text{silicon}} = 6.4 \cdot 10^2 \Omega \cdot m$
insulator → $\rho_{\text{quartz}} \approx 5 \cdot 10^{16} \Omega \cdot m$

PS

Resistive Touchscreen (Cont)


Physical:

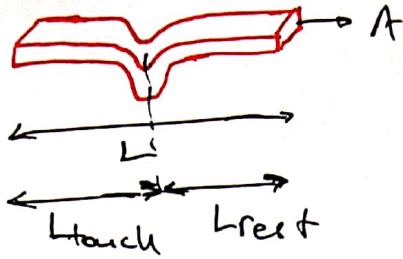


$$R_2 = \rho \cdot \frac{L_{touch}}{A}$$

$$R_1 = \rho \cdot \frac{L_{rest}}{A}$$

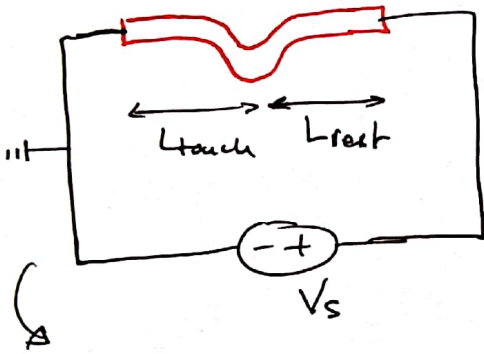Goal Reminder: I want to build a ckt to measure $\frac{L_{touch}}{L}$ as an electrical quantity!



Voltage Divider:

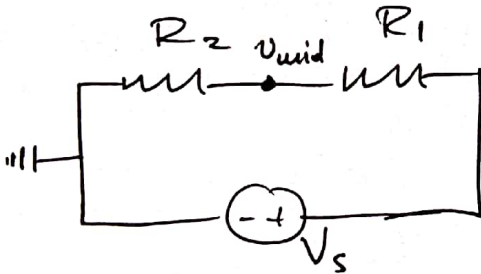

$$V_{uid} = \frac{R_2}{R_1 + R_2} V_s$$

$$= \frac{\rho \cdot \frac{L_{touch}}{A}}{\rho \cdot \frac{L_{rest}}{A} + \rho \cdot \frac{L_{touch}}{A}} \cdot V_s$$

$$= \frac{L_{touch}}{L_{rest} + L_{touch}} \cdot V_s$$

$$= \frac{L_{touch}}{L} \cdot V_s$$

$$V_{uid} = \frac{L_{touch}}{L} \cdot V_s$$

can always measure $\frac{L_{touch}}{L}$ by measuring V_{uid} and knowing V_s .

Note: This is independent of the material type!

P6

More realistic Model

