

Pl

# Module 2, Lecture 3

EECS 16A  
Panos Zarkos


- Last time:
- \* NVA on voltage divider
  - \* Resistive Touchscreen Construction
  - \* Resistive Touchscreen Analysis + Modeling


} Note 12


- Today:
- \* Revisit 1D Touchscreen
  - \* Measuring Voltage and Current
  - \* Power
  - \* An interesting circuit

} Note 13

## 1D - Resistive Touchscreen (Revisited)

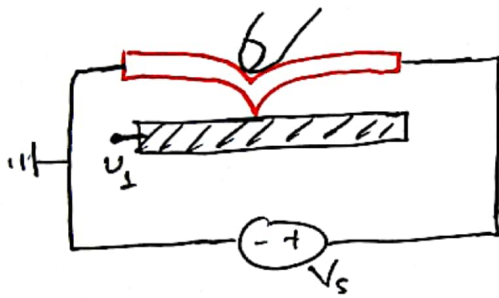

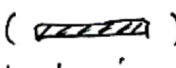Model 1  
  
 ideal wire

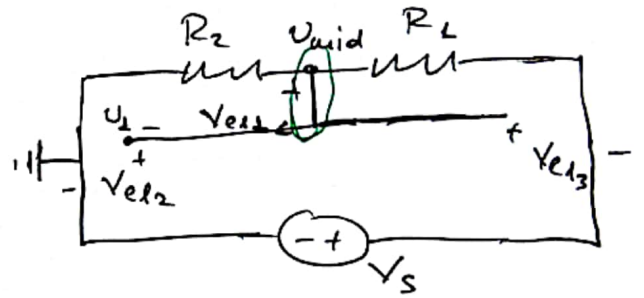

### Additions to Simple Volt. Div.

- 1 Wire ( $v_{el1}$ )
- 2 Open-ckt ( $v_{el2}$ )
- 3 Open-ckt ( $v_{el3}$ )

$$v_{el2} = u_1 - 0 \quad (\text{def. of element voltage})$$

$$v_{el1} = v_{mid} - u_1 \quad (\text{---||---})$$

$$v_{el3} = 0 \quad (\text{wire I-V curve})$$

$$\Rightarrow v_{el2} = v_{mid} - u_1$$


$$\Rightarrow v_{mid} = u_1$$

$$\Rightarrow \boxed{v_{el2} = v_{mid}}$$

What I want is to measure  $v_{el2}$  all the time and get  $v_{mid}$  for any  $L_{touch}$ .

P2

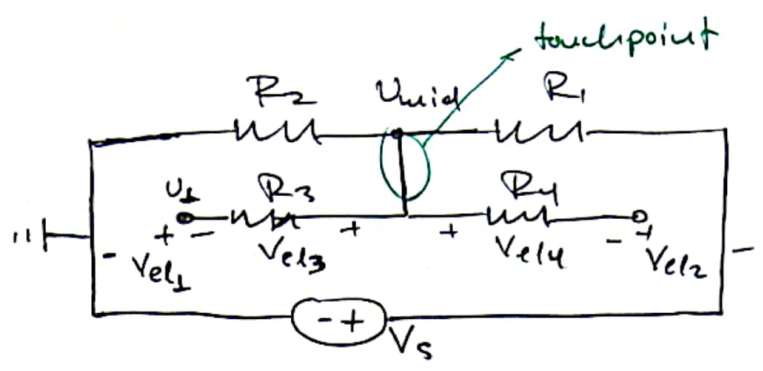Model 2  
 ( ~~resistor~~ )  
 imperfect conductor  
 aka resistor



Addition to simple volt. div.

- ① Open-ckt ( $V_{elt1}$ )
- ② Open-ckt ( $V_{elt2}$ )
- ③  $R_3$  ( $V_{elt3}$ )
- ④  $R_4$  ( $V_{elt4}$ )

$$V_{elt1} = v_1 - 0 \quad (\text{element voltage def.})$$

$$I_{elt1} = 0 \quad (\text{open-ckt def of I-V})$$

"KCL" on  $v_1$ :

$$I_{elt3} = I_{elt1} = 0$$

$$V_{elt3} = R \cdot I_{elt3} = 0 \quad (\text{Ohm's law})$$

$$V_{elt3} = v_{mid} - v_1 \quad (\text{element voltage def.})$$

$$\Rightarrow 0 = v_{mid} - v_1 \Rightarrow v_{mid} = v_1$$


$V_{elt1} = v_1 - 0 = v_{mid}$  ✓

Again I want to measure  $V_{elt1}$  all the time and get  $v_{mid}$  for any  $L_{touch}$ .




Note: Resistors who are connected on one terminal to our ckt and on the other terminal to an open-circuit have no current flowing through them and no voltage drop across them.

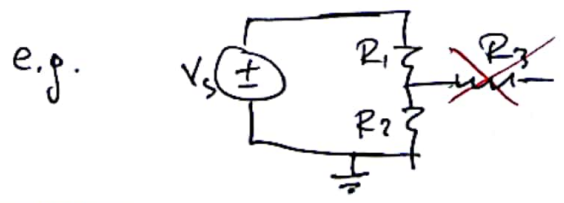$\Rightarrow$  they don't affect our circuit!



P3

# Voltage Measurement

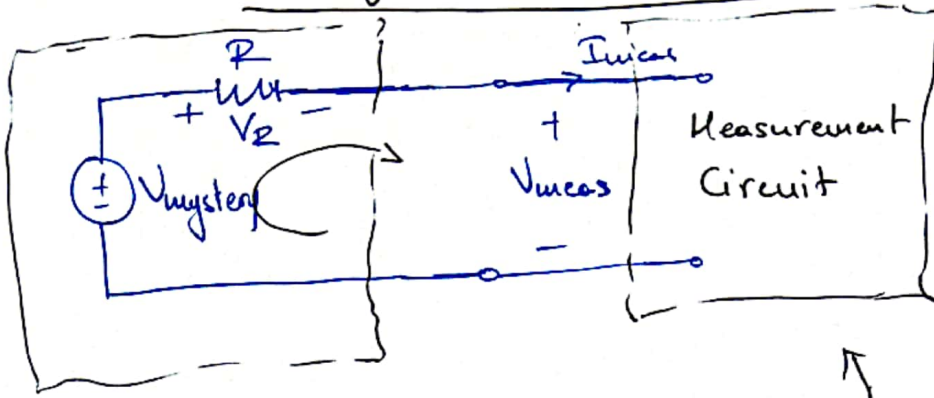

Goal:

Measure  $V_{mystery}$   
i.e.  $V_{meas} = V_{mystery}$

Problem:

$R$  is "in the way"

$$\begin{aligned} \text{KVL: } & V_{mystery} - V_R - V_{meas} = 0 \\ \Rightarrow & V_{mystery} = I_{meas} \cdot R + V_{meas} \\ \Rightarrow & V_{mystery} = V_{meas} \quad \text{if } I_{meas} = 0 \end{aligned}$$

measurement circuit  
needs to look like  
an open-circuit

→ Measurement circuit should not change the energy of the circuit (cause energy dissipation)

Defined voltage between points A and B as:

$$V_{AB} = \frac{dE}{dq}$$

$dE$  is the energy spent to move  $dq$  from point A to point B.

Power (rate of change of energy)

$$P = \frac{dE}{dt} = \underbrace{\frac{dE}{dq}}_V \cdot \underbrace{\frac{dq}{dt}}_I = V \cdot I$$

Units: Power [W] = [V] · [A] = [J] / [s]

← Watts


P4

# Power + Passive Sign Convention

$$P_{el} = V_{el} \cdot I_{el}$$

$$R = \rho \cdot \frac{l}{A}$$


For a resistor:

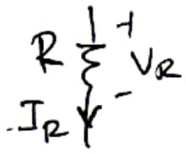


$$P_R = V_R \cdot I_R = I_R \cdot R \cdot I_R = I_R^2 \cdot R \geq 0$$

$$P_R = V_R I_R = V_R \cdot \frac{V_R}{R} = \frac{V_R^2}{R} \geq 0$$

Resistors always dissipate power!

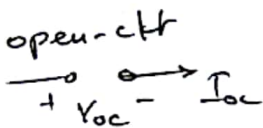


$$P_{oc} = V_{oc} \cdot I_{oc} = 0$$

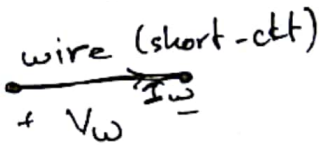

$$P_w = V_w \cdot I_w = 0$$

Example #1

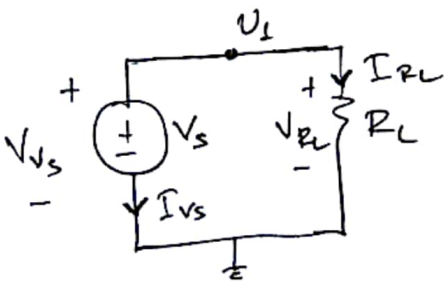

Resistor:

$$V_1 = V_s$$
$$I_{R_L} = \frac{V_{R_L}}{R_L} = \frac{V_1 - 0}{R_L} = \frac{V_s}{R_L}$$

$$P_{R_L} = I_{R_L} \cdot V_{R_L} = \frac{V_s^2}{R_L} \geq 0$$

Voltage Source:

$$\text{KCL on } V_1: 0 = I_{V_s} + I_{R_L}$$

$$\Rightarrow I_{V_s} = -I_{R_L} = -\frac{V_s}{R_L}$$

$$V_{V_s} = V_s (= V_1 - 0)$$

$$P_{V_s} = V_{V_s} \cdot I_{V_s} = -\frac{V_s^2}{R_L} \leq 0$$


$$P_{V_s} = -P_{R_L}$$
$$\Rightarrow P_{V_s} + P_{R_L} = 0$$

Energy (and power) are conserved!



PS

# Current Measurement

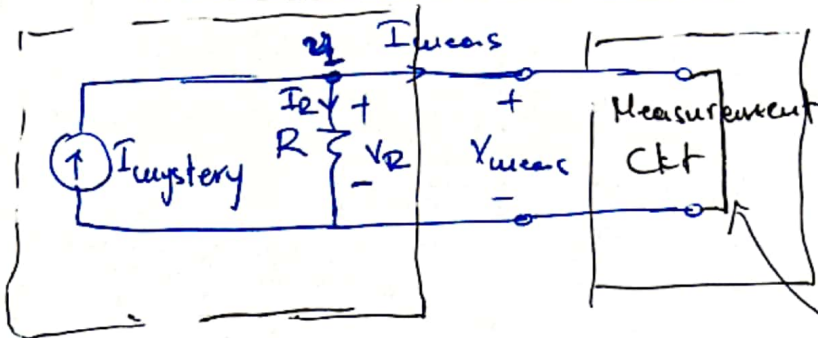

Goal:  
 Measure  $I_{mystery}$   
 i.e.  $I_{meas} = I_{mystery}$


Problem:  
 R is "in the way"

KCL on  $v_1$ :  $I_{mystery} = I_R + I_{meas}$   
 $\Rightarrow I_{mystery} = \frac{V_{meas}}{R} + I_{meas}$   
 $\Rightarrow I_{mystery} = I_{meas}$  (if  $V_{meas} = 0$ )


needs to look like a wire

$P_{meas} = V_{meas} \cdot I_{meas} = 0 \checkmark$  (measurement ckt does not dissipate any power)

## Demo ckt:

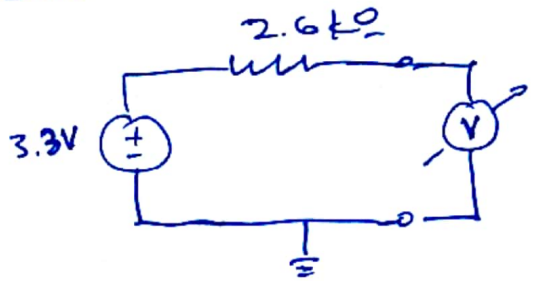


$V = 3.3V$

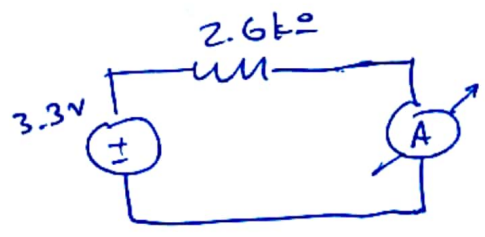

$I = \frac{V}{R} = \frac{3.3V}{2.6k\Omega}$

Example #2

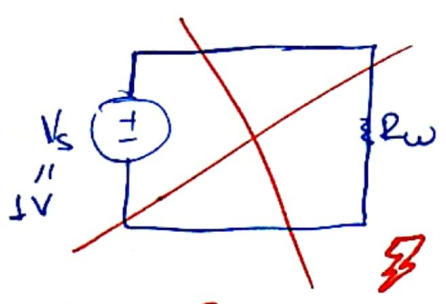

BOOM  
Don't do this!

$R_w \rightarrow 0$

Let's say  $R_w = 10^{-3} \Omega$ ,  $V_s = 1V$


$P_w = I_w \cdot V_w$

$V_w = V_s$ ,  $I_w = \frac{V_w}{R_w} = 1000 A$ !

$P_w = I_w V_w = 1kW$ !

Too BIG  
(something will get fried)

Example #3

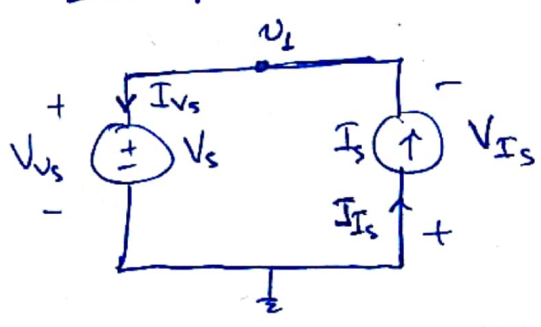

Voltage Source:

$V_{V_s} = u_1 - 0 = V_s$

$I_{V_s} = I_{I_s} = I_s$  (KCL on  $u_1$ )

$P_{V_s} = V_{V_s} \cdot I_{V_s} = V_s \cdot I_s = 1W > 0$   
dissipates

Current Source:

$V_{I_s} = 0 - u_1 = -V_s$

$I_{I_s} = I_s$

$P_{I_s} = V_{I_s} \cdot I_{I_s} = -1W < 0$   
generates

Note: If more than one sources exist in the ckt you have to use nodal analysis (NVA) to determine whether they ~~both~~ ~~that~~ generate or dissipate power.

At least one needs to generate the power dissipated by the rest.