

(P1)

Module 2, Lecture 5

EECS 16A

Panos Zarkos

Last time:
 * An interesting circuit
 * 2D Resistive Touchscreen
 * Superposition - Intro
 } Note 14

Today:
 * Superposition (Cont.)
 * Equivalence
 } Ckt Jedi techniques - Note 15 A, B

Goal: Build Interesting Systems!

→ Need: tools to provide insight (analysis techniques)

Superposition (aka ckt analysis Jedi technique #1)

Reminder: Linear function $f(x+y) = f(x) + f(y)$

* Imagine a circuit with multiple sources (voltage or current)

Superposition says that we can analyze the ckt by looking at the effect of each source independently and summing up all these at the end.


* Procedure:
 1) For each source k : zero-out all other sources and compute the output $V_{out,k}$ due to just source k .

$$2) V_{out} = \sum_k V_{out,k}$$

P2



What does it mean to zero-out a source?

A) Voltage Source

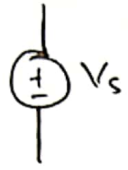

\Rightarrow




wire

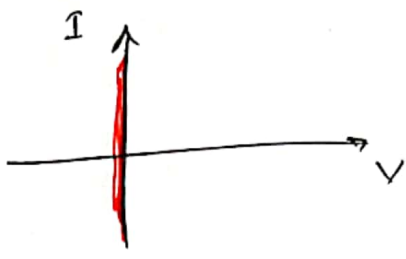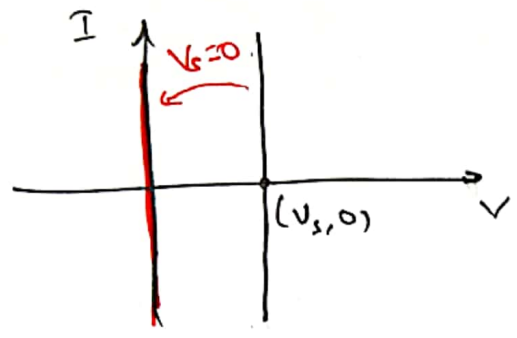

B) Current Source

\Rightarrow

open-circuit

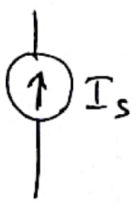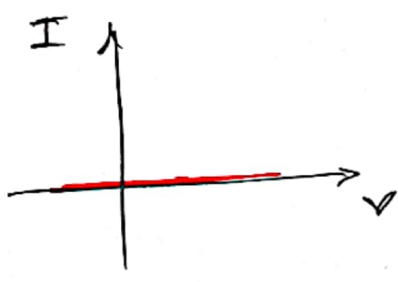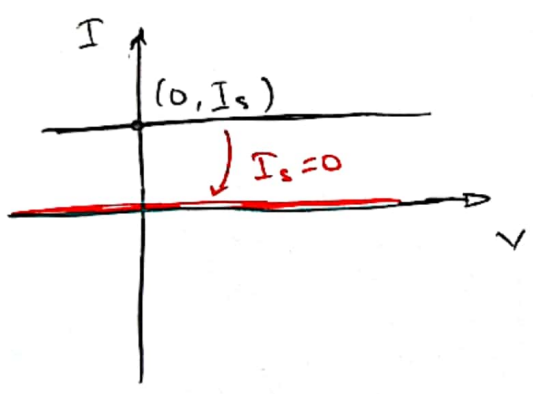


\Rightarrow



open-circuit


P3

Example: Voltage Summer

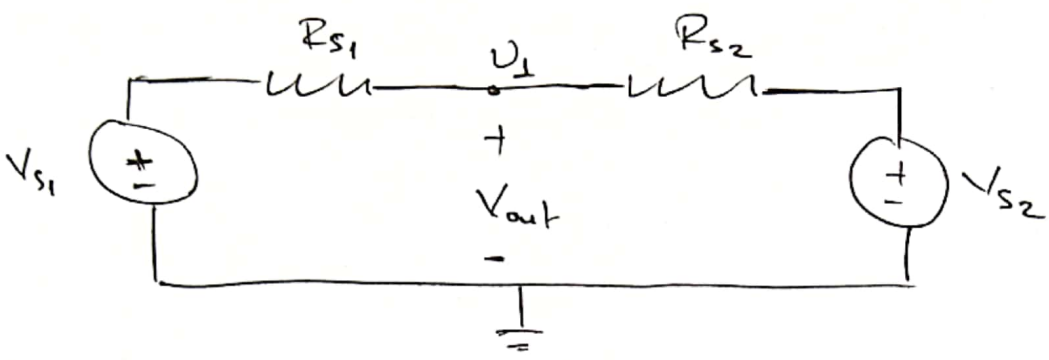


Step 1:

a) Compute the response due to V_{s2} :

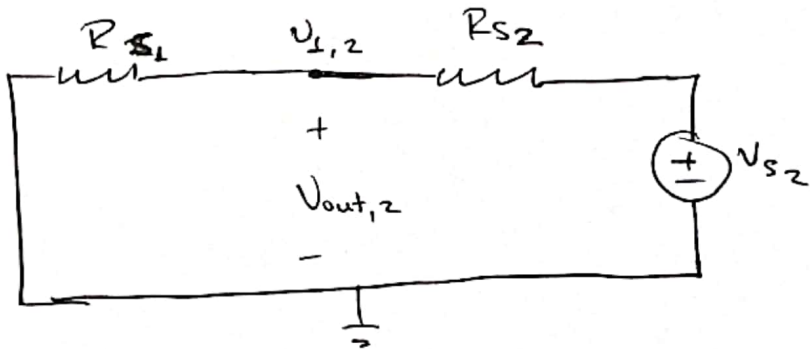

Volt. divider: $V_{out,2} = U_{1,2} - 0 = \frac{R_{s1}}{R_{s1} + R_{s2}} \cdot V_{s2}$

b) Compute the response due to V_{s1} :

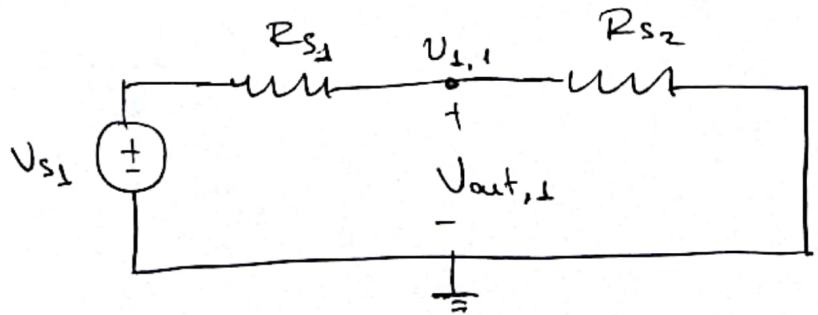

Volt. divider: $V_{out,1} = U_{1,1} - 0 = \frac{R_{s2}}{R_{s1} + R_{s2}} V_{s1}$

created a weighted sum of V_{s1}, V_{s2} !


Step 2:

$$V_{out} = V_{out,1} + V_{out,2} = \frac{R_{s2}}{R_{s1} + R_{s2}} V_{s1} + \frac{R_{s1}}{R_{s1} + R_{s2}} V_{s2}$$

$$V_{out} = \alpha V_{s1} + \beta V_{s2}$$


$\alpha < 1$ $\beta < 1$

P4 Example #2: Some "scary-loading" ct.


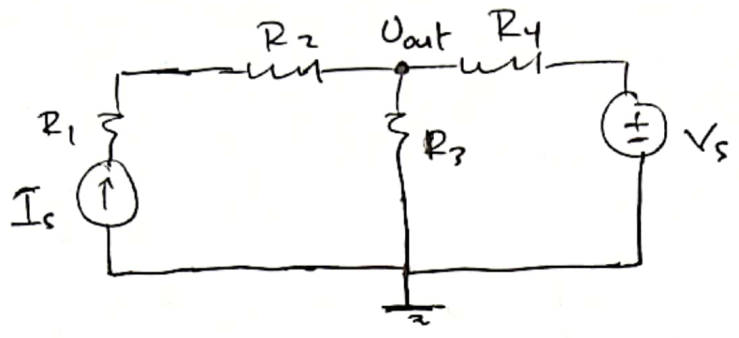


Step 1:

a) Response due to V_s

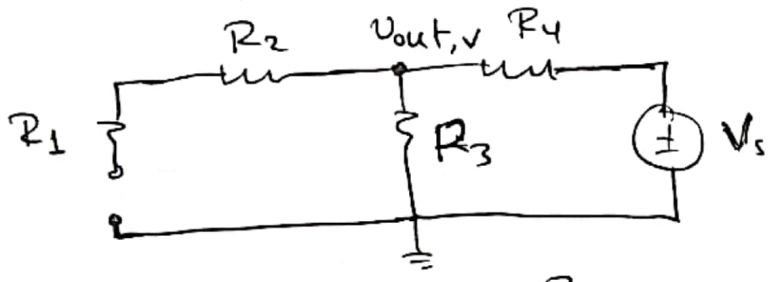


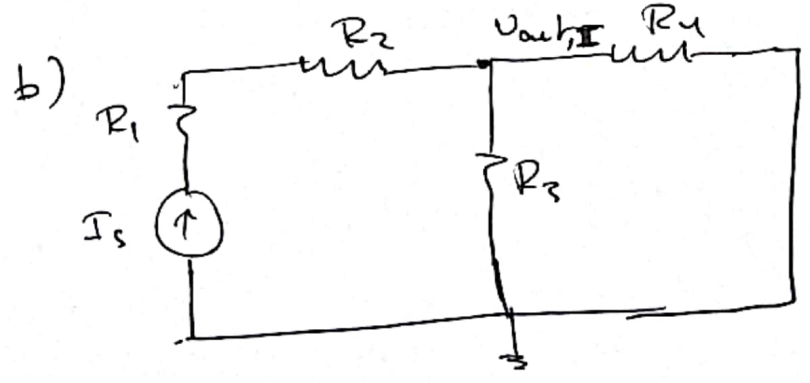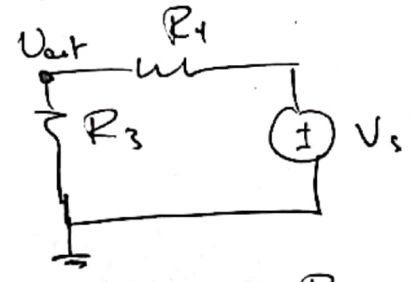R_1, R_2
are open!
No voltage drop
across them!




Step 2: $V_{out} = V_{out,V} + V_{out,I}$

Equivalence (aka ckt Jodi technique #2)

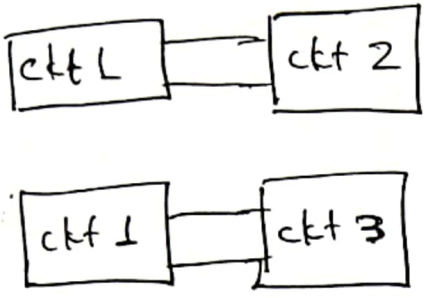


example :

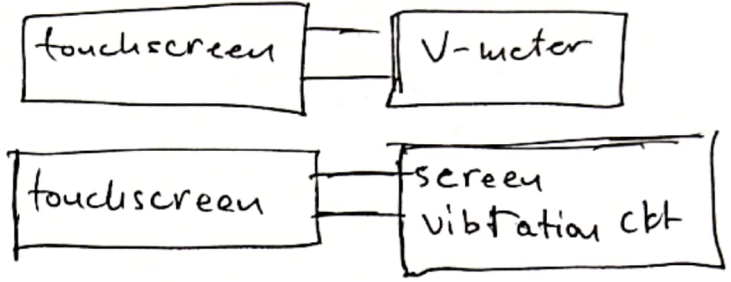


Definition : Two circuit are equivalent if they have the same I-V characteristics.

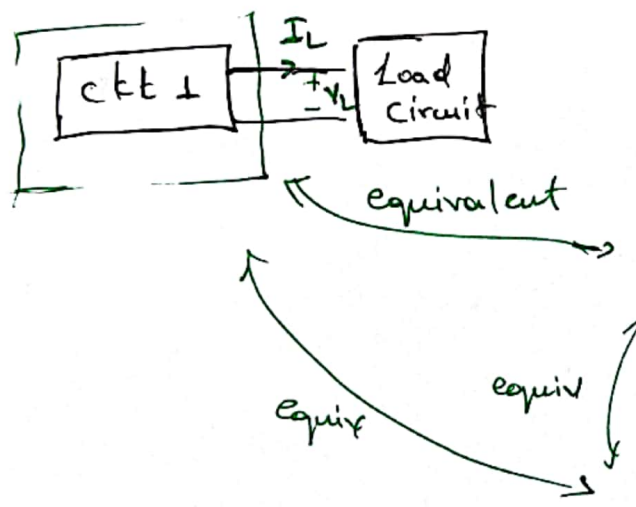
Theorem : Any linear circuit (no matter how complicated) can be replaced with an equivalent simpler linear circuit with only 2 elements.





Thevenin equivalent

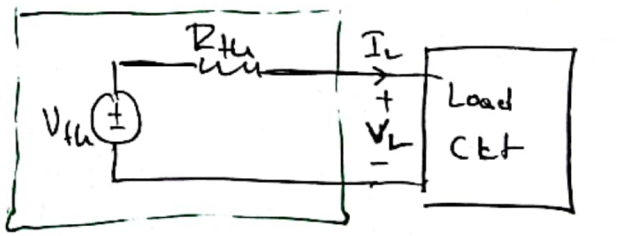

Norton equivalent


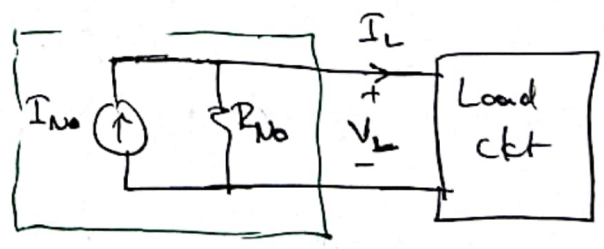


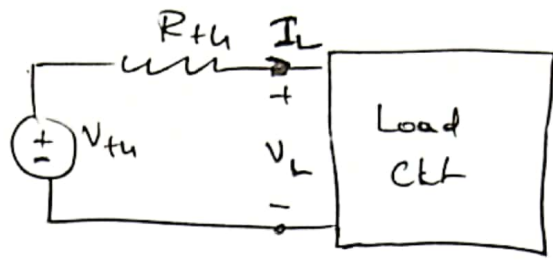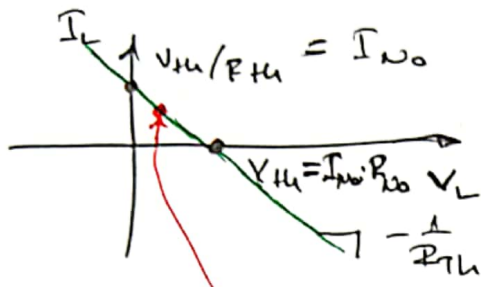P6 Let's find $I_L - V_L$ for the Thévenin equivalent:




Load ckt is a wire:

What if Load-ckt is a resistor?

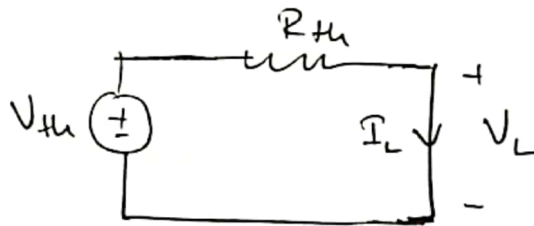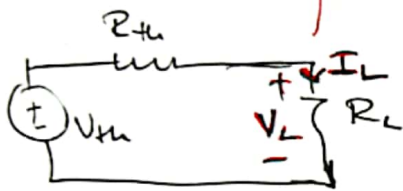

$$V_L = 0, I_L = \frac{V_{th}}{R_{th}} \text{ (y-intercept)}$$

Load ckt is an open-ckt:

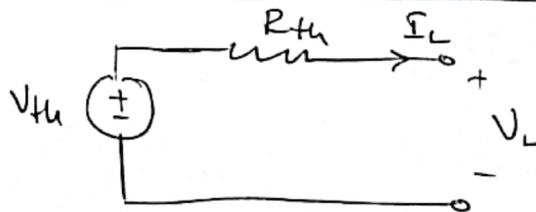


$$I_L = 0, V_L = V_{th} \text{ (x-intercept)}$$


Note: Each load corresponds to a different point in the $I_L - V_L$ line.

Algorithm to find V_{th}, R_{th} (i.e. the Thévenin equiv.)

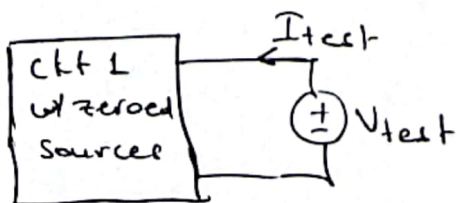- 1) To find V_{th} : "Connect" an open-circuit across the two output terminals and measure/compute $V_{open-circuit} = V_{th}$
- 2) To find R_{th} : Zero-out all independent sources and apply a test voltage or current. (find the slope of the I-V)




$$R_{th} = \frac{V_{test}}{I_{test}}$$

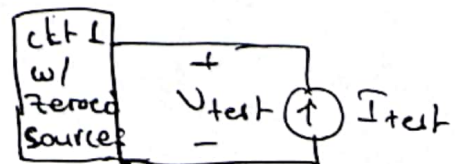


(p7)

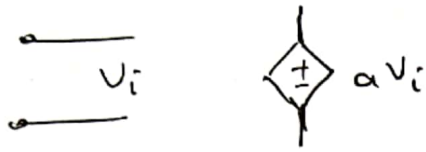Dependent sources (used to model some ckt block or element)
they don't get zeroed out when calculating R_{th} !



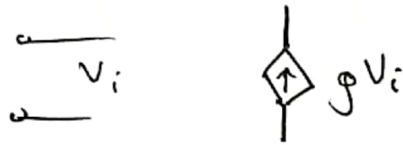Voltage - Controlled Voltage Source
(V C V S)
 α : unitless



Voltage - Controlled Current Source
(V C C S)
 g : $\frac{A}{V}$




Current - Controlled Current Source
(C C C S)
 α : unitless



Current - Controlled Voltage Source
(C C V S)
 r : $[\Omega]$


examples:

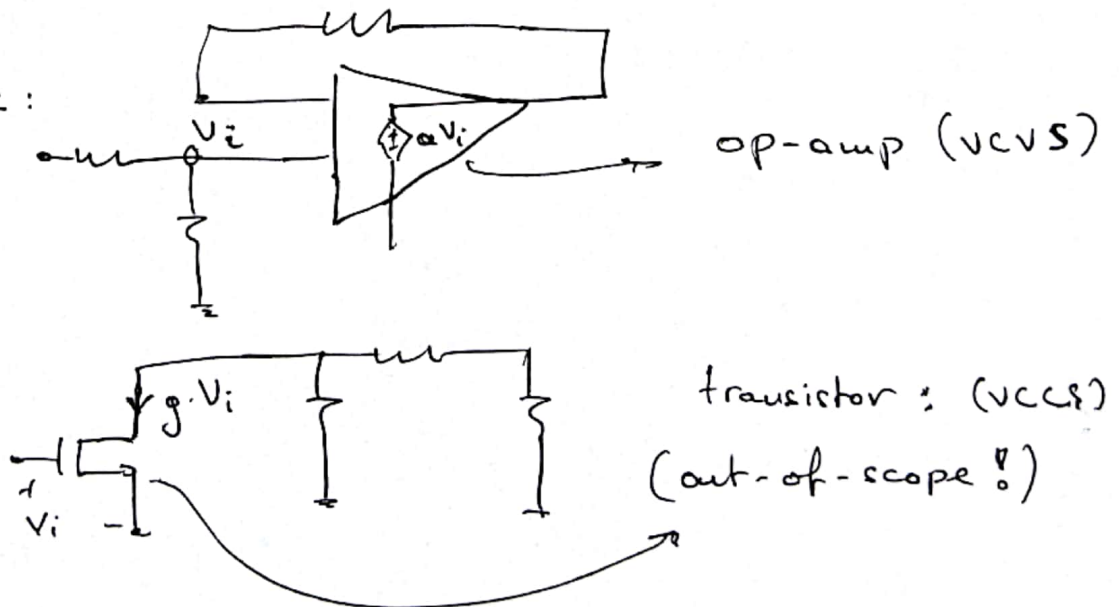


Ⓟ Example:

Ex. 1) "Series Resistors"

Step 1

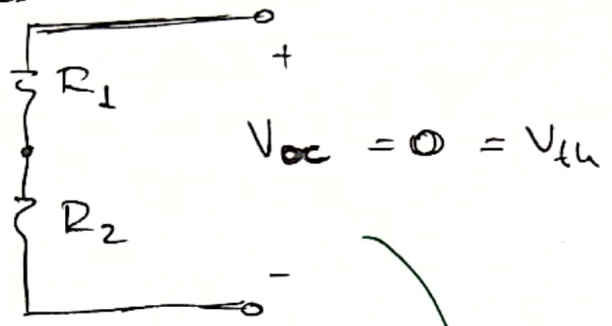


Step 2

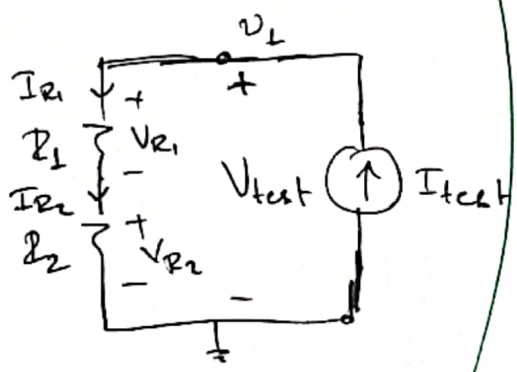

$$\begin{aligned}
 V_{test} &= V_{R1} + V_{R2} \\
 &= I_{R1} \cdot R_1 + I_{R2} \cdot R_2 \\
 &= I_{test} R_1 + I_{test} R_2 \\
 V_{test} &= I_{test} (R_1 + R_2) \\
 \Rightarrow R_{th} &= \frac{V_{test}}{I_{test}} = R_1 + R_2
 \end{aligned}$$


Thevenin Equivalent:

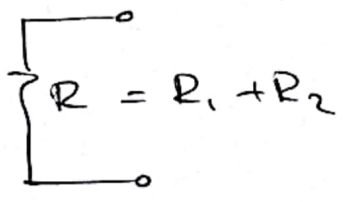

equiv.

Two resistors are connected "in series" when the same current flows through them.


e.g.

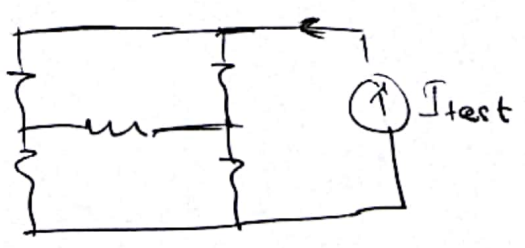


Nothing is in series here!

Ex. 2) "Parallel Resistors"

Step 1

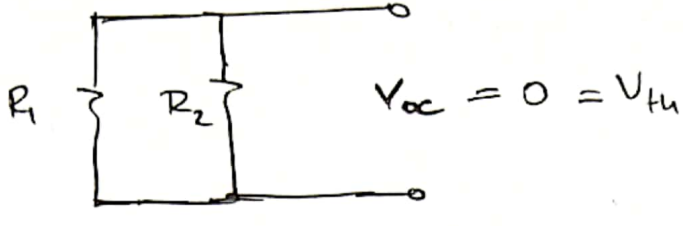

Step 2

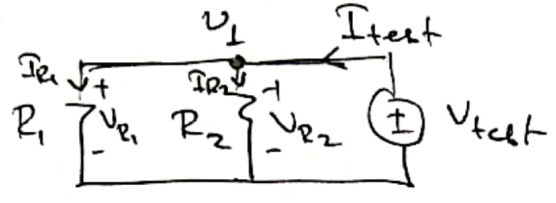

$$V_{R1} = V_{test} = I_{R1} \cdot R_1$$


$$V_{R2} = V_{test} = I_{R2} \cdot R_2$$

$$I_{test} = I_{R1} + I_{R2} \quad (\text{KCL on } v_1)$$

$$= \frac{V_{R1}}{R_1} + \frac{V_{R2}}{R_2}$$

$$= \frac{V_{test}}{R_1} + \frac{V_{test}}{R_2}$$
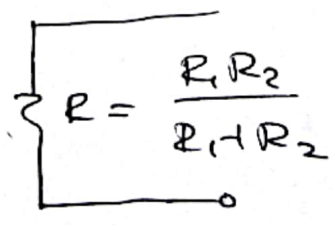
$$\Rightarrow \frac{V_{test}}{I_{test}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2}$$



Two resistors are connected in "parallel," when the voltage drop across them is the same.