

Last Time: * NFB Inspection

* Trol problem w/ Op-Amps

* Cascading Ckt Blocks

Note 19



* Cascading + Composing Ckt Blocks (cont.)

* Design Procedure

* Design Examples

Note 20

Cascading Ckt Blocks

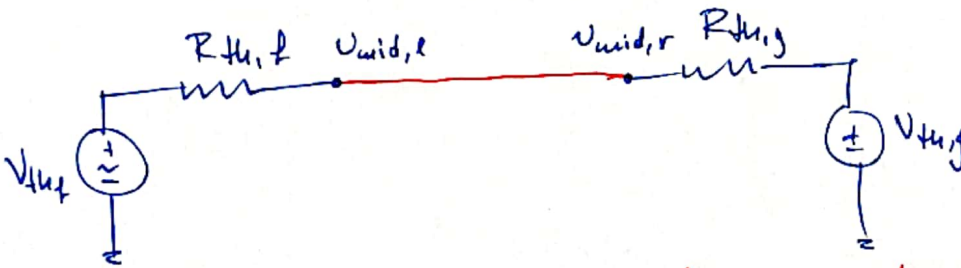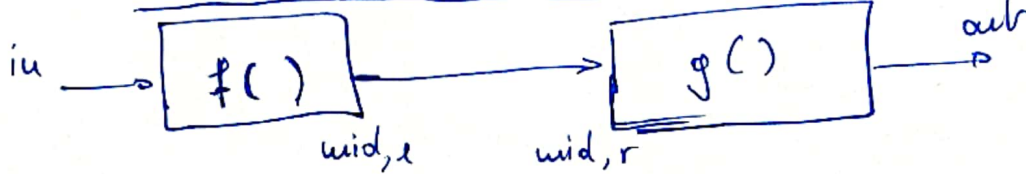

(most likely zero since we are looking at the in of block g())

Before connection:

$V_{mid,l} = V_{th,f}$

After connection:

$V_{mid,l} = V_{mid,r} = \frac{R_{th,g}}{R_{th,g} + R_{th,f}} V_{th,f} + \frac{R_{th,f}}{R_{th,g} + R_{th,f}} V_{th,g}$
in general


∴ except when: $R_{th,f} = 0$ (wire)

or $R_{th,g} = \infty$ (open-circuit)

Ideal Isolation




From the perspective of block f: see an open-circuit $R_{th,g} = \infty$

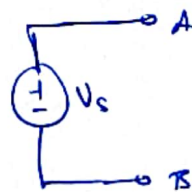From the perspective of block g: see a voltage source $V_{th,f} =$




$R_{th, \text{voltage source}} = 0$

P2

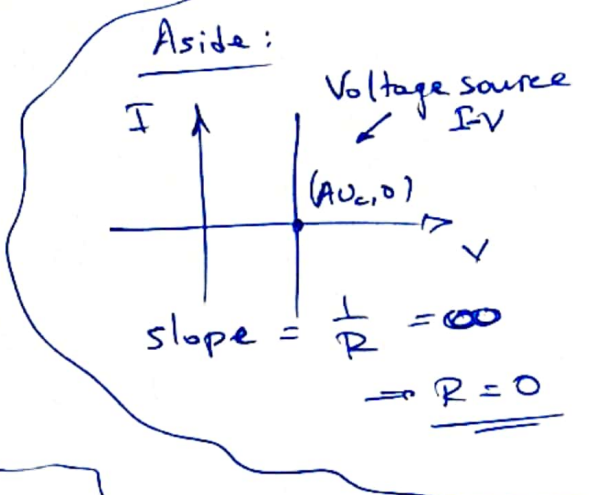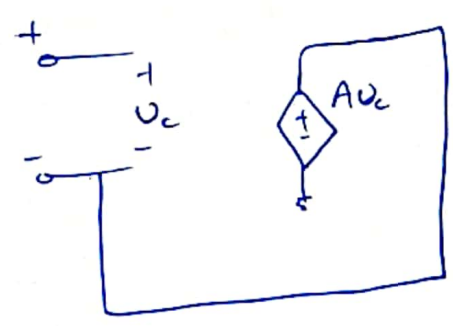
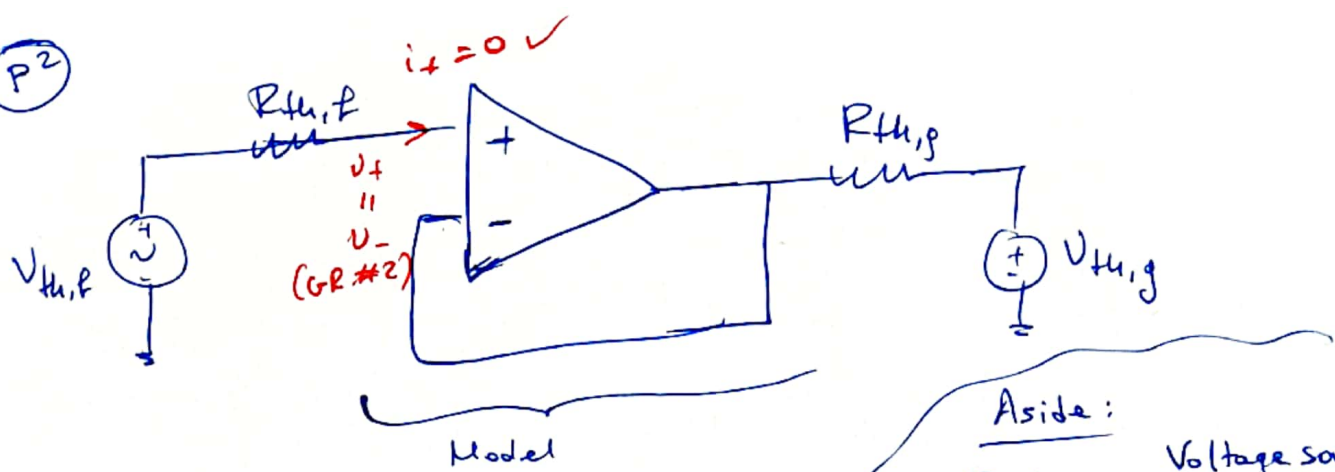


Aside 2 : For current in - current out :

Ideally :

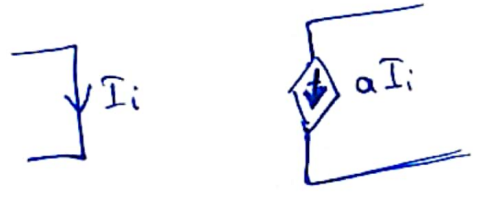


Example #1 : Want this:

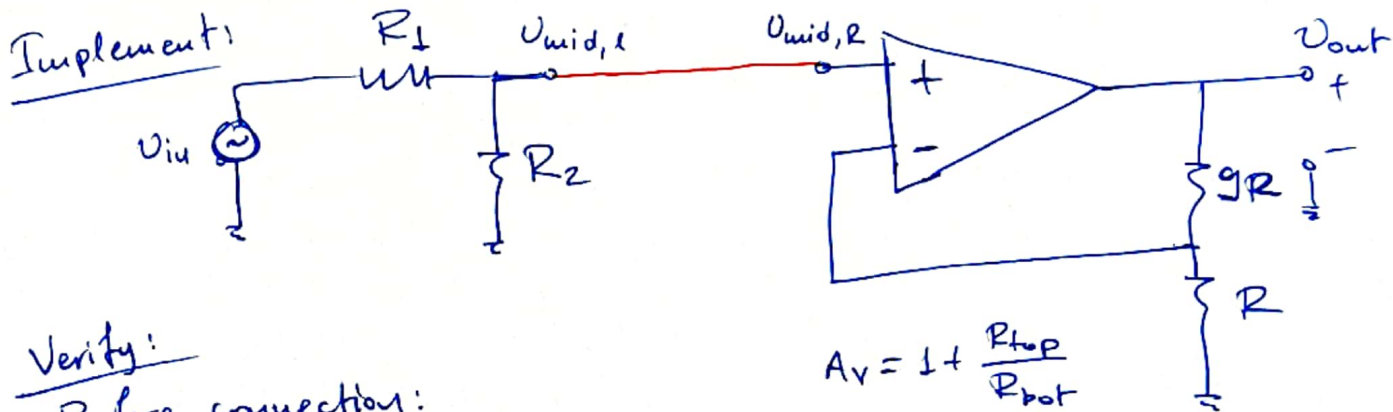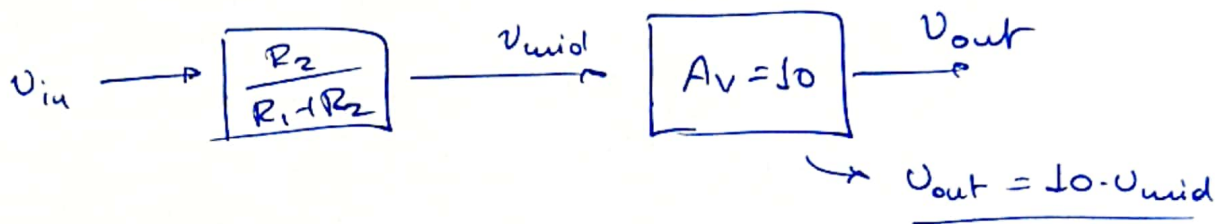


P4

Example #2: Want this:

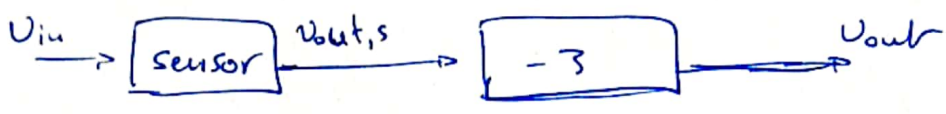

Implement:

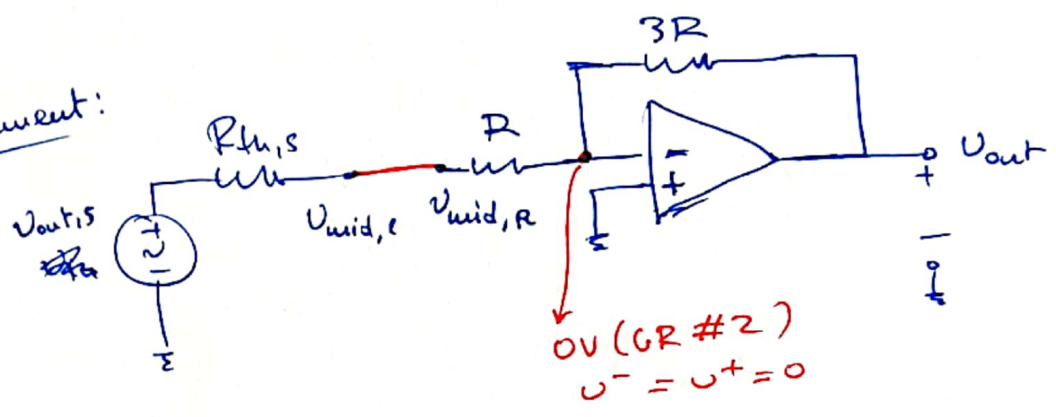


Verify: Before connection:

$$V_{mid,L} = V_{out,s}$$

After connection:


$$V_{mid,L} = V_{mid,R} = \frac{R}{R + R_{th,s}} \cdot V_{out,s} \neq V_{out,s} \therefore$$

Solution: Add a unity gain buffer

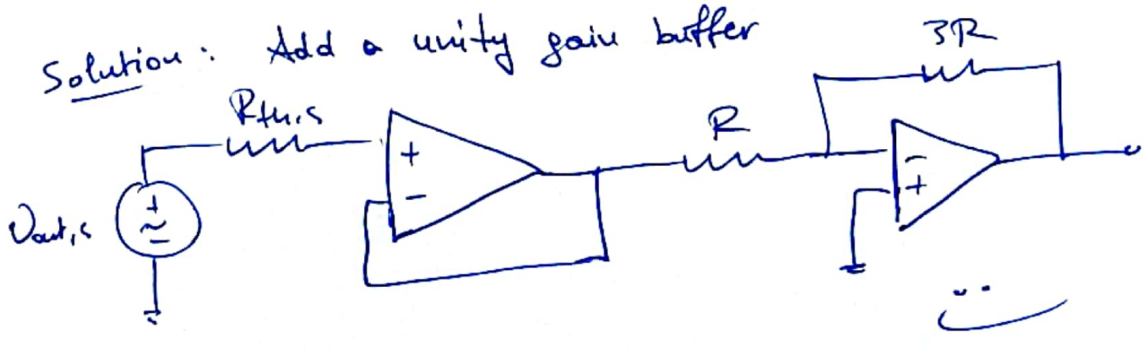



ps

Example #3

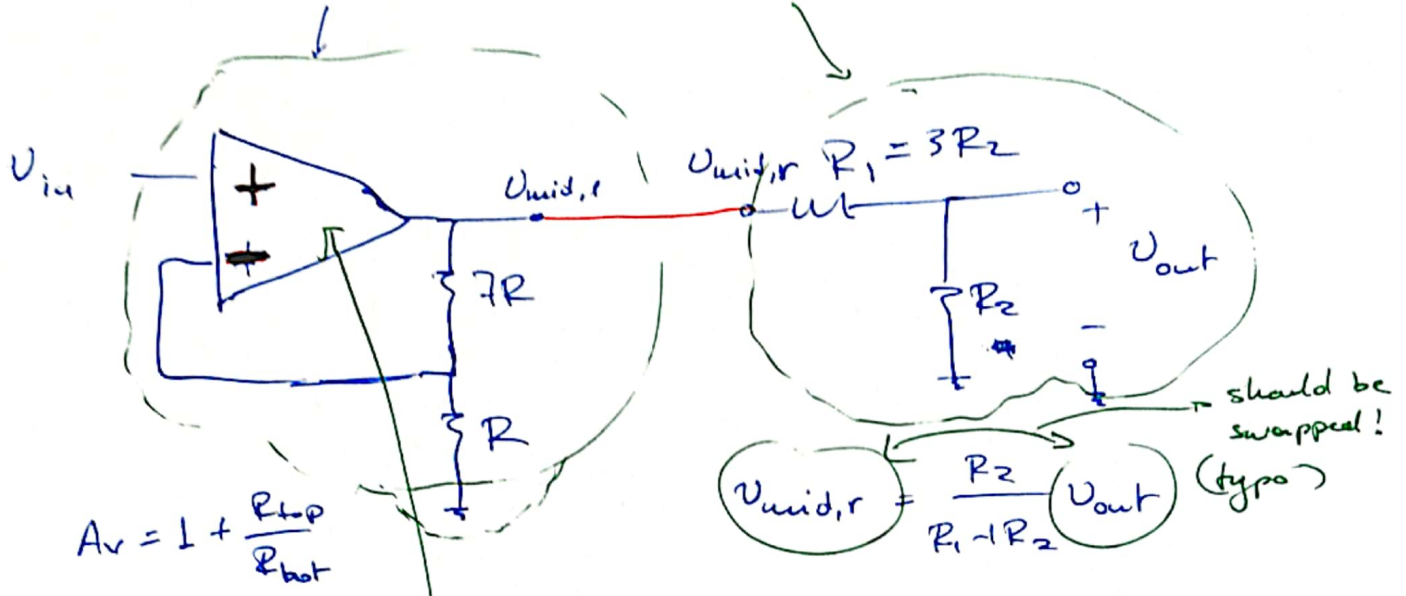

$V_{mid,r} = \frac{R_2}{R_1 + R_2} V_{out}$ (typo)

should be swapped!

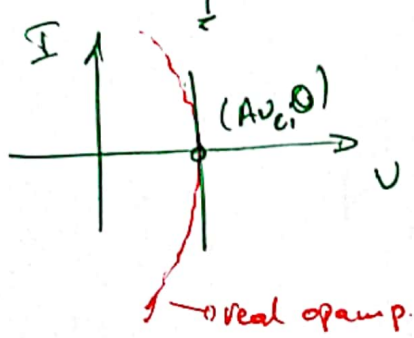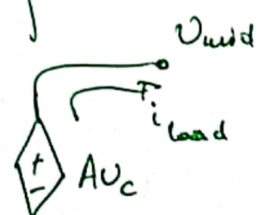

😊
Fine because $V_{mid,r}$ is set by A_{vc} (voltage source)

After conn.:

$V_{mid,r} = V_{mid} = V_{in} \cdot 8 \checkmark$
 $V_{out} = 8 \cdot \frac{1}{4} \cdot V_{in} \checkmark$

Design Procedure

Step 1: Concretely (re)-state your goal for the design
(specification) (most often from a word spec)

Step 2: Describe (often as a block diagram) the strategy
(Strategy) to achieve the goal.

↳ review what you can measure vs what you wanted to know

↳ what is the relationship between the two (e.g. touch / no-touch)




Step 3: Implement the components within the strategy
(Implementation) ↳ Remind yourself of you know what can provide the desired block diagram function.


↳ Think about how do extend/modify the blocks for know (attempt #1000)

Step 4: Does the implementation in step 3 do what is specified in step 1?
(Verification/analysis) ↳ check for block-to-block connections

97 Example Design #1 Countdown timer

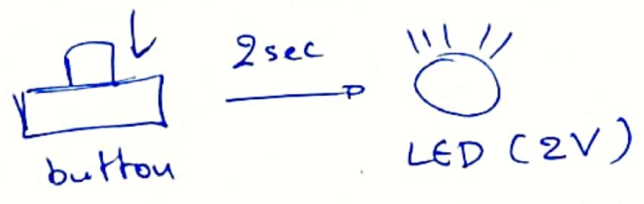

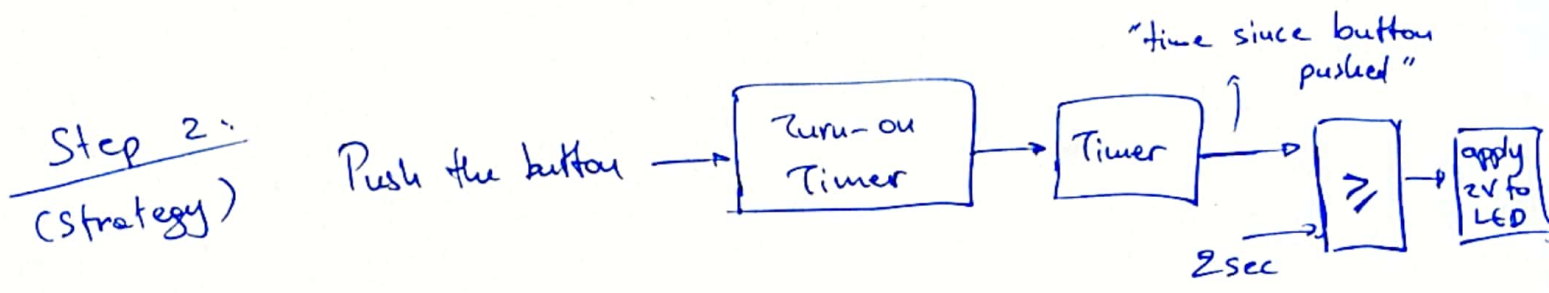Step 1:
(Specification) Build a circuit that after a button is pushed measure 2s and then applies 2V across an LED. (I assume you can only push the button once).



Step 3:
(Implementation)



Timer:

