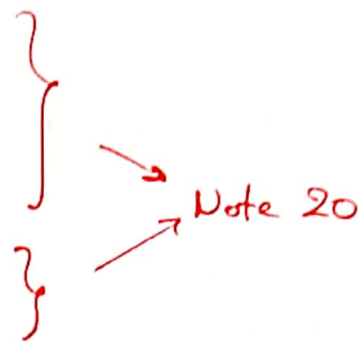


- Last time:
- * Safely Cascading Ckt Blocks
 - * Design Procedure
 - * Design Examples




- Today:
- * Design Examples (cont.)

Countdown Timer Circuit (cont.)



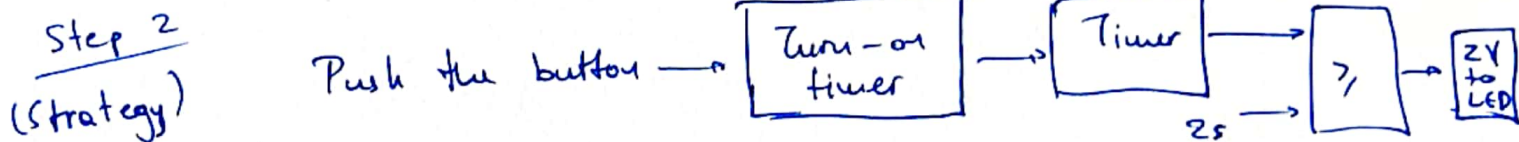
Step 1: (Specification) Build a circuit that after a button is pushed measures 2s and then applies 2V to an LED




Step 3: (Implementation)

Turn-on ckt: (switch)


Timer:

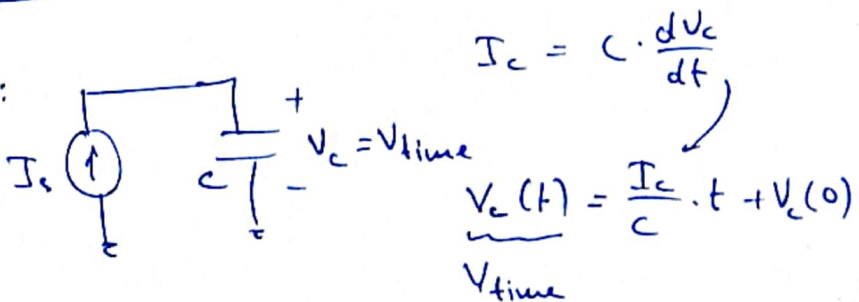

>

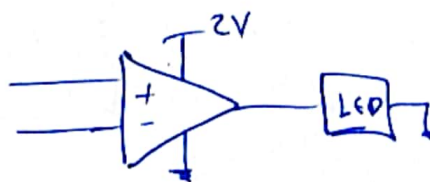

P2 Putting it all together:

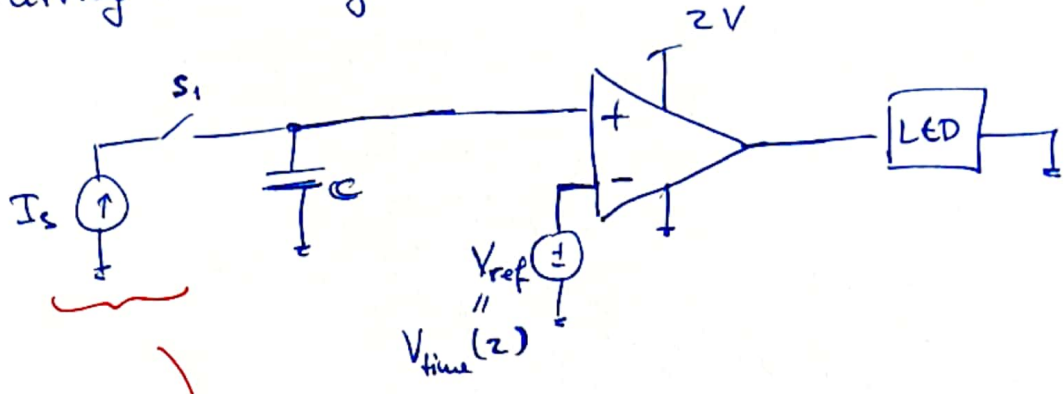


Step 4:
(Verify)

$$V_c(t) = V_{time} = \frac{I_s}{C} \cdot t + V_c(0)$$

Prob. #1
? unknown

Before button pushed:

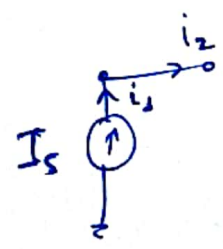

current source

$i_1 = I_s$ (element I-V relationship)
 $i_2 = 0$ (element open-ckt) —||—)


KCL: $i_1 = i_2$

Prob. #2

$\hookrightarrow I_s = 0$ contradiction/inconsistency.


- Solutions:
- a) Shut-off the I_s when S_1 is OFF (impose a safe voltage limit across I_s)
 - b) Reconfigure the switch

Revisit
Step 3
(Implem.)

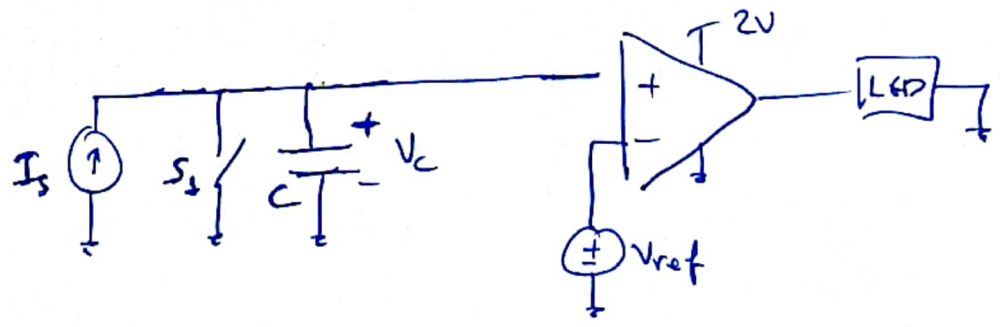


P3
Step 4
 (Verification)

Before button pushed:

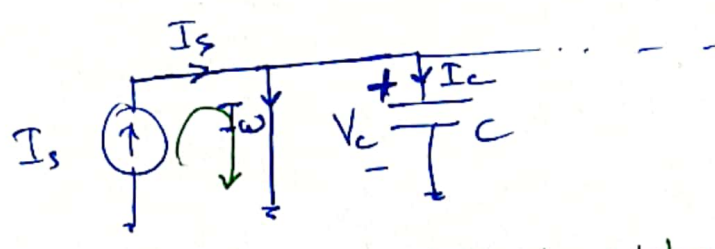

$I_w = I_s$ (path of least resistance)

After button pushed: (assuming at $t=0$)

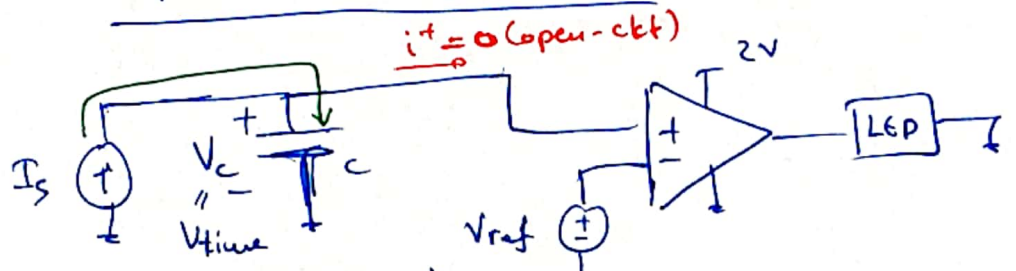

$$V_c(t) = V_{time}(t) = \frac{I_s t}{C} + V_c(0)$$

$$V_{ref} = V_c(2) = \frac{I_s}{C} \cdot 2 \quad \checkmark$$

☺


Pr4 Example Design #2 : Current Source.

Step 1:
(Specification) Build a circuit that can create a constant current through its output terminals regardless of the voltage across them.

To do so you can use opamps, voltage sources and resistors.

Step 2:
(Strategy) Ohm's law: $V = I \cdot R \Rightarrow I = \frac{V}{R} \rightarrow$ make constant

Step 3:
(Implementation)

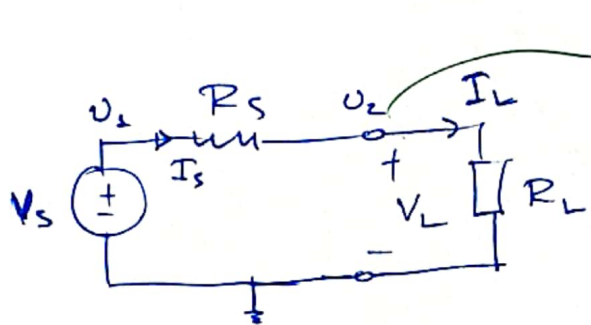


What if I could fix this voltage at 0V?

Step 4:
(Verify) Ohm's law: $I_s = \frac{V_{R_s}}{R_s} = \frac{v_1 - v_2}{R_s} = \frac{V_s - V_L}{R_s}$

KCL: $I_s = I_L = \frac{V_s - V_L}{R_s} = f(V_L)$

since I wanted I_L indep. of V_L

Revisit Step 3:
(Implem.)

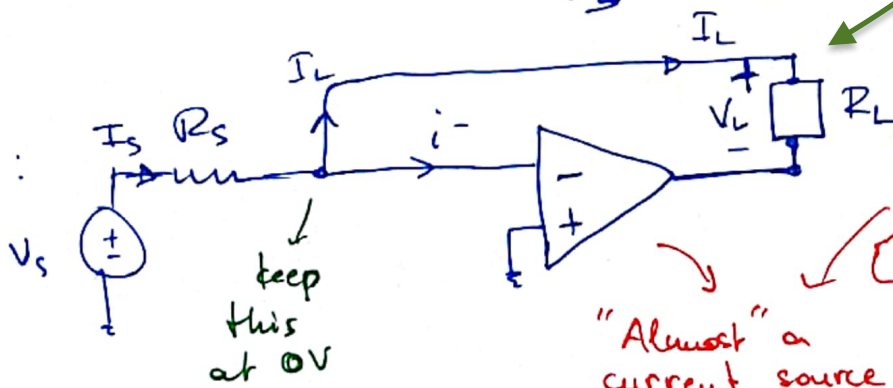

Caveats:

- 1) Op-Amp needs to be in UFS.
- 2) $v^- = 0$ may have implications for the rest of the ckt

"Almost" a current source


Step 4:
(Verify) $I_s = \frac{V_s}{R_s}$ (Ohm's law)
KCL at v^- : $I_s = I_L + i^- \rightarrow 0$ (GR #1)

$\Rightarrow I_L = \frac{V_s}{R_s} \neq f(V_L) \quad \ddot{\smile}$

RPS

Let's tie it back to our timer circuit:


Step 3: (Implem.)

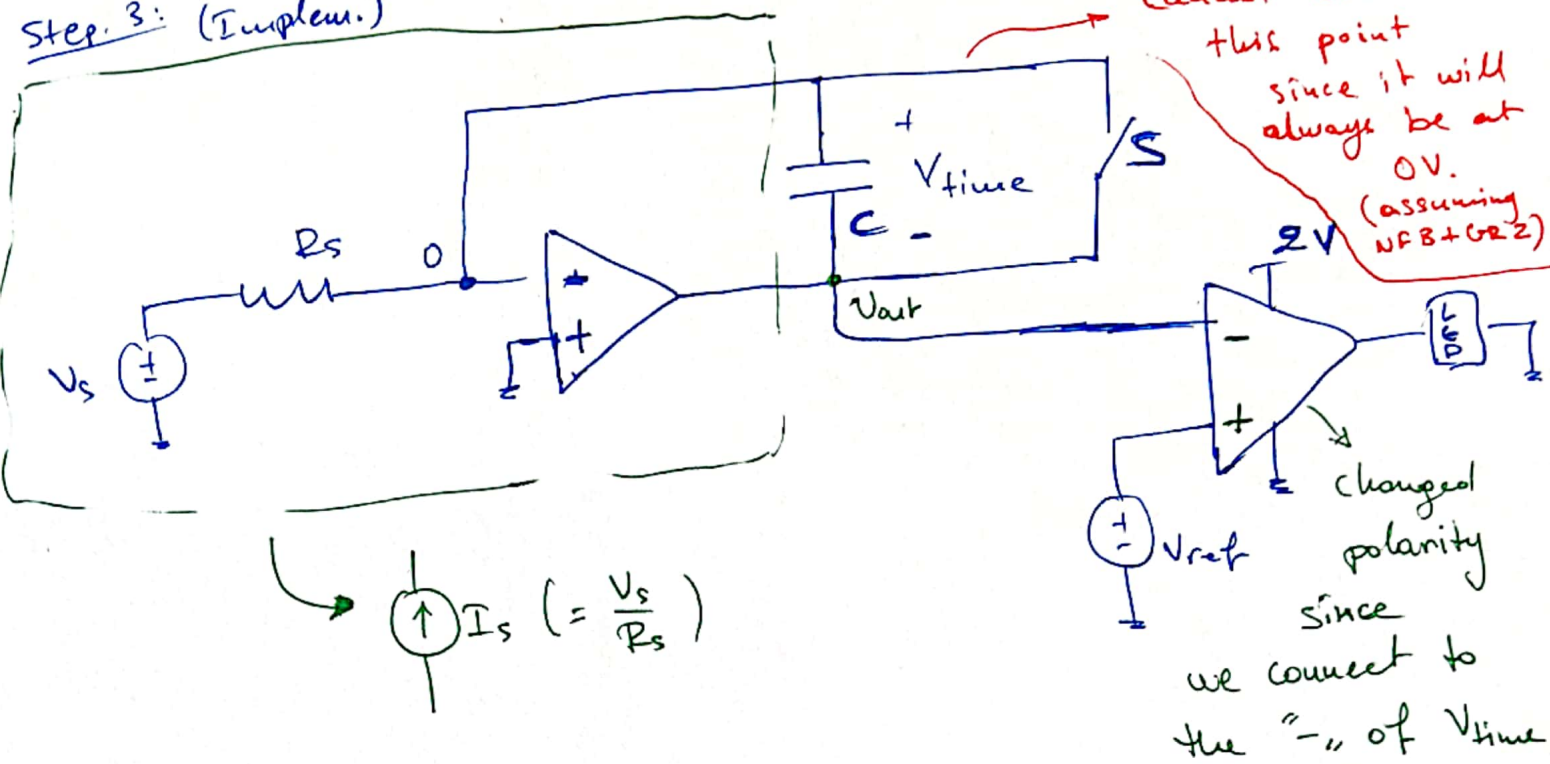

$I_s (= \frac{V_s}{R_s})$


Step 4:

(Verify) Check for NFB:

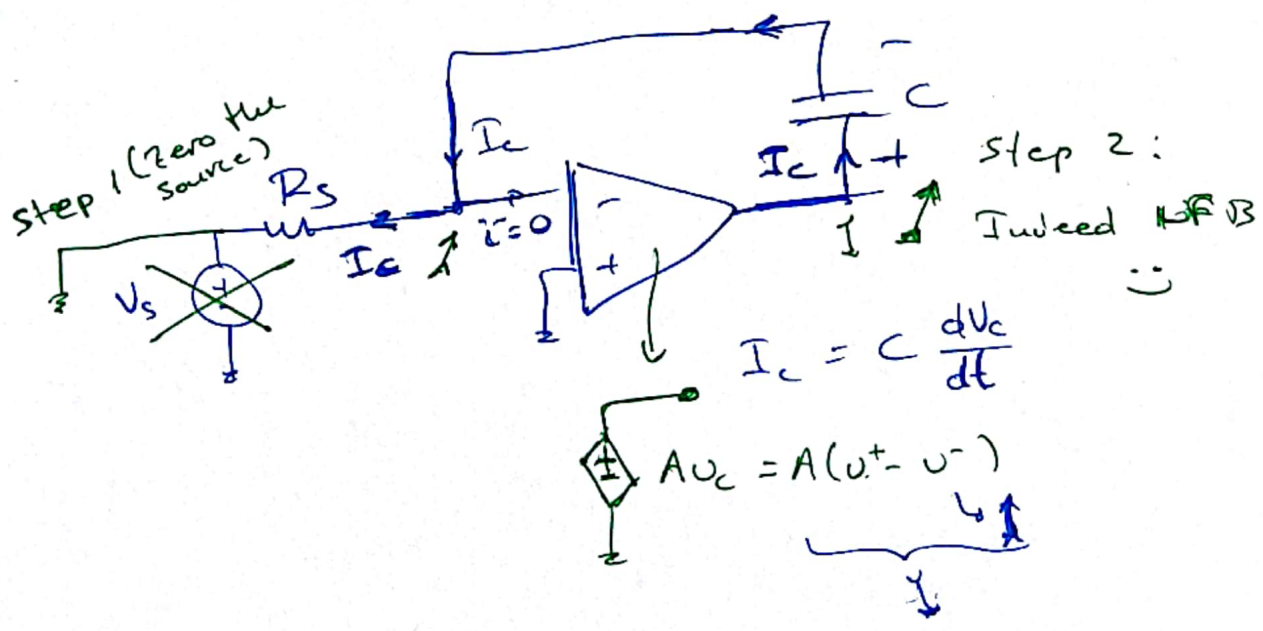

P6

Thoroughly checking for NFB:

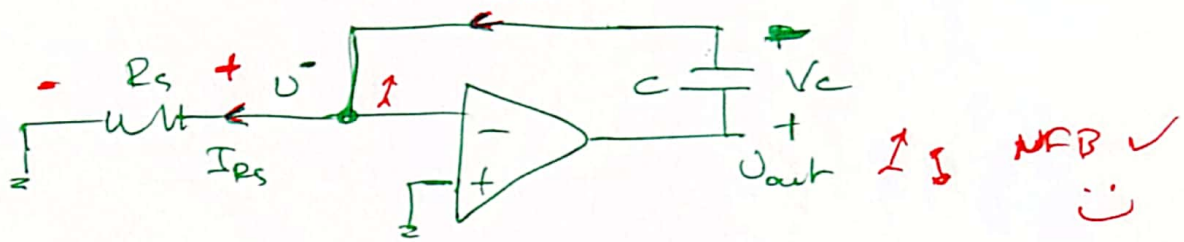

Steady state: i.e. all voltages are constant.

$$I_{R_s} = \frac{u^- - 0}{R_s} = \text{const.} \quad (1)$$

$$I_c = I_{R_s} \quad \text{(KCL)} \quad (2)$$


$$I_c = C \cdot \frac{dV_c}{dt} = 0 \quad (3)$$

$$(2) \stackrel{(3)}{\Rightarrow} I_{R_s} = 0 \stackrel{(1)}{\Rightarrow} \underline{\underline{u^- = 0}}$$

→ At steady state $u^- = 0$ w/o assuming NFB?

$$I_c = I_{R_s} \Rightarrow u^- = I_{R_s} \cdot R_s > 0$$

P7

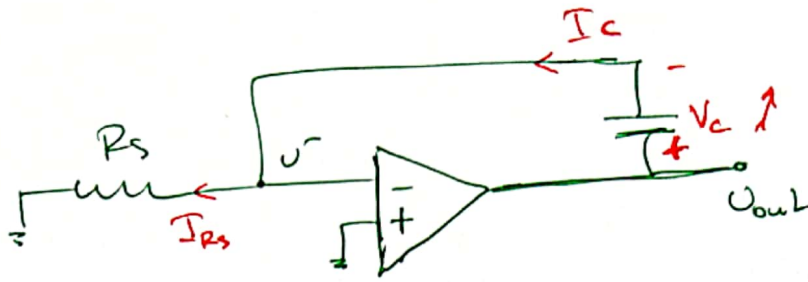

Since $v^- = 0$ at steady state let's "yank" the output \uparrow


~~$I_c = C \frac{dv_c}{dt}$~~ $I_c = C \cdot \frac{dv_c}{dt}$ (Since $v_{out} \uparrow$ I_c has to obey passive sign convention and follow the ckt diagram direction).

KCL at v^- :

$I_c = I_{R_s}$ (no current into the opamp) GR #1

$v^- = 0 = I_{R_s} R_s \Rightarrow v^- \neq 0 \Rightarrow v^- \uparrow \Rightarrow v_{out} \downarrow \Rightarrow$ NFB

Aside:

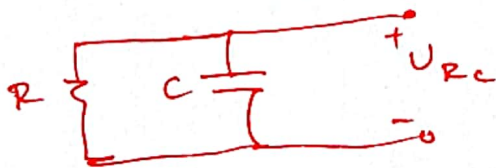

At steady state:

$V_{RC} = 0$
more in ΔB !