

Module 2, Lecture 12


EECS 16A
Pavlos Zarkos

TOPIC REVIEW:

- * Fundamentals
- * NVA
- * Power, I & V Measurements
- * Resistor & Capacitor Physics
- * Thevenin and Norton equiv
 - Dep. Sources
 - // + series
- * Op Amps
 - NFB
 - Comparators
- * Charge Sharing
- * Practice Problems

Fundamentals:

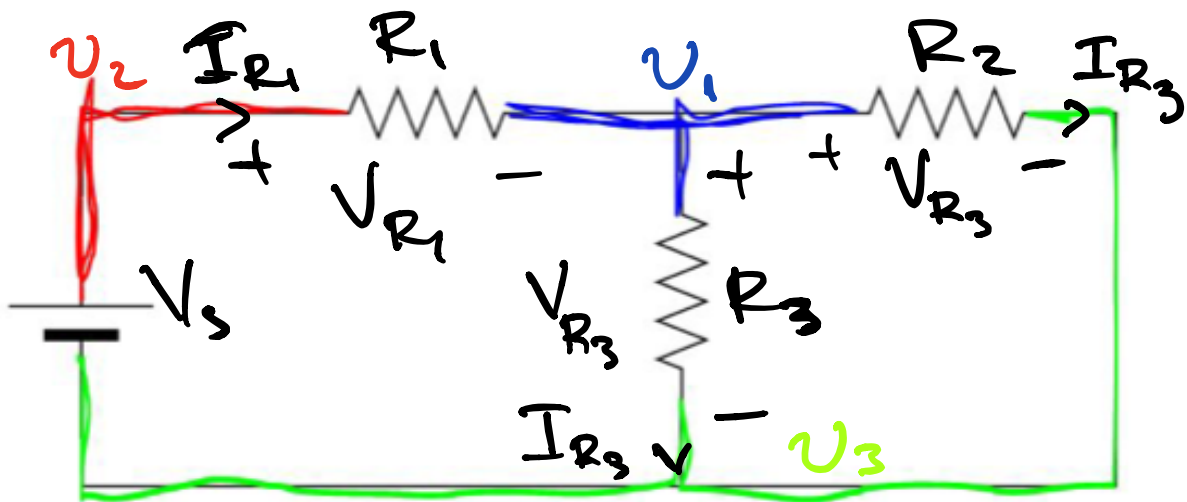Voltages & Currents } Lec 2D
Nodes & Branches } Note 11



Node: Any point where 2 or more elements intersect.


e.g. $V_{R_1} = U_2 - U_1$

Node Voltage Analysis

Knowns: Source values, Resistor values

Unknowns: Node voltages

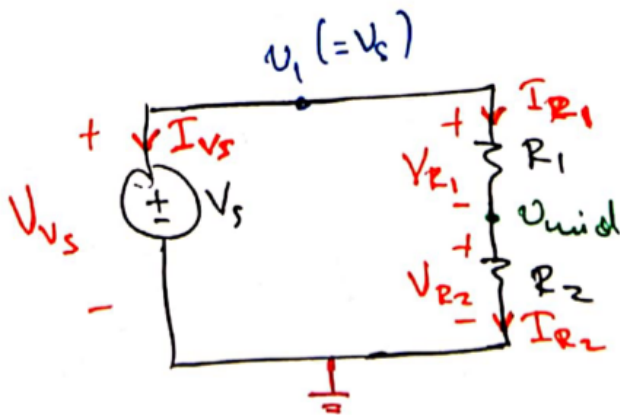
1. Select a reference node
2. Label nodes with known voltages
3. Label remaining nodes
4. Label element voltages & currents, following passive sign convention
5. Write KCL Equations at each unknown node voltage
6. Write Element Current Equations
7. Substitute Element Currents into KCL equations
8. Solve!



$$\underline{\underline{v_{mid} = \frac{R_2}{R_1 + R_2} \cdot V_s}}$$

Universal algorithm:
never fails!

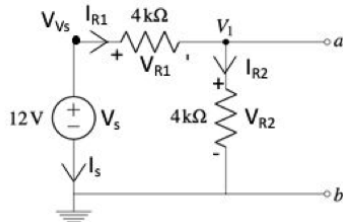Labeling elements: What if we flip the current directions?



KCL:

$$I_{R1} = I_{R2} \quad I_{R1} - I_{R2} = 0$$


Element Equations:

$$I_{R1} = \frac{V_{R1}}{4k\Omega} = \frac{V_{Vs} - V_1}{4k\Omega}$$

$$I_{R2} = \frac{V_{R2}}{4k\Omega} = \frac{V_1 - 0}{4k\Omega}$$

Substituting element equations into KCL:
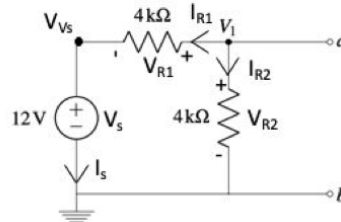
$$\frac{V_{Vs} - V_1}{4k\Omega} = \left(\frac{V_1 - 0}{4k\Omega} \right)$$



KCL:

$$I_{R1} + I_{R2} = 0$$

Element Equations:

$$I_{R1} = \frac{V_{R1}}{4k\Omega} = \frac{V_1 - V_{Vs}}{4k\Omega}$$

$$I_{R2} = \frac{V_{R2}}{4k\Omega} = \frac{V_1 - 0}{4k\Omega}$$

Substituting element equations into KCL:

$$0 = \left(\frac{V_1 - 0}{4k\Omega} \right) + \frac{V_1 - V_{Vs}}{4k\Omega}$$

Notice that if we rearrange the equations a bit, they should give the same solution for V_1 .

I_{R1} will be equal in magnitude but negative, however, the "real" direction of the current is the same


Common Practice:

Invoke already done analysis results on "common" ckt that show up often:

⇓ Dividers
(Voltage, Current)

Voltage Divider

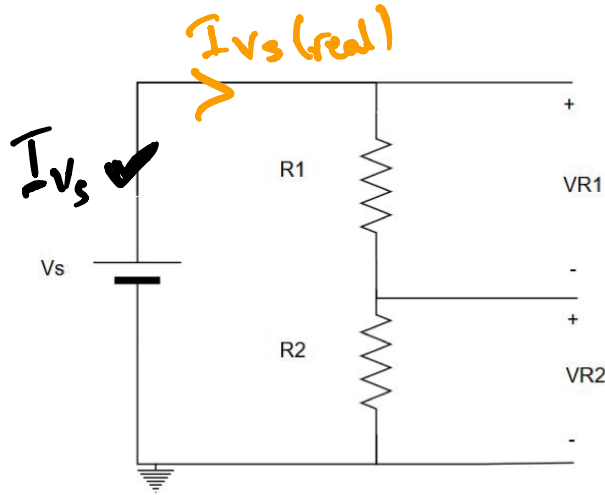Note, the resistors MUST be in SERIES to use this equation




$$V_{R1} = V_s \frac{R_1}{R_1 + R_2}$$

$$V_{R2} = V_s \frac{R_2}{R_1 + R_2}$$

Current Divider

Note, the resistors MUST be in PARALLEL to use this equation

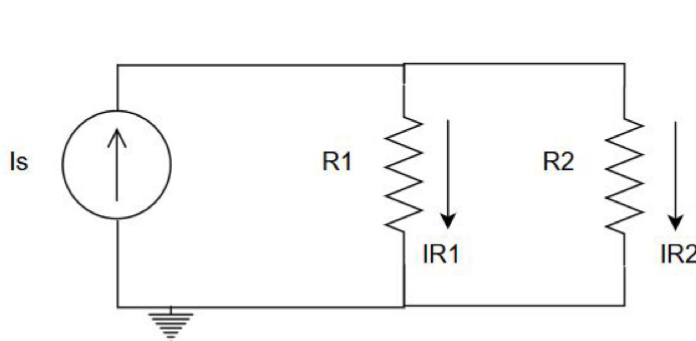
Also note that the resistor in the numerator is opposite of the one you'd expect. Intuitively, path of least resistance*.



$$I_{R1} = I_s \frac{R_2}{R_1 + R_2}$$

$$I_{R2} = I_s \frac{R_1}{R_1 + R_2}$$

Power:

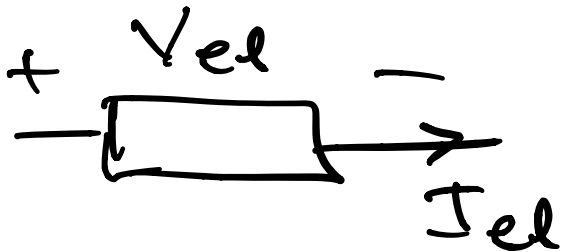

$$P_{el} = V_{el} \cdot I_{el}$$

ALWAYS!

$$P_{el} > 0 \Rightarrow$$

- 1) Element **dissipates** power
- 2) It **follows** passive sign convention
- 3) It is **"passive"**

$$V_{el} > 0, I_{el} > 0 \}$$

$$V_{el} < 0, I_{el} < 0 \}$$

$$V_{el} > 0, I_{el} < 0 \}$$

$$V_{el} < 0, I_{el} > 0 \}$$

$$P_{el} < 0 \Rightarrow$$

- 1) Element **generates** power
- 2) It **"violates"** passive sign convention
- 3) It is **"active"**

(i.e. current flows out of the "+" in reality)
e.g. in voltage source + resistors

* For Resistors :

$$P_R = I_R V_R = I_R^2 R = \frac{V_R^2}{R} \geq 0$$

⇒ A resistor always
dissipates power!

* Power is always
conserved!

$$P_{el,tot} = 0$$




V & I Measurements:

Ideal Measurement Device
Should dissipate 0 power

Ref: Lec 3B - Note 13

(P3)

Voltage Measurement

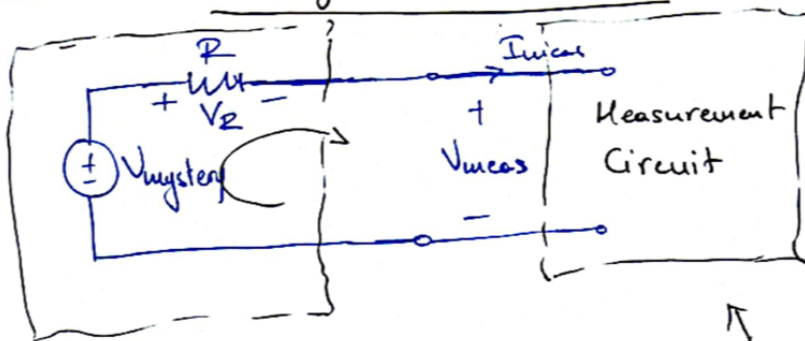

Goal:

Measure $V_{mystery}$
i.e. $V_{meas} = V_{mystery}$

Problem:

R is "in the way"

$$\text{KVL: } V_{mystery} - V_R - V_{meas} = 0$$


$$\Rightarrow V_{mystery} = I_{meas} \cdot R + V_{meas}$$

$$\Rightarrow V_{mystery} = V_{meas} \quad \text{if } I_{meas} = 0$$

measurement circuit
needs to look like
an open-circuit

PS

Current Measurement

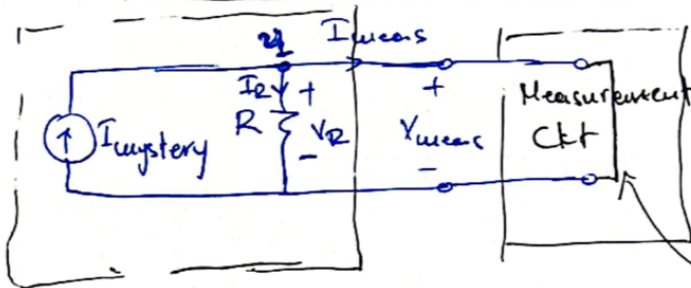

Goal:

Measure $I_{mystery}$
i.e. $I_{meas} = I_{mystery}$

Problem:

R is "in the way"

$$\text{KCL on } v_1: I_{mystery} = I_R + I_{meas}$$

$$\Rightarrow I_{mystery} = \frac{V_{meas}}{R} + I_{meas}$$

$$\Rightarrow I_{mystery} = I_{meas} \text{ if } V_{meas} = 0$$


needs to look
like a
wire

$$P_{meas} = \cancel{V_{meas}} \cdot I_{meas} = 0 \quad \checkmark \quad (\text{measurement ckt does not dissipate any power})$$

Disclaimer:


If approximations are required we will explicitly tell you so in an exam. (i.e. $\frac{R_{VM} \cdot R_x}{R_{VM} + R_x} \rightarrow R_x$ if $R_{VM} \rightarrow \infty$)

Resistors and Capacitors

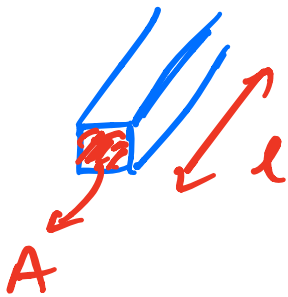

$$R = \rho \cdot \frac{l}{A}$$

↓
material
resistivity

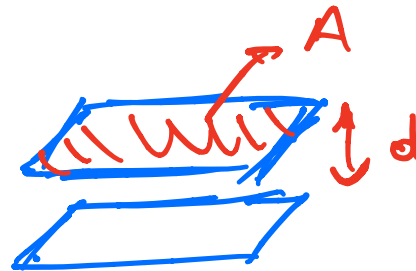

$$C = \epsilon \cdot \frac{A}{d}$$

↓
material (insulator)
permittivity

Superposition


Def of linear: $T(ax + by) = aT(x) + bT(y)$

The passive components we use have linear I-V relations, so we can solve for the effect of each source individually and add the responses to get the same result.


When to use? When you have **multiple sources** and **considering all at the same time is confusing**

Note: you can solve any circuit in this class without superposition with just normal nodal analysis.

Zero a voltage source

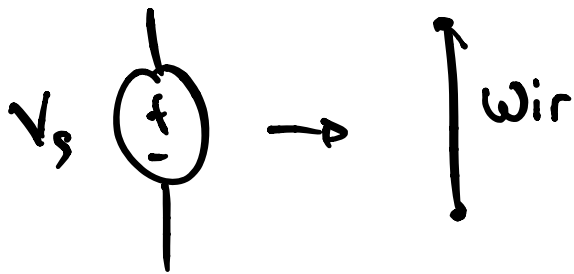


Zero a current source

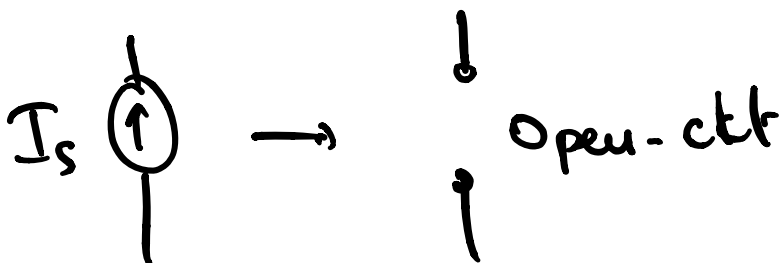

Series?


Two ways to tell if components are in series:

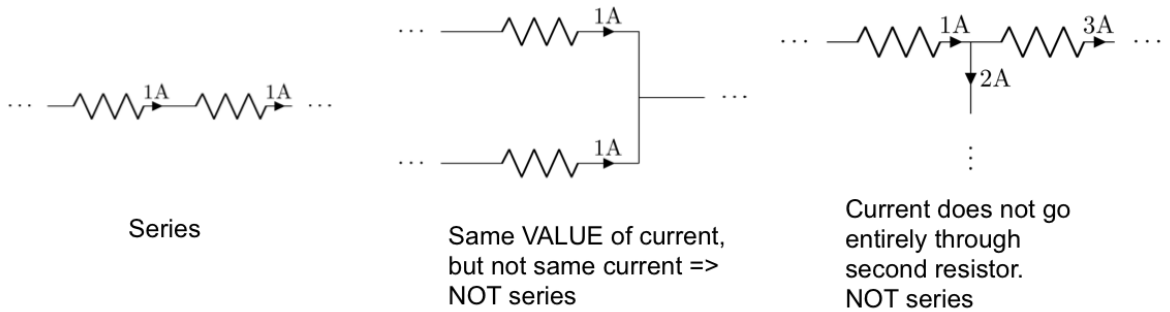1. same EXACT current. Not same value of current, but same exact current through elements by KCL. If the current can split off then they aren't series!
2. **If two and only two elements are connected to a single node** (no other elements are connected to that node), the elements are in series.




Parallel?

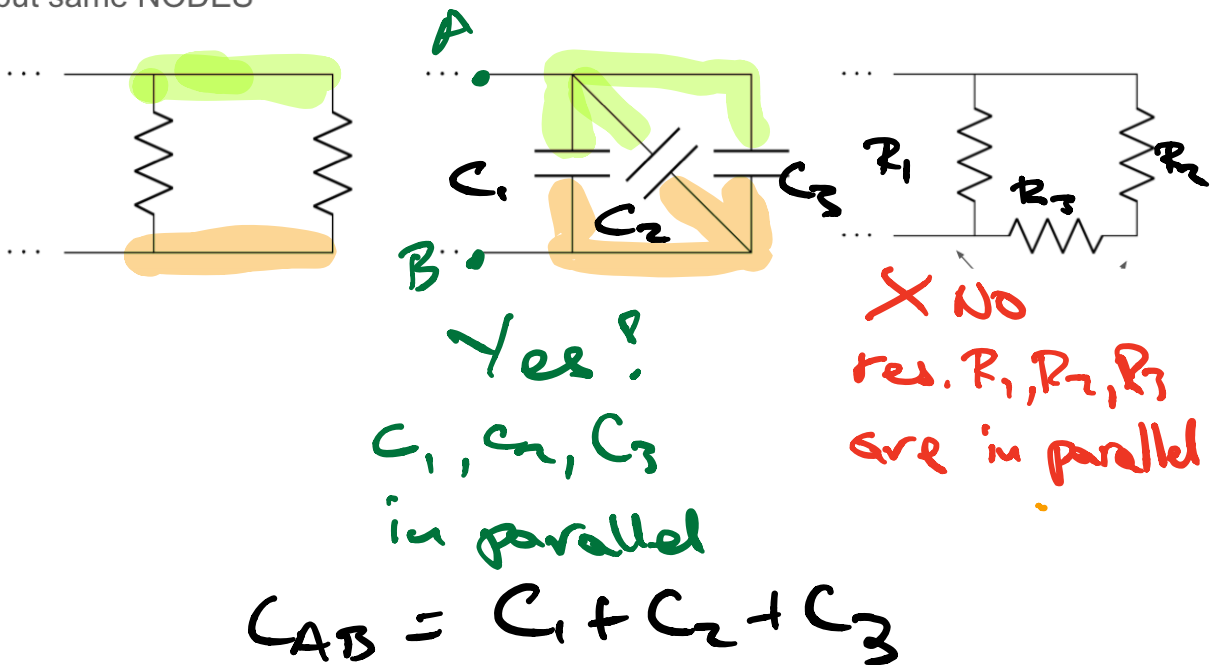Parallel: they share the same NODES on either side. Not just the same voltage, but same NODES



Resistors

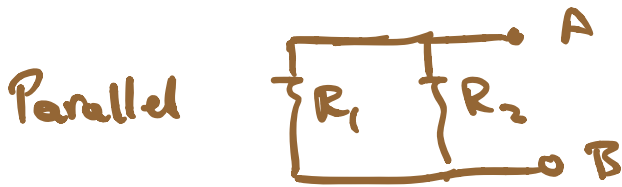

$$R_{AB} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$


Capacitors




$$C_{AB} = C_1 + C_2$$




$$R_{AB} = R_1 + R_2$$

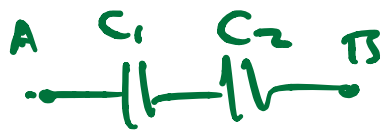
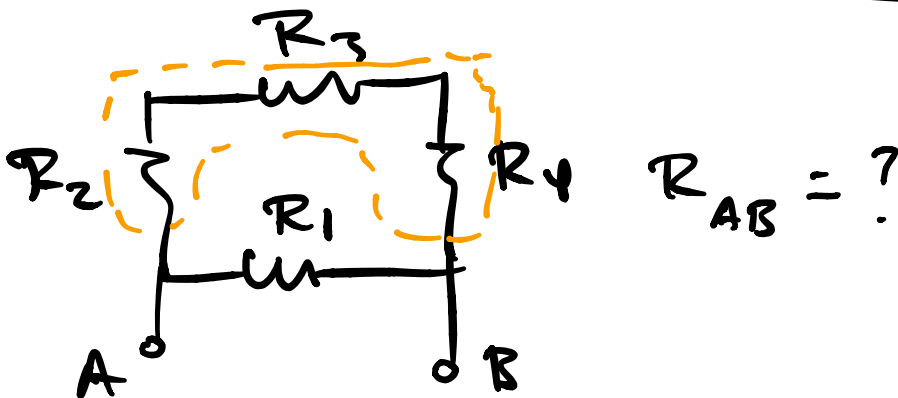
$$C_{AB} = C_1 \parallel C_2 = \frac{C_1 C_2}{C_1 + C_2}$$




$$R_5 = R_2 + R_3 + R_4$$

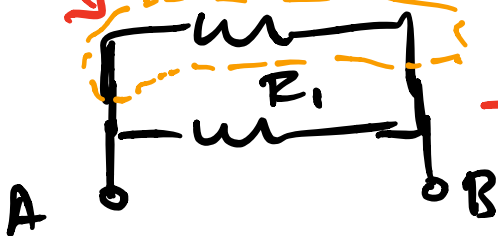

$$R_{AB} = R_1 \parallel R_5$$

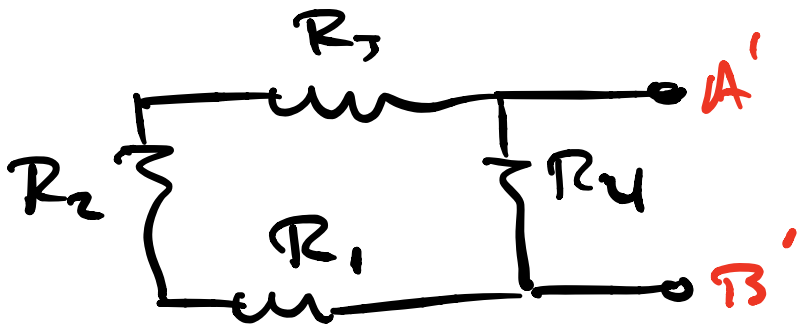
Note: R_{eq} depends on where I connect my terminals:



$$R_{A'B'} = R_4 \parallel (R_1 + R_2 + R_3)$$





$\neq R_{AB}$ from above

Capacitor Example

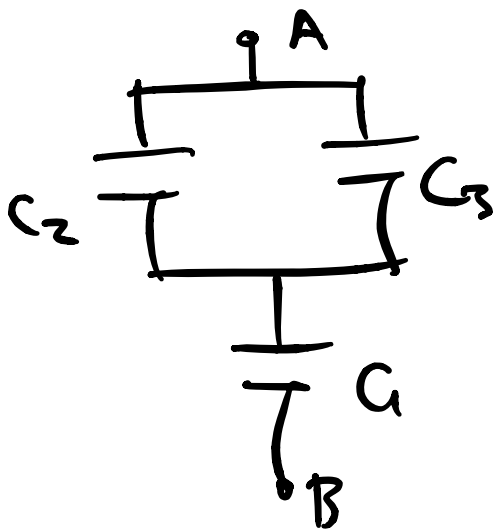

$$C_{AB} = C_1 \parallel (C_2 + C_3)$$

Thevenin and Norton Equiv.:

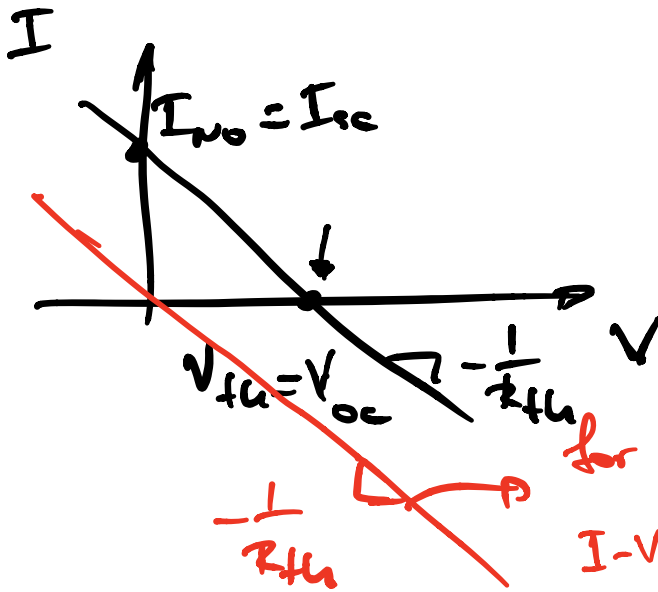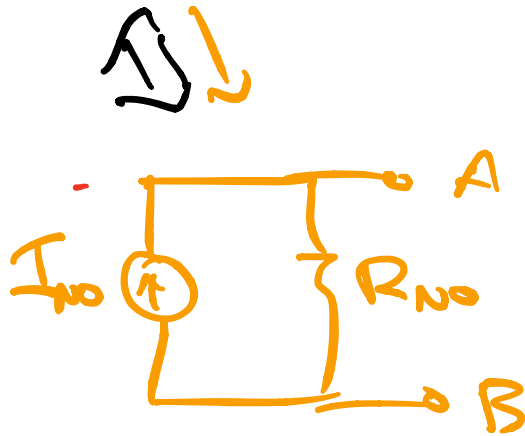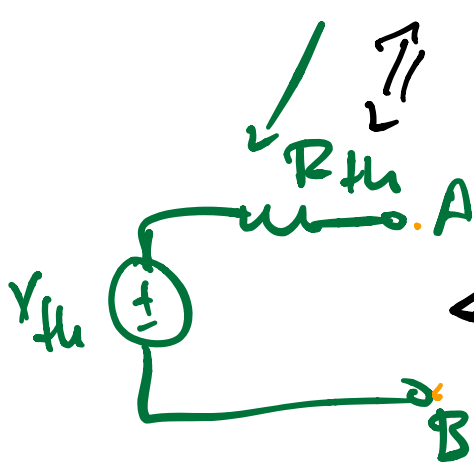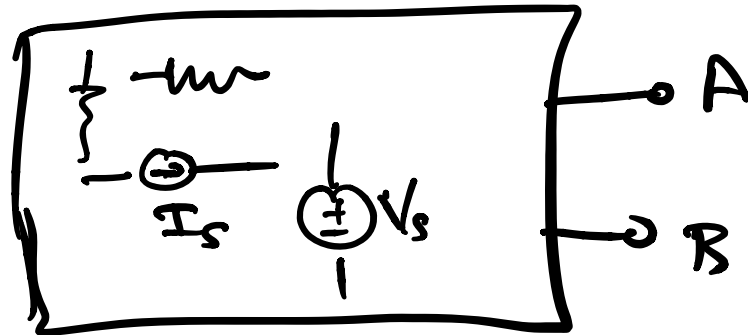

1) $V_{th} = I_{no} \cdot R_{no}$

2) $I_{no} = \frac{V_{th}}{R_{th}}$

3) $R_{th} = R_{no}$

for resistive only ckt's

I-V goes through the origin

Finding Thevenin + Norton Equiv.:

1) Find V_{th} by open-circuiting the terminals A-B and finding $V_{oc} = V_{th}$

How: NVA or Superposition


2) Find I_{No} by short-circuiting the terminals A-B (i.e. connect them with a wire) and find $I_{sc} = I_{No}$

How: NVA or Superposition

3) Find R_{th} :

How: 3 options \rightarrow pick the easiest!

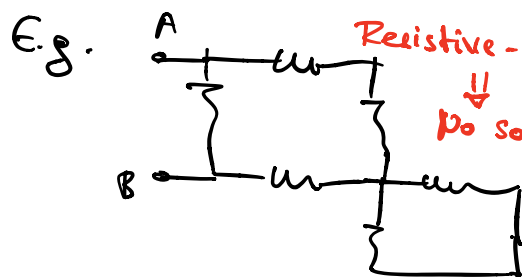a) $R_{th} = V_{th} / I_{No}$ \rightarrow fails with res. only ckt where $V_{th} = I_{No} = 0$ *



\Downarrow
no source \rightarrow cannot apply method a)

since $V_{th} = I_{No} = 0$

b) Use // and series combination with independent source zeroed-out

↳ fastest 😊

→ fails when dep. sources are not zeroed out (see ex. below)

c) Use $V_{test} - I_{test}$ method with independent sources zeroed



→ (ALWAYS WORKS) 😊

↳ But takes the longest 😊

Procedure:

With Indep. Sources zeroed-out

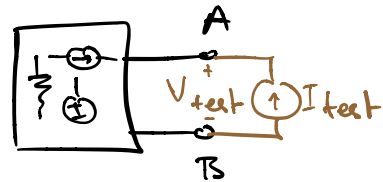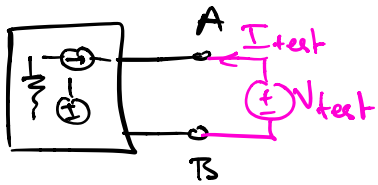
Apply $V_{test} \rightarrow$ measure I_{test} OR Apply $I_{test} \rightarrow$ measure V_{test}



$$R_{th} = \frac{V_{test}}{I_{test}}$$

Dependent Sources:

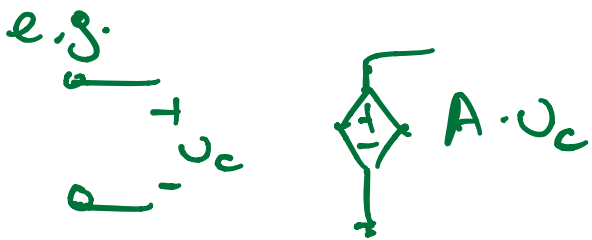
Model Some Complicated
Circuit Element in our "Black
Box" ckt (e.g. transistors, opamps)



Should not be shut off when
finding R_{th} .


Independent Sources:

Inputs to our ckt.

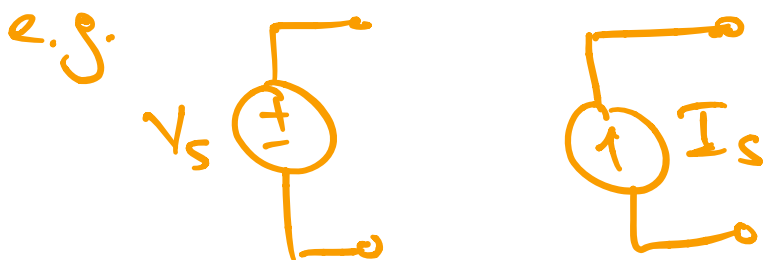

Find V_{th} , R_{th} looking into terminals C,D:
 Disclaimer: g has units of $\frac{1}{\Omega}$

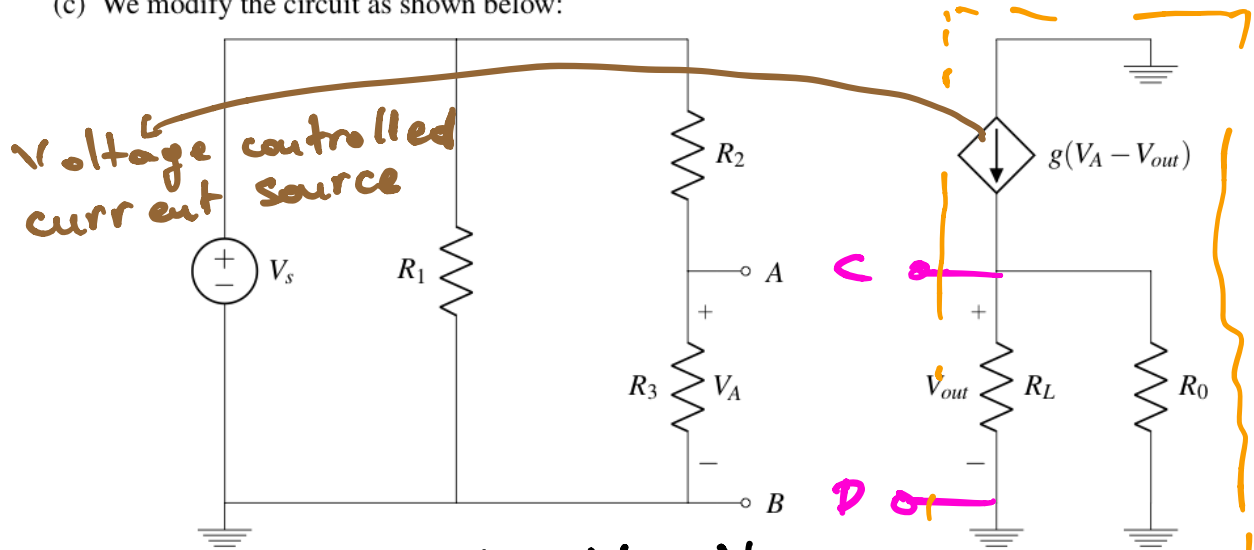(c) We modify the circuit as shown below:



Step 1: Find $V_{th} = V_{oc} = V_{out}$


$$V_{AB} = V_A = \frac{R_3}{R_3 + R_2} \cdot V_s \quad (1)$$

$$V_{out} = g(V_A - V_{out}) \cdot R_L \parallel R_0$$

$$\Rightarrow V_{out} = \frac{g \cdot R_L \parallel R_0}{1 + g R_L \parallel R_0} \cdot V_A$$

$$\stackrel{(1)}{=} \frac{g R_L \parallel R_0}{1 + g R_L \parallel R_0} \cdot \frac{R_3}{R_3 + R_2} \cdot V_s$$


$$V_{out} = V_{oc} = V_{th}$$

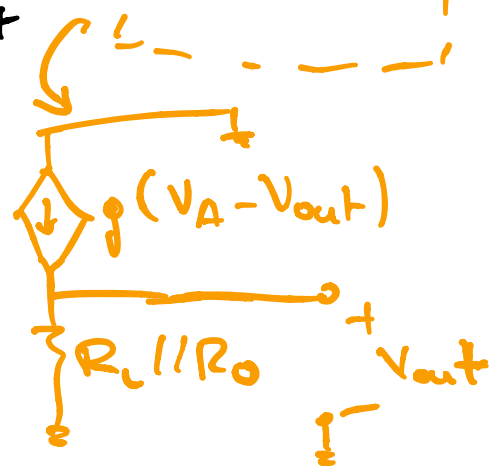

Step 2: Find R_{th}

a) zero out indep. sources

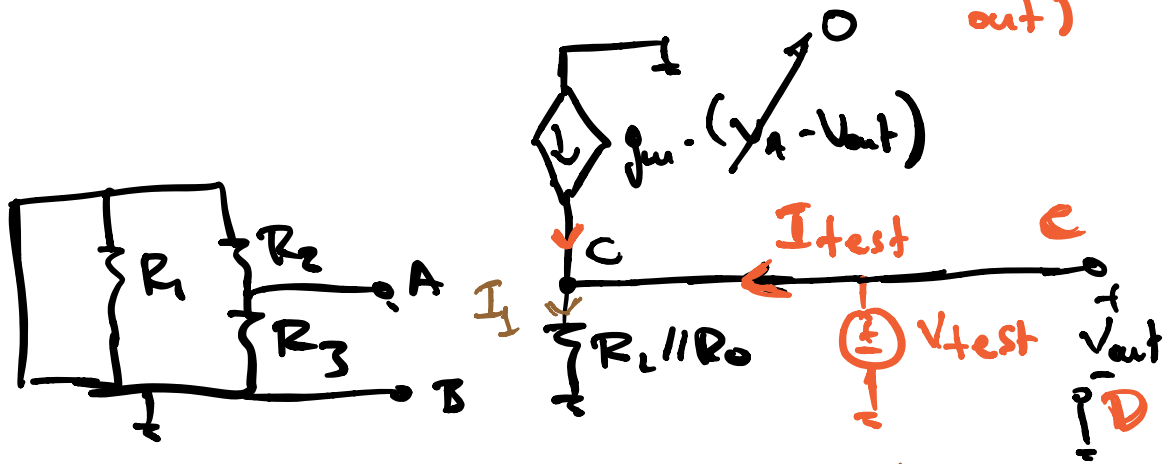b) Apply V_{test} and measure I_{test} using NVA. (I need to do this here since the dep. source is not zeroed out)



KCL: $I_{test} + g_m(-V_{out}) - I_1 = 0$
 (on node C) entering exiting


$$I_{test} + g_m(-V_{out}) - V_{out}/R_L // R_o = 0$$

$$\Rightarrow -\left(g_m + \frac{1}{R_L // R_o}\right) \cdot V_{test} = -I_{test}$$

$$\Rightarrow \frac{V_{test}}{I_{test}} = \frac{1}{g_m + \frac{1}{R_c \parallel R_o}}$$

$$R_{th} = \frac{1}{g_m + \frac{1}{R_c \parallel R_o}}$$

Looking only at this:

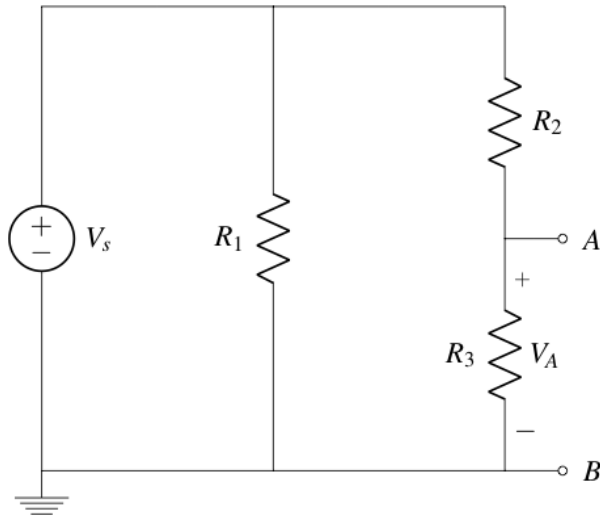


Find V_{th} ,
 R_{th} looking
at A-B.

$$V_{th} = V_{AB} = \frac{R_3}{R_2 + R_3} V_s$$

R_{th} : (zero V_s)

Now I can use
series and //
comb!

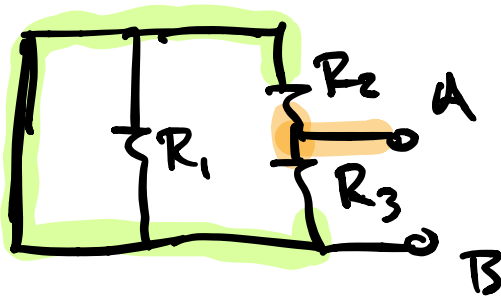


$$R_{AB} = R_2 // R_3$$

R_2, R_3 are comb. in parallel since
 $V_s \rightarrow$ wire


(R_1 is shorted so neglect - was done wrong in lec.)

Op Amps

Model:

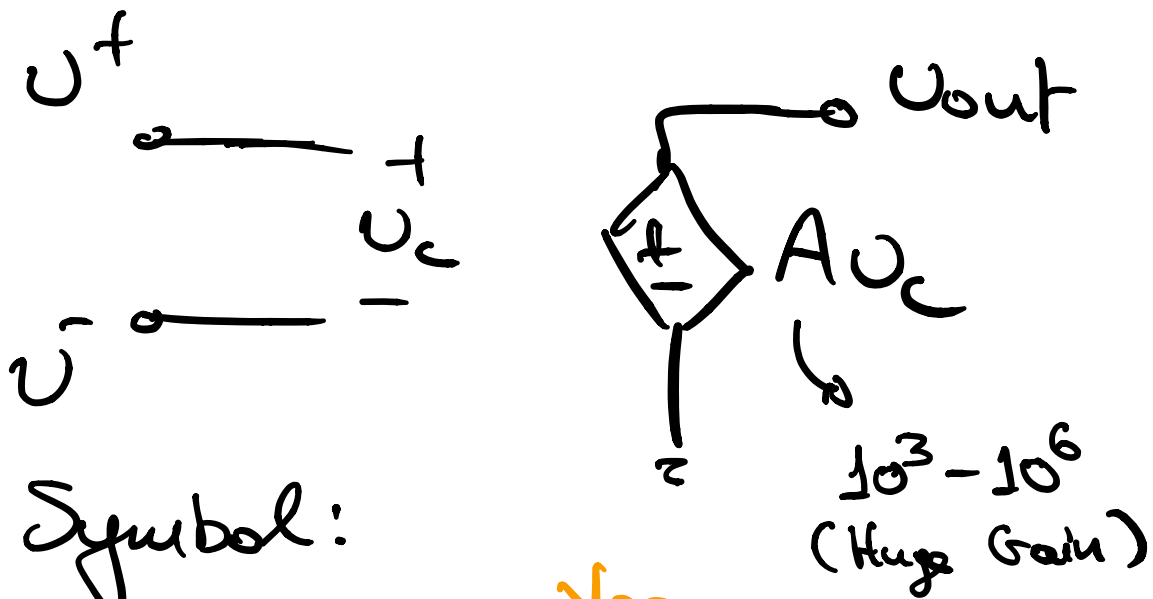



Symbol:

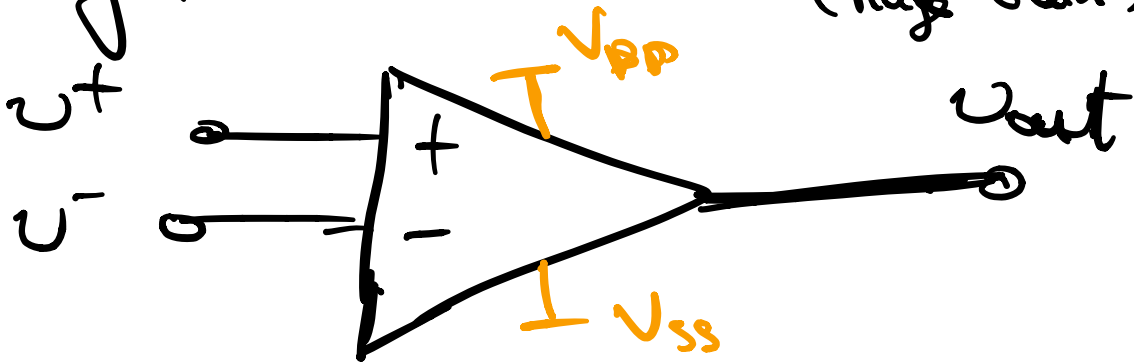

Caveat: V_{DD} and V_{SS} supply power to the op amp (often not drawn for convenience)

Uses :



a) As a comparator

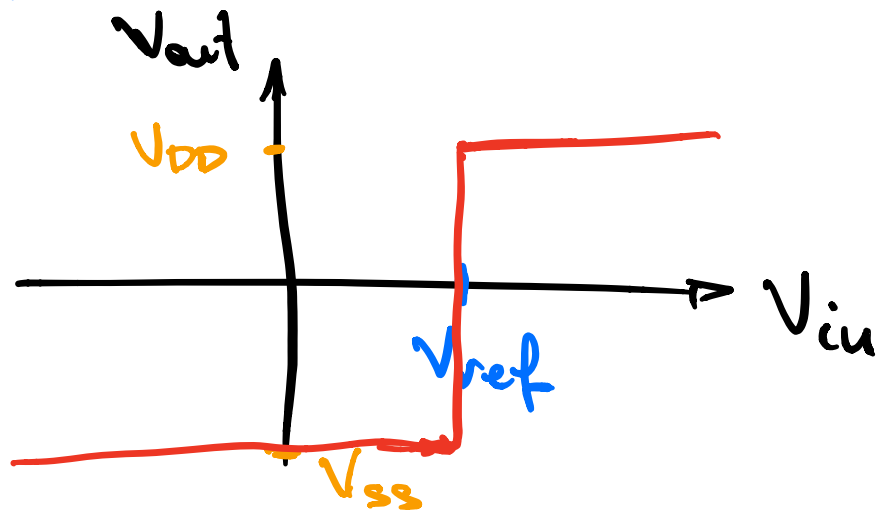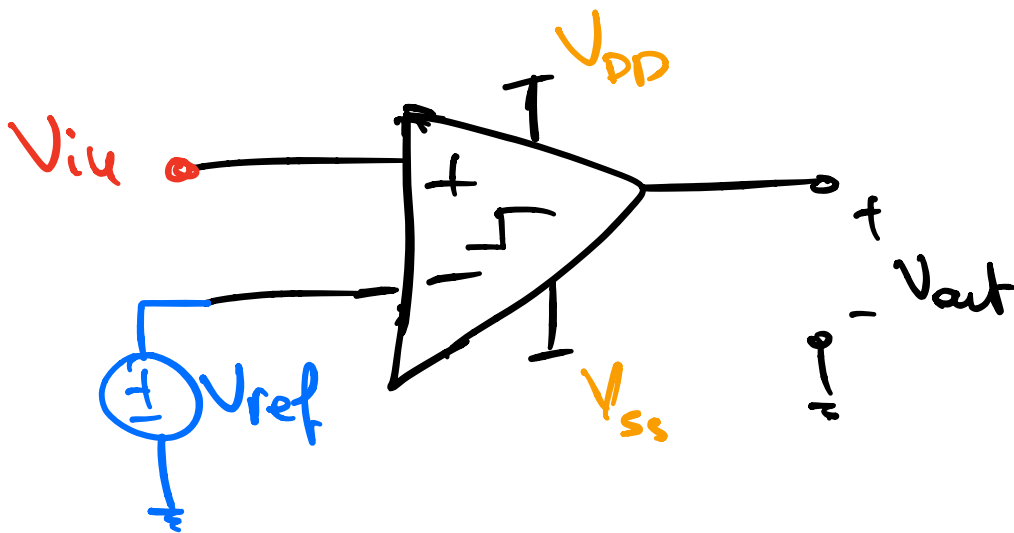

Is this a linear function?

NO!

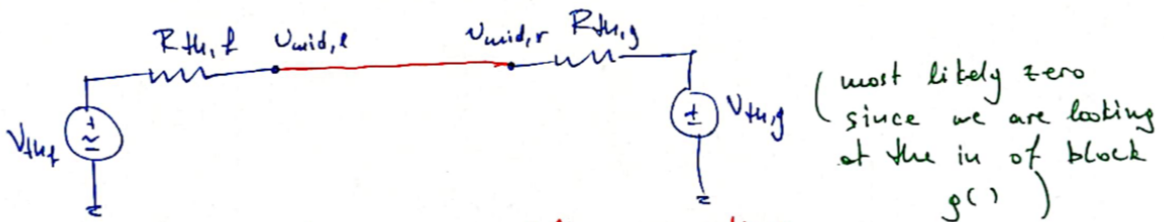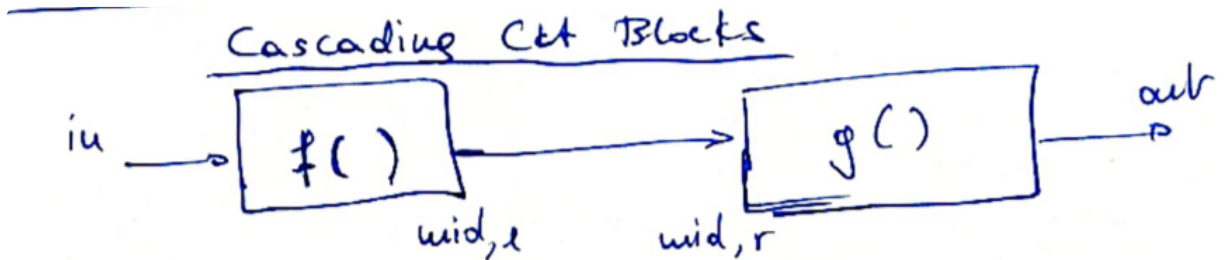b) As an amplifier and
 a means of cascading blocks
 → Lec. 4D, 5A!



Before connection:

$$V_{mid,l} = V_{th,f} \neq V_{mid,r}$$

After connection:

$$V_{mid,l} = V_{mid,r} = \frac{R_{th,g}}{R_{th,g} + R_{th,f}} V_{th,f} + \frac{R_{th,f}}{R_{th,g} + R_{th,f}} V_{th,g}$$

in general


∴ except when: $R_{th,f} = 0$ (wire)

or $R_{th,g} = \infty$ (open-circuit)

Ideal Isolation

From the perspective of block f: see an open-circuit $R_{th,g} = \infty$

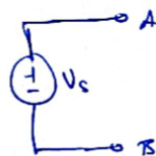— " — " — " — g: see a voltage source $R_{th,f} =$





$R_{th, \text{voltage source}} = 0$

Motivation:

④ Audio System - "16A Boombox"

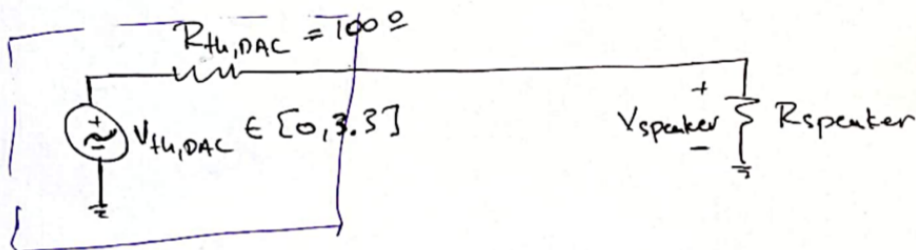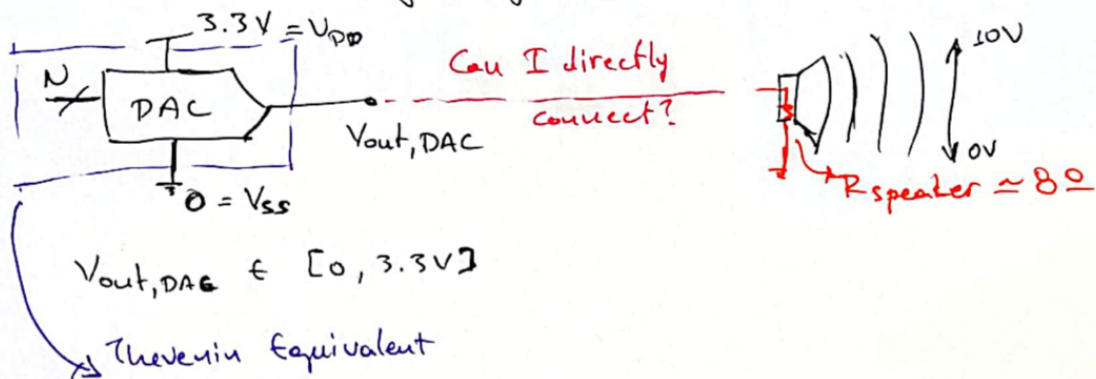Digital to Analog Converter (DAC)
 Converts a digital-binary value to
 an analog voltage



Voltage Divider

$$V_{speaker} = \frac{R_{speaker}}{R_{speaker} + R_{th,DAC}} \cdot V_{th,DAC}$$

$$= \frac{8\Omega}{8\Omega + 100\Omega} \cdot V_{th,DAC} \approx 0.1 V_{th,DAC}$$

Loading Effect!



Want Linear Amplification

$$V_{out} = A_V \cdot V_{in}$$


A_V linear gain factor!


→ Goal: A_V needs

to be reasonable and well contr

→ Problem: huge uncertain gain → non-linear $V_{in} - V_{out}$

→ Solution: Use NFB!

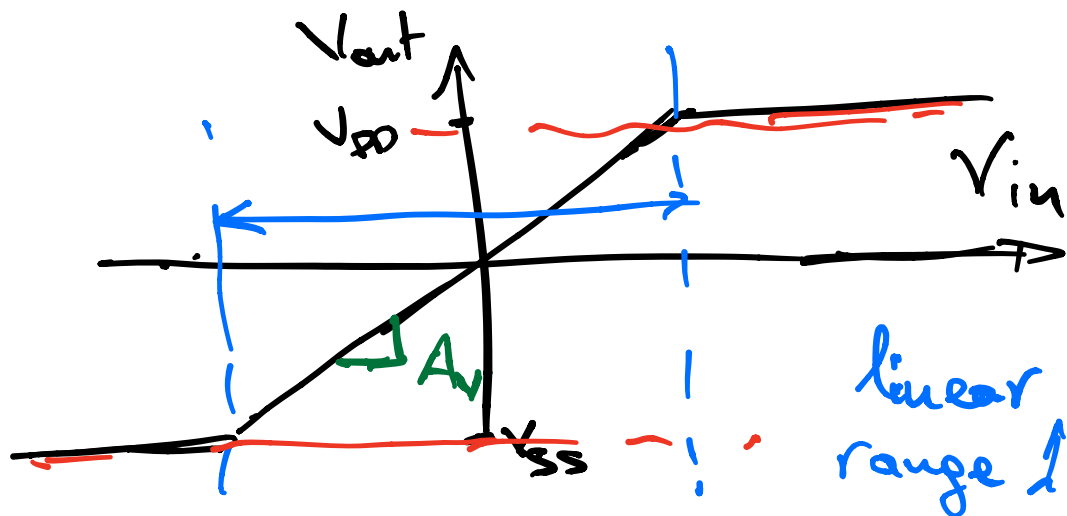

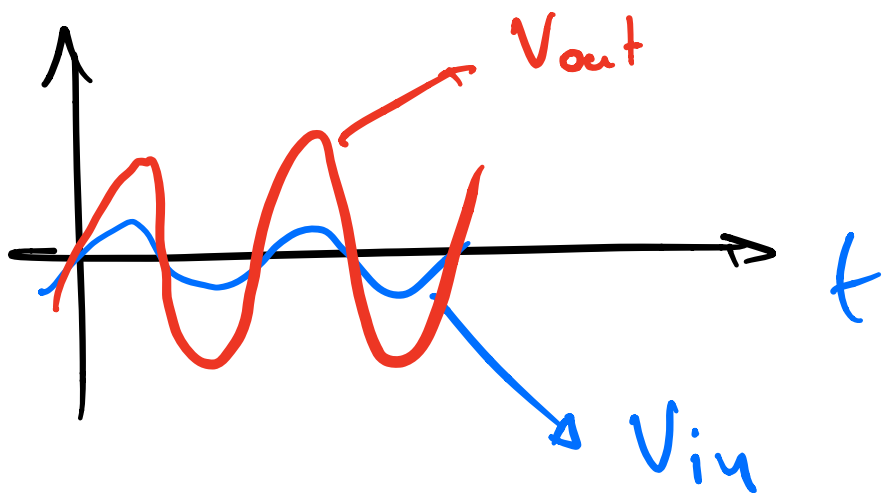

$$V_{out} = A_V \cdot V_{in}$$

different than A_V (total ckt gain in NFB)

opamp gain

$$A_V = \frac{A}{1 + A f}$$

↖

↗

↘ feedback

$A \rightarrow \infty$

$\frac{1}{f}$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{1}{f} \rightarrow \text{not that easy to calculate.}$$

That's why we invoked
the ...

GOLDEN RULES!







1 $i^+ = i^- = 0$ (ALWAYS)

2 $v^+ = v^-$ when $A \rightarrow \infty$
and op-amp is in NFB.

(+ NVA)

Using Golden Rules we
derived the following:




For Reference: Example Circuits
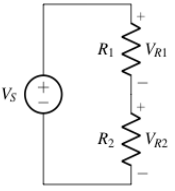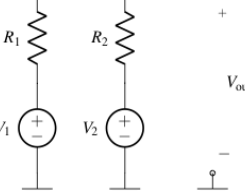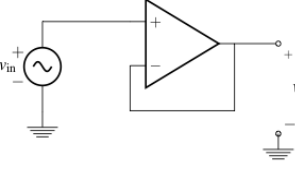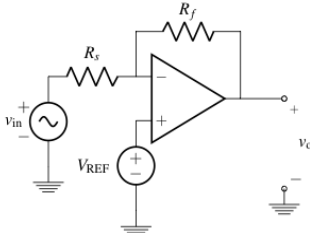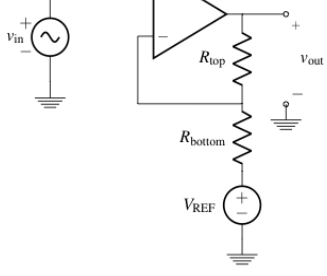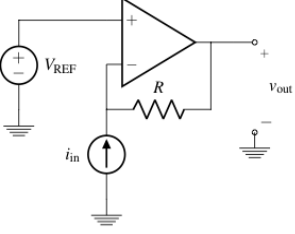
<p style="text-align: center;">Voltage Divider</p>  $V_{R2} = V_S \left(\frac{R_2}{R_1 + R_2} \right)$	<p style="text-align: center;">Voltage Summer</p>  $V_{out} = V_1 \left(\frac{R_2}{R_1 + R_2} \right) + V_2 \left(\frac{R_1}{R_1 + R_2} \right)$	<p style="text-align: center;">Unity Gain Buffer</p>  $\frac{v_{out}}{v_{in}} = 1$
<p style="text-align: center;">Inverting Amplifier</p>  $v_{out} = v_{in} \left(-\frac{R_f}{R_s} \right) + V_{REF} \left(\frac{R_f}{R_s} + 1 \right)$	<p style="text-align: center;">Non-inverting Amplifier</p>  $v_{out} = v_{in} \left(1 + \frac{R_{top}}{R_{bottom}} \right) - V_{REF} \left(\frac{R_{top}}{R_{bottom}} \right)$	<p style="text-align: center;">Transresistance Amplifier</p>  $v_{out} = i_{in} (-R) + V_{REF}$

Keep them handy - Learn to
pattern match and recognize them

P3

Example #1: Want this:

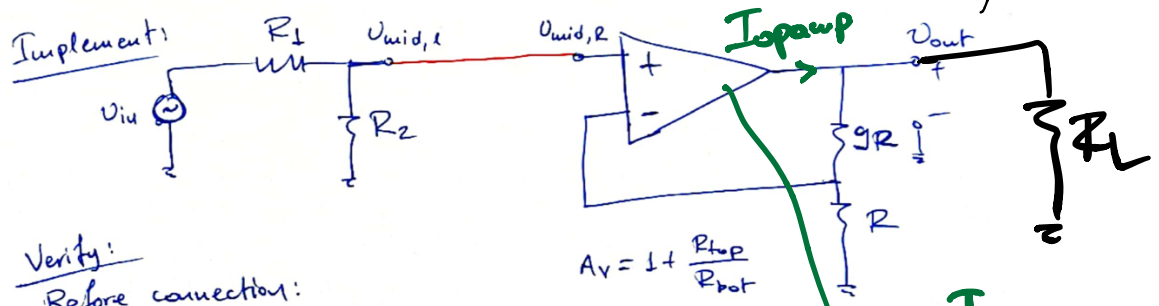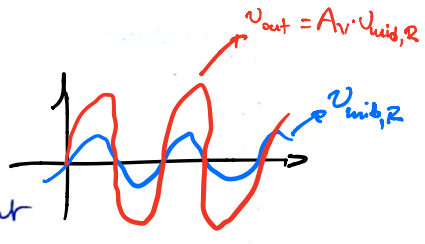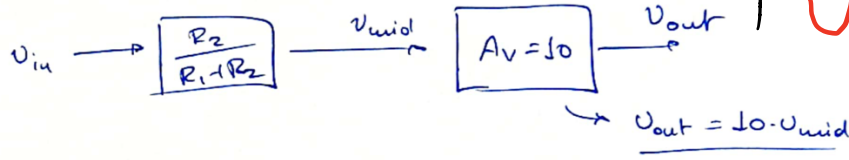

Verify:


Before connection:

$$U_{mid,1} = \frac{R_2}{R_1 + R_2} \cdot U_{in}$$




After connection:

$$U_{mid,1} = U_{mid,2} = \frac{R_2}{R_1 + R_2} \cdot U_{in} \quad \text{☺}$$

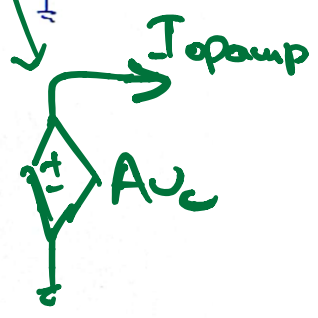
$$\Rightarrow U_{out} = \frac{R_2}{R_1 + R_2} \cdot \underbrace{\left(1 + \frac{R_{top}}{R_{bot}}\right)}_{10} \cdot U_{in} \quad \checkmark$$



Practice Handout

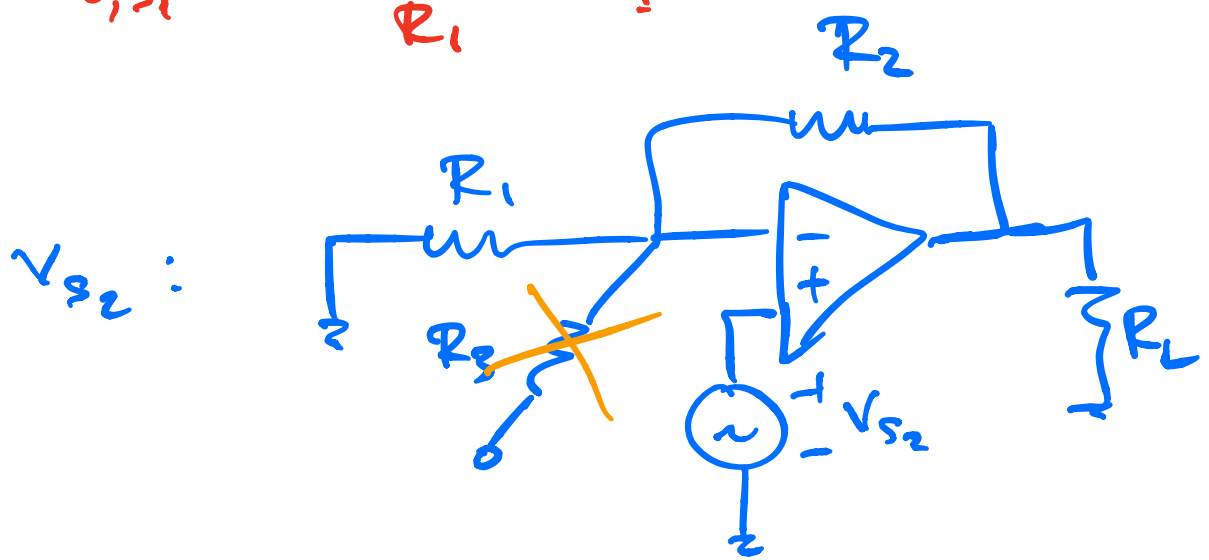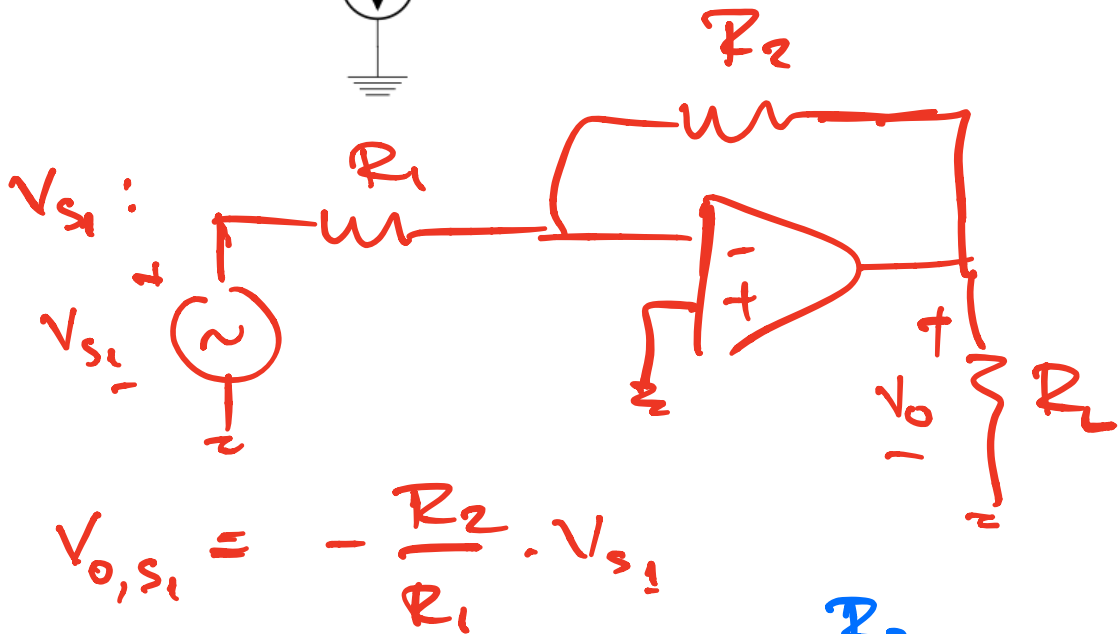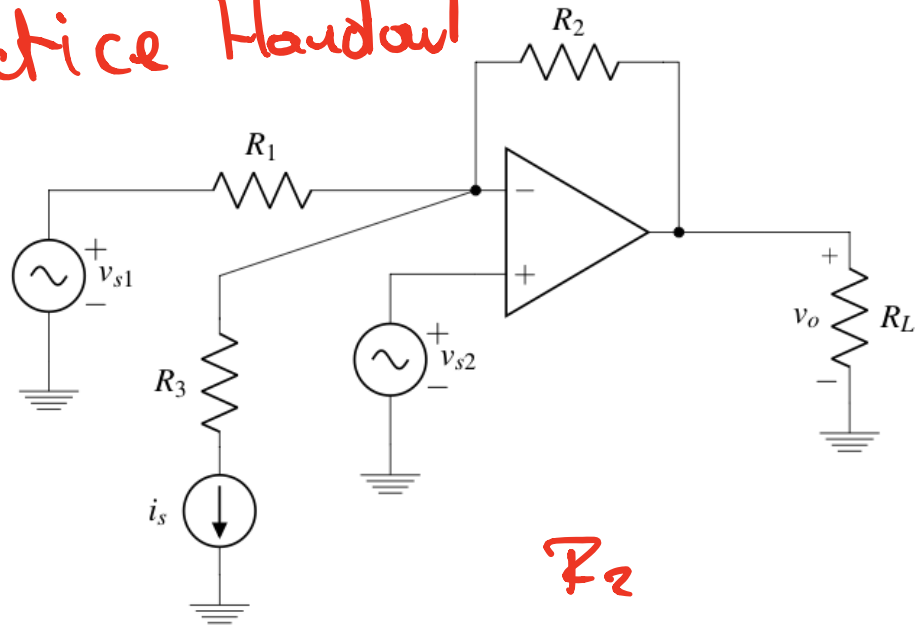
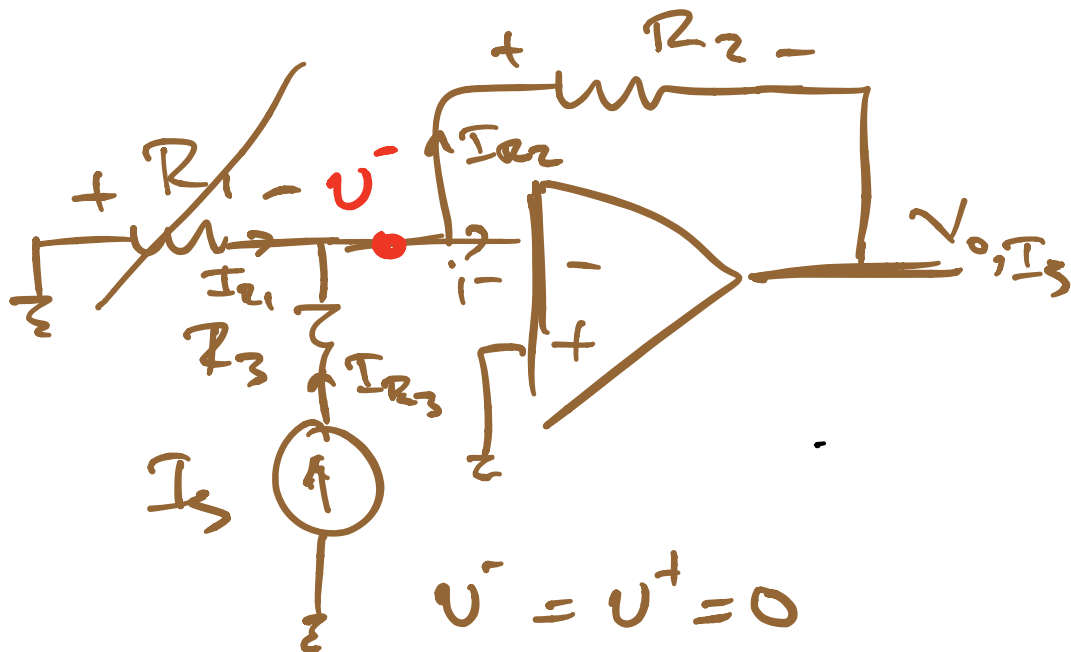
$$V_{o,s} = \left(1 + \frac{R_2}{R_1}\right) \cdot V_{s2}$$



$$v^- = v^+ = 0$$

$$\Rightarrow V_{R_1} = ?$$

$$\text{KCL on } v^- : \quad \begin{aligned} &= 0 - v^- \\ &= 0 \end{aligned}$$

$$I_{R_3} = I_{R_2} = I_s$$

$$\text{Ohm's law : } V_{R_2} = I_s \cdot R_2$$

$$\Rightarrow 0 - V_{o, I_s} = I_s \cdot R_2$$

$$\Rightarrow V_{oI_s} = -I_s R_2$$


$$V_o = V_{o s_1} + V_{o s_2} + V_{o I_s}$$

$$= -\frac{R_2}{R_1} V_{s_1} + \left(1 + \frac{R_2}{R_1}\right) V_{s_2} = -I_s R_2$$

(sol also on ^{Class} website)

(a) Determine the voltage at O for the following configuration.

Sp 2020
4+2

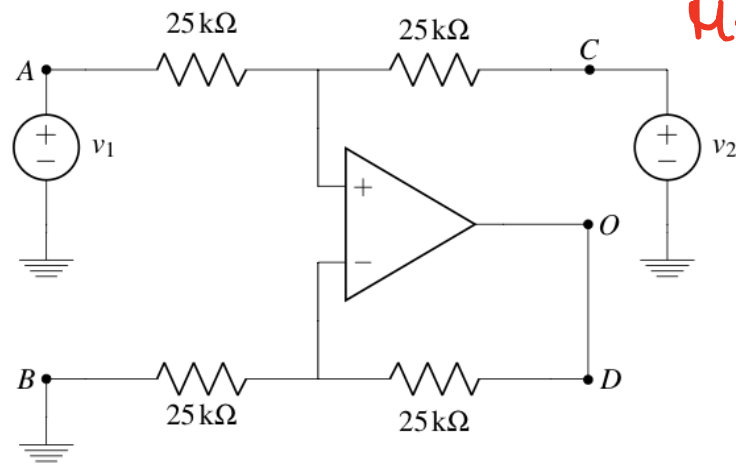

Practice: show that

$$v_o = v_1 + v_2$$

(solved on Piazza)