



EECS 16A


Power and Voltage/Current Measurement

Previously on 16A.....

- NVA -
- ① Identify nodes
 - ② Choose a ground
 - ③ Label all elements (currents + voltages) & node potentials
 - ④ KCL
 - ⑤ Ohm's law
 - ⑥ Current / Voltage sources
 - ⑦ Set up $A\vec{x} = \vec{b}$ and solve

Previously on 16A.....

{ Voltage Divider }

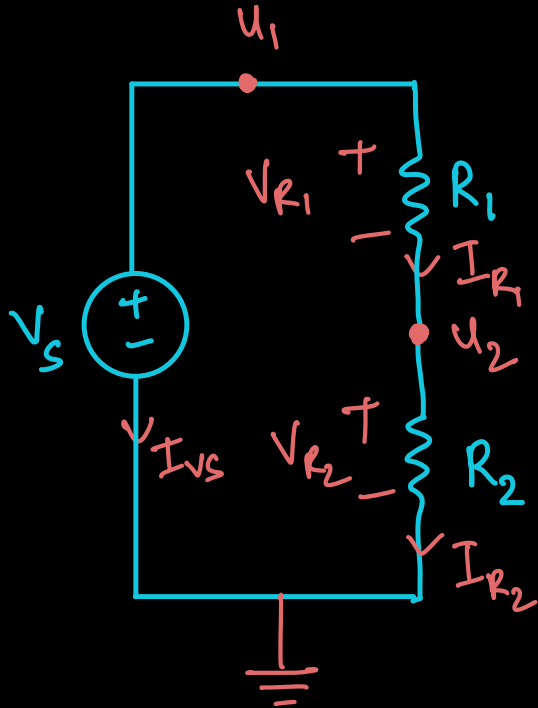


$$\rightarrow u_2 = \frac{R_2}{R_1 + R_2} V_s$$

$$u_2 = \frac{1}{\frac{R_1}{R_2} + 1} V_s \quad \left\{ \frac{R_1}{R_2} = \alpha \right.$$


$$u_2 = \frac{1}{\alpha + 1} V_s$$

Energy and Power

Current - Rate of flow of charge

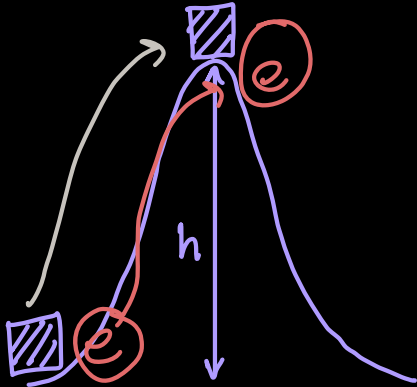

$$E \propto h$$
$$E \propto m$$

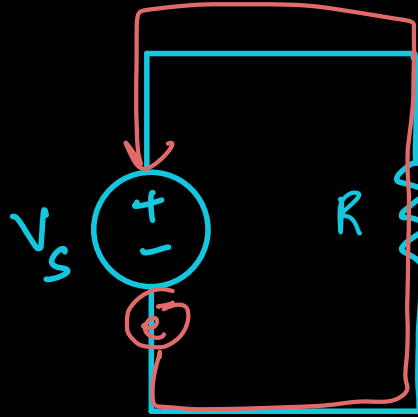

$$E \propto V$$

$$E \propto q$$

$$q, V$$


$$E = qV$$

DC analysis \hookrightarrow charge

$$P = \frac{dE}{dt} = \frac{d(q \cdot V)}{dt} = V \cdot \frac{dq}{dt} = VI$$

How to think about Energy and Power in circuits?

$P \rightarrow \text{Watt (W)}$



$P = I_{el} V_{el}$

$V = IR$

$P = VI = I^2 R = \frac{V^2}{R}$

For a resistor only


≥ 0

any passive element $P \geq 0$ is the passive sign convention

consumes power \leftarrow

supplies power \leftarrow active element $P < 0$

Power in Circuits Example

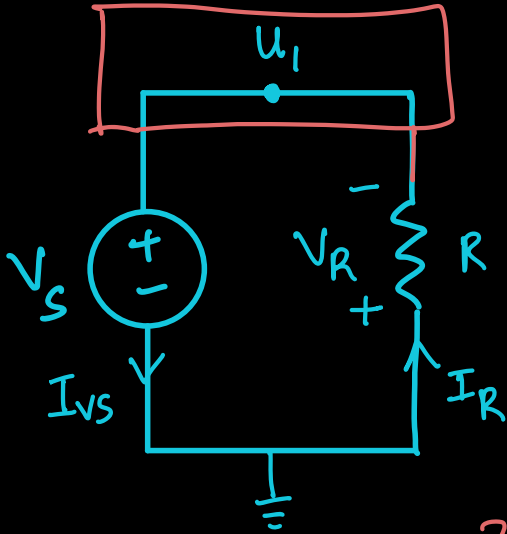

KCL: $I_{Vs} = I_R$

Ohm's law: $V_R = I_R \cdot R = 0 - u_1$

VS: $u_1 - 0 = V_S$

$P_{Vs} = -\frac{V_S^2}{R}$

$I_{Vs} = I_R$

$u_1 = V_S$


$R \cdot I_R = -u_1$

$\left[I_R = -\frac{V_S}{R} \right]$

$P_R = I_R^2 R = \left(\frac{V_S}{R}\right)^2 R = \frac{V_S^2}{R}$

$P_{Vs} = I_{Vs} V_S = -\frac{V_S^2}{R}$

Power in Circuits Example

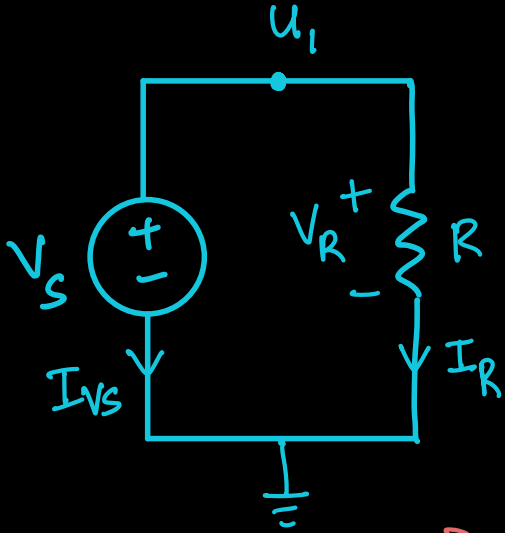

$$\underline{KCL} - 0 = I_{VS} + I_R$$

$$\underline{OL} - V_R = I_R \cdot R = u_1$$

$$\underline{US} - u_1 - 0 = V_S$$


$$I_R = \frac{V_S}{R}$$

$$I_{VS} = -I_R = \frac{-V_S}{R}$$

$$P_R = I_R^2 R = \frac{V_S^2}{R}$$

$$P_{VS} = V_S \cdot I_{VS} = \frac{-V_S^2}{R}$$

How to measure voltage? with a Voltmeter

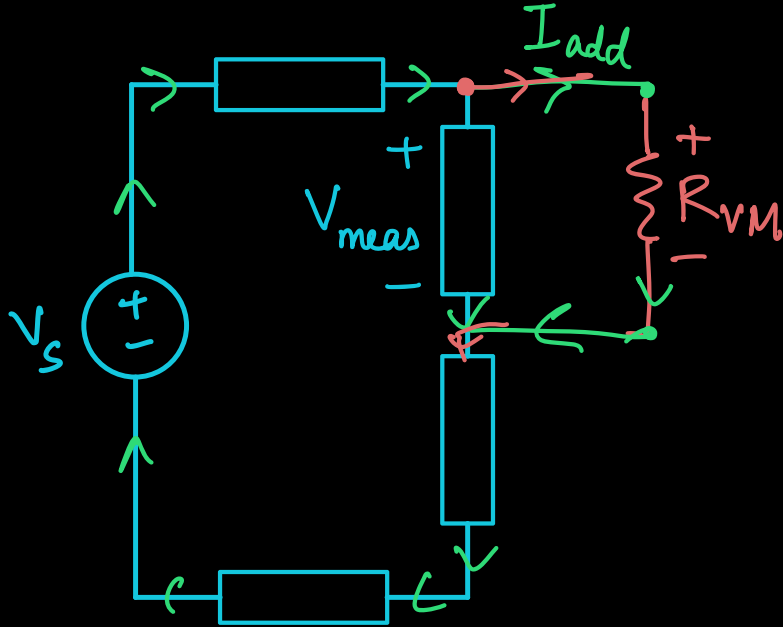


$$I_{add} = 0$$

$$R_{VM} \rightarrow \infty$$

Ideal

$$R_{VM} \rightarrow \infty$$

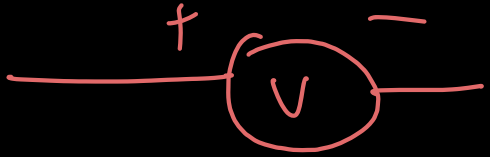


Ideal

\equiv




$$R = 200\text{M}\Omega$$

How to measure current? with an Ammeter

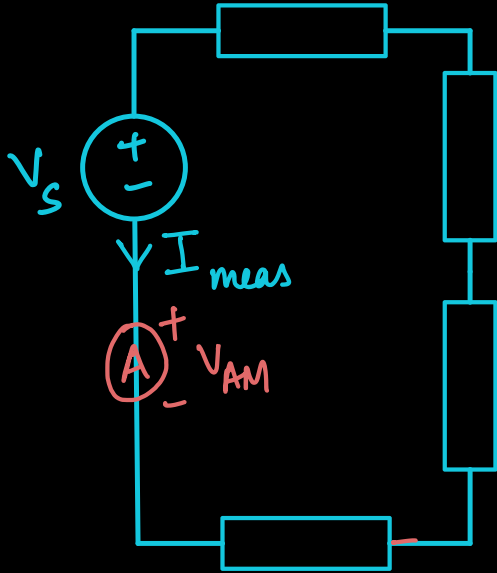


$$I_{meas} \times$$
$$\underbrace{R_{AM} = 0}$$
$$(V_{AM} = 0)$$

Ideal

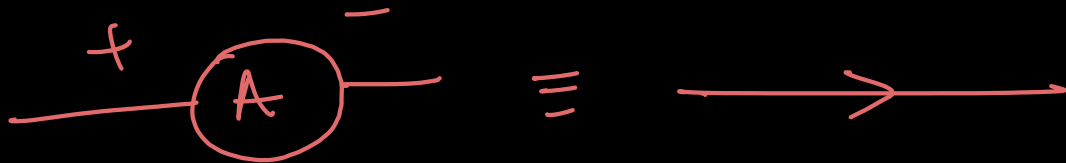

Resistivity

(Material Property)

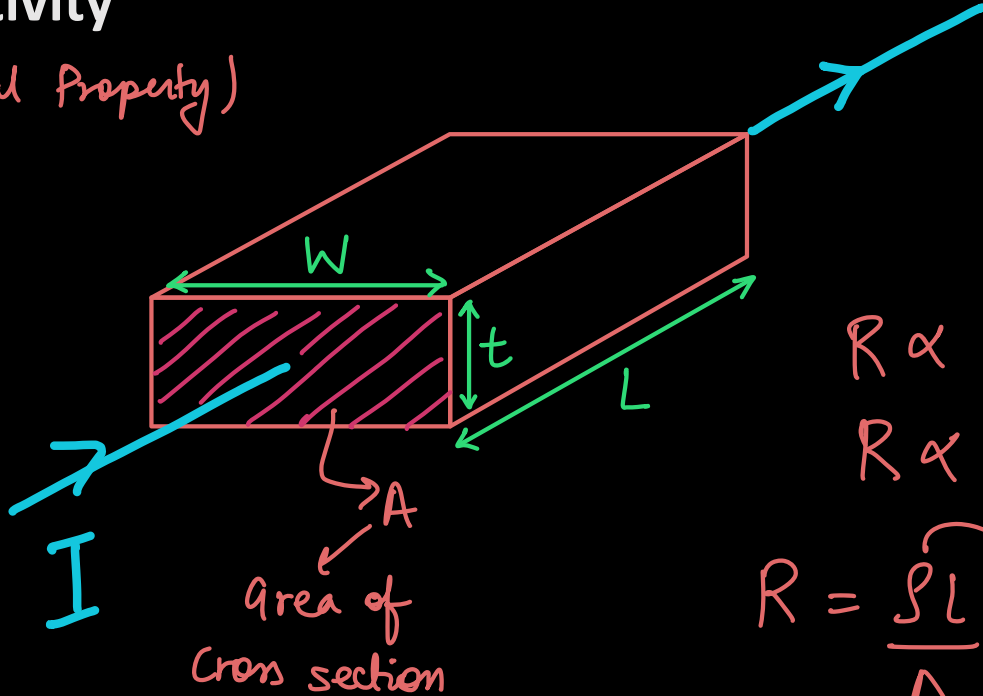


$$R \propto L$$

$$R \propto 1/A$$

$$R = \frac{\rho L}{A}$$

resistivity
(rho)

Analogy

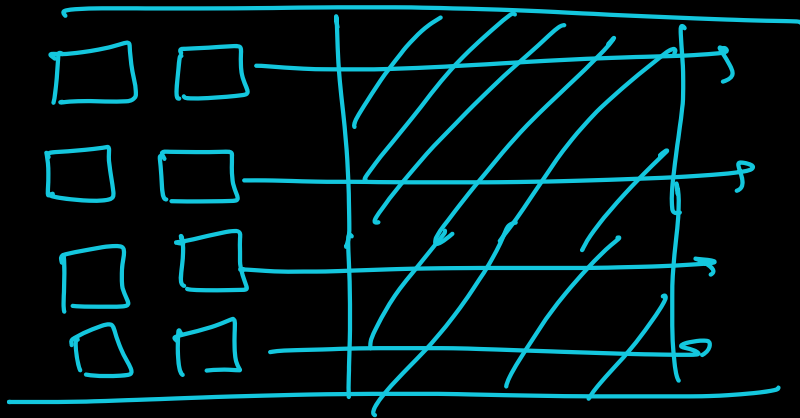

Resistivity (Example)

$$\rho_{\text{Cu}} = 1.7 \times 10^{-8} \Omega \text{m}$$

(rho)

$$\rho_{\text{wood}} = 10^{14} \Omega \text{m}$$


∞

$$l = 50 \text{cm} \quad A = 5 \text{cm}^2$$

$$R = \frac{\rho l}{A} = \frac{1.7 \times 10^{-8} \times 50 \times 10^2}{5 \times 10^{-4}}$$

$$= 1.7 \times 10^5 \Omega$$

$$l = 50 \times 10^5 = 1.7 \Omega$$

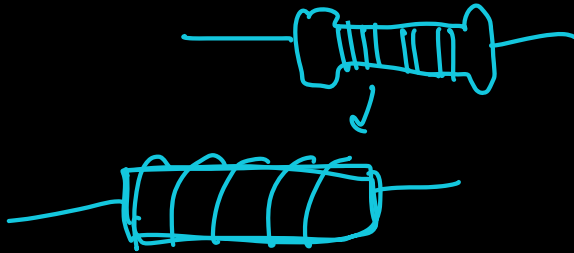


Resistive Touchscreen Design

$$R = \frac{\rho l}{A}$$


1D touchscreen




1D Resistive Touchscreen (Approach)

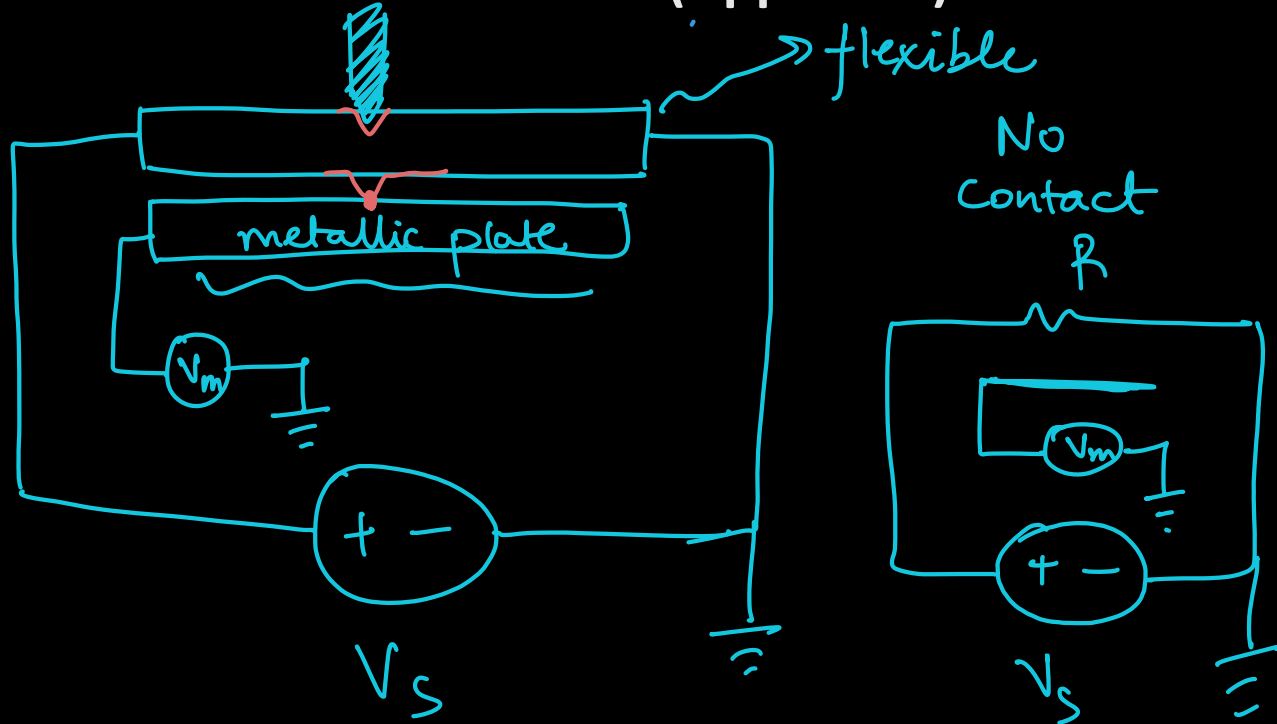

1D Resistive Touchscreen (Basic Model)

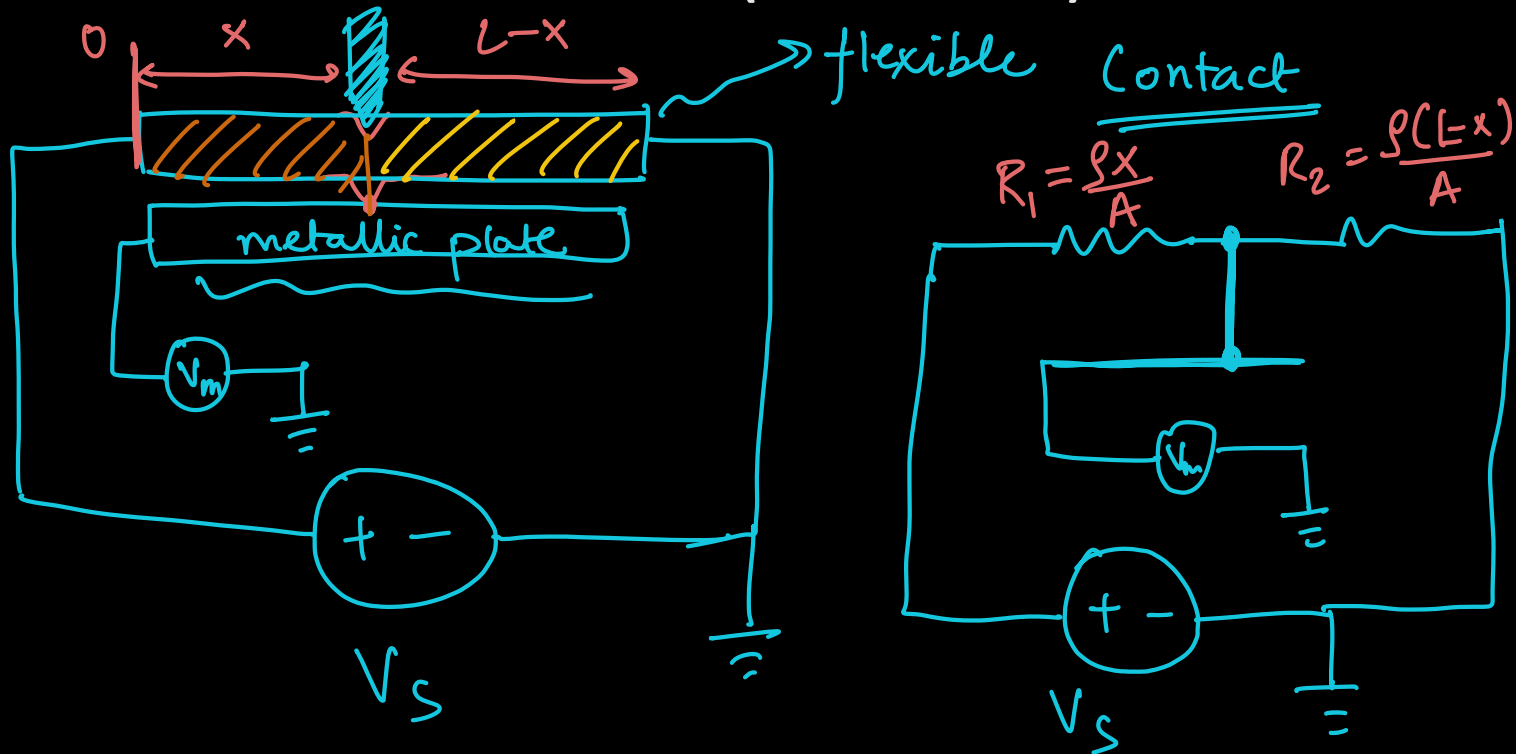

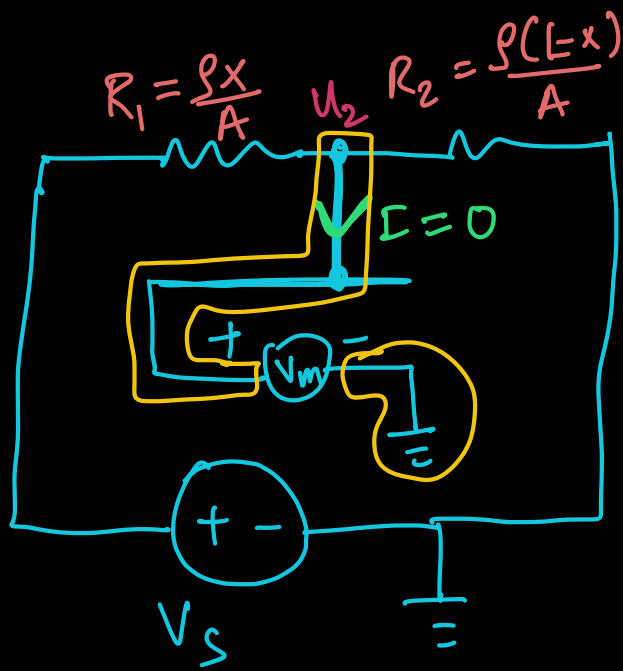

$$V_m = u_2 - 0$$

$$u_2 = \frac{R_2}{R_1 + R_2} V_s$$

$$u_2 = \frac{\frac{\rho(L-x)}{A}}{\frac{\rho L}{A}} V_s = \frac{L-x}{L} V_s$$

$$u_2 = \left(1 - \frac{x}{L}\right) V_s$$