



# EECS 16A


## Power and Voltage/Current Measurement

## Previously on 16A.....

- NVA -
- ① Identify nodes
  - ② Choose a ground
  - ③ Label all elements (currents + voltages) & node potentials
  - ④ KCL
  - ⑤ Ohm's law
  - ⑥ Current / Voltage sources
  - ⑦ Set up  $A\vec{x} = \vec{b}$  and solve

Previously on 16A.....

{ Voltage Divider }

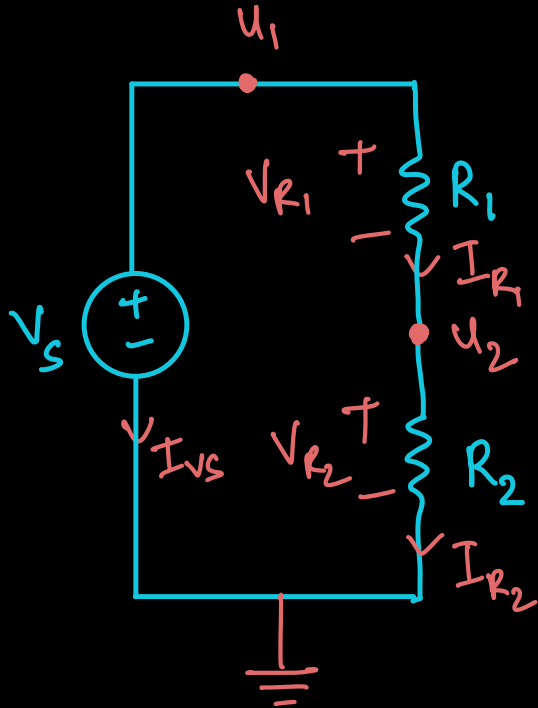



$$\rightarrow u_2 = \frac{R_2}{R_1 + R_2} V_s$$

$$u_2 = \frac{1}{\frac{R_1}{R_2} + 1} V_s \quad \left\{ \frac{R_1}{R_2} = \alpha \right.$$

$$u_2 = \frac{1}{\alpha + 1} V_s$$

# Energy and Power


Current - Rate of flow of charge

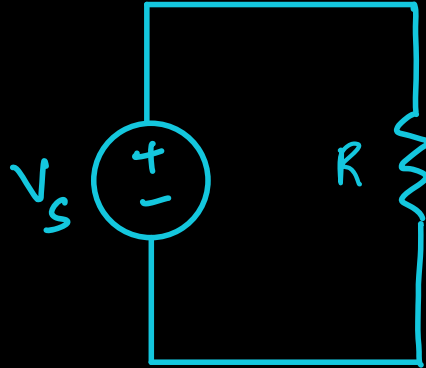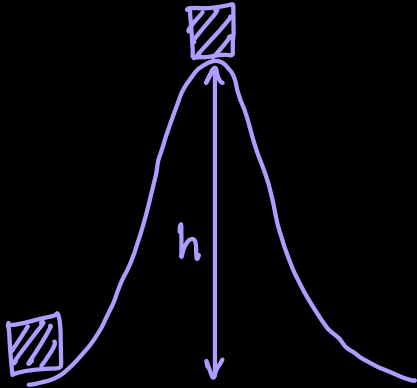


# How to think about Energy and Power in circuits?




# Power in Circuits Example

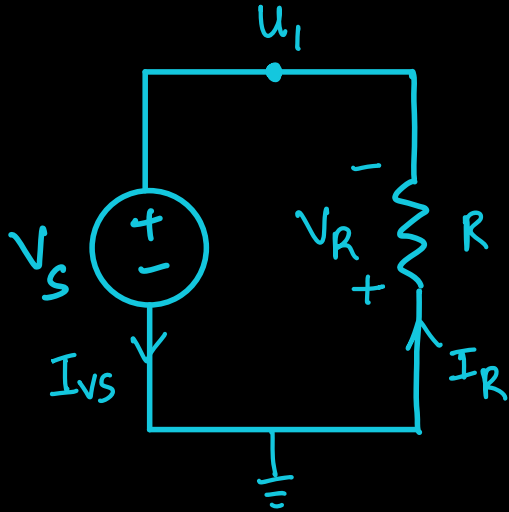

# Power in Circuits Example

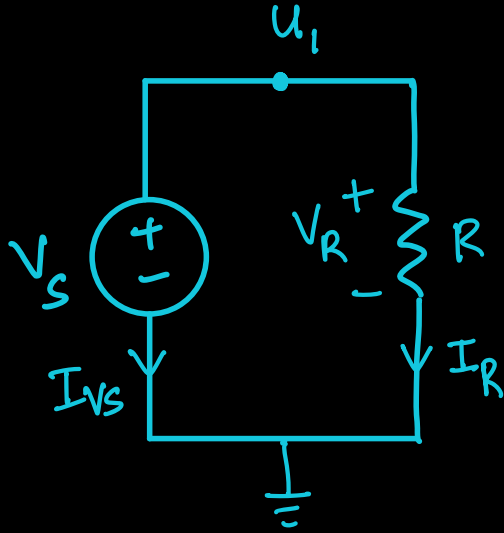

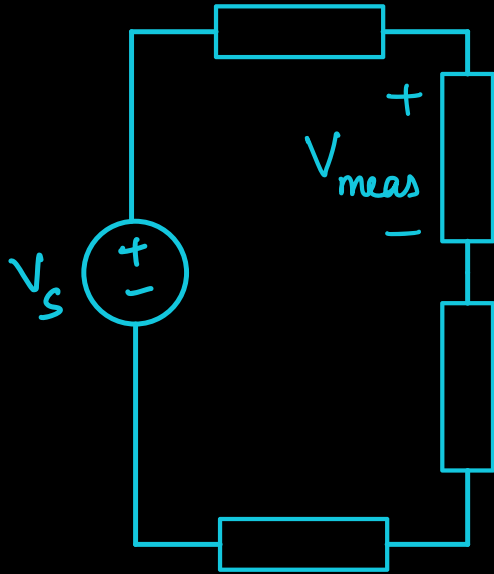
# How to measure voltage? with a Voltmeter






Ideal
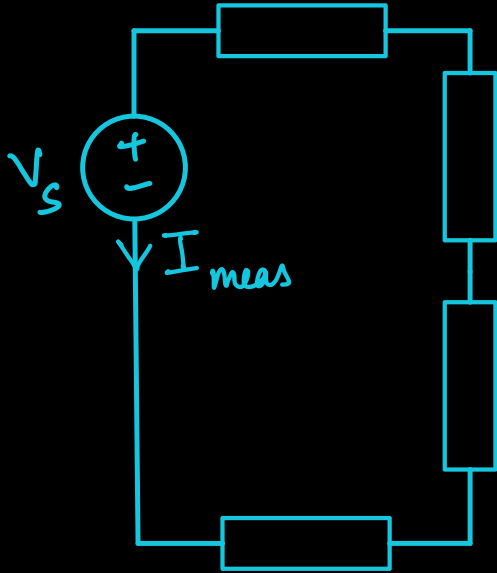
# How to measure current? with an Ammeter



Ideal

# Resistivity

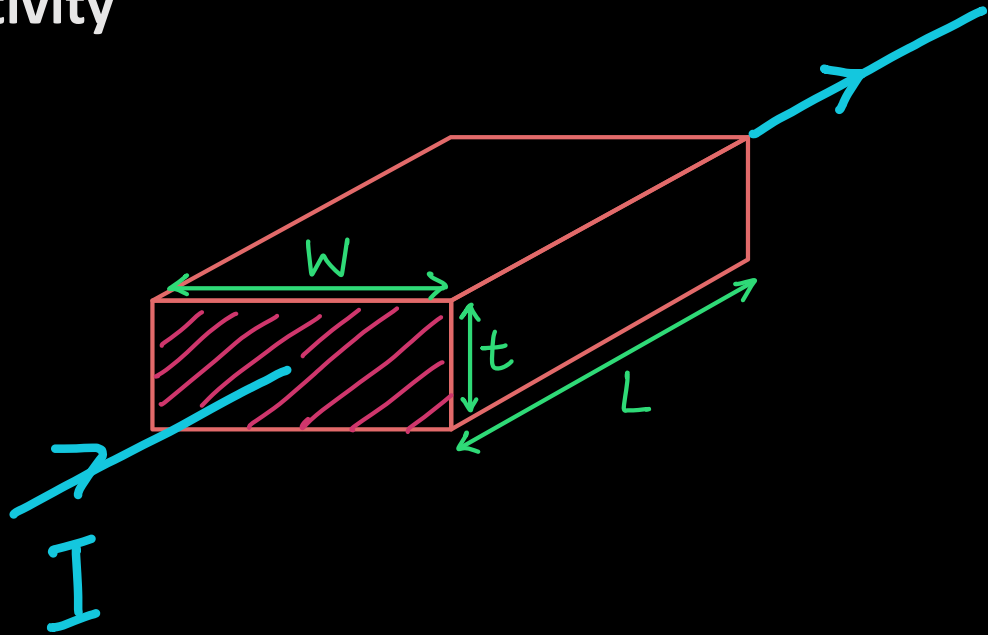

Analogy

## Resistivity (Example)

$$l = 5 \text{ cm} \quad A = 5 \text{ cm}^2$$

$$\rho_{\text{cu}} = 1.72 \times 10^{-8} \Omega \text{m}$$

$$\rho_{\text{wood}} = 10^{14} \Omega \text{m}$$

# Resistive Touchscreen Design

# 1D Resistive Touchscreen (Approach)



# 1D Resistive Touchscreen (Basic Model)