

## Lecture 5B

Admin:

- ① Mid-Semester Survey
- ② Midterm Redo

Agenda:


- Op Amp Circuit Analysis
- Inverting and Non-Inverting Amplifiers
- Circuit Design (Intro)

# Review


Golden Rules - (1) No input current  $I_+ = I_- = 0$  } Ideal  
(2) In NFB,  $u^+ = u^-$  } Op-Amps  
( $A \rightarrow \infty$ )

## Buffer

Isolated

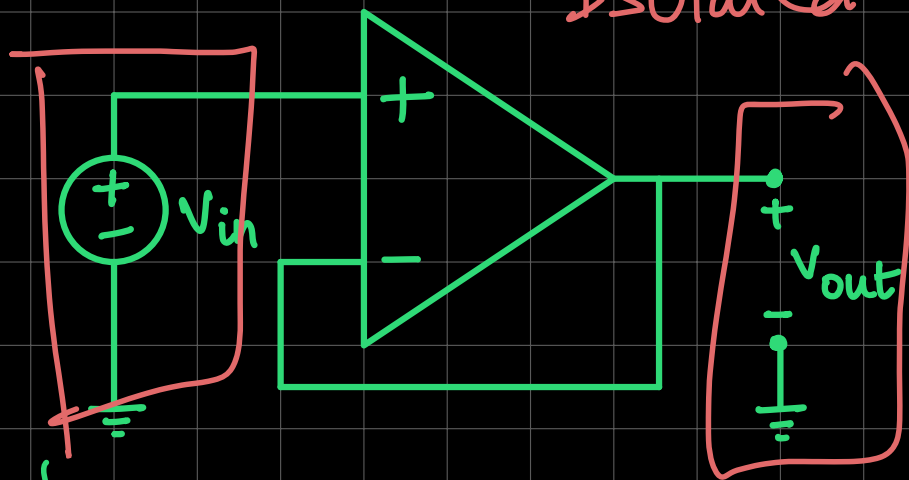


$$V_{in} = V_{out}$$

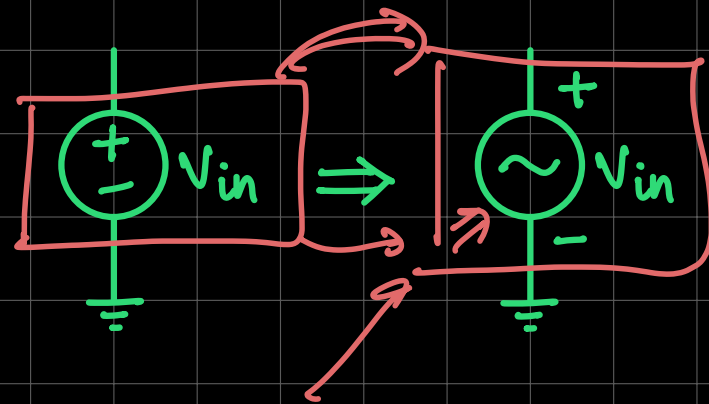

Voltage Source


Voltage Signal

# Inverting Amplifier

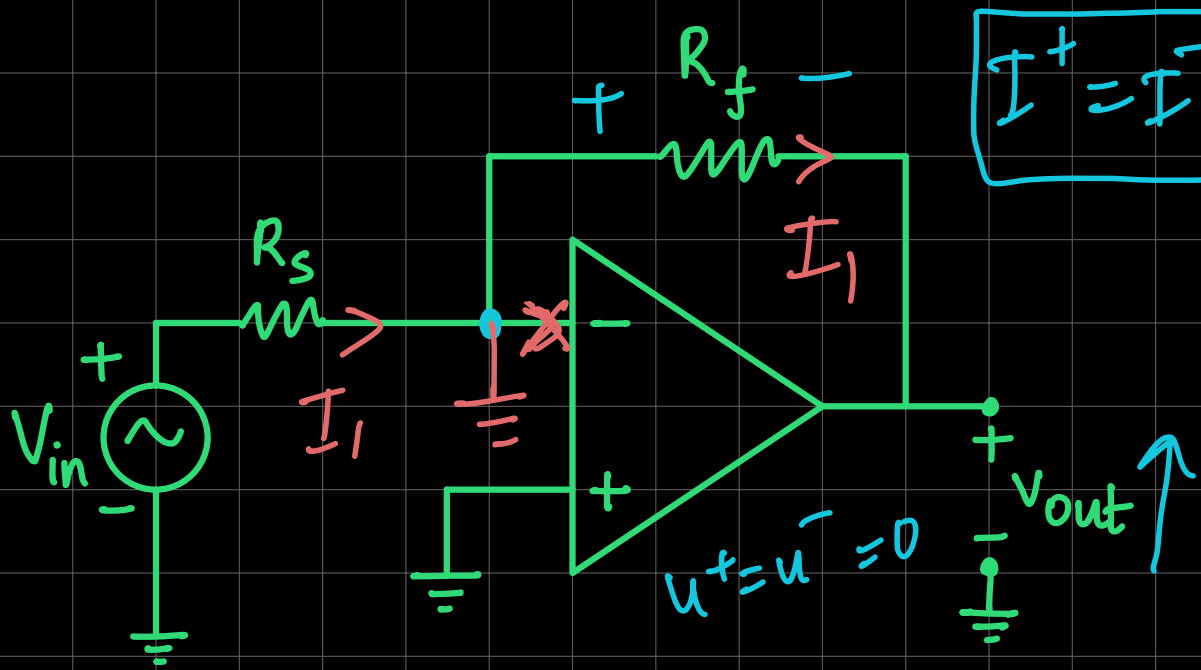

$V_{out}?$  (1) Check -ve feedback

$$I^+ = I^- = 0$$

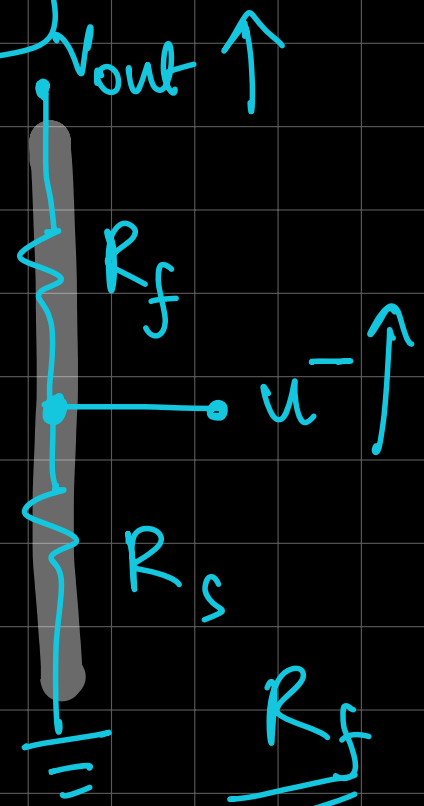


o/p  $\rightarrow A(u^+ - u^-)$

$$u^+ = u^- = 0$$

$$I_1 = \frac{V_{in} - 0}{R_s}$$

$$V_{R_f} = 0 - V_{out} = I_1 R_f$$

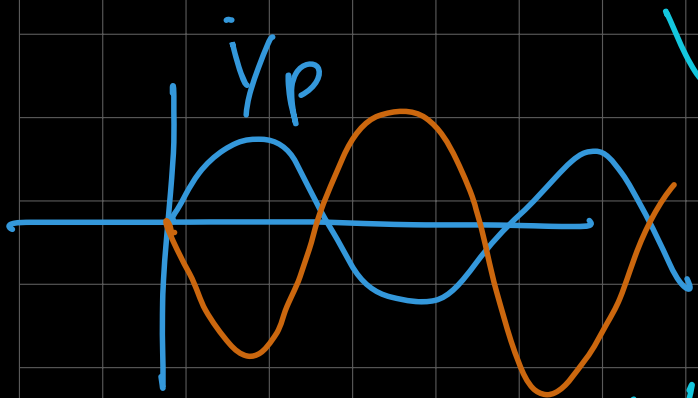

$$V_{R_f} = 0 - V_{out} = I_1 R_f$$

$$I_1 = \frac{V_{in}}{R_s}$$

$$V_{R_f} = -V_{out} = I_1 R_f$$


Check NFB.

$$-V_{out} = \frac{V_{in}}{R_s} R_f$$


① zero out all independent sources

②  $V_{out} \uparrow$

$\downarrow$  o/p  $A(u^+ - u^-)$

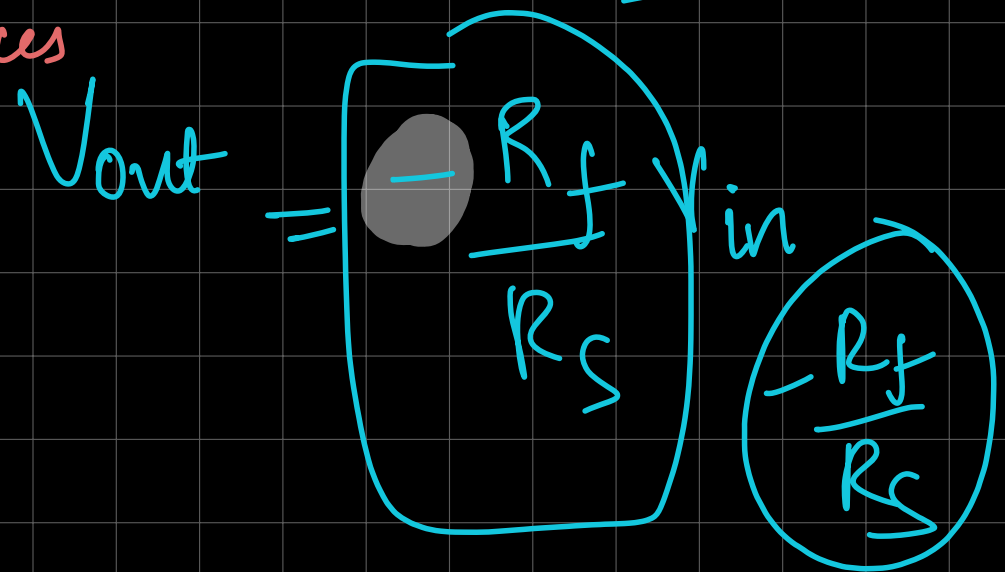

# Non-Inverting Amplifier

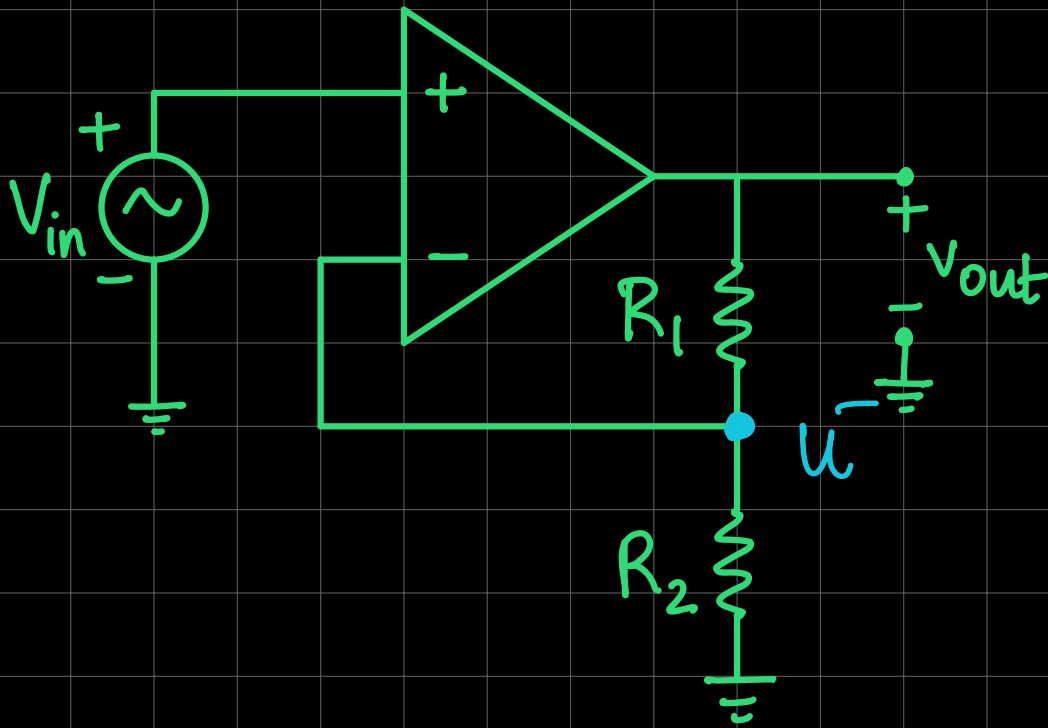

$V_{out} \uparrow$

$u^- \uparrow$

O/P

NFB ✓

$A(u^+ - u^-) \downarrow$

$V_{out}?$

$$u^+ = u^- = V_{in} \left( 1 + \frac{R_1}{R_2} \right)$$

$$u^- = \frac{R_2}{R_1 + R_2} V_{out} = V_{in}$$


$$V_{out} = 10 V_{in}$$

$$\frac{R_1}{R_2} = 9$$

$$V_{out} = \frac{R_1 + R_2}{R_2} V_{in} = \left( 1 + \frac{R_1}{R_2} \right) V_{in}$$


# OP-AMP CHEAT SHEET

### Voltage Divider

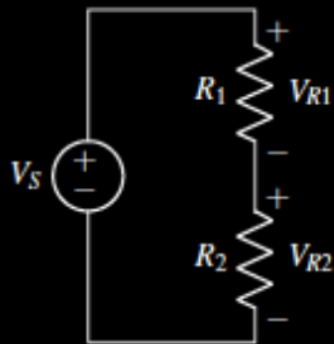


$$V_{R2} = V_S \left( \frac{R_2}{R_1 + R_2} \right)$$

### Voltage Summer

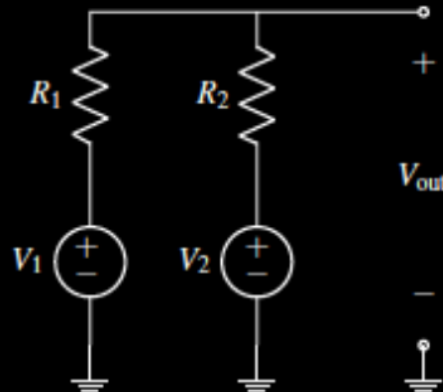


$$V_{out} = V_1 \left( \frac{R_2}{R_1 + R_2} \right) + V_2 \left( \frac{R_1}{R_1 + R_2} \right)$$

### Unity Gain Buffer

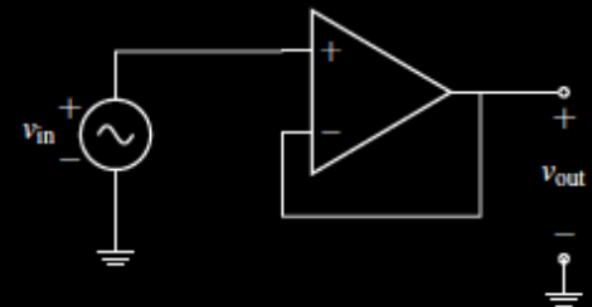


$$\frac{v_{out}}{v_{in}} = 1$$

### Inverting Amplifier

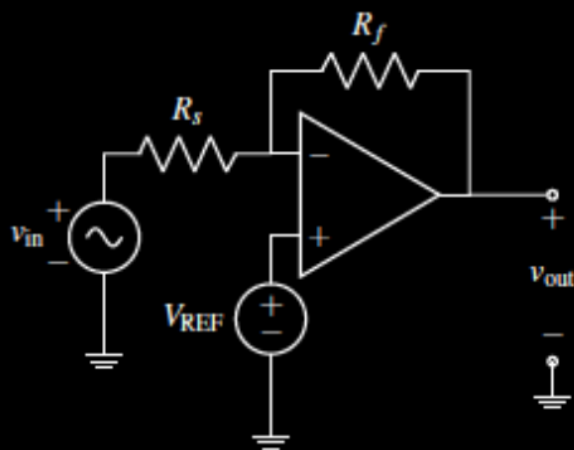


$$v_{out} = v_{in} \left( -\frac{R_f}{R_s} \right) + V_{REF} \left( \frac{R_f}{R_s} + 1 \right)$$

### Non-inverting Amplifier

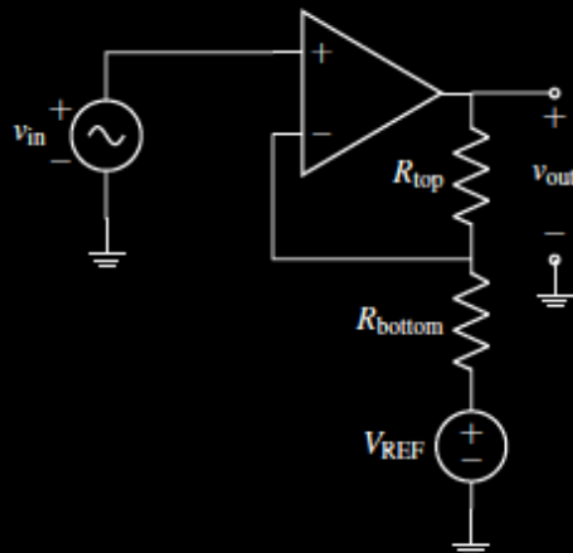

$$v_{out} = v_{in} \left( 1 + \frac{R_{top}}{R_{bottom}} \right) - V_{REF} \left( \frac{R_{top}}{R_{bottom}} \right)$$

### Transresistance Amplifier

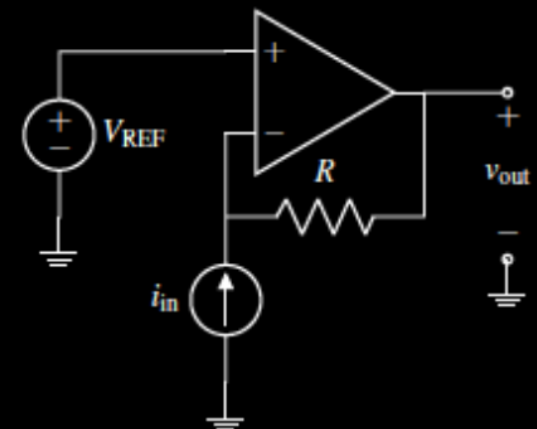


$$v_{out} = i_{in}(-R) + V_{REF}$$

# Artificial Neuron

Inputs

Weights

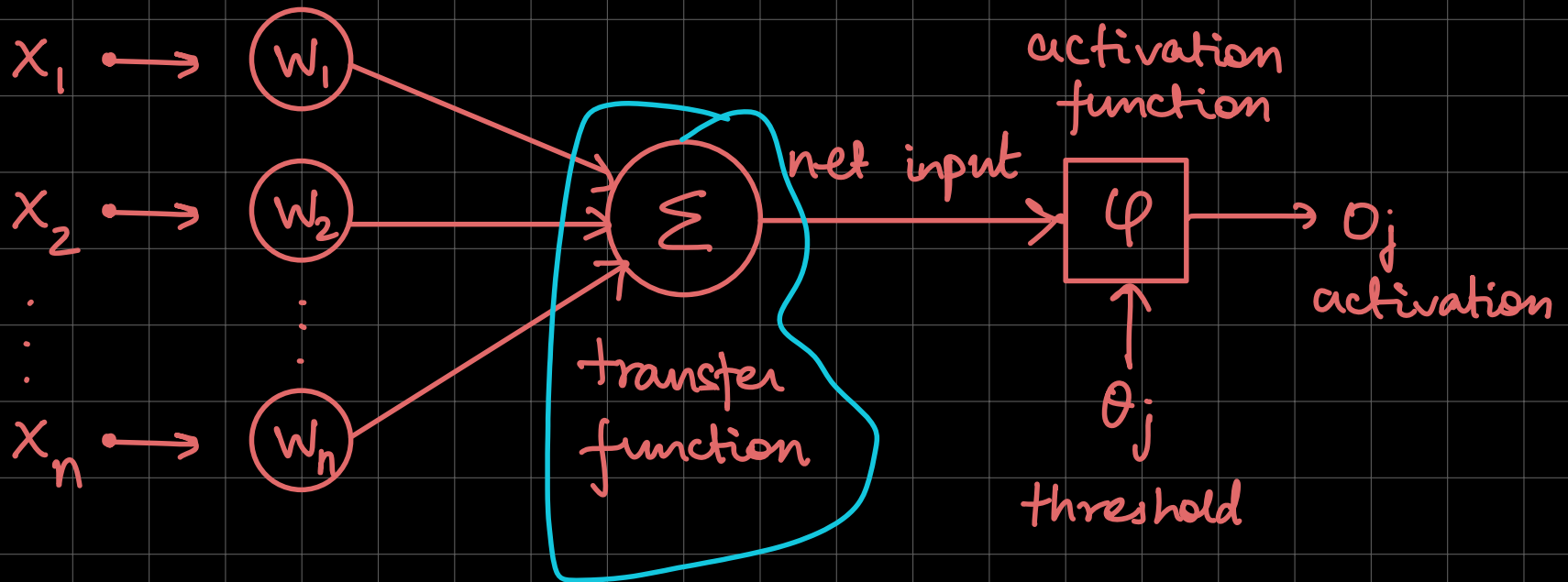


Output  $\Rightarrow$

$$x_1 w_1 + x_2 w_2 + \dots + x_n w_n$$


$\downarrow$                        $\downarrow$                        $\downarrow$

$\geq 0$                        $\geq 0$                        $\geq 0$

# Artificial Neuron

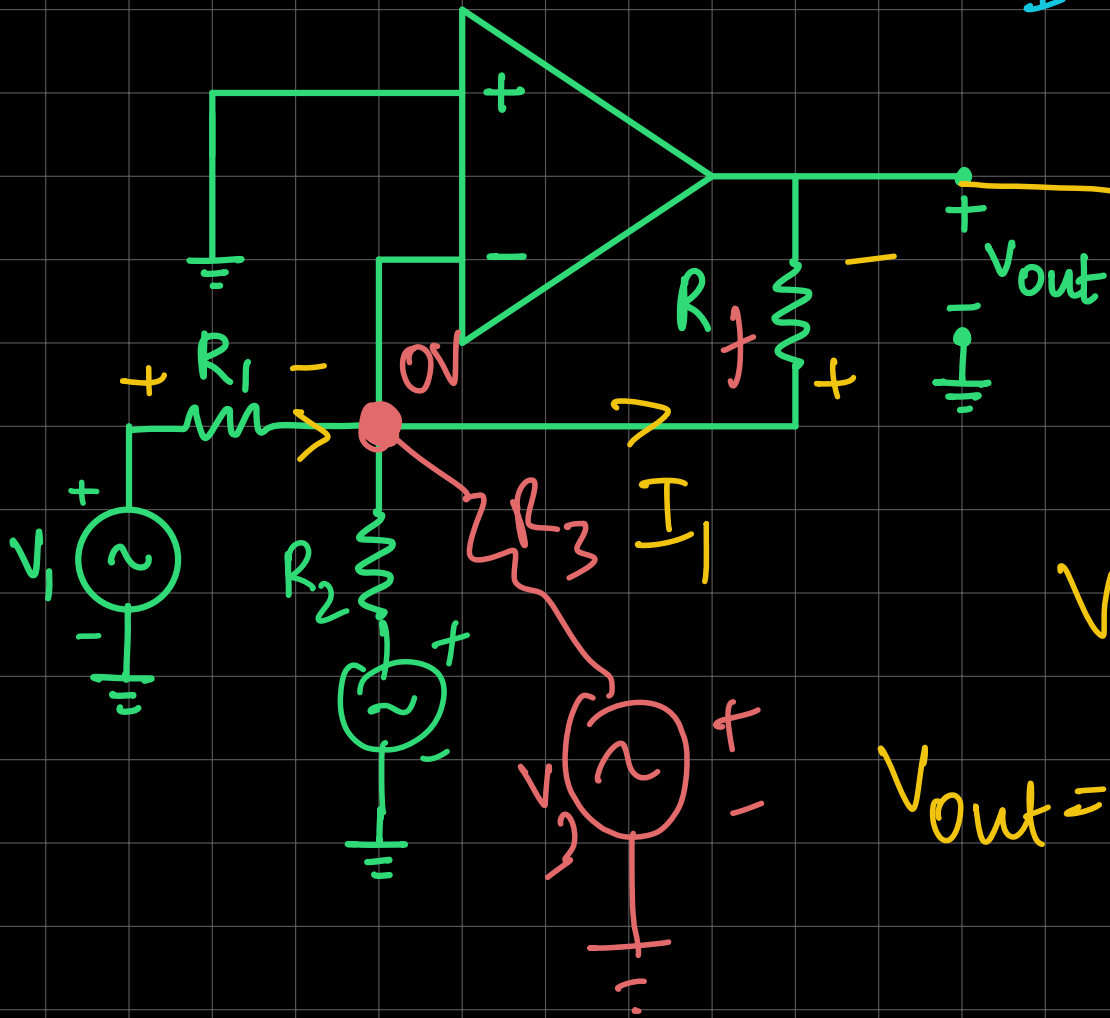

$$I^+ = I^- = 0 \quad u^+ = u^- = 0$$

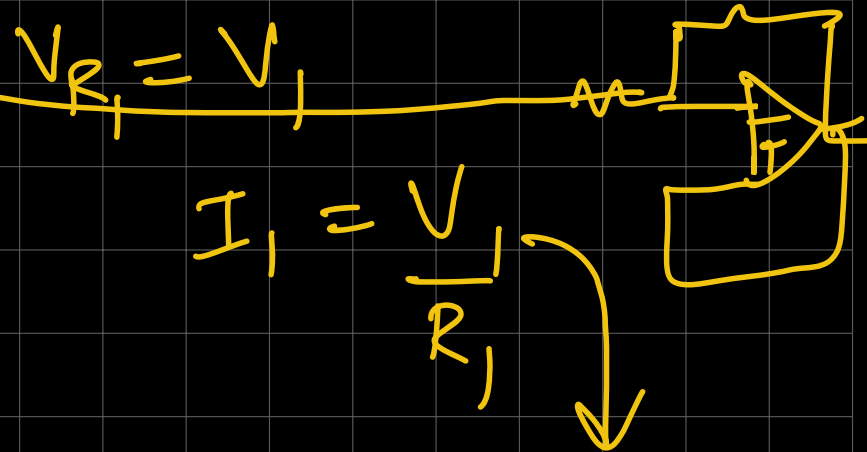


$$V_{R_1} = V_1$$

$$I_1 = \frac{V_1}{R_1}$$



$$V_{R_3} = 0 - v_{out} = I_1 R_3$$
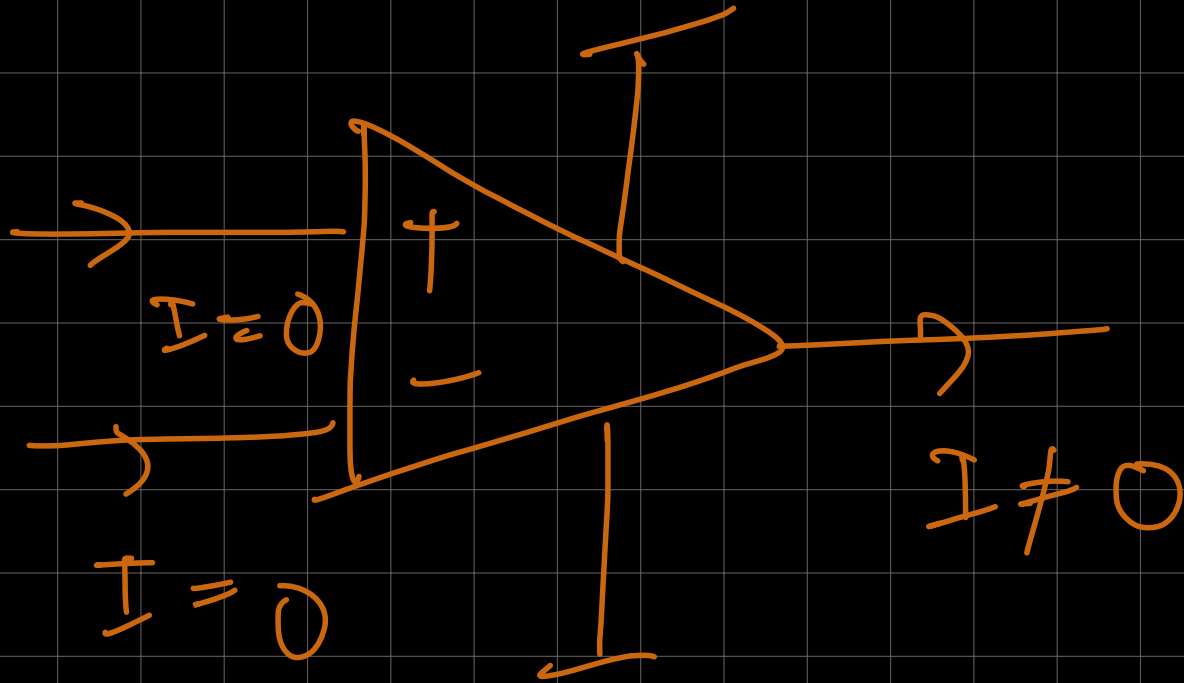
$$v_{out} = \left[ -\frac{R_f}{R_1} V_1 - \frac{R_f}{R_2} V_2 - \dots - \frac{R_f}{R_n} V_n \right]$$







# Loading and Cascading

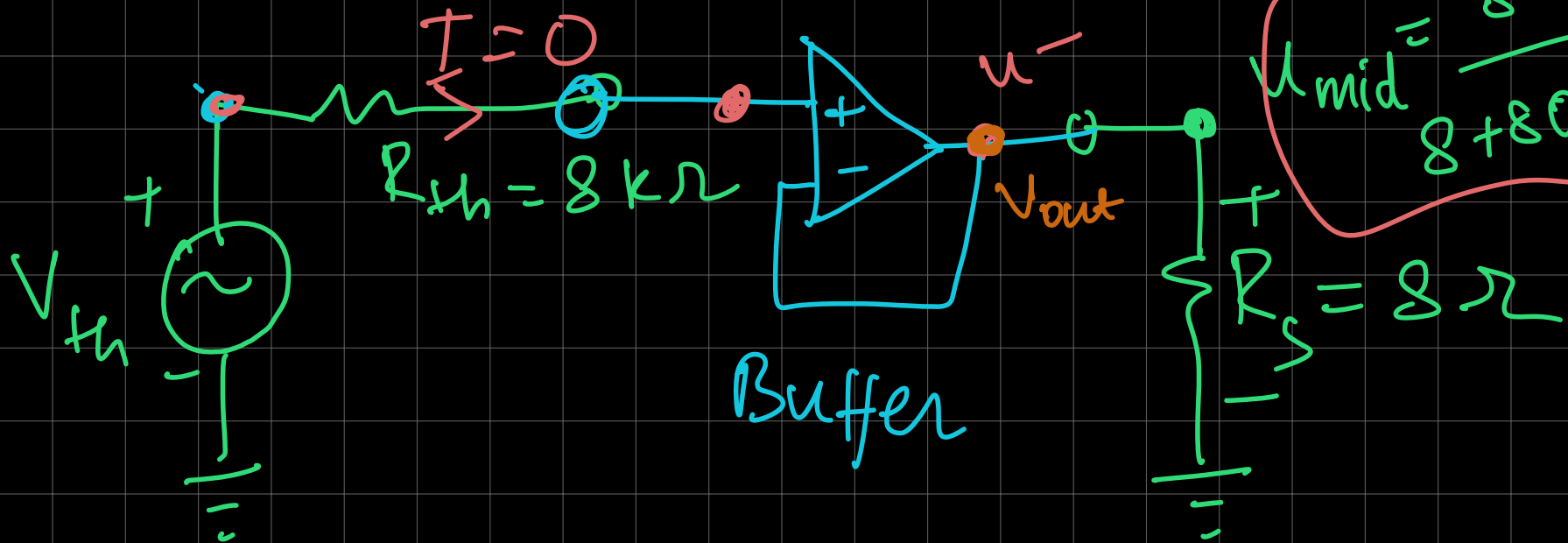
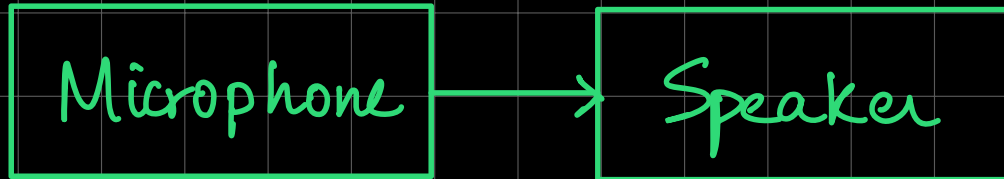


$$U_{mid} = \frac{8}{8+8000} V_{th}$$

$$U^+ = V_{th} = U^-$$

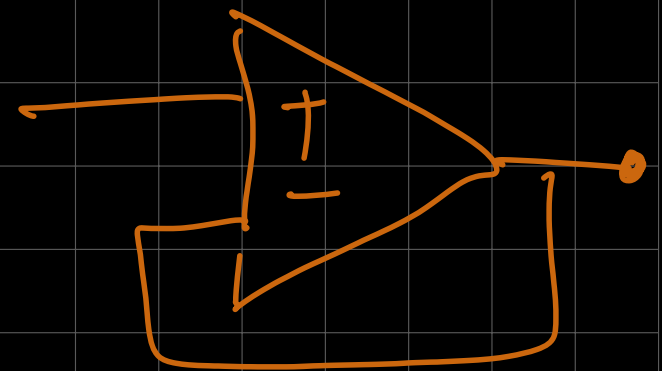


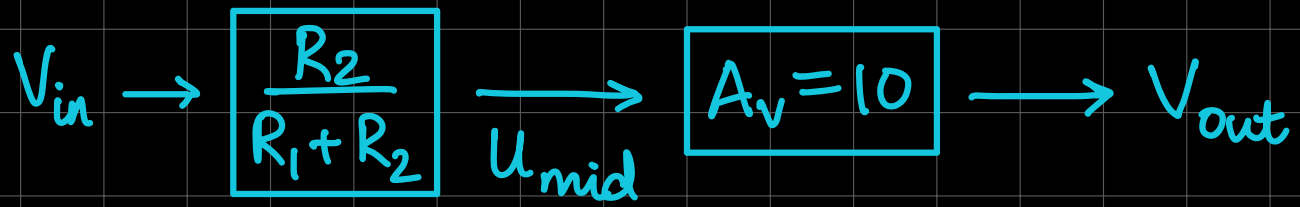

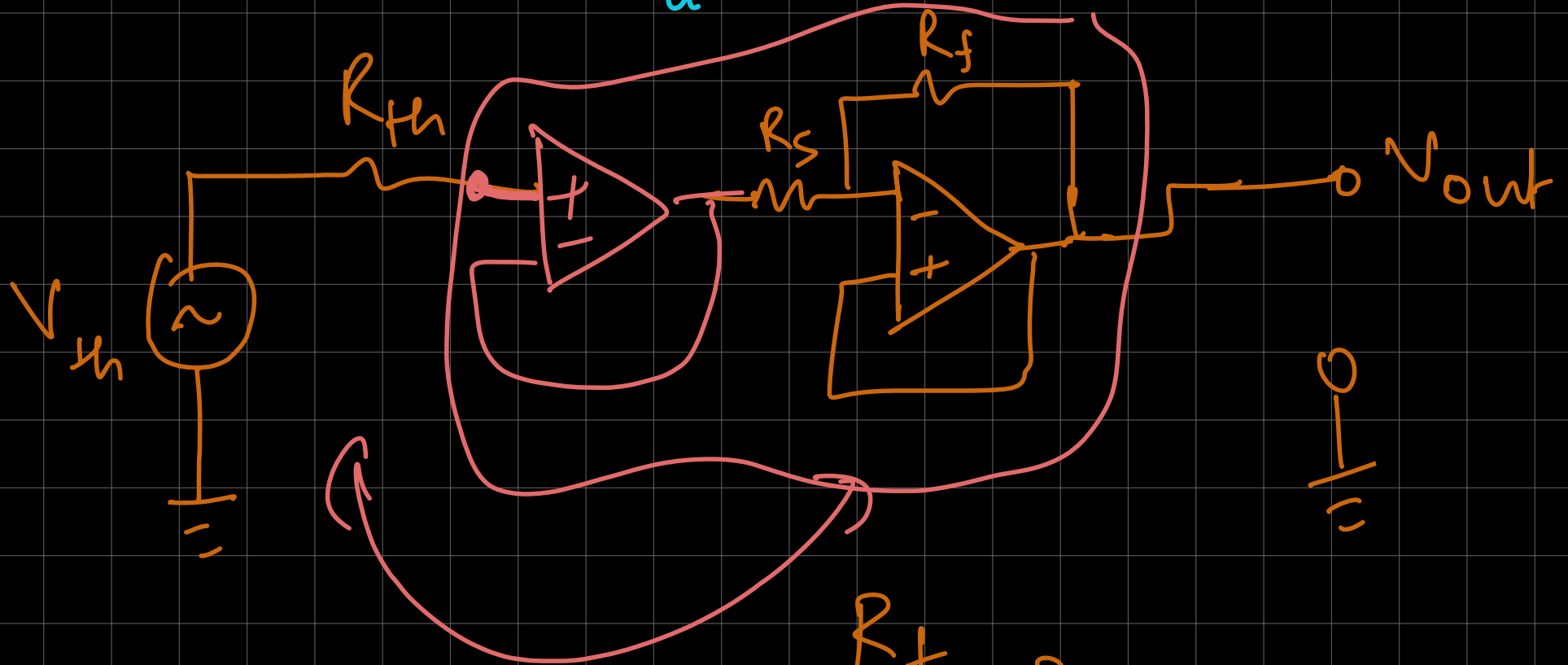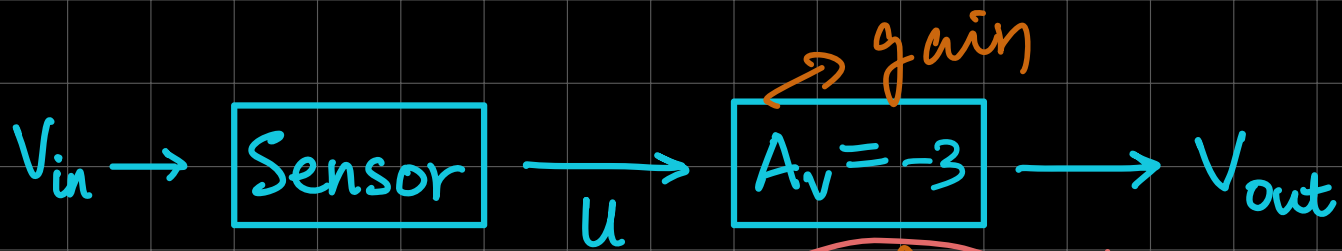

$$\frac{R_f}{R_s} = 3$$

# Loading and Cascading

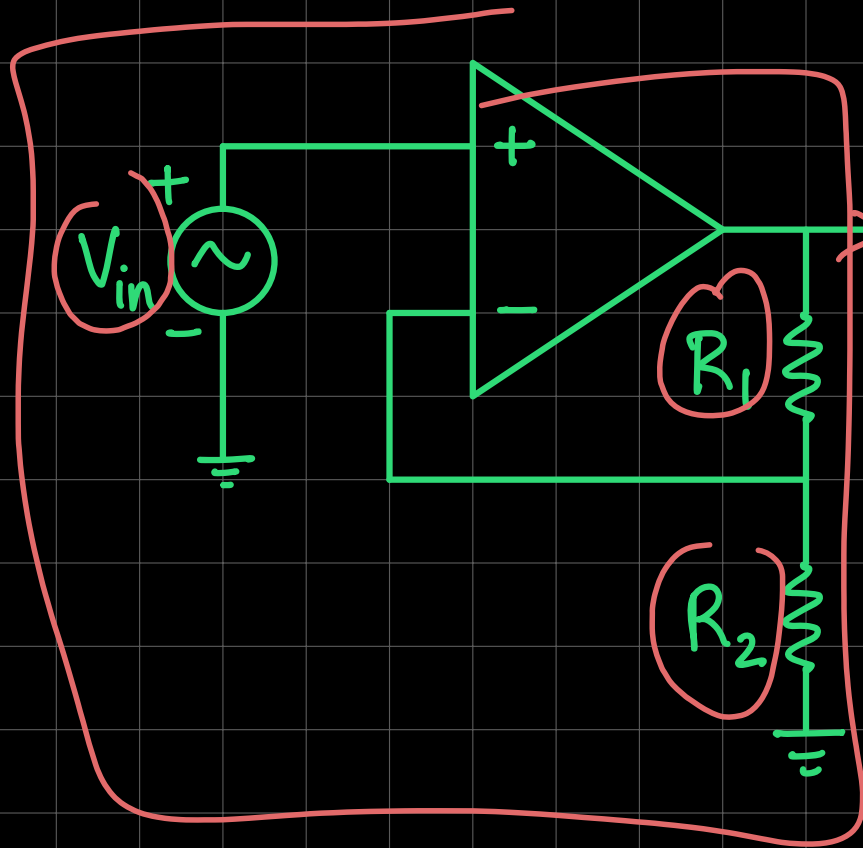

Before Connecting  $V_{out} = 2V$   
After Connecting  $V_{out} = 2V$

