

## Lecture 5B

### Agenda:


- Op Amp Circuit Analysis
- Inverting and Non-Inverting Amplifiers
- Circuit Design (Intro)

# Review


Golden Rules - (1)

(2)

## Buffer

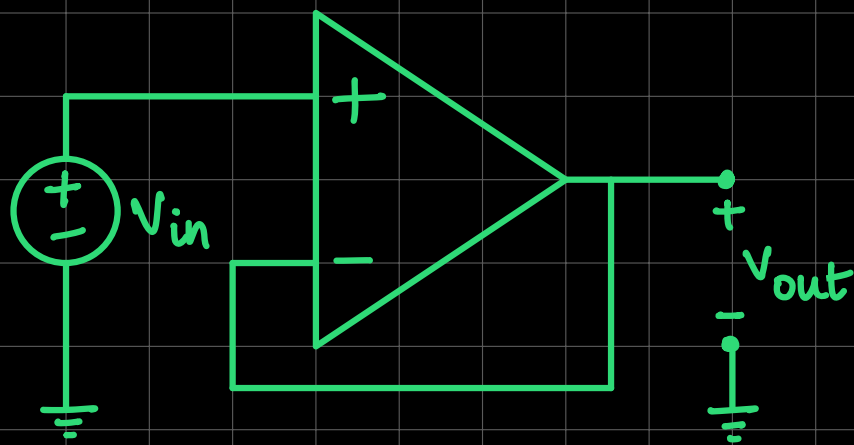


Voltage  
Source

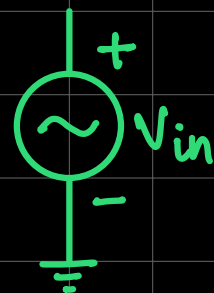


Voltage  
Signal

# Inverting Amplifier

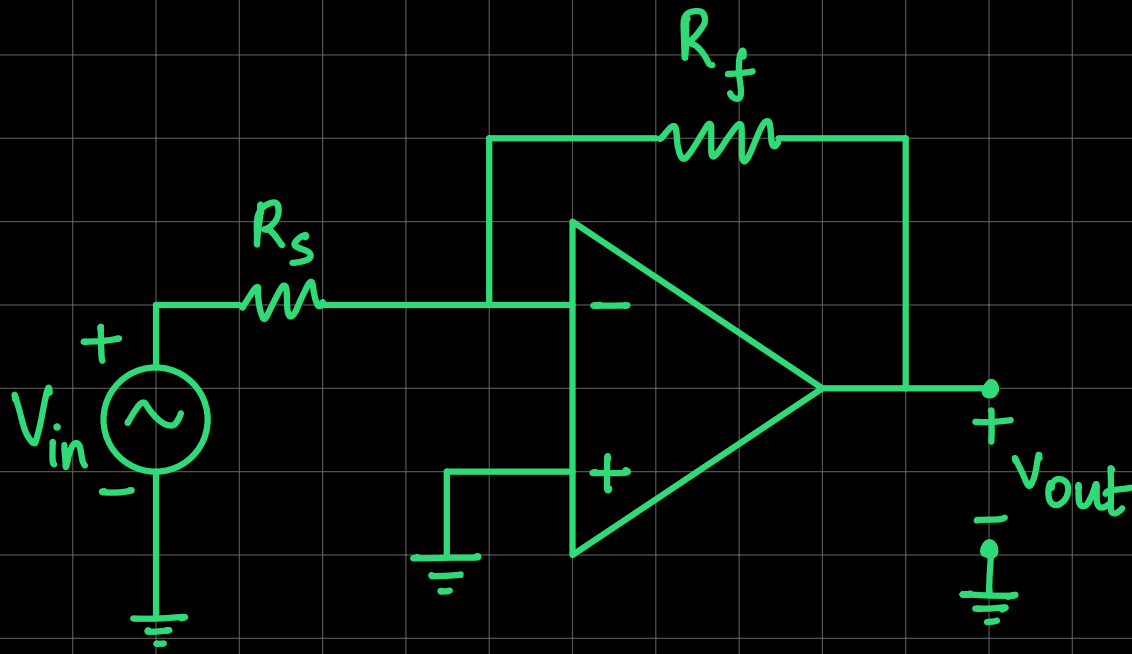


# Non-Inverting Amplifier

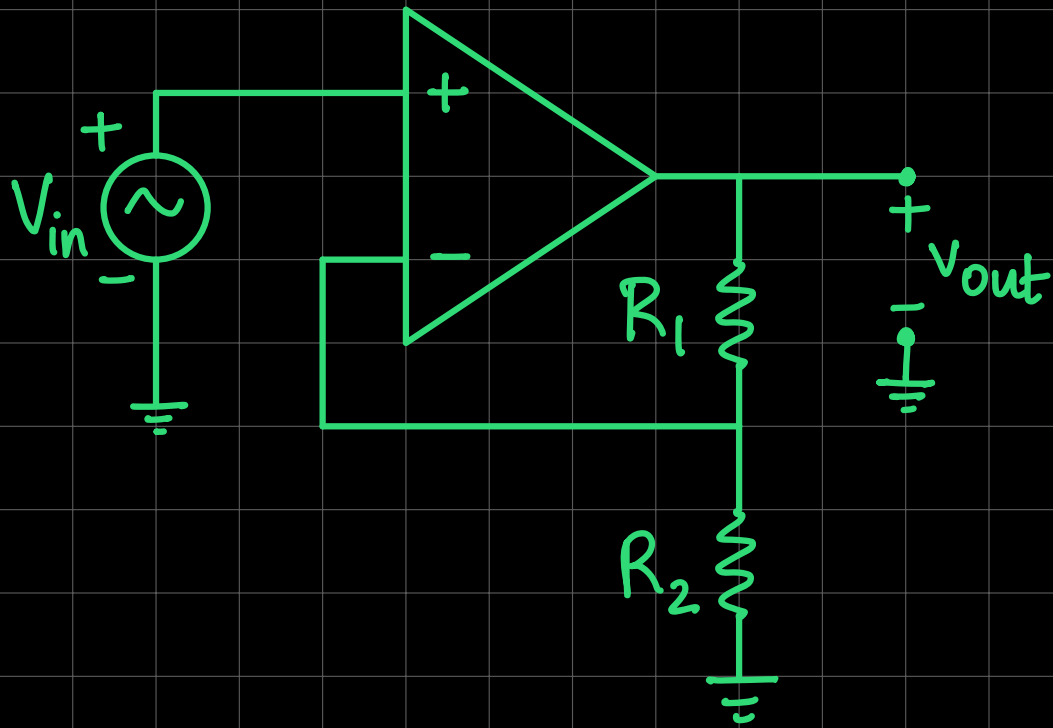


# OP-AMP CHEAT SHEET

### Voltage Divider

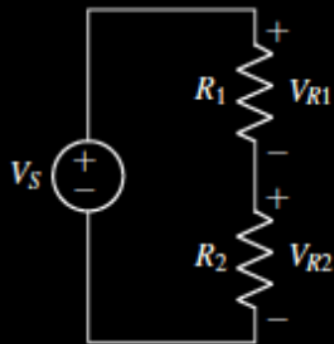


$$V_{R2} = V_S \left( \frac{R_2}{R_1 + R_2} \right)$$

### Voltage Summer

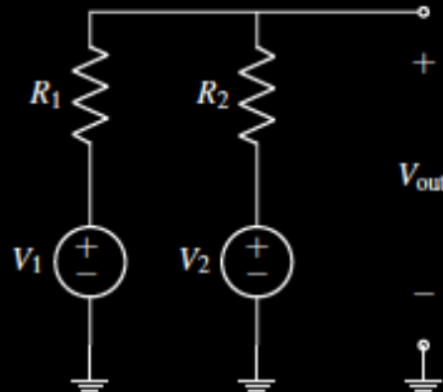


$$V_{out} = V_1 \left( \frac{R_2}{R_1 + R_2} \right) + V_2 \left( \frac{R_1}{R_1 + R_2} \right)$$

### Unity Gain Buffer

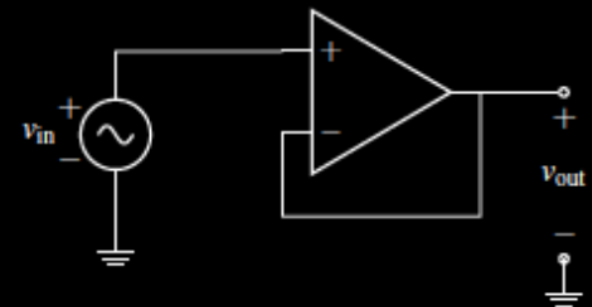


$$\frac{v_{out}}{v_{in}} = 1$$

### Inverting Amplifier

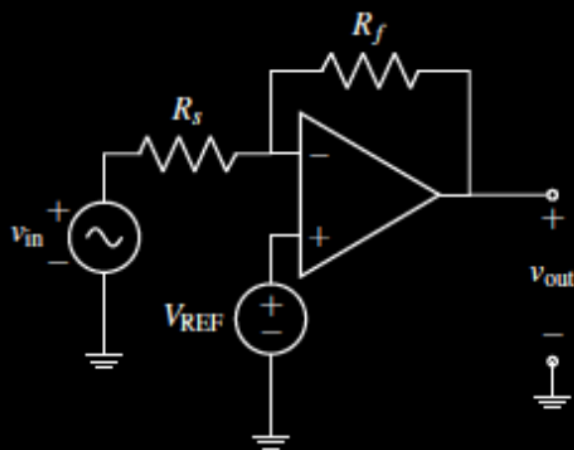


$$v_{out} = v_{in} \left( -\frac{R_f}{R_s} \right) + V_{REF} \left( \frac{R_f}{R_s} + 1 \right)$$

### Non-inverting Amplifier

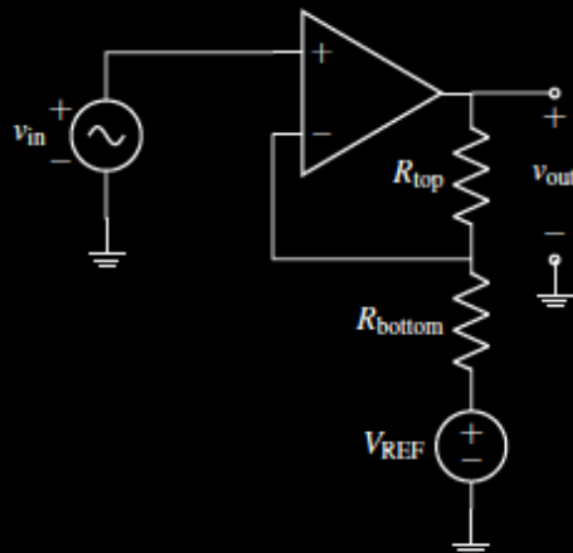

$$v_{out} = v_{in} \left( 1 + \frac{R_{top}}{R_{bottom}} \right) - V_{REF} \left( \frac{R_{top}}{R_{bottom}} \right)$$

### Transresistance Amplifier

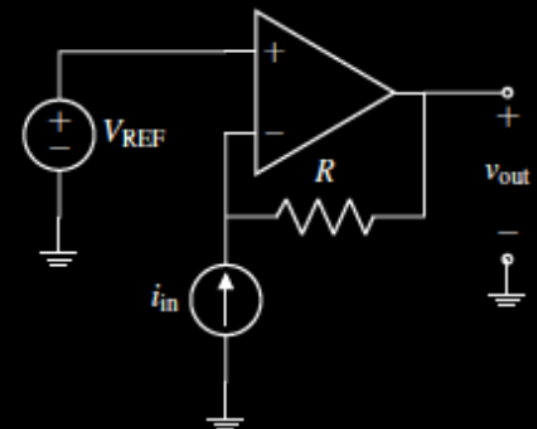


$$v_{out} = i_{in}(-R) + V_{REF}$$


# Artificial Neuron

Inputs

Weights

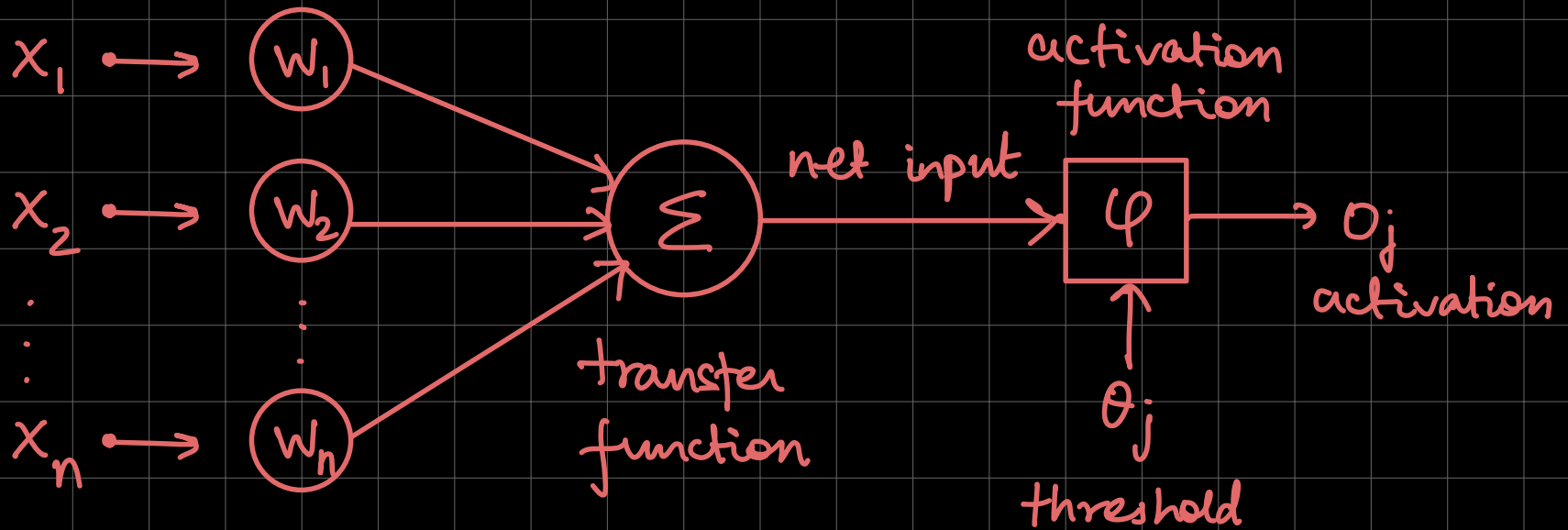


# Artificial Neuron

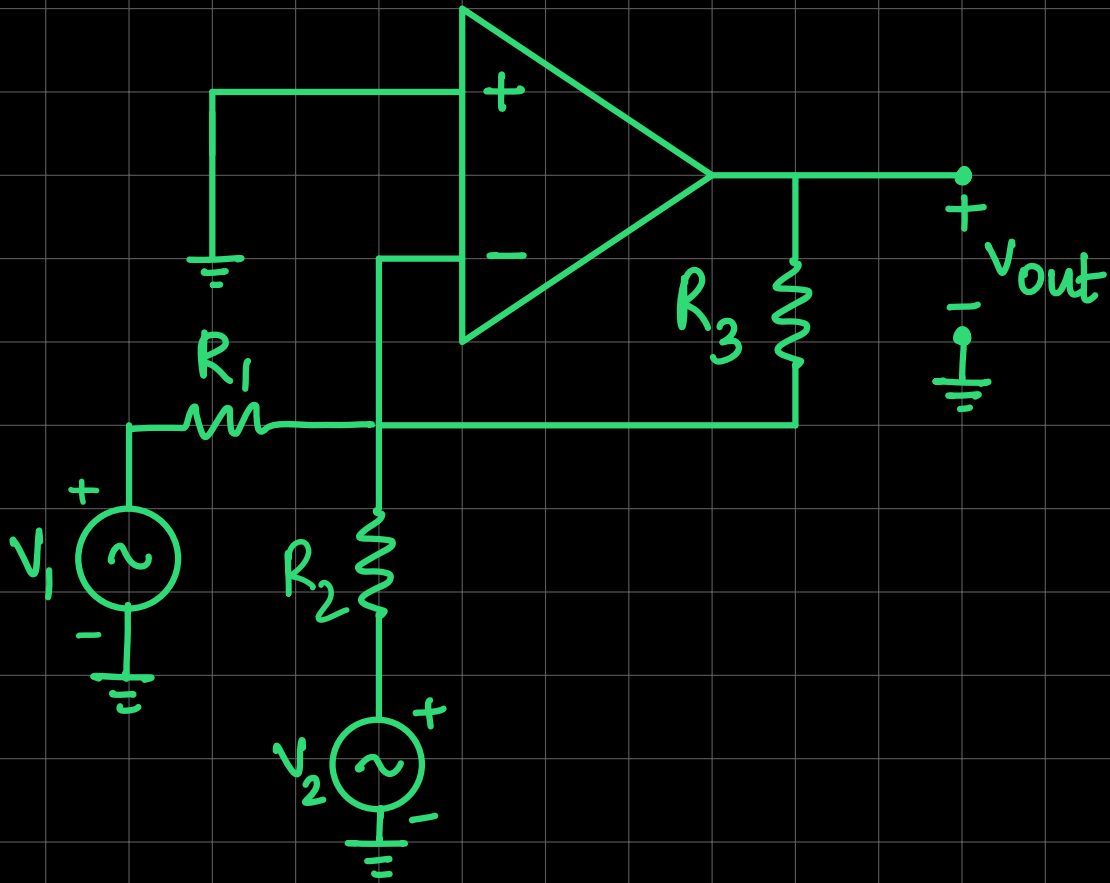








# Loading and Cascading

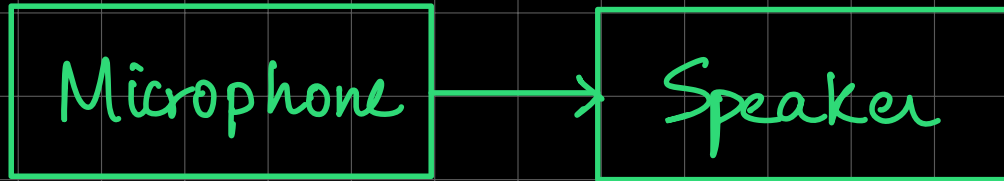

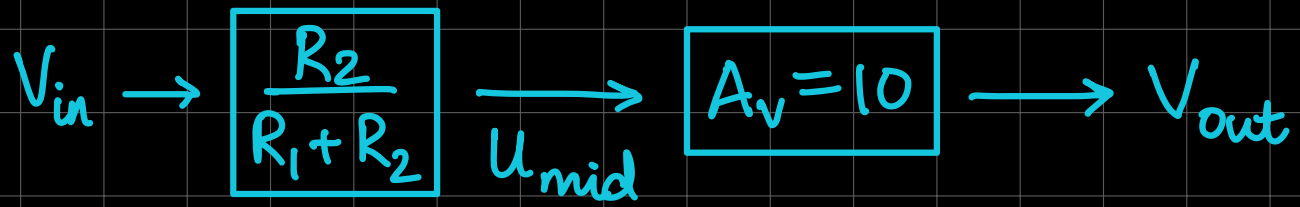

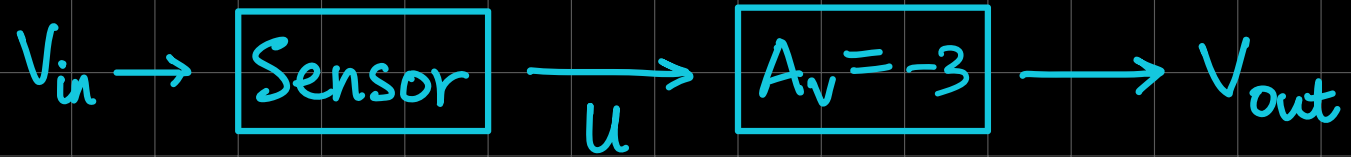


# Loading and Cascading

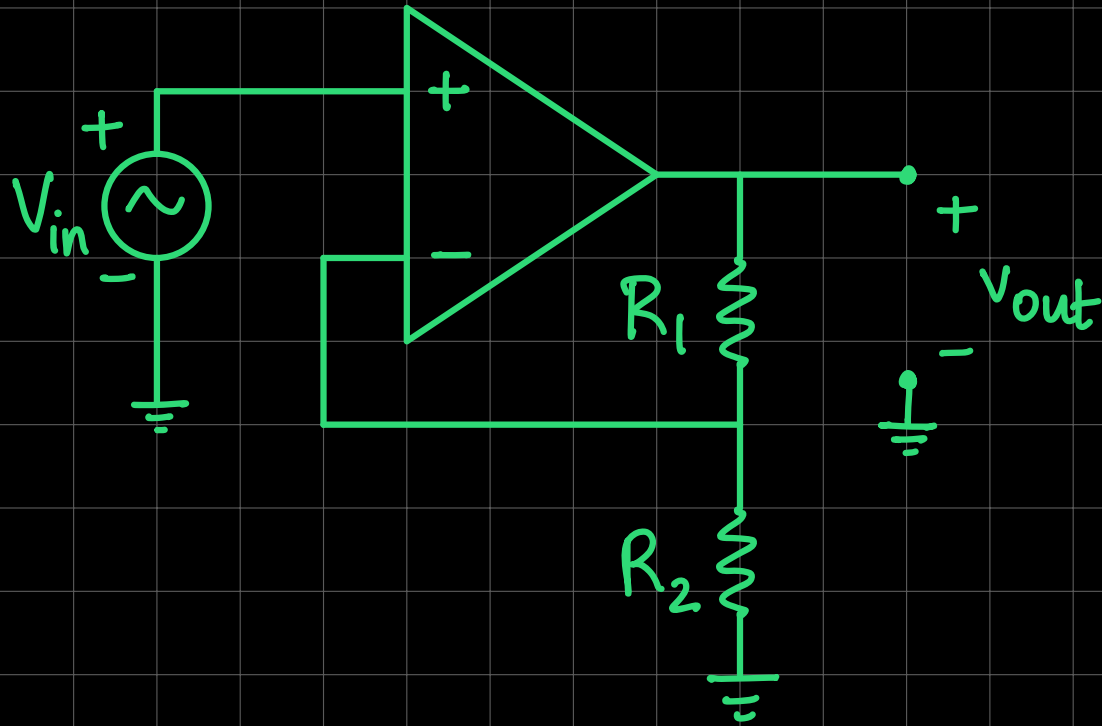

# Design

- ① Specification - Restate your design goals
- ② Strategy - Describe your strategy
- ③ Implementation - Implement components of your strategy
- ④ Verification - Check your design from step 3

# Countdown Timer

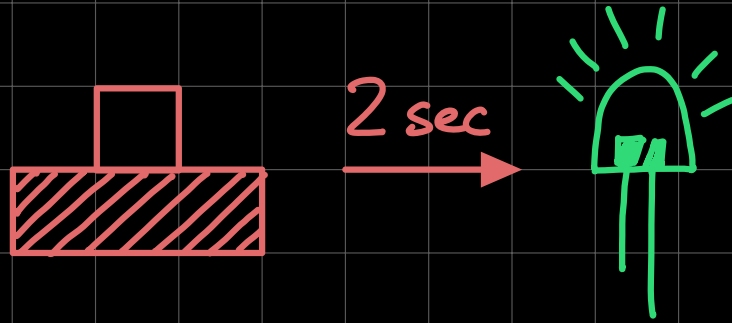

Objective →