

Lecture 5C


Agenda:

→ Circuit Design (Examples)

→ Intro to GPS


OP-AMP CHEAT SHEET

Voltage Divider

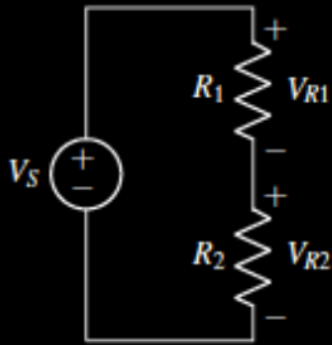


$$V_{R2} = V_S \left(\frac{R_2}{R_1 + R_2} \right)$$

Voltage Summer

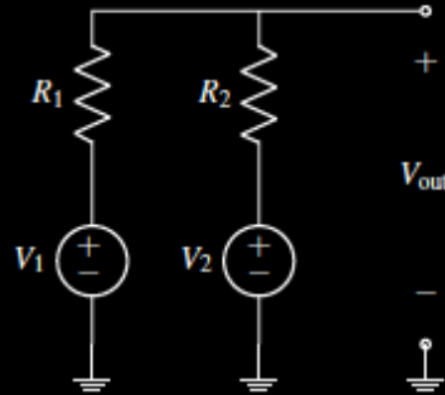


$$V_{out} = V_1 \left(\frac{R_2}{R_1 + R_2} \right) + V_2 \left(\frac{R_1}{R_1 + R_2} \right)$$

Unity Gain Buffer

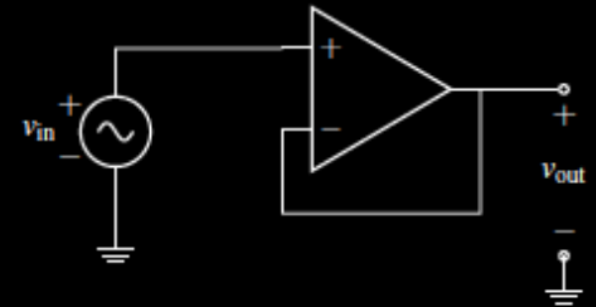


$$\frac{v_{out}}{v_{in}} = 1$$

Inverting Amplifier

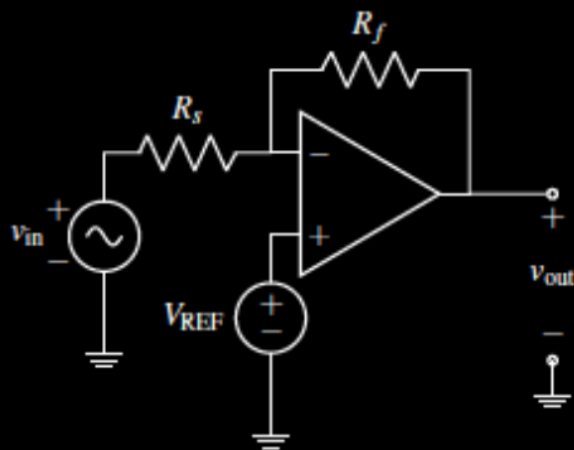


$$v_{out} = v_{in} \left(-\frac{R_f}{R_s} \right) + V_{REF} \left(\frac{R_f}{R_s} + 1 \right)$$

Non-inverting Amplifier

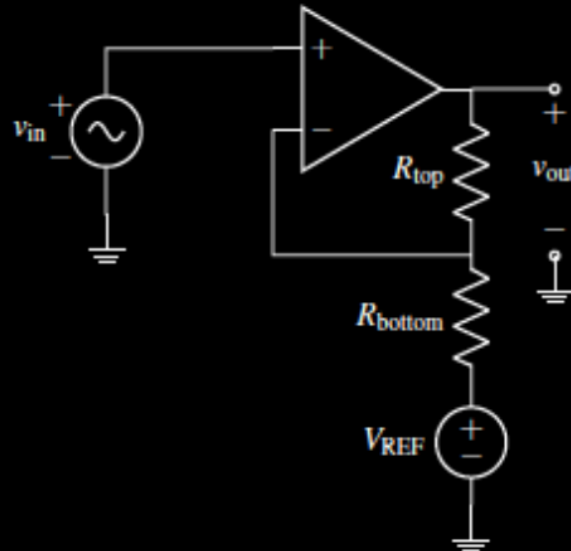

$$v_{out} = v_{in} \left(1 + \frac{R_{top}}{R_{bottom}} \right) - V_{REF} \left(\frac{R_{top}}{R_{bottom}} \right)$$

Transresistance Amplifier

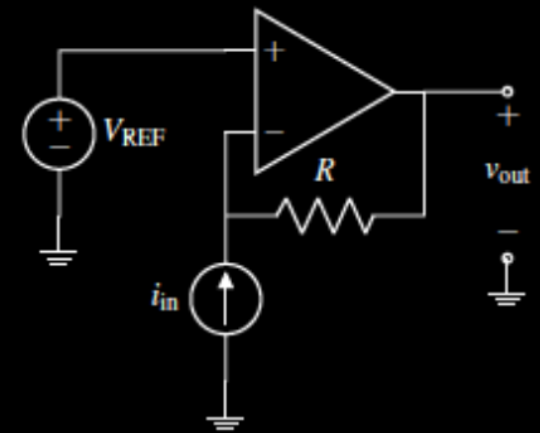


$$v_{out} = i_{in}(-R) + V_{REF}$$

Design


- ① Specification - Restate your design goals
- ② Strategy - Describe your strategy
- ③ Implementation - Implement components of your strategy
- ④ Verification - Check your design from step 3

Countdown Timer

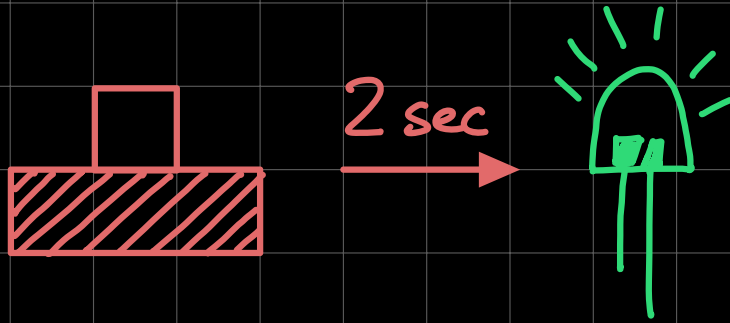

Objective →

Current Source

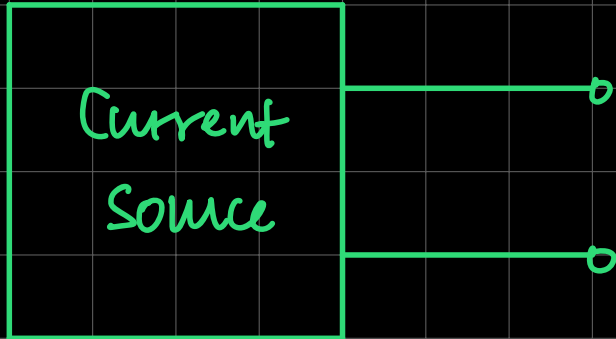

Integrator

Differentiator

Navigation (Intro to GPS)

In 1 Dimension

In 2 Dimension