

Lecture 7A

Agenda:

- Energy stored in capacitors
- NVA Hack
- Steady State analysis for capacitors
- Thevenin/Norton Equivalence

Energy Stored in a Capacitor

$$P = IV = \frac{dE}{dt}$$

$$\frac{dE}{dt} = I \cdot V \Rightarrow dE = V I dt$$

$$\Rightarrow dE = V I dt$$


$$I = c \frac{dV}{dt}$$

$$dE = V \cdot c dV = \underline{cV dV}$$


$$\int dE = \int cV dV \Rightarrow E = c \left(\frac{V^2}{2} \right) \quad I dt = c dV$$


$$(Q = cV)$$
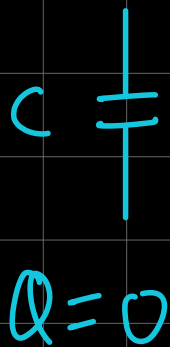
$$E = \frac{1}{2} c V^2 = \frac{c^2 V^2}{2c} = \frac{Q^2}{2c}$$



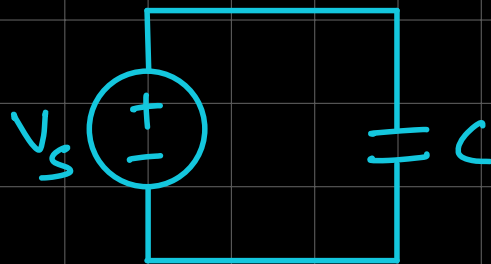
A circuit diagram showing a capacitor with capacitance C . The capacitor is represented by two parallel vertical lines. Below the capacitor, it is noted that the charge $Q = 0$.



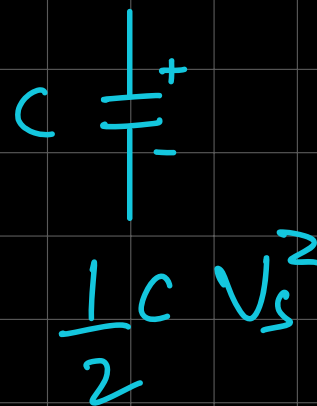

A circuit diagram showing a capacitor with capacitance C . The capacitor is represented by two parallel vertical lines. Below the capacitor, the energy stored is given as $\frac{1}{2} c V_s^2$.

NVA Hack

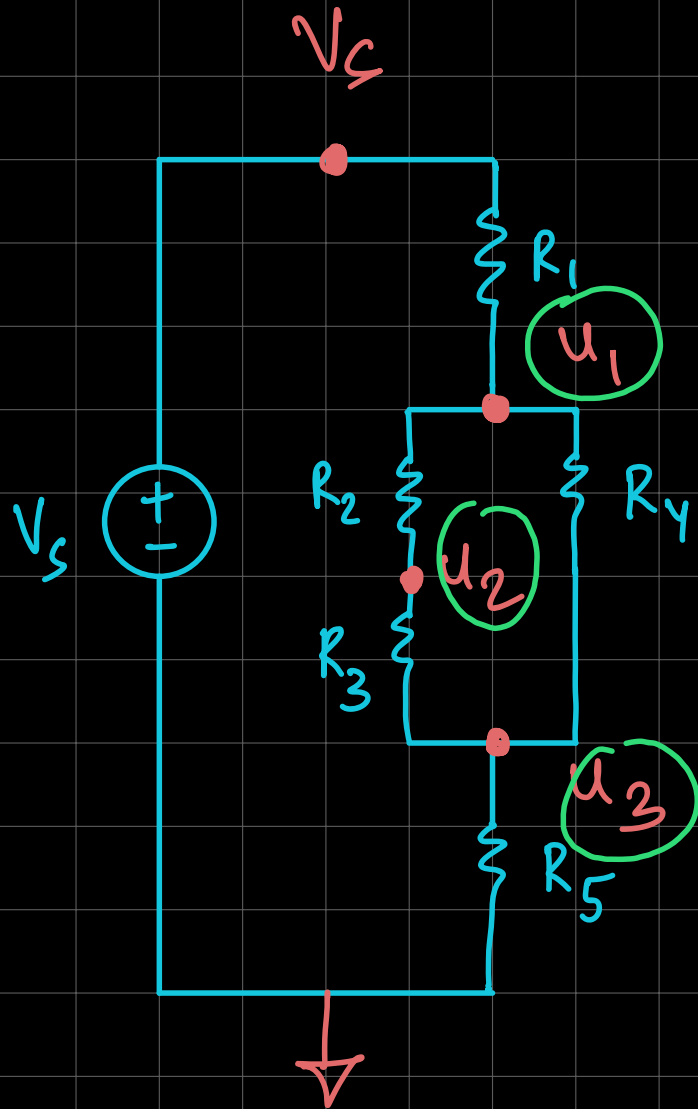

$$\underbrace{\frac{u_1}{R_1} + \frac{u_1}{R_2} + \frac{u_1}{R_4}} - \underbrace{\frac{u_2}{R_2}} - \underbrace{\frac{u_3}{R_4}} = \boxed{\frac{V_S}{R_1}}$$

$$\text{At } u_1: \boxed{\frac{u_1 - V_S}{R_1} + \frac{u_1 - u_2}{R_2} + \frac{u_1 - u_3}{R_4} = 0}$$

$$u_2: \frac{u_2 - u_1}{R_2} + \frac{u_2 - u_3}{R_3} = 0$$

$$u_3: \frac{u_3 - u_2}{R_3} + \frac{u_3 - 0}{R_5} + \frac{u_3 - u_1}{R_4} = 0$$

$$\underbrace{\frac{u_1}{R_1} + \frac{u_1}{R_2} + \frac{u_1}{R_4}} - \underbrace{\frac{u_2}{R_2}} - \underbrace{\frac{u_3}{R_4}} = \boxed{\frac{V_s}{R_1}}$$

$$\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4} \right) u_1 - \frac{1}{R_2} u_2 - \frac{1}{R_4} u_3 = \frac{V_s}{R_1}$$



$$\left[\begin{array}{ccc|c} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4} \right) & -\frac{1}{R_2} & -\frac{1}{R_4} & \frac{V_s}{R_1} \\ \cdot & \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot & \cdot \end{array} \right]$$


Capacitors (Steady State)

$$V = \frac{Q}{C} \leftarrow$$

U_A, U_B, U_C

Capacitors were initially uncharged

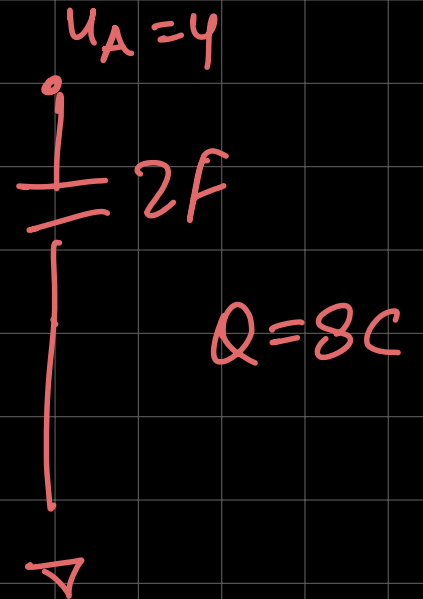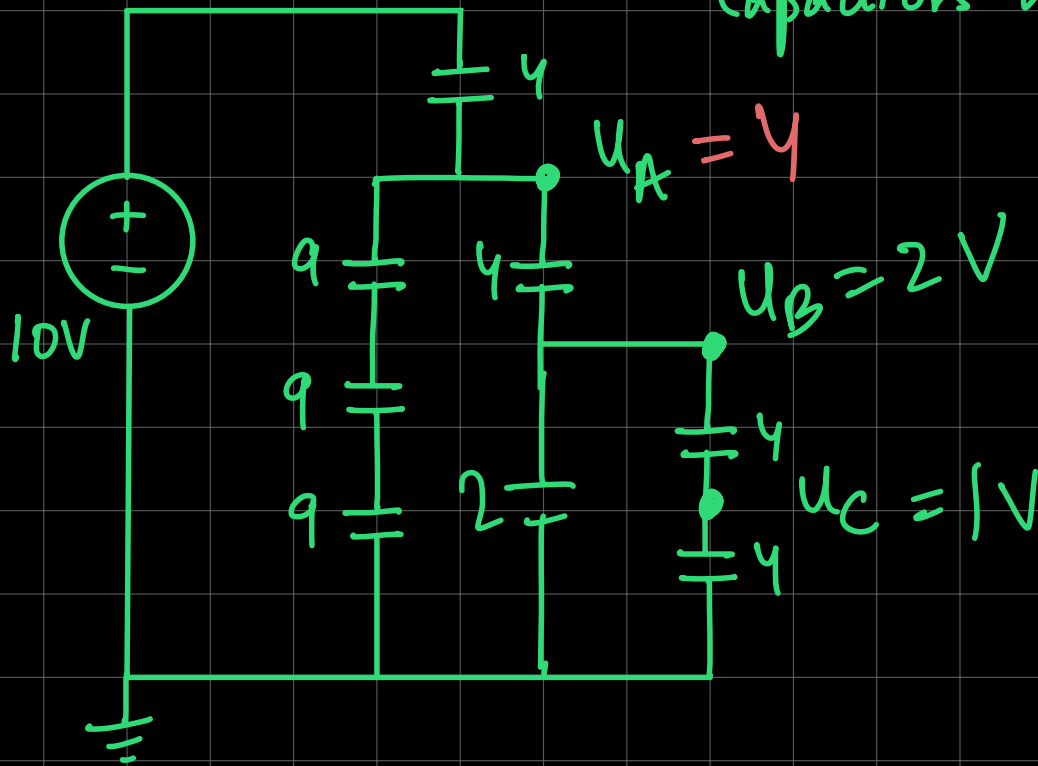

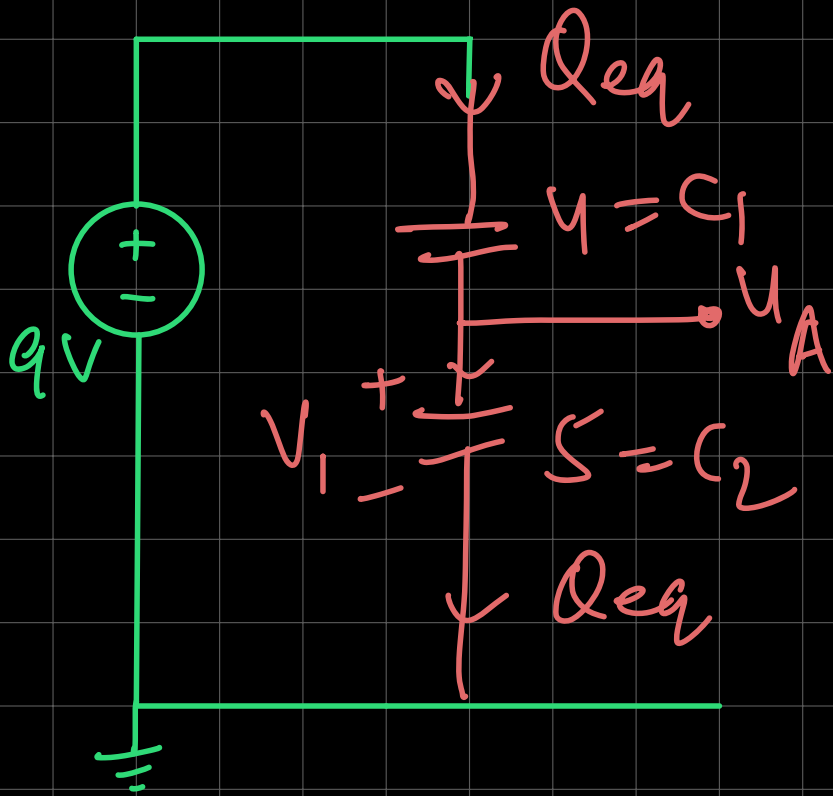

$$Q_{eq} = CV = \frac{20}{9} \times 9 = \boxed{20}$$


$$Q_{eq} = 20 = 5V_1$$

$$V_1 = 4$$

$$U_A = 0 = 4$$

$$\boxed{U_A = 4}$$


$$U_A = \frac{4}{4+5} \times 9 = 4V$$

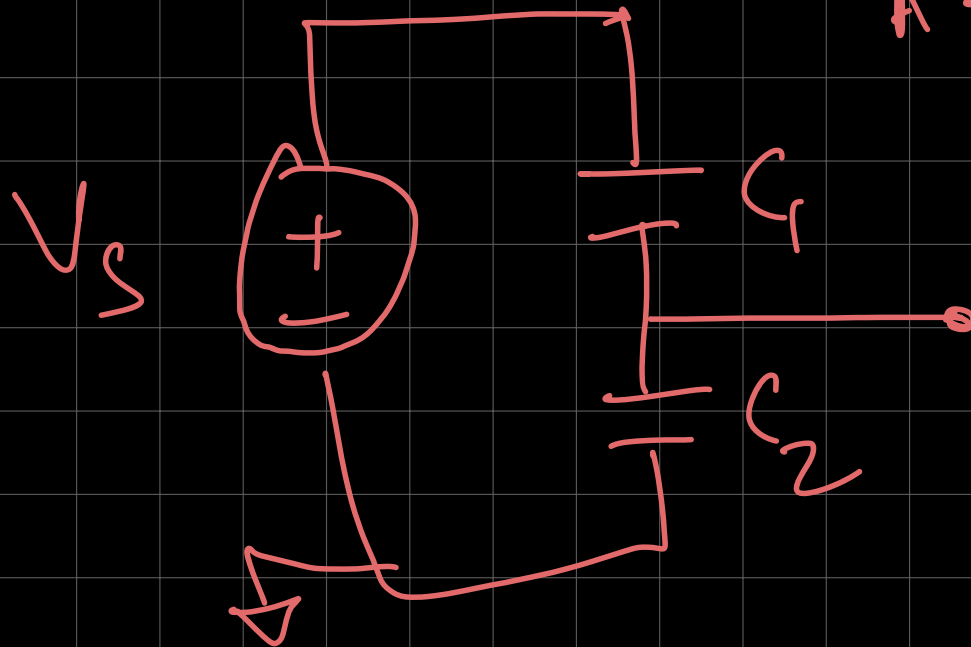


$$U_{mid} = \frac{C_1}{C_1 + C_2} V_S$$

Thevenin/Norton Equivalence


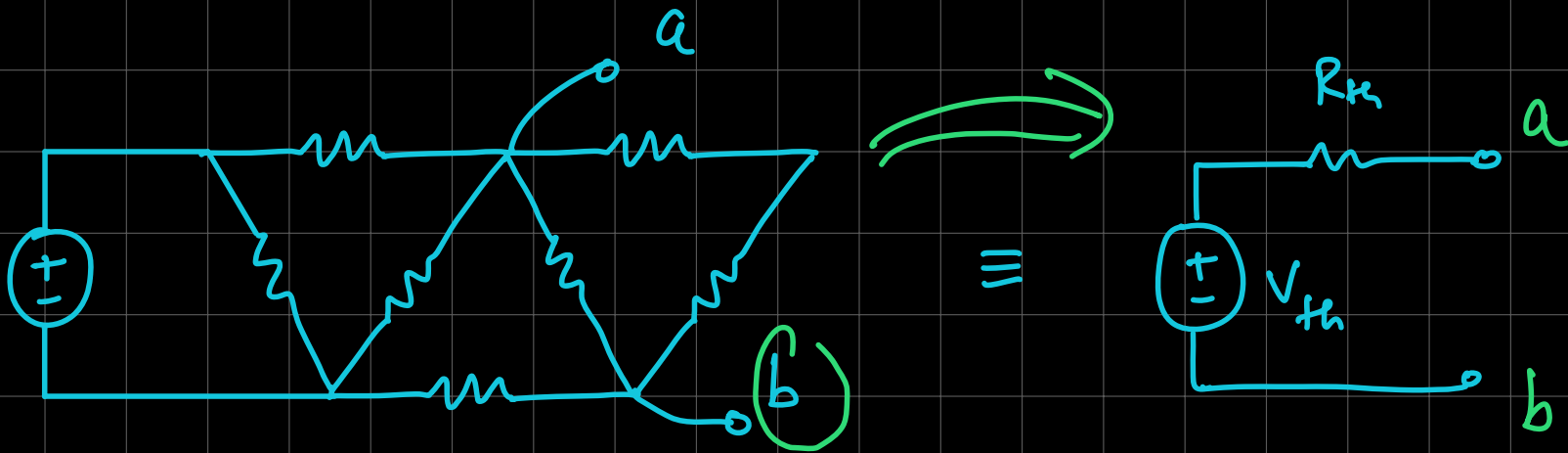
Any linear electrical network containing only voltage sources, current sources, and resistors can be replaced at terminals A-B by a single voltage source (V_{th}) and resistance (R_{th}).



Norton Equivalent


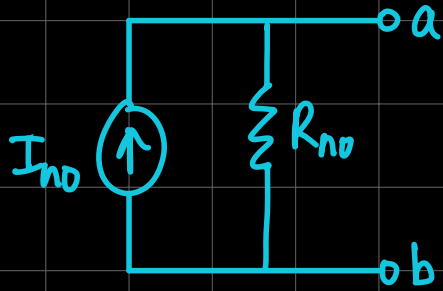


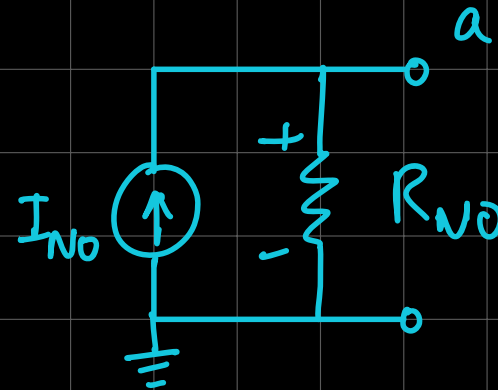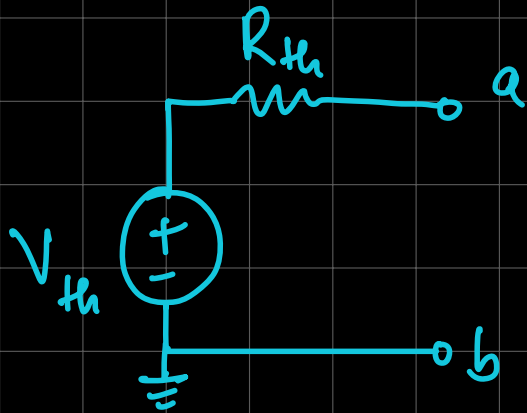Let's see how these are equivalent \rightarrow



$$I_{ab} = 0$$

$$V_{ab} = I_{No} R_{No}$$

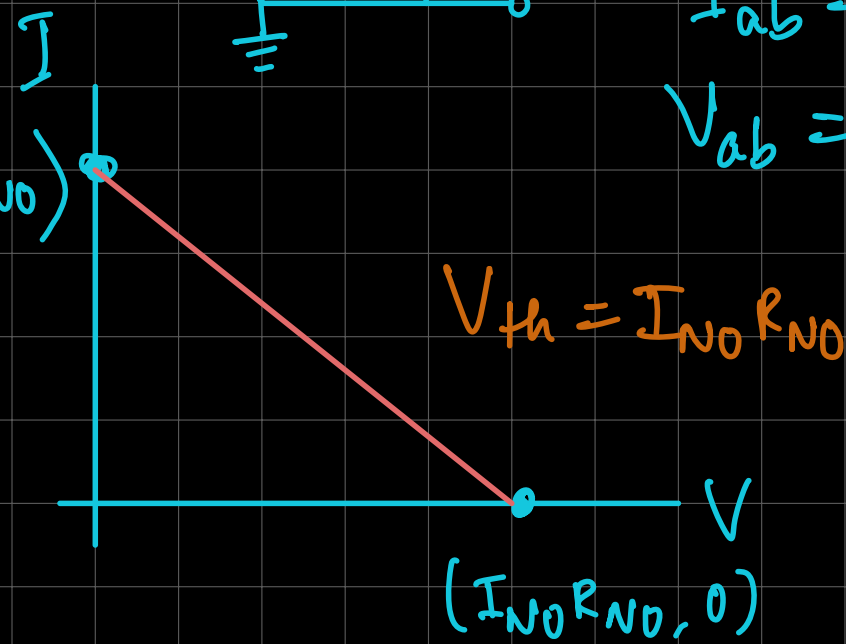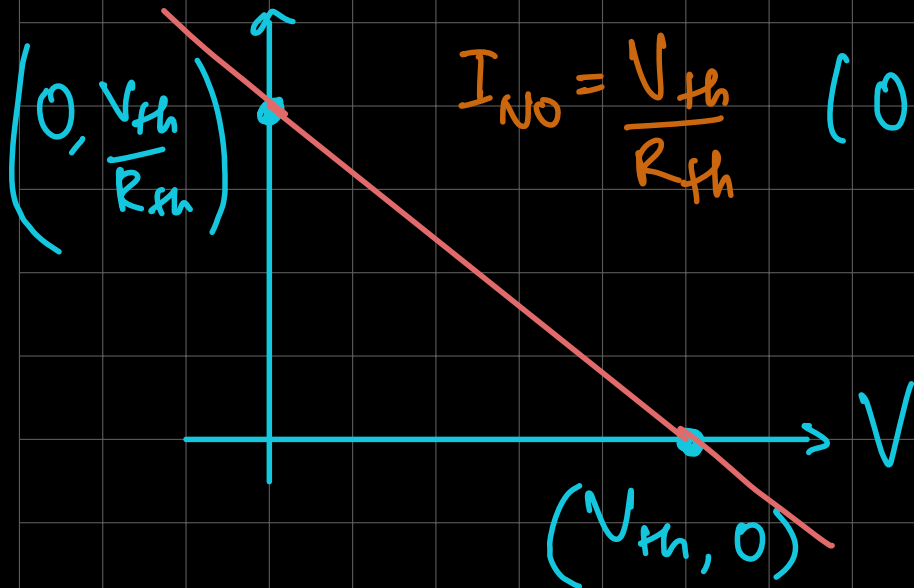




$$I_{NO} = \frac{V_{th}}{R_{th}}$$

$$V_{th} = I_{NO} R_{NO}$$

$$\cancel{V_{th}} = \frac{\cancel{V_{th}} R_{NO}}{R_{th}}$$

$$R_{NO} = R_{th}$$

Example

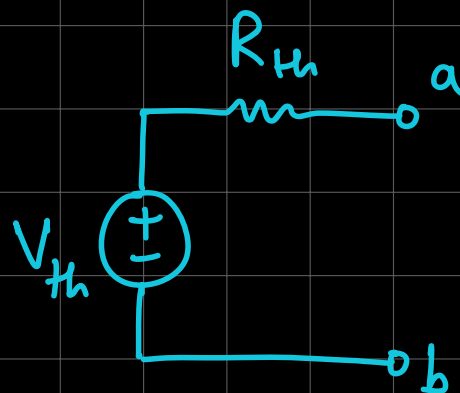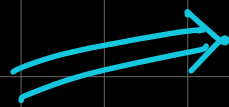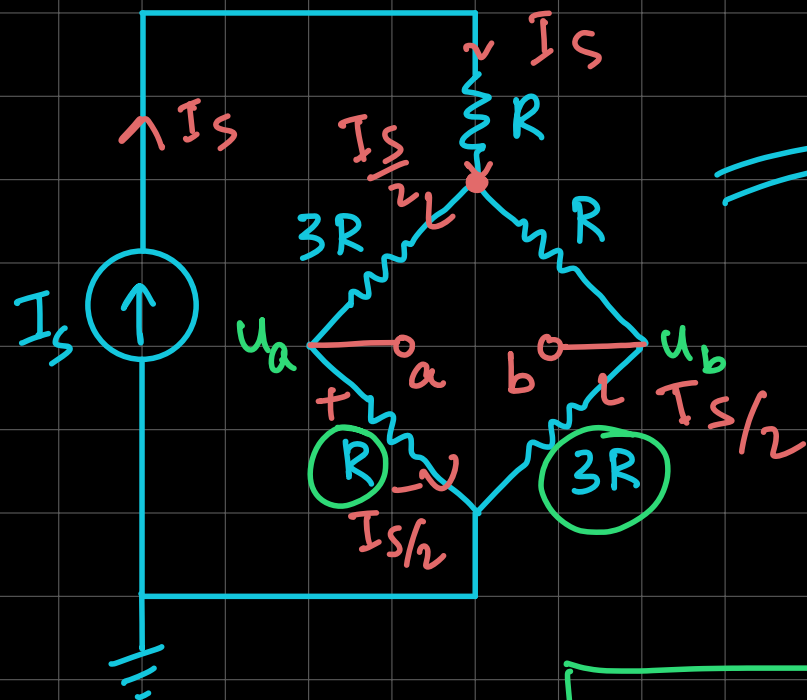


$$V_R = U_A - 0 = \frac{I_s R}{2} = \frac{1}{2} I_s R$$

$$V_R = U_b - 0 = \frac{I_s}{2} (3R) = \frac{3}{2} I_s R$$


$$\boxed{U_A - U_b = (-I_s R) = V_{th}} \Rightarrow \text{open circuit voltage}$$

$$R_{ab} = (3R + R) \parallel (3R + R)$$

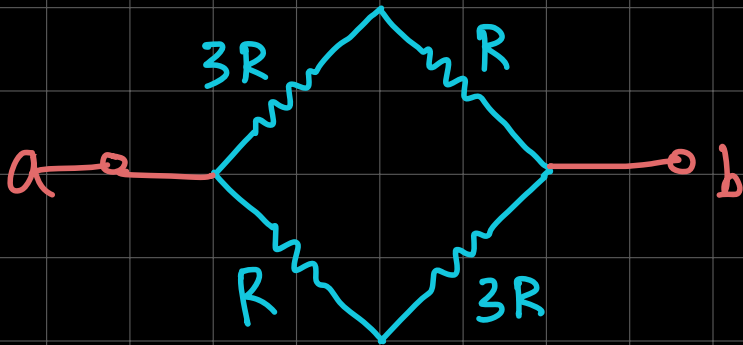
$$= 4R \parallel 4R = \underline{\underline{2R}}$$



Additional Questions during lecture

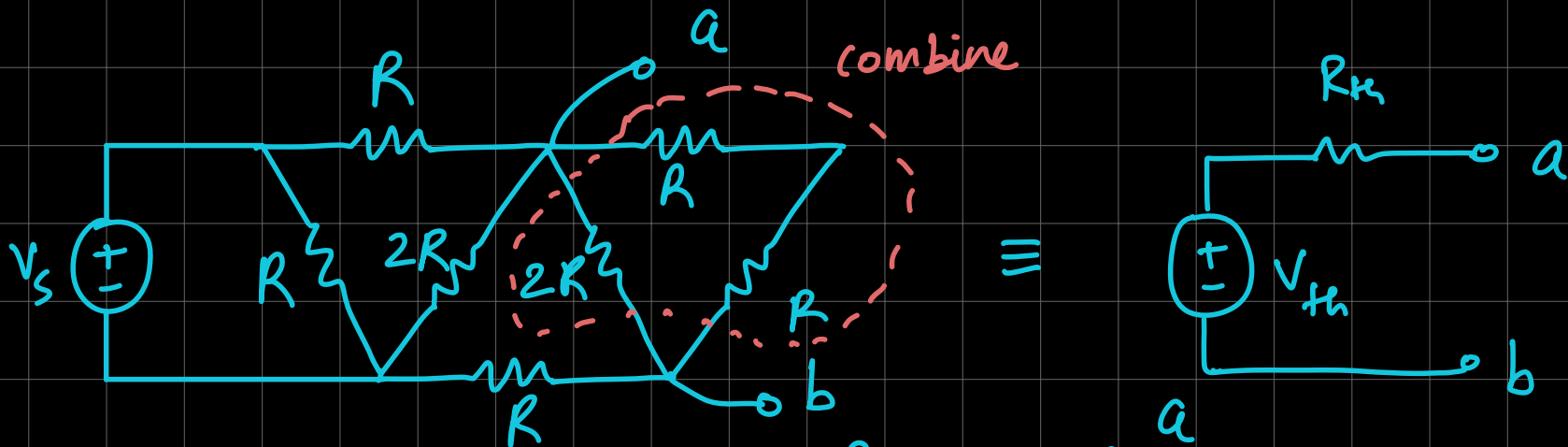


Finding V_{th} →


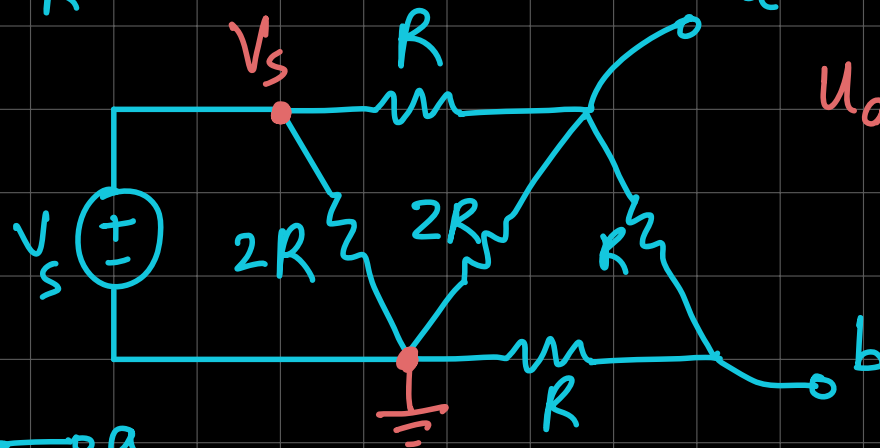


$$U_a = \frac{V_s}{2} \quad U_b = \frac{U_a}{2} = \frac{V_s}{4}$$

$$V_{ab} = V_{th} = \frac{V_s}{4}$$

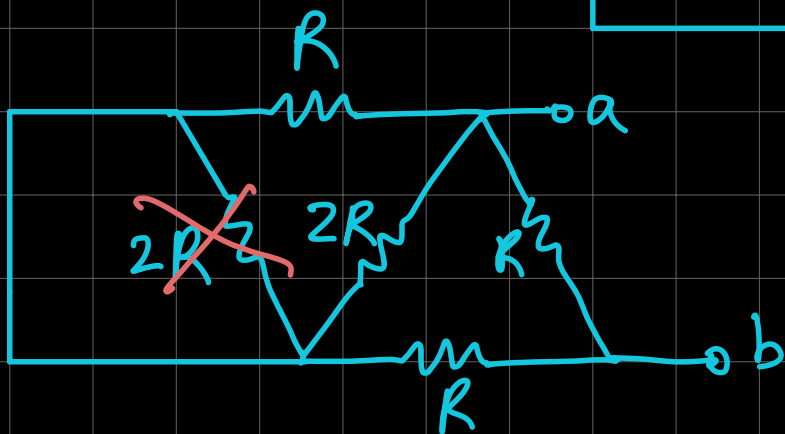
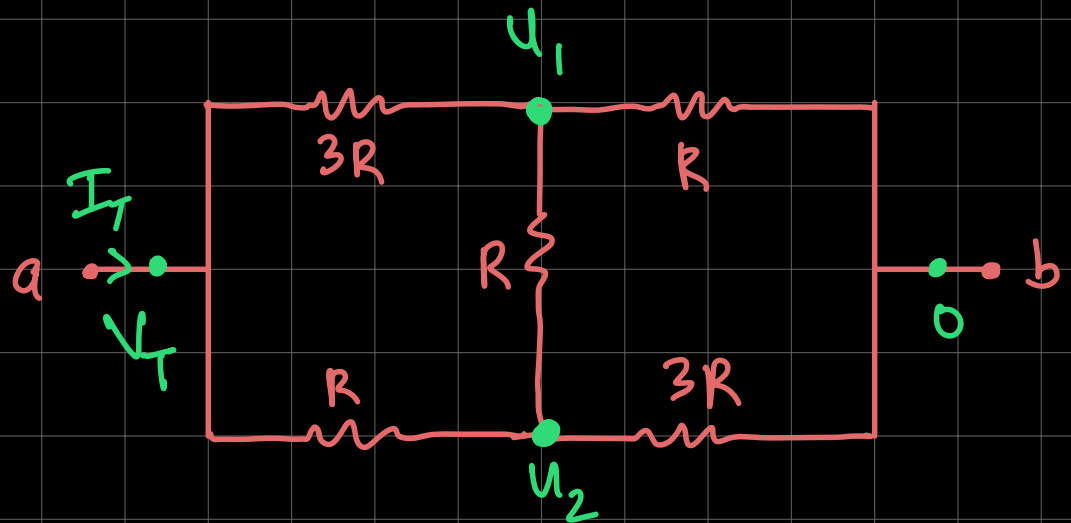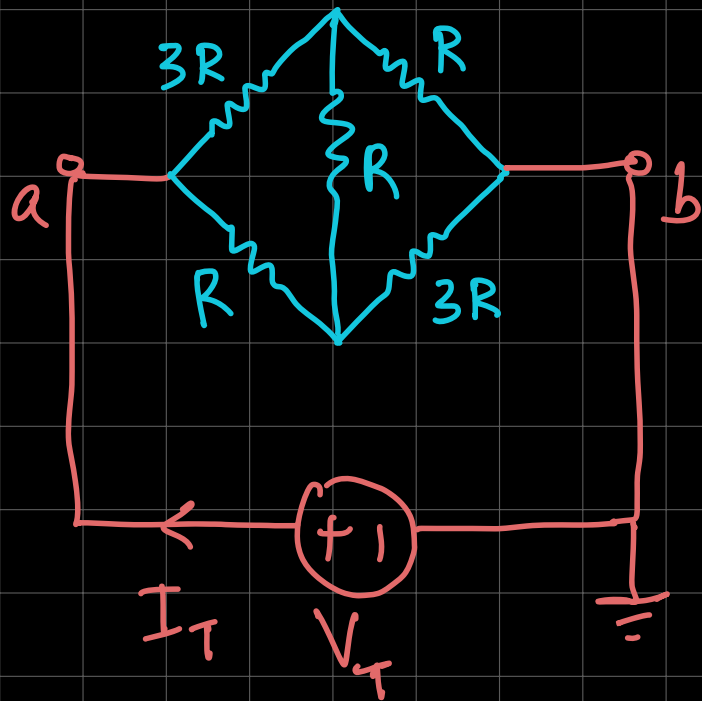
$$R_{ab} = R \parallel (R + R \parallel 2R) = \frac{5R}{8}$$



$$u_1: \frac{u_1 - V_T}{3R} + \frac{u_1 - u_2}{R} + \frac{u_1 - 0}{R} = 0$$

$$u_2: \frac{u_2 - u_1}{R} + \frac{u_2 - 0}{3R} + \frac{u_2 - V_T}{R} = 0$$

$$\frac{7}{3R} u_1 - \frac{u_2}{R} = \frac{V_T}{3R} \quad (1)$$

$$(1) + \frac{7}{3}(2) \Rightarrow \frac{40}{9} \frac{u_2}{R} = \frac{8V_T}{3R}$$

$$\frac{7}{3R} u_2 - \frac{u_1}{R} = \frac{V_T}{R} \quad (2)$$

$$u_2 = \frac{3V_T}{5} \quad u_1 = \frac{2V_T}{5}$$

$$\frac{V_T}{I_T} = \frac{5R}{3}$$

$$I_T = \frac{V_T - u_1}{3R} + \frac{V_T - u_2}{R} = \frac{3V_T}{5R}$$

$$R_{ab} = \frac{V_T}{I_T} = \frac{5R}{3}$$