



Lecture 7B

Agenda:

- Op Amps and Comparators
- Op Amp Circuit Analysis
- Circuit Design
- Capacitors and Charge Sharing
- Superposition
- Eigenstuff / least squares

Op Amps and Comparators

$$-V_{DD} = V_{SS}$$

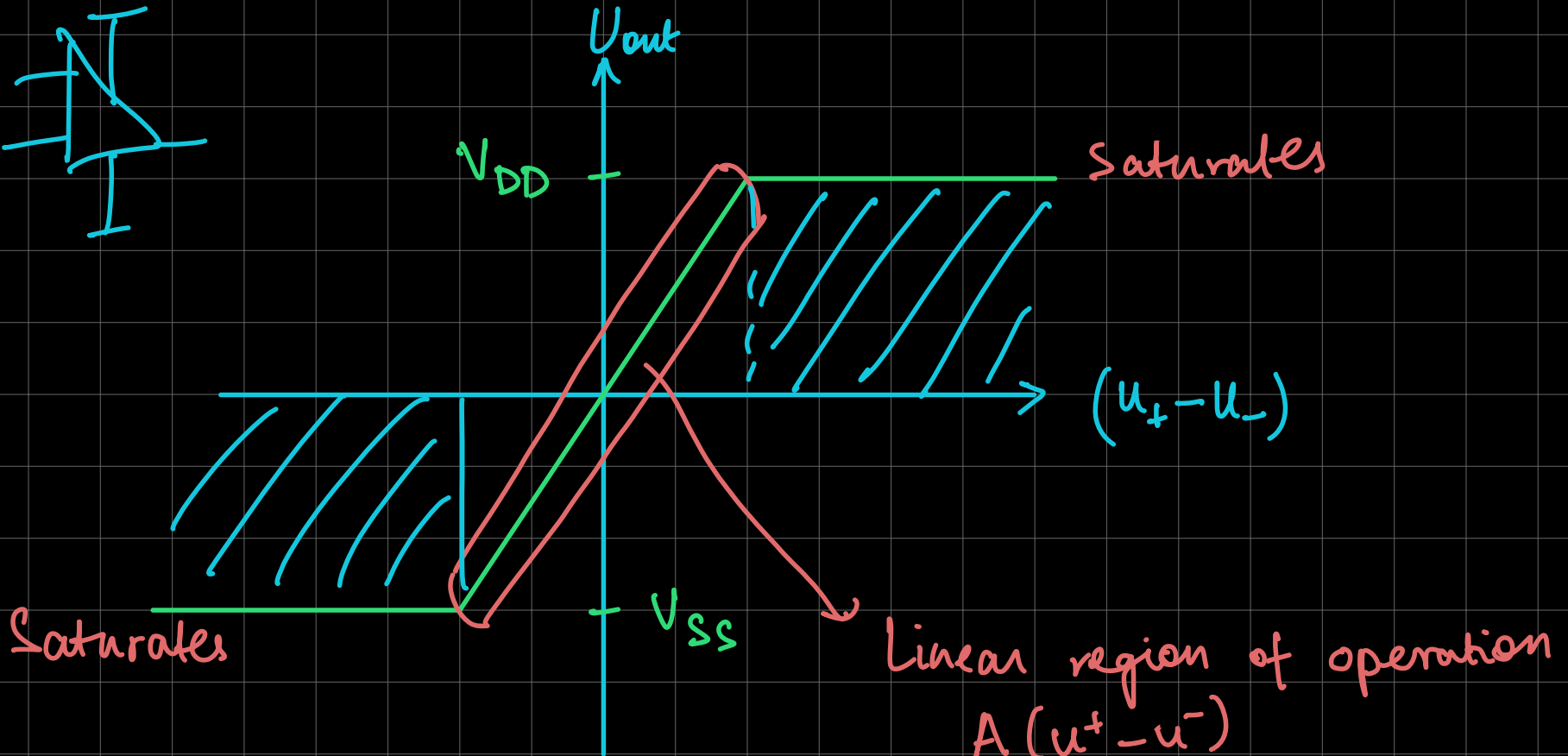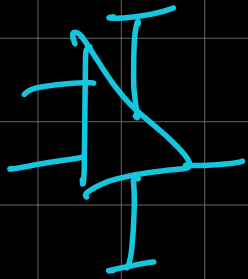

NFB \rightarrow $(A \rightarrow \infty)$
 $(u_+ - u_-)$


Golden Rules
Ideal Op Amp

$$I^+ = I^- = 0$$
$$u^+ = u^- \text{ in NFB}$$

OpAmp Circuit Analysis

$V_{out} = ?$

(SPI9 MT2)

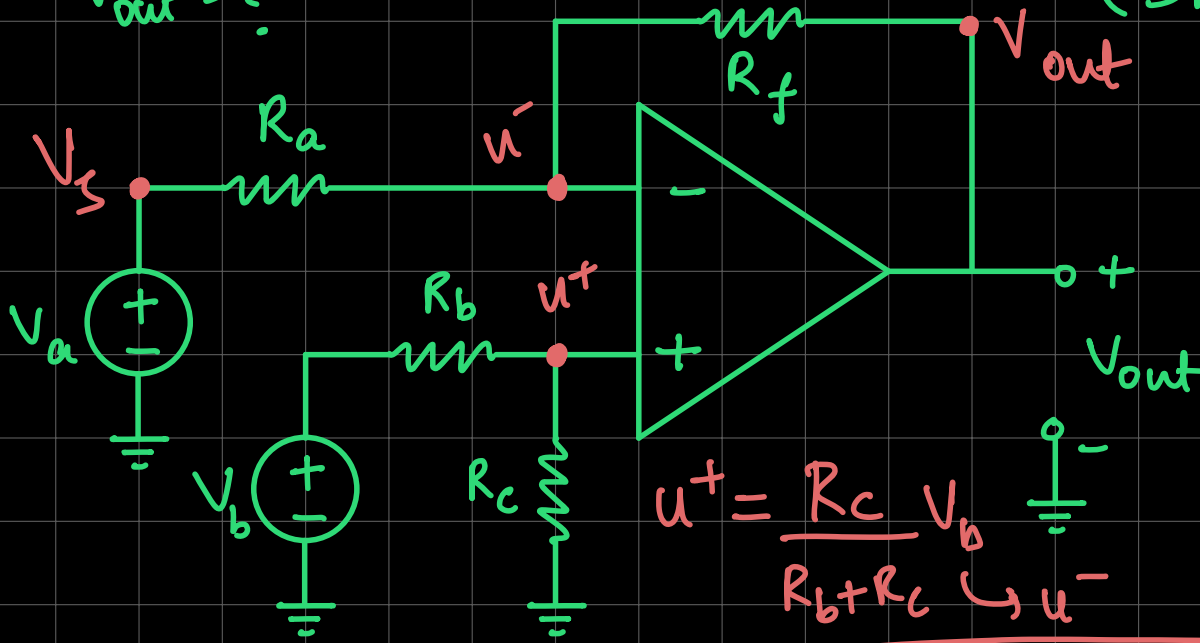

$$\frac{u^- - V_s}{R_a} + \frac{u^- - V_{out}}{R_f} = 0$$


$$u^+ = \frac{R_c}{R_b + R_c} V_b \rightarrow u^-$$

$$u^- \left(\frac{1}{R_a} + \frac{1}{R_f} \right) - \frac{V_s}{R_a} = \frac{V_{out}}{R_f}$$

$$R_f \left(\left(\frac{V_b R_c}{R_b + R_c} \right) \left(\frac{1}{R_a} + \frac{1}{R_f} \right) - \frac{V_s}{R_a} \right) = V_{out}$$

OpAmp Circuit Analysis

(SU20 MT2)

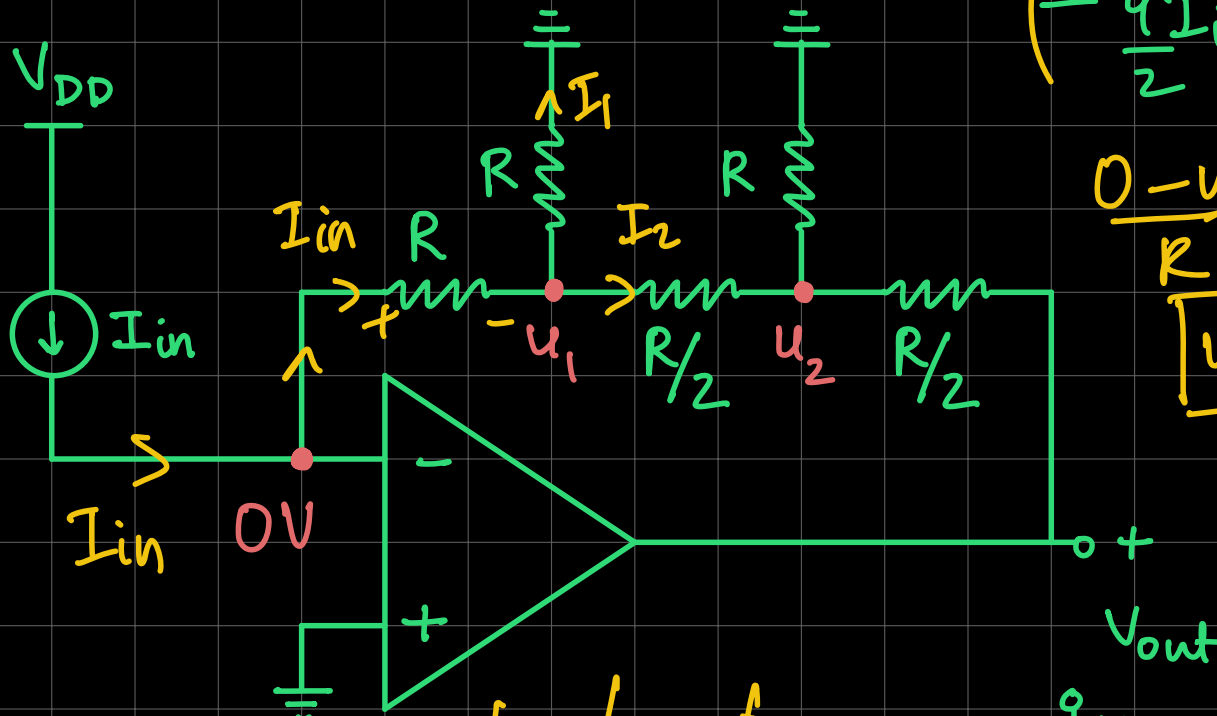

$$\begin{pmatrix} -4.5 I_{in} R \\ -\frac{9 I_{in} R}{2} \end{pmatrix}, \begin{matrix} 0 \\ X \end{matrix}$$

$$\frac{0 - u_1}{R} = I_{in}$$

$$\boxed{u_1 = -I_{in} R}$$


$$I_{in} = \frac{u_1}{R} + \frac{u_1 - u_2}{R/2}$$

$$\frac{u_2 - 0}{R} + \frac{u_2 - u_1}{R/2} + \frac{u_2 - V_{out}}{R/2} = 0$$




$$I_{in} = \frac{-I_{in} R}{R} + \frac{-I_{in} R}{R/2} - \frac{u_2}{R/2}$$

$$\boxed{u_2 = -2 I_{in} R}$$

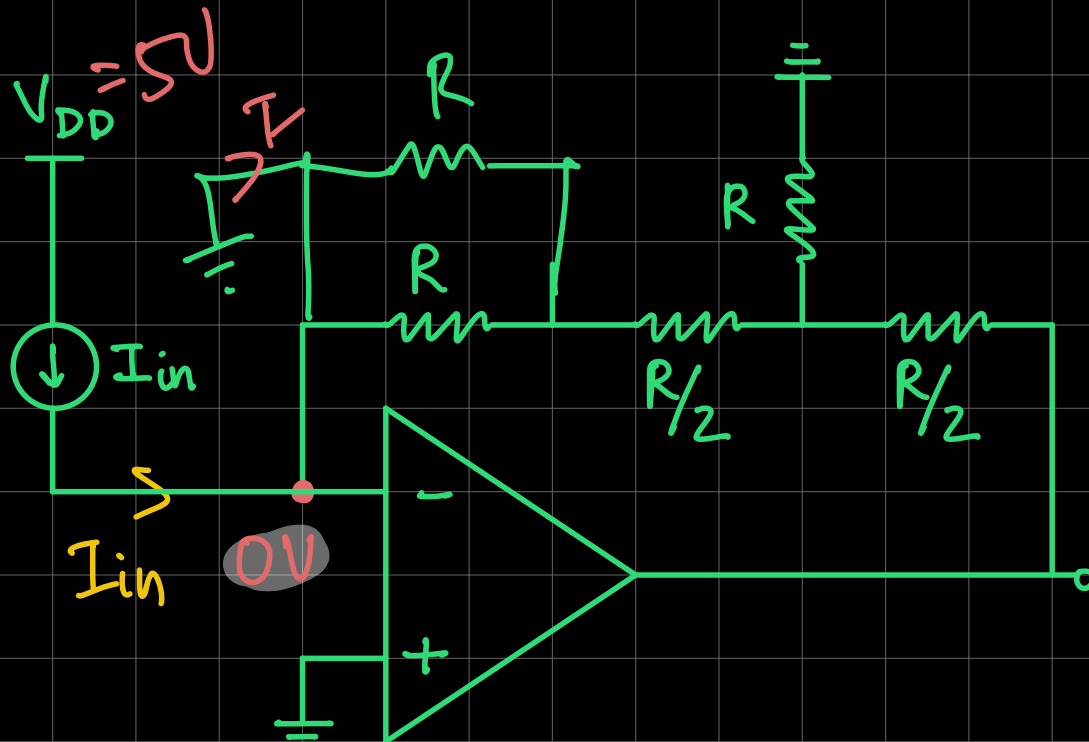
$$-2 I_{in} - 4 I_{in} + 2 I_{in} - 4 I_{in} = \frac{2 V_{out}}{R} \Rightarrow \boxed{V_{out} = -4 I_{in} R}$$



Circuit Design (SU20 Final Q14)

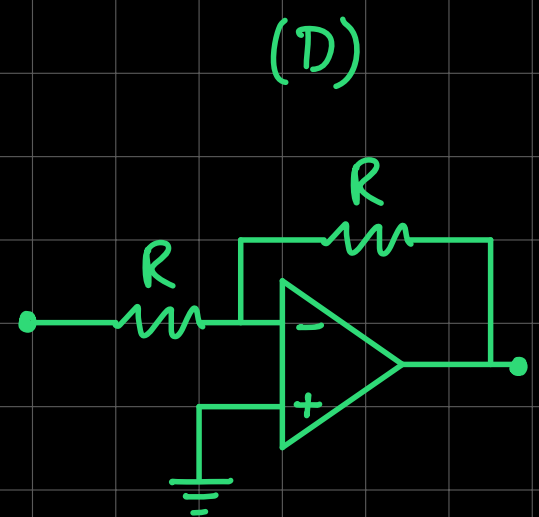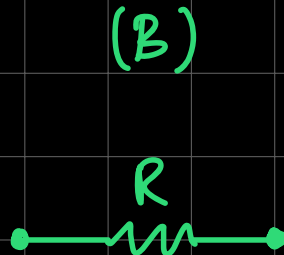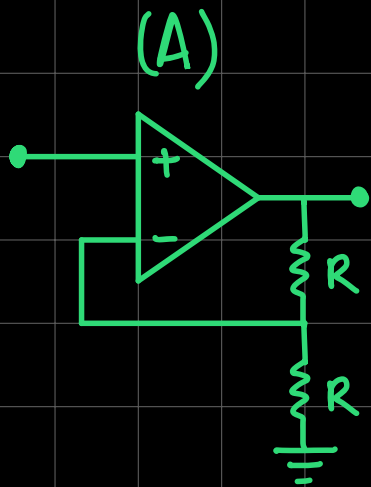


Outline

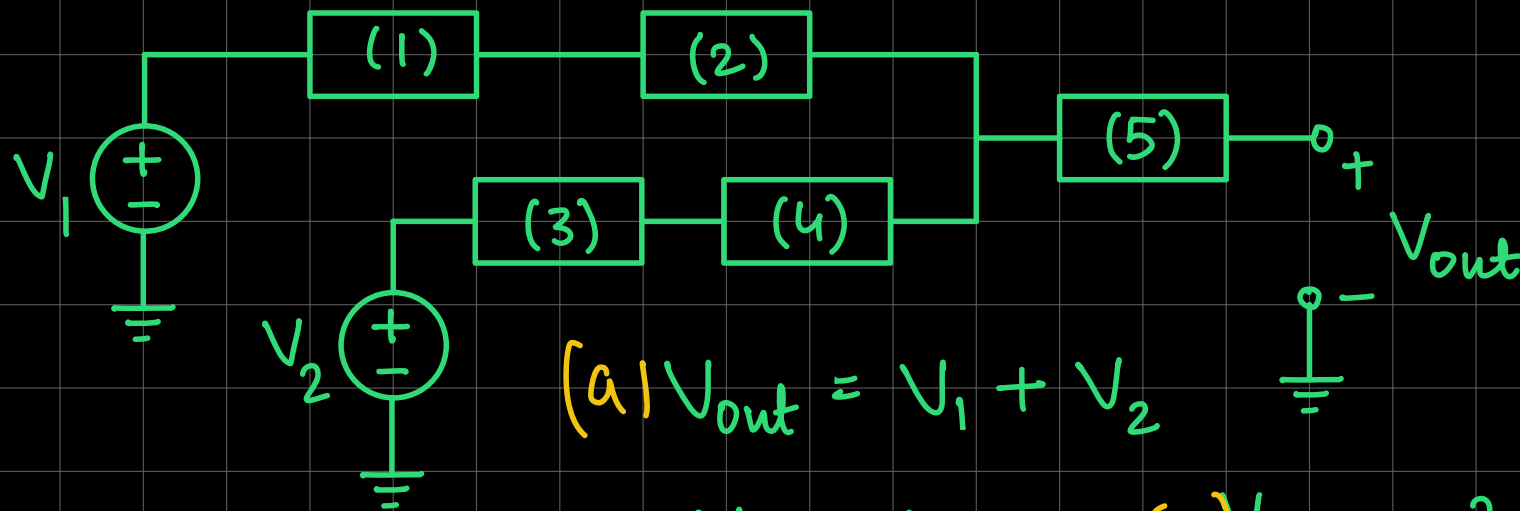

(a) $V_{out} = V_1 + V_2$

(b) $V_{out} = V_1 - V_2$ (c) $V_{out} = \frac{2}{3} V_1 + \frac{4}{3} V_2$

Example:

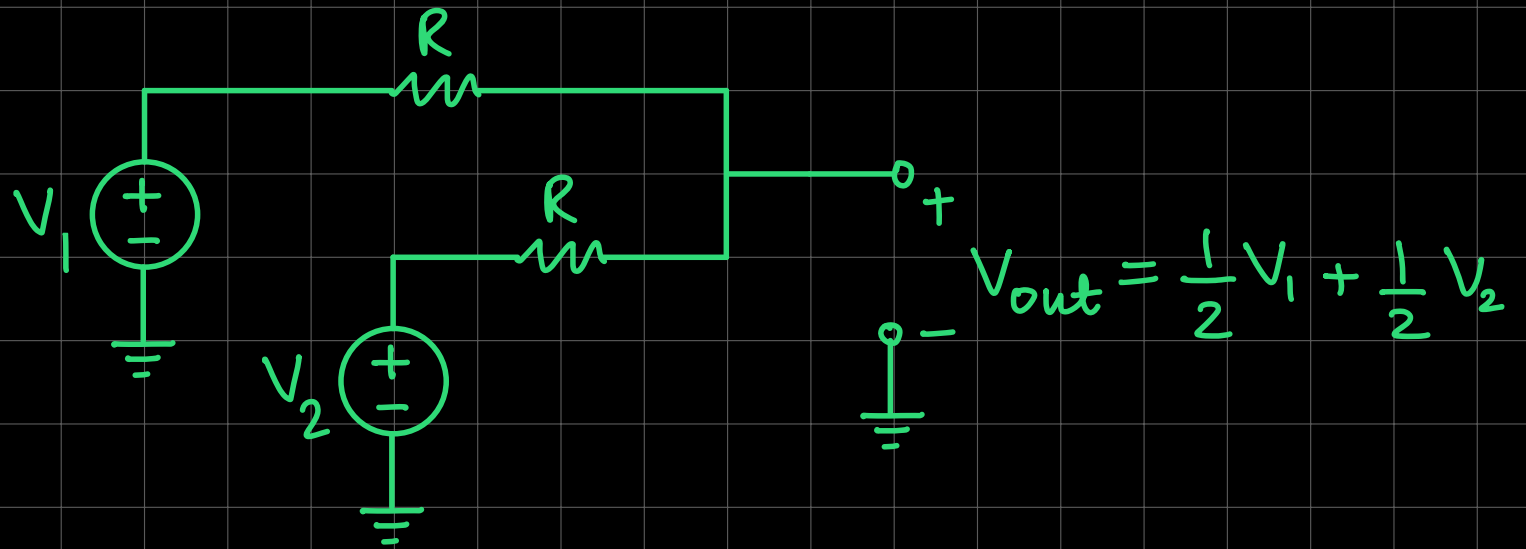

$$V_{out} = \frac{1}{2} V_1 + \frac{1}{2} V_2$$



Design a circuit using ABCD & the outline such that:

(a) $V_{out} = V_1 + V_2$



(b) $V_{out} = V_1 - V_2$

(c) $V_{out} = \frac{2}{3} V_1 + \frac{4}{3} V_2$


(a)

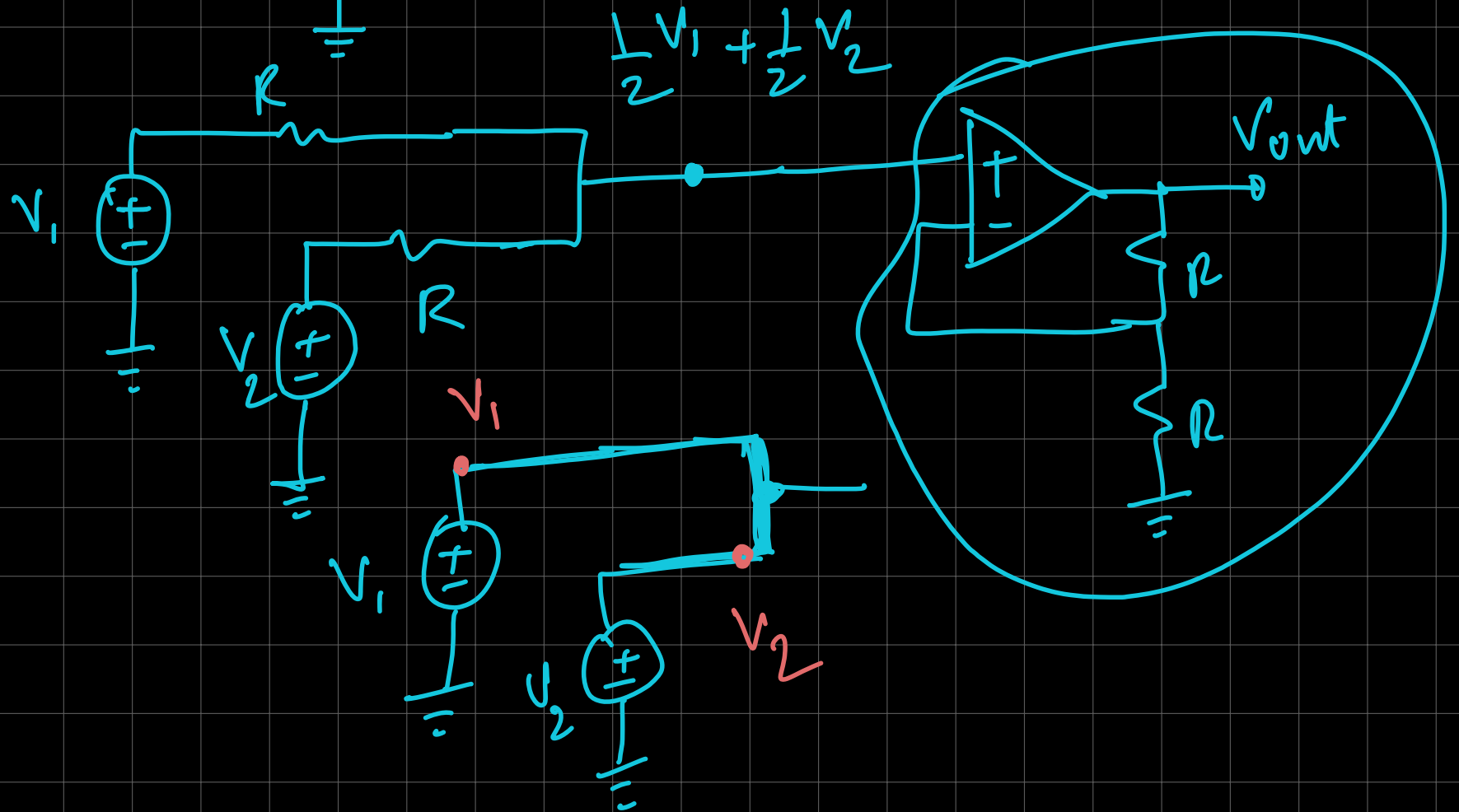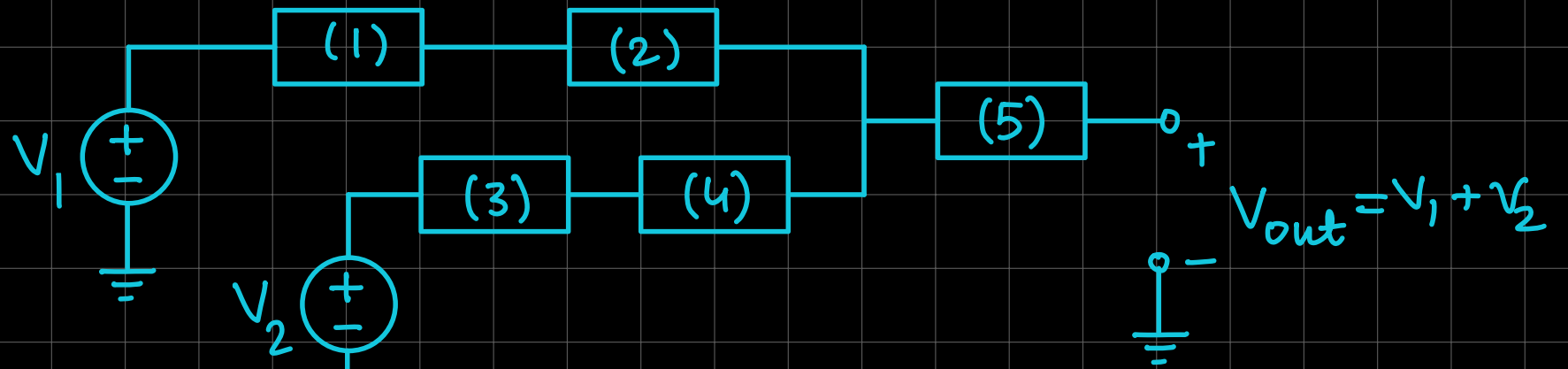


(b)

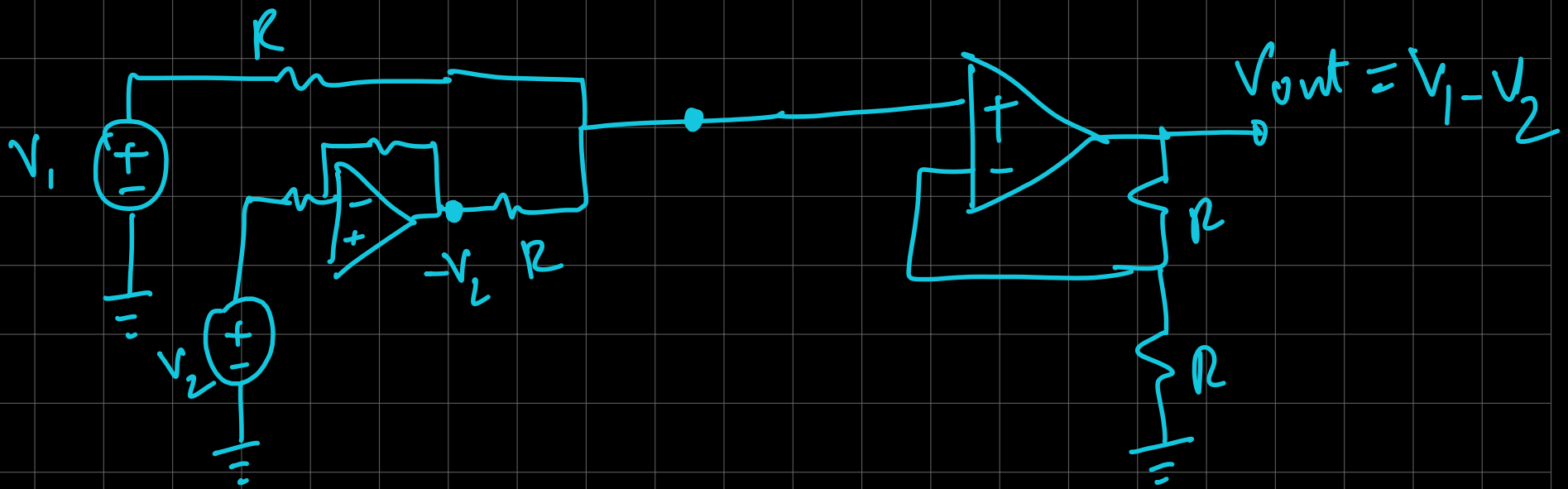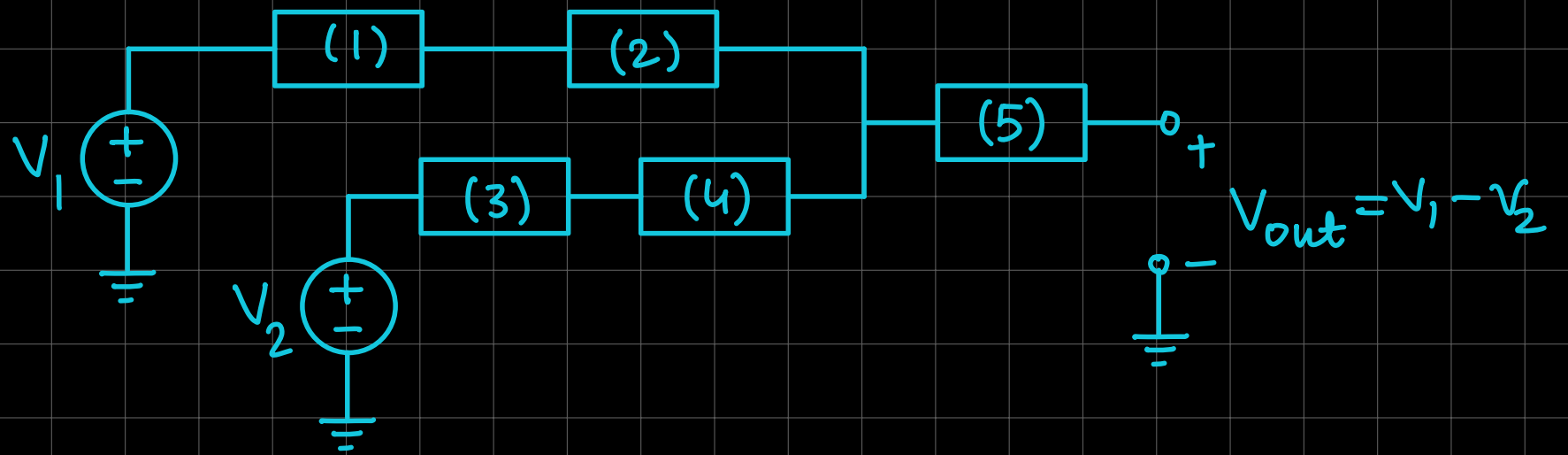

(c)

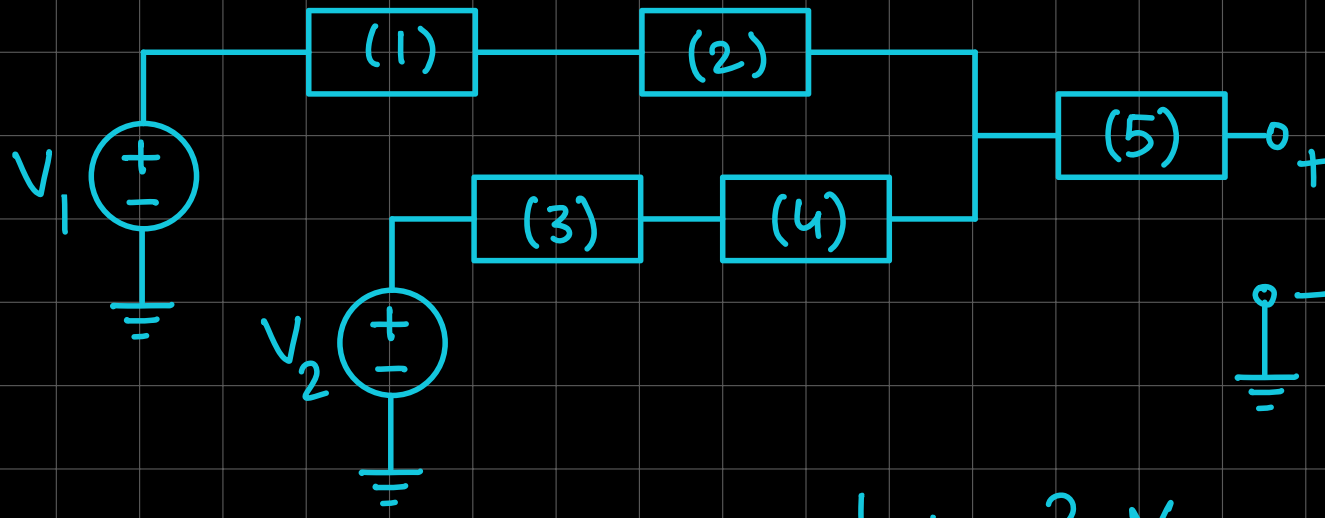

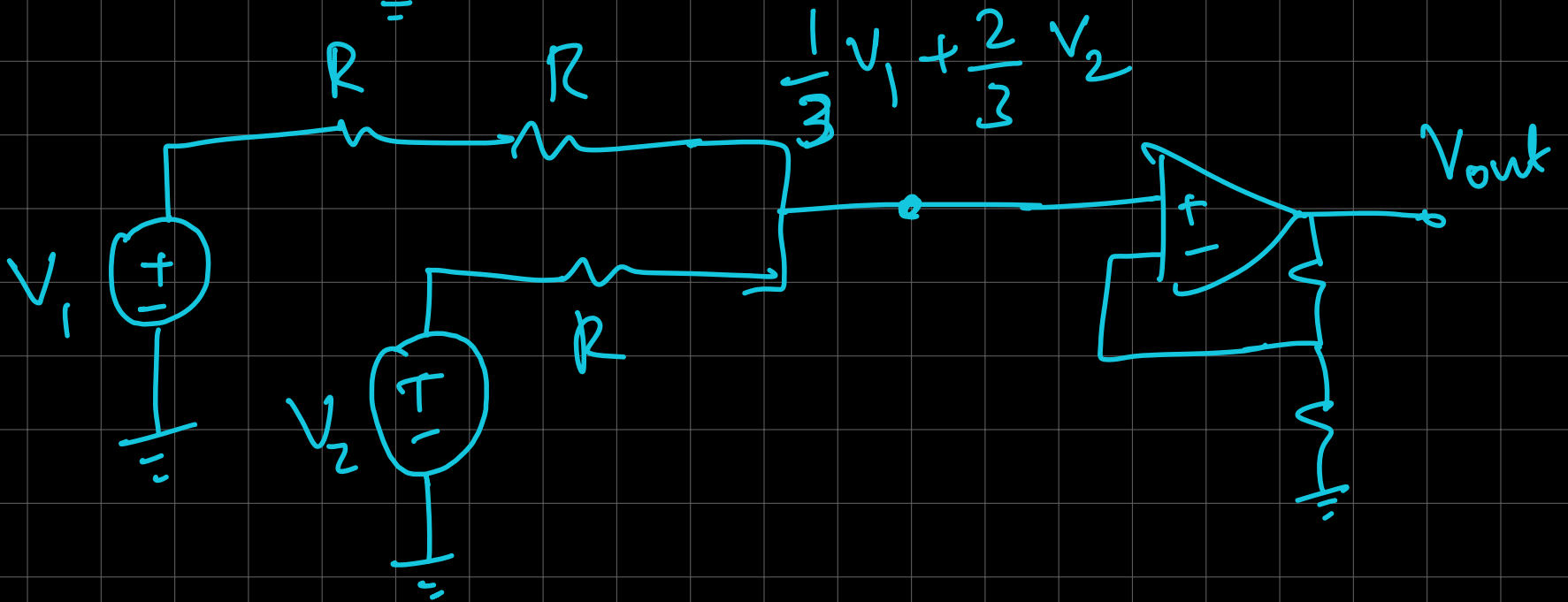
$$V_{out} = \frac{2}{3}V_1 + \frac{4}{3}V_2$$



$$\frac{1}{3}V_1 + \frac{2}{3}V_2$$

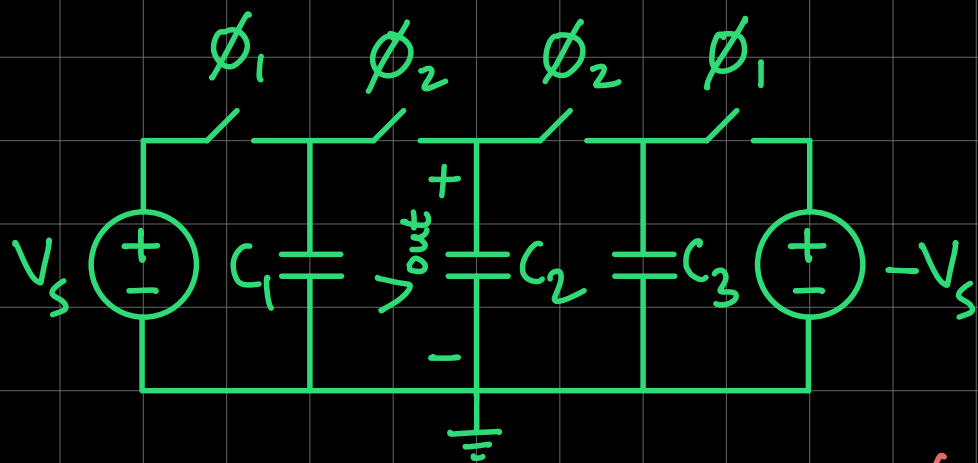Capacitors and Charge Sharing (FA19 Final Q9)



Find V_{out} after ϕ_1 & ϕ_2 .



$$\phi_1 \rightarrow 0$$

$$\phi_2 \rightarrow \frac{V_s(C_1 - C_3)}{C_1 + C_2 + C_3}$$

$$\phi_2 \rightarrow \frac{V_s(C_1 - C_3)}{C_1 + C_2 + C_3}$$


$$\phi_1 \rightarrow V_{out} = 0$$

$$q_1 = C_1 V_s$$

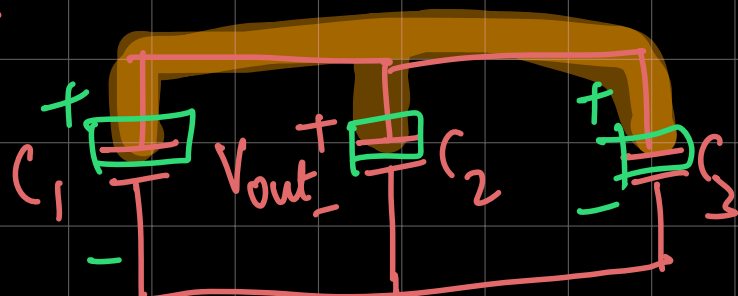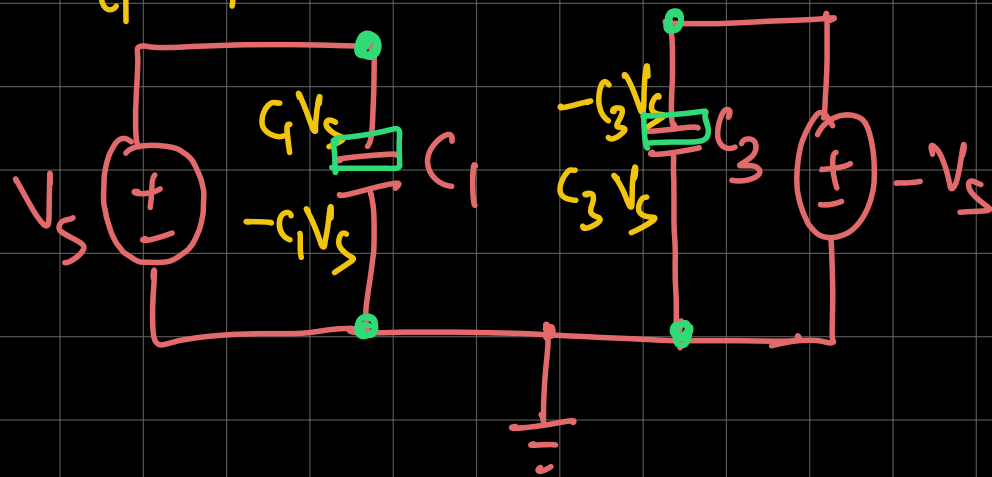

$$Q_{\phi_1} \rightarrow C_1 V_s - C_3 V_s = V_{out} C_1 + V_{out} C_2 + V_{out} C_3$$

$$Q = C_2 V_{out}$$

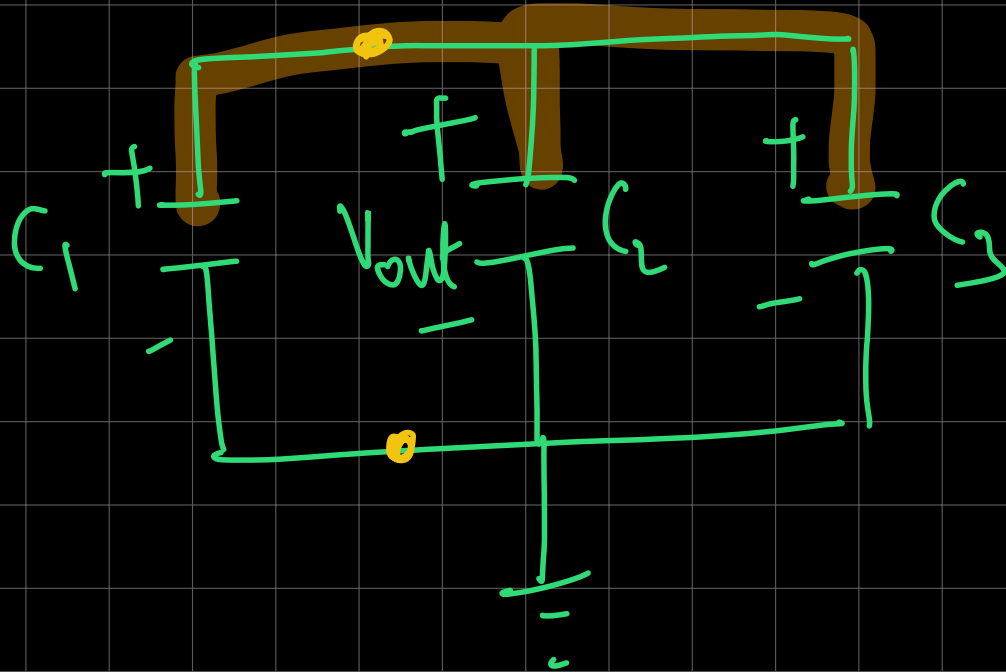


$$C_1 V_S - C_3 V_S = V_{out} C_1 + V_{out} C_2 + V_{out} C_3$$

$$\phi_2 \quad V_{out} = \frac{(C_1 - C_3) V_S}{C_1 + C_2 + C_3}$$

Superposition

(SP20 Final Q9)

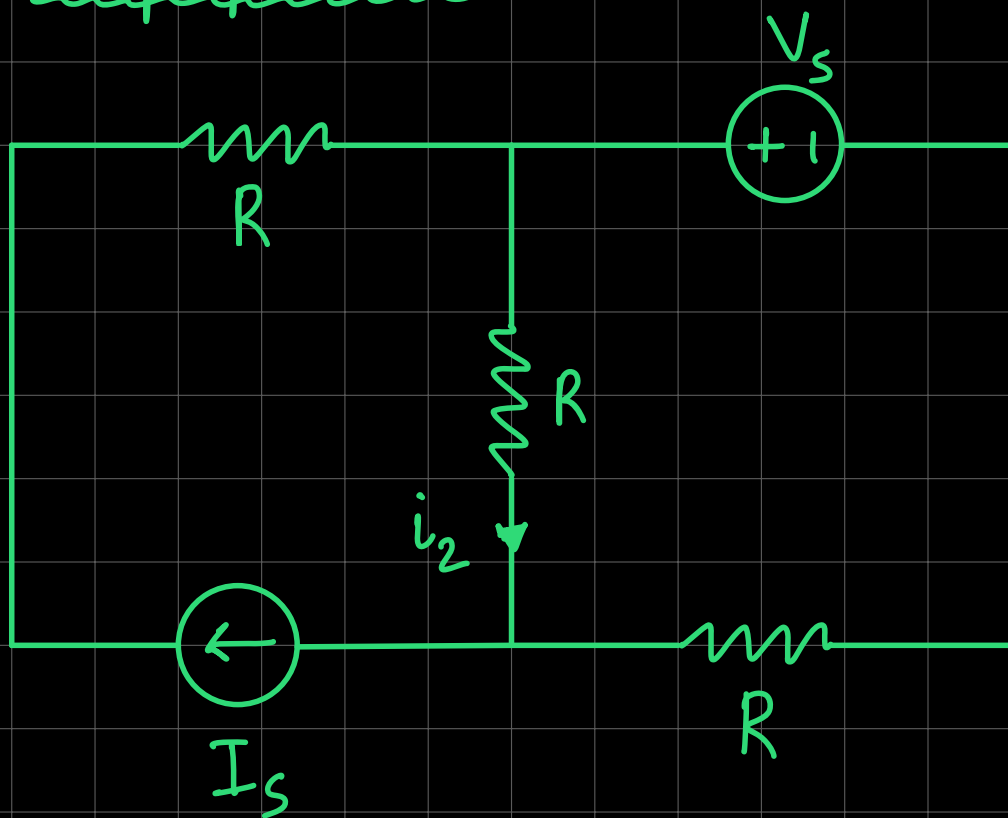

Find i_2

Eigenstuf
auf