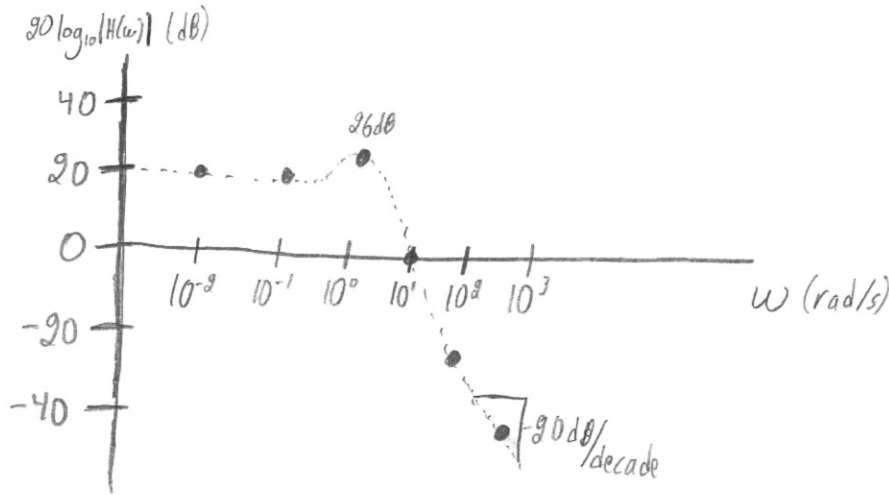


EE16B Section 8B Notes

Warmup





- Why do we plot $20 \log_{10} |H(j\omega)|$?
 - decibels are a measure of power.
- Where is $\omega=0$ on this plot?
 - Nowhere! (Infinitely far off to the left.)

Questions from Lecture?

Better Living Through (Complex) Impedance

- Define impedance $\frac{V}{I} = Z = R + jX = |Z|e^{j\theta_z}$
 - resistance
 - reactance

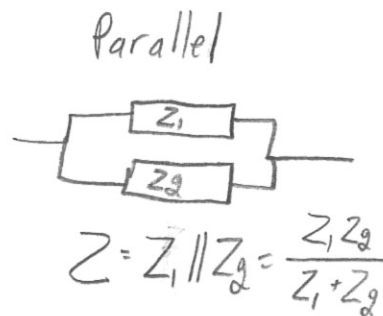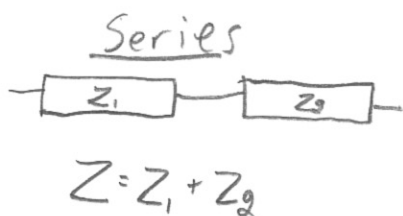The network rules for impedance are the same as those for resistance:



The imaginary part of impedance comes from:

Capacitors

$$\text{---} \parallel \text{---} C \quad Z_c = \frac{1}{j\omega C}$$

Inductors

$$\text{---} \text{---} \text{---} \text{---} \text{---} \text{---} \text{---} \text{---} L \quad Z_L = j\omega L$$

Mathematically, these quantities behave the same as $Z_R = R$, but there are some important conceptual differences:

- The impedance varies with ω , the frequency through the element.

Z_c decreases with increasing ω Z_L increases with increasing ω

- They have an imaginary term, which implies a phase shift:

$$Z_c = \frac{1}{e^{j\pi/2}\omega C} = \frac{1}{\omega C} e^{-j\pi/2} \quad Z_L = \omega L e^{j\pi/2}$$

so voltage and current are out of phase!

SPICE demo.