

Solutions: Provided by John Noonan and Quincy Huynh.


1. Proof of Induction

Given the voltage-current relationship of an inductor $V = L \frac{di}{dt}$, show that its complex impedance is $Z_L = j\omega L$.

Solutions: Since $V(t)$ is an eigenfunction and impedance is a constant, then $i(t)$ is also an eigenfunction such that $\frac{di}{dt} = j\omega \cdot i(t)$.

$$\begin{aligned} V &= L \frac{di}{dt} \\ V &= Lj\omega \cdot i(t) \\ V &= (j\omega L)i(t) \\ Z_L &= j\omega L \end{aligned}$$

2. L-R Filter

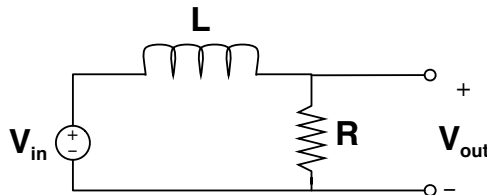


(a) Write the frequency response function $H(\omega) = \frac{V_{out}}{V_{in}}$ for the circuit.

Solutions: $H(\omega) = \frac{V_{out}}{V_{in}} = \frac{Z_R}{Z_L + Z_R} = \frac{R}{j\omega L + R} = \frac{1}{j\omega \frac{L}{R} + 1}$

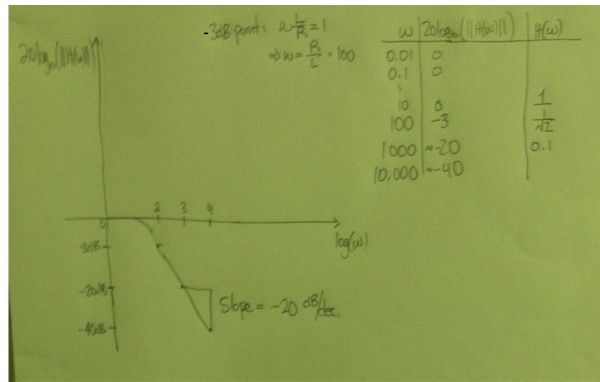(b) If $R = 10\Omega$ and $L = 100\text{mH}$, plot the log-magnitude of $H(\omega)$ and label important magnitudes and frequencies.

Solutions: $\omega_c = \frac{R}{L} = 10/0.100 = 100\text{rad/s}$



(c) If $V_{in}(t) = \cos(10t) + \cos(100t) + \cos(1000t)$, what is $V_{out}(t)$? (Assume that $H(-\omega) = H(\omega)$.)

Caveat: We have not yet discussed how the *phase* of V_{in} is affected by the circuit. Ignore this for now; assume the phase of the output is the same as the phase of the input.

Solutions: $|H(\omega)| = \frac{1}{\sqrt{\omega^2 L^2 + 1}} = \frac{1}{\sqrt{10000 + 1}}$


$|H(10)| \approx 1$

$|H(100)| = \frac{1}{\sqrt{2}}$

$|H(1000)| = \frac{1}{10}$

$V_{out} = 1 \cdot \cos(10t) + \frac{1}{\sqrt{2}} \cdot \cos(100t) + \frac{1}{10} \cdot \cos(1000t)$

3. Op-Amps: What *Can't* They Do?

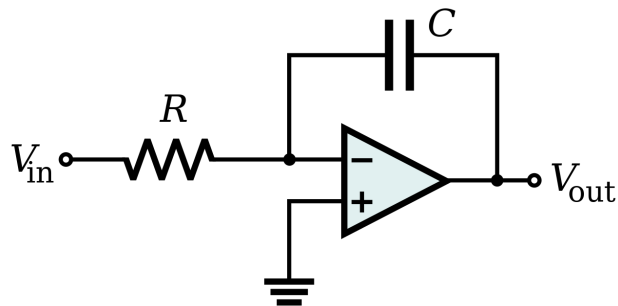

(a) Write the frequency response function $H(\omega) = \frac{V_{out}}{V_{in}}$ for the circuit.

Solutions: By Golden Rules:

$V_n = V_p$

$i_n = 0$

$i_p = 0$

$V_n = 0$ by the first golden rule, and using the second rule with KCL, we find that:

$$\frac{V_{in}}{Z_R} = -\frac{V_{out}}{Z_C}$$


$$\frac{V_{out}}{V_{in}} = -\frac{Z_C}{Z_R}$$

$$\frac{V_{out}}{V_{in}} = -\frac{1}{j\omega RC}$$

$$H(\omega) = -\frac{1}{j\omega RC}$$

- (b) If $R = 1\text{k}\Omega$ and $C = 100\text{nF}$, plot the log-magnitude of $H(\omega)$ and label important magnitudes and frequencies. (Again assume that $H(-\omega) = H(\omega)$.)

Solutions:

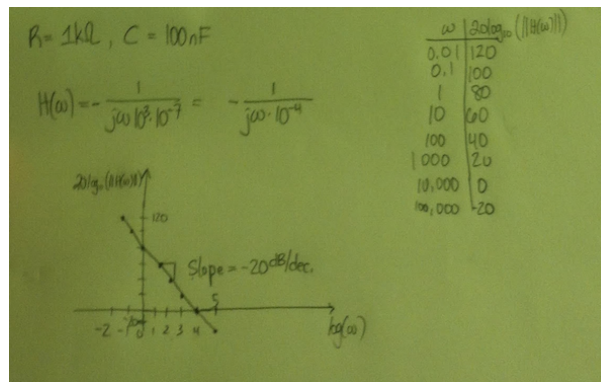

- (c) **Challenge:** What does this circuit do?

Hint: You will probably need to set up the differential equation relating V_{out} and V_{in} to work this out.

Solutions:

$$\frac{V_{in}}{R} = -C \frac{dV_{out}}{dt}$$

$$-\frac{1}{RC} \int V_{in} dt = V_{out}$$

The circuit takes in V_{in} and integrates it.