

RC Circuits / Differential Equations

OUTLINE

- Review: CMOS logic circuits & voltage signal propagation
- Model: RC circuit \rightarrow differential equation for $V_{\text{out}}(t)$
- Derivation of solution for $V_{\text{out}}(t) \rightarrow$ propagation delay formula

EE16B, Fall 2015

Meet the Guest Lecturer




Prof. Tsu-Jae King Liu


- Joined UCB EECS faculty in 1996
- Courses taught: 40, 105, 130, 143, 290D, 375
- Research in nanoelectronic & nanomechanical devices

The MOSFET

 Metal-Oxide-Semiconductor
Field-Effect Transistor:





Intel's 32nm MOSFETs

 

- Current flowing between the heavily doped SOURCE & DRAIN regions is controlled by the voltage on the GATE electrode
- N-channel & P-channel MOSFETs operate in a complementary manner


CIRCUIT SYMBOLS:

  

3


The CMOS Inverter

CIRCUIT

 

- ✓ Low static power consumption, since one transistor is always off in steady state


SWITCH MODELS

 

4

Pull-Down and Pull-Up Devices

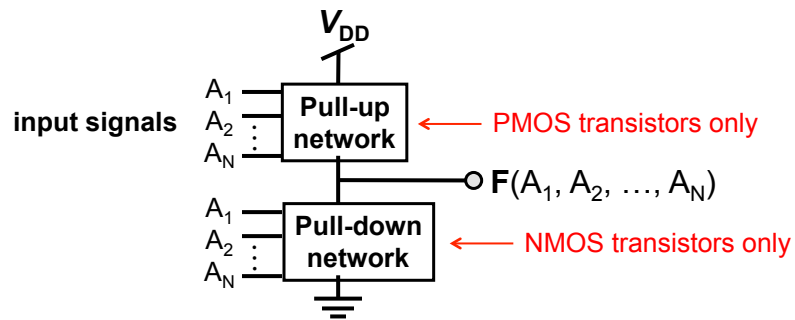- In CMOS logic gates, **NMOS transistors** are used to connect the output to **GND**, whereas **PMOS transistors** are used to connect the output to **V_{DD}** .
 - An NMOS transistor functions as a **pull-down device** when it is turned on (gate voltage = V_{DD})
 - A PMOS transistor functions as a **pull-up device** when it is turned on (gate voltage = **GND**)





5

Voltage Signal Propagation

- When an input voltage of a logic gate is changed, there is a **propagation delay** before the output of the logic gate changes, due to capacitive loading at the output.

CMOS inverter chain

  


Propagation delay is measured between the 50% transition points of the input and output signals.

6

RC Circuit Model for High-Low Transition

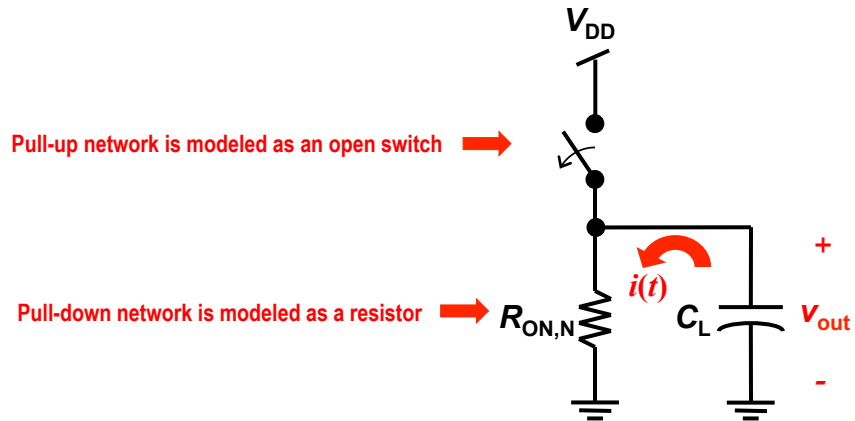Initially $V_{out} = V_{DD}$; then NMOSFET(s) connect V_{out} to GND:




$$v_{out} = -R_{ON,N} C_L \frac{dv_{out}}{dt}$$

7

Output Load Capacitance of a Logic Gate

- The output load capacitance of a logic gate comprises several components:

 - “intrinsic capacitance” → • pn-junction capacitance
for both NMOS and PMOS transistors
- “extrinsic capacitance” { • capacitance of connecting wires
- input capacitances of the “fan-out” gates
 $C_{gate,N}, C_{gate,P}$



8

Derivation of RC Model

Derivation of $V_{\text{out}}(t)$ for High-Low Transition

By separation of variables:

11


Derivation of $V_{\text{out}}(t)$ for High-Low Transition

With eigenfunctions:

12

Derivation of Formula for t_{pHL}

 
$$V_{out}(t) = V_{DD} e^{-t/R_{ON,N}C_L}$$



13

RC Circuit Model for Low-High Transition

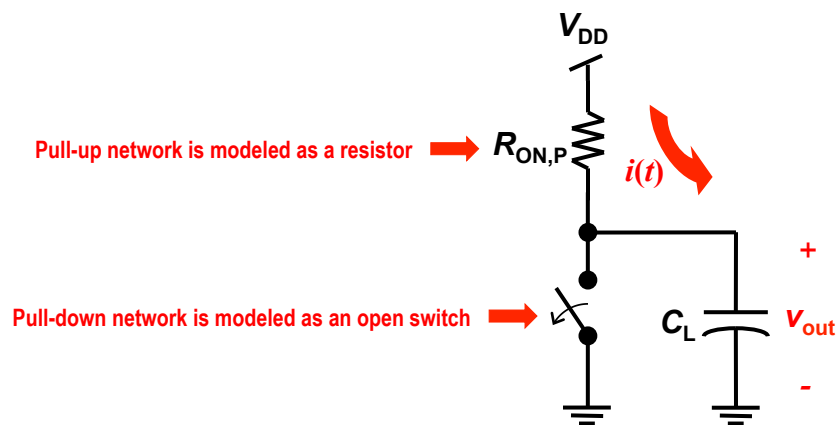Initially $V_{out} = 0$; then PMOSFET(s) connect V_{out} to V_{DD} :



$$V_{DD} - v_{out} = -R_{ON,P} C_L \frac{dv_{out}}{dt}$$


14

Derivation of $V_{\text{out}}(t)$ for Low-High Transition

15


Derivation of Formula for t_{pLH}
 
$$V_{out}(t) = V_{DD} \left(1 - e^{-t/R_{ON,p}C_L} \right)$$



17

Minimizing Propagation Delay

 

A fast CMOS logic circuit is built by

- 1. Keeping the output capacitance C_L small**
 - Minimize the area of drain pn junctions.
 - Lay out devices to minimize interconnect capacitance.
 - Avoid large fan-out.
- 2. Decreasing the equivalent resistance of the transistors**
 - Decrease gate length L_G
 - Increase transistor width W
 - ... but this increases pn junction area and hence C_L
- 3. Increasing V_{DD}**
 - trade-off with power consumption...

18

Classroom Analogy

