

This homework is due August 29th, 2016, at Noon.

1. Homework process and study group

- (a) Who else did you work with on this homework? List names and student ID's. (In case of hw party, you can also just describe the group.)
- (b) How long did you spend working on this homework? How did you approach it?

2. KVL/KCL review

Kirchoff's Circuit Laws are two important laws used for analyzing circuits. Kirchoff's Current Law (KCL) says that the sum of all currents entering a node must equal 0. For example, in Figure 1, the sum of all of the currents entering node 1 is $I_1 - I_2 - I_3 = 0$. Assuming I_1 and I_3 are known, we can easily obtain a solvable equation for V_x by plugging in Ohm's law: $I_1 - \frac{V_x}{R_1} - I_3 = 0$

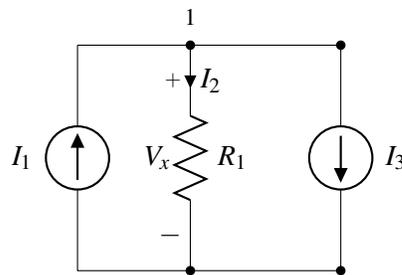


Figure 1: KCL Circuit

Kirchoff's Voltage Law (KVL) states that the sum of all voltages in a circuit loop must equal 0. To apply KVL to the circuit shown in Figure 2, we can add up voltages in the loop in the counterclockwise which yields $-V_1 + V_x + V_y = 0$. Using the relationships $V_x = i * R_1$ and $i = I_1$ we can solve for all unknowns in this circuit. You can use these two laws to solve any circuit that is planar and linear.

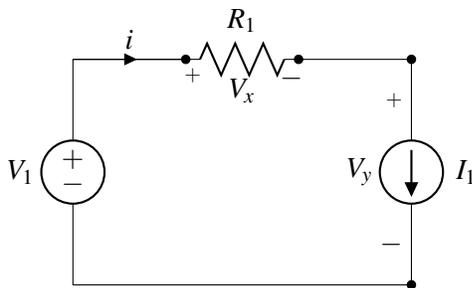


Figure 2: KVL Circuit

Use Kirchoff's Laws on the circuit below to find v_x , i_s , i_{in} and the power provided by the dependent current source. You can use $R_1 = 2\Omega$, $R_2 = 4\Omega$, and $R_3 = 2\Omega$. To help with solving the problem, we have already found the voltage difference across R_1 and R_3 .

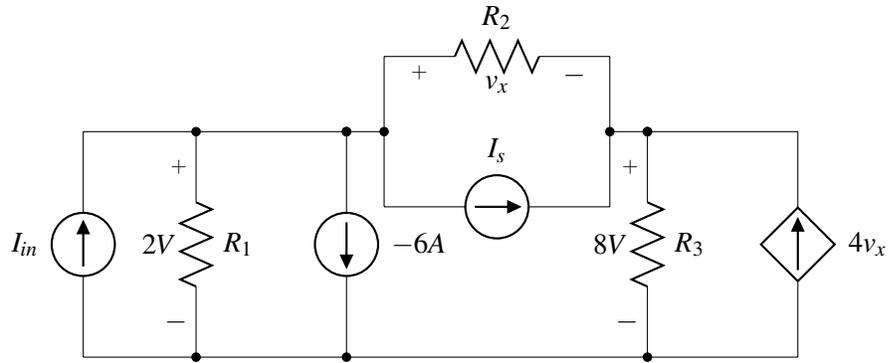


Figure 3: Example Circuit

- (a) What is v_x ?
- (b) What is I_s ?
- (c) What is I_{in} ?
- (d) What is the power output of the dependent current source on the far right?

3. KCL

Now consider the circuit shown below:

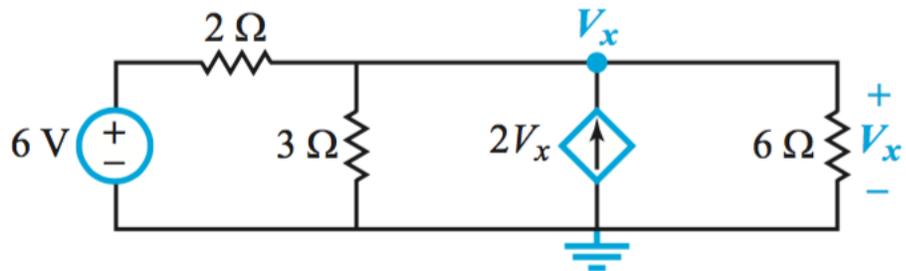


Figure 4: From Ulaby, Maharbiz, Furse. *Circuits*. Third Edition

Determine the voltage V_x .

4. KVL

Now consider the circuit shown below:

Determine the amount of power supplied by the voltage source.

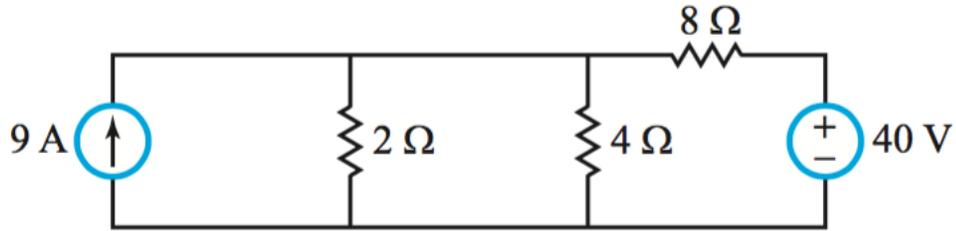


Figure 5: From Ulaby, Maharbiz, Furse. *Circuits*. Third Edition

5. Circuits and Gaussian Elimination

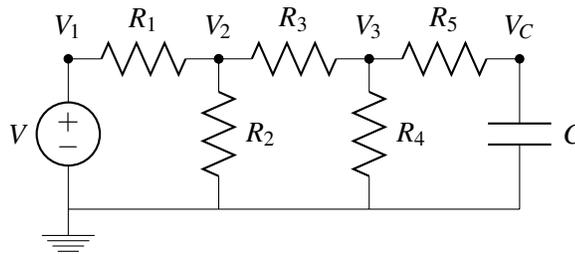


Figure 6: Example Circuit

- Find a system of linear equations that could be solved to find the node voltages.
- Given that the component values are $R_1 = 500\Omega$, $R_2 = 3\text{k}\Omega$, $R_3 = 1\text{k}\Omega$, $R_4 = 2\text{k}\Omega$, and $R_5 = 4\text{k}\Omega$, Solve the circuit equations using Gaussian elimination.
- What's the voltage V_C across the capacitor?
- How would you check your work? Do so.

6. Solving Recurrence Relations

For this problem, we'll work with a sequence defined by the following recurrence relation, where $S[n]$ is the n th number in the sequence:

$$S[n + 1] = 3S[n] - 2S[n - 1]$$

$$S[0] = 0$$

$$S[1] = 1$$

You can probably see how this could be computed recursively or iteratively, but let's try a linear-algebraic approach and see where it takes us.


- Starting from the definition of the sequence, determine the matrix A to calculate $S[n + 1]$ such that:

$$A \begin{pmatrix} S[n] \\ S[n - 1] \end{pmatrix} = \begin{pmatrix} S[n + 1] \\ S[n] \end{pmatrix}$$


- (b) Find the eigenvalues λ_+ and λ_- of the matrix A .
- (c) Find the eigenvectors associated with λ_+ and λ_- from above.
- (d) How would you check your work? Do so. (Hint: Based on the eigenvalues you determined, how should this sequence behave for different initial conditions? Does it?)
- (e) Using your previous results, diagonalize A .
- (f) How can you use this new information to more efficiently compute any arbitrary $S[n]$ *without using any iteration or recursion*? (Hint: if a matrix $M = PDP^{-1}$ where D is a diagonal matrix, then think about $M^2 = MM$, M^3 , and even M^n .)
- (g) Finally, using your results from above, derive a closed-form expression with no summations, no recursion, and no matrix multiplications for $S[n]$.

7. Op-Amp Review

Now let's look at the circuit below:

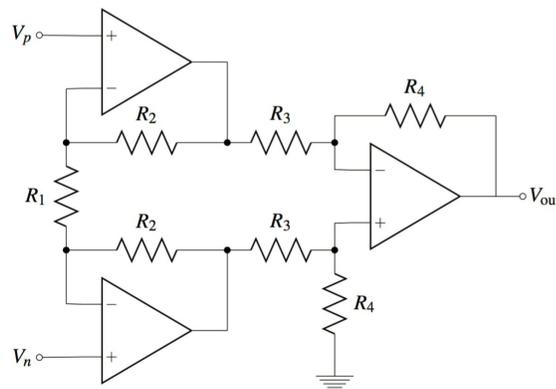

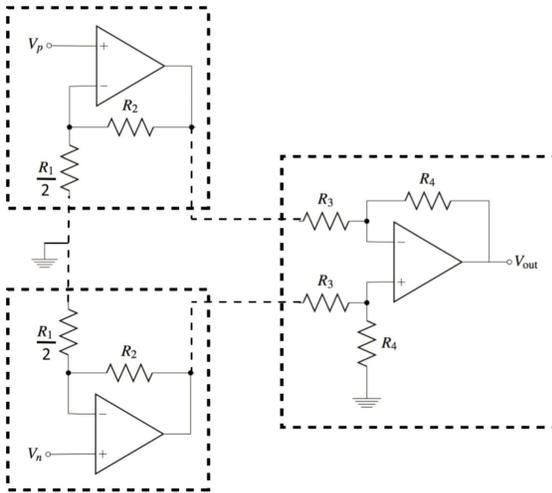- (a) Write down all the branch and node equations using the golden rules of Op-Amps.
- (b) Notice that there exists a symmetry between the two op-amps at the first stage of this circuit. What are the directions of the currents going through the two R_2 s? How do the currents of R_2 s influence the current through R_1 ?
- (c) What is the current through R_1 ?
- (d) What are the output voltages of the two op-amps at the first stage?
- (e) Compute the voltage at the + terminal of the second-stage op-amp.
- (f) What is V_{out} ?
- (g) What is the voltage in the middle of the resistor R_1 ?
- (h) Based on the above analysis, we could introduce a "fake ground" in the middle of the resistor R_1 and come up with the following circuit:



Now, each of the first two op-amps is being used in a form that resembles building blocks that you have seen before. What are the gains of those blocks?

What is $V_{out}/(V_p - V_n)$ for this revised circuit?

Contributors:

- Nathan Mailoa.
- Emily Naviasky.